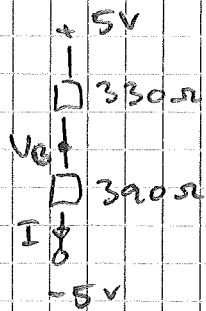


K4) a) Diod spannar


(27)



$$\underline{I} = \frac{10}{330 + 390} = \underline{13,9 \mu A}$$

$$\underline{V_B} = -5 + 390 \cdot I = -5 + 390 \cdot 13,9 \cdot 10^{-3} = \underline{0,417 V}$$


b) Diod leder

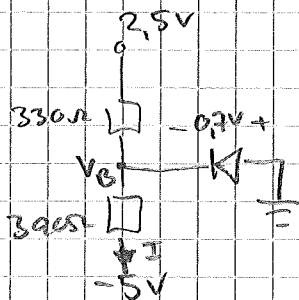

$$\underline{V_B} = -0,7 V$$

$$\underline{I} = \frac{V_B - (-5)}{390} = \frac{-0,7 + 5}{390} = \underline{11,0 \mu A}$$

K6

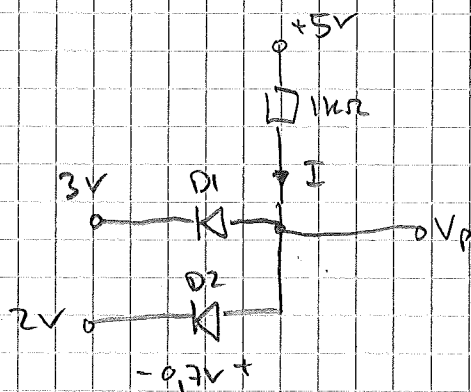


D2 leder
D1 spannar


$$\underline{V_P} = 2 + 0,7 = \underline{2,7 V}$$

$$\underline{I} = \frac{5 - V_P}{1000} = \frac{5 - 2,7}{1000} = \underline{2,3 \mu A}$$

K7

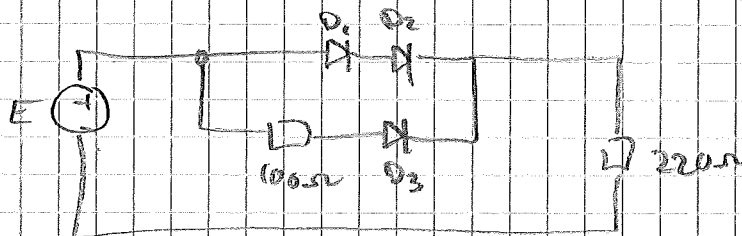

D3 leder da $E > 0,7 V$

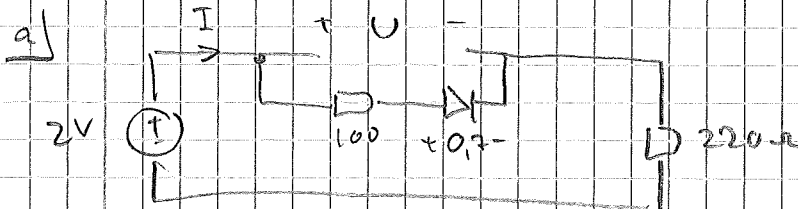


$$\underline{I} = \frac{2 - 0,7}{100 + 220} = \underline{4,06 \mu A}$$

$$U = 0,7 + 100I = 1,11 V$$

$$U < 2,0,7 \Rightarrow D2 = D3 \text{ leder ej} \Rightarrow \underline{I_D = 0}$$


K7) b)

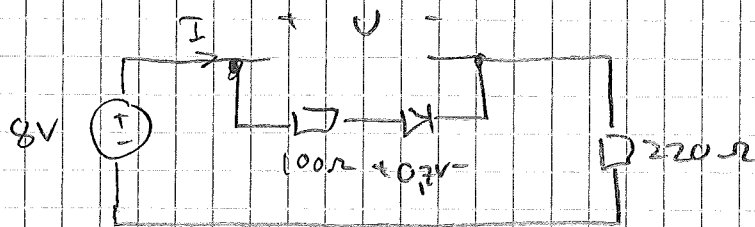

$$I = \frac{8 - 0,7}{100 + 220} = 22,81 \mu\text{A}$$

$$U = 0,7 + 100I = 2,98\text{V}$$
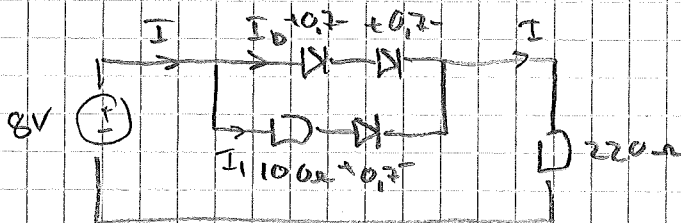
$$U > 2 \cdot 0,7\text{V} \Rightarrow D_1 \text{ u } D_2 \text{ lede}$$



$$I = \frac{8 - 0,7 - 0,7}{220} = \underline{\underline{30 \mu\text{A}}}$$

$$I_1 = \frac{0,7}{100} = 7 \mu\text{A}$$

$$\underline{\underline{I_0 = I - I_1 = 30 - 7 = 23 \mu\text{A}}}$$

K8Diod leder då $u(t) > 0,7V$


(29)

Då gäller $v(t) = u(t) - 0,7V$

Se facit för Figur

K9

Dioder leder

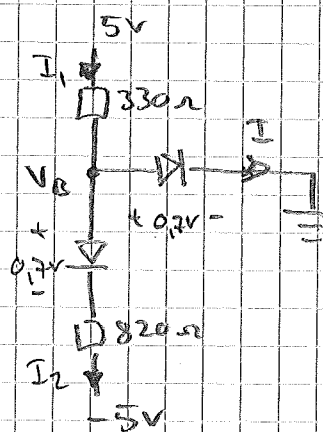


$$\underline{\underline{V_B = +0,7V}}$$

$$I_1 = \frac{5 - 0,7}{330} = 13,0 \mu A$$

$$I_2 = \frac{(V_B - 0,7) - (-5)}{820} = \frac{5}{820} = 6,1 \mu A$$

$$\underline{\underline{I = I_1 - I_2 = 13,0 - 6,1 = 6,9 \mu A}}$$

K
①

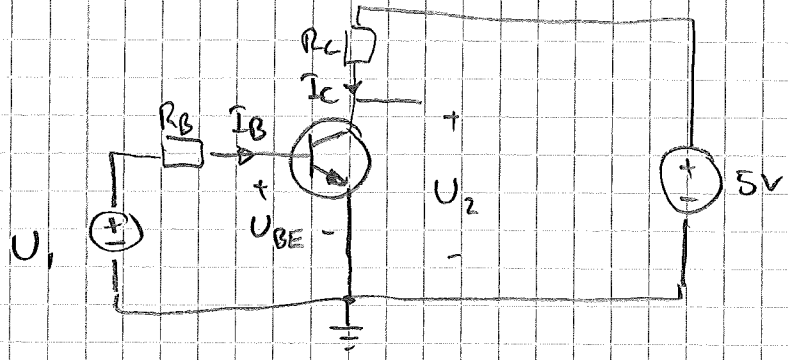

$$R_B = 120 \text{ k}\Omega \quad R_C = 1 \text{ k}\Omega \quad h_{fe} = 100 \quad U_1 = 4 \text{ V} \quad U_{BE} = 0,7 \text{ V}$$

a) $U_1 - R_B I_B - U_{BE} = 0 \quad (1) \Rightarrow$

$$I_B = \frac{U_1 - U_{BE}}{R_B} = \frac{4 - 0,7}{120 \cdot 10^3} = 27,5 \text{ }\mu\text{A}$$

$$I_C = h_{fe} \cdot I_B = 100 \cdot 27,5 \text{ }\mu\text{A} = 2,75 \text{ mA}$$

$$5 - R_C I_C - U_2 = 0 \quad (2) \Rightarrow$$

$$\underline{U_2 = 5 - R_C I_C = 5 - 1000 \cdot 2,75 \cdot 10^{-3} = 2,25 \text{ V}}$$

b) Ur ② $I_C = \frac{5 - U_2}{R_C} = \frac{5 - 3,8}{1000} = 1,2 \text{ mA}$

$$I_B = \frac{I_C}{h_{FE}} = \frac{1,2 \text{ mA}}{100} = 12 \text{ }\mu\text{A}$$

Ur ③ $\underline{U_1 = U_{BE} + R_B I_B = 0,7 + 120 \cdot 10^3 \cdot 12 \cdot 10^{-6} = 2,14 \text{ V}}$

c) Botherad $\Rightarrow U_2 = U_{CEsat} = 0,1 \text{ V}$

Ur ② $I_C = \frac{5 - U_2}{R_C} = \frac{5 - 0,1}{1000} = 4,9 \text{ mA}$


$$I_B = \frac{I_C}{h_{FE}} = \frac{4,9 \text{ mA}}{100} = 49 \text{ }\mu\text{A}$$

Ur ① $\underline{U_1 = U_{BE} + R_B I_B = 0,7 + 120 \cdot 10^3 \cdot 49 \cdot 10^{-6} = 6,58 \text{ V}}$

Även längre sp ger botherad transistor $\Rightarrow \underline{U_1 \geq 6,58 \text{ V}}$

K
②

31

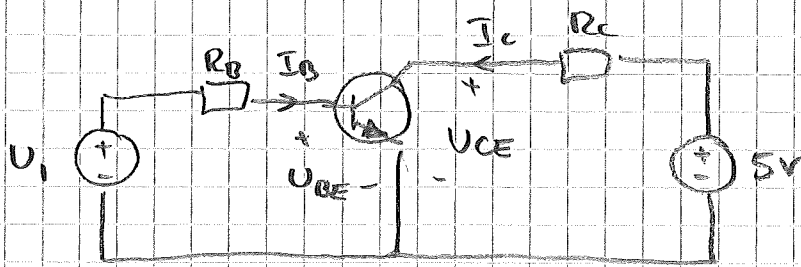

$$R_B = 100 \text{ k}\Omega \quad R_C = 2,2 \text{ k}\Omega \quad h_{FE} = 100 \quad U_{BE} = 0,7 \text{ V} \\ U_{CEsat} = 0,1 \text{ V}$$

a) $U_1 - R_B I_B - U_{BE} = 0 \Rightarrow$

$$I_B = \frac{U_1 - U_{BE}}{R_B} = \frac{2 - 0,7}{100 \cdot 10^3} = 13 \mu\text{A}$$

$$\underline{I_C = h_{FE} \cdot I_B = 100 \cdot 13 \mu\text{A} = 1,3 \text{ mA}}$$

Kontroll $U_{CE} + R_C I_C - 5 = 0 \Rightarrow$

$$U_{CE} = 5 - R_C I_C = 5 - 2200 \cdot 1,3 \cdot 10^{-3} = 2,14 \text{ V}$$

$$U_{CE} > 0,1 \text{ V} \Rightarrow E_1 \text{ biased}$$


b) $I_B = \frac{U_1 - U_{BE}}{R_B} = \frac{10 - 0,7}{100 \cdot 10^3} = 93 \mu\text{A}$

$$I_C = h_{FE} \cdot I_B = 100 \cdot 93 \mu\text{A} = 9,3 \text{ mA}$$

Kontroll $U_{CE} = 5 - R_C I_C = 5 - 2200 \cdot 9,3 \cdot 10^{-3} = -15,46 \text{ V}$

$$U_{CE} \leq 0,1 \text{ V} \Rightarrow \text{Balknad} \Rightarrow U_{CE} = U_{CEsat} = 0,1 \text{ V} \Rightarrow$$

$$\underline{I_C = \frac{5 - U_{CEsat}}{R_C} = \frac{5 - 0,1}{2200} = 2,23 \text{ mA}}$$

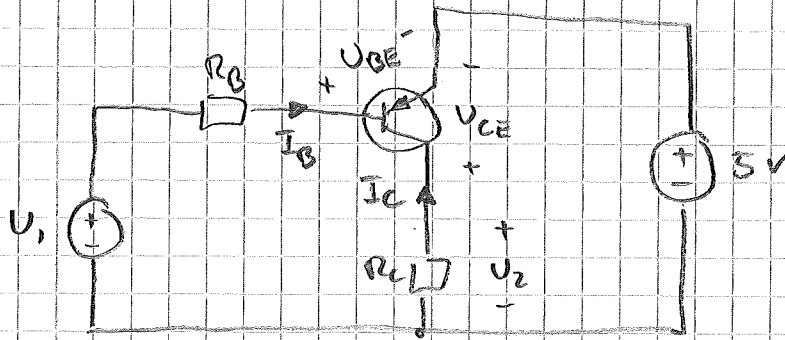K
3

$$R_B = 82 \text{ k}\Omega \quad R_L = 2,2 \text{ k}\Omega \quad h_{FE} = 100 \quad U_{BE} = -0,7 \text{ V} \quad U_2 = 2 \text{ V}$$

$$I_C = - \frac{U_2}{R_L} = - \frac{2}{2200} = -0,909 \text{ mA}$$


$$I_B = \frac{I_C}{h_{FE}} = - \frac{0,909 \text{ mA}}{100} = -9,09 \text{ }\mu\text{A}$$

$$U_1 - R_B I_B - U_{BE} - 5 = 0$$

$$\begin{aligned} U_1 &= R_B I_B + U_{BE} + 5 = 82 \cdot 10^3 \cdot (-9,09) \cdot 10^{-6} - 0,7 + 5 = \\ &= \underline{\underline{3,55 \text{ V}}} \end{aligned}$$

K

4

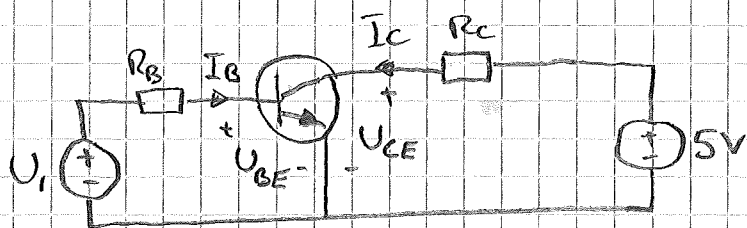

$$R_C = 1 \text{ k}\Omega \quad U_1 = 5 \text{ V} \quad h_{FE} = 100 \quad U_{BE} = 0,7 \text{ V} \quad U_{CEsat} = 0,1 \text{ V}$$

$$\text{Transistor bottnad} \Rightarrow U_{CE} = U_{CEsat} = 0,1 \text{ V}$$

$$U_{CE} + R_C I_C - 5 = 0 \Rightarrow$$


$$I_C = \frac{5 - U_{CE}}{R_C} = \frac{5 - 0,1}{1000} = 4,9 \text{ mA}$$

$$I_B = \frac{I_C}{h_{FE}} = \frac{4,9 \text{ mA}}{100} = 49 \mu\text{A}$$

$$U_{BE} + R_B I_B - U_1 = 0 \Rightarrow$$

$$\underline{R_B} = \frac{U_1 - U_{BE}}{I_B} = \frac{5 - 0,7}{49 \cdot 10^{-6}} = \underline{87,8 \text{ k}\Omega}$$

Även $R_B < 87,8 \text{ k}\Omega$ ger bottnad transistor

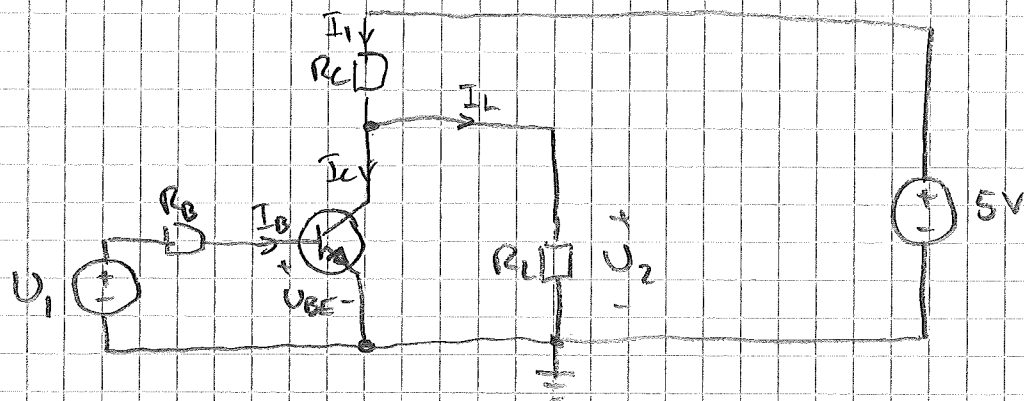K
(5)

$$R_C = 1 \text{ k}\Omega \quad R_B = 100 \text{ k}\Omega \quad R_L = 10 \text{ k}\Omega \quad h_{FE} = 100 \quad U_2 = 3 \text{ V} \quad U_{BE} = 0.7 \text{ V}$$

$$I_L = \frac{U_2}{R_L} = \frac{3}{10000} = 0.3 \text{ mA}$$

$$U_2 + R_C I_1 - 5 = 0 \Rightarrow$$


$$I_1 = \frac{5 - U_2}{R_C} = \frac{5 - 3}{1000} = 2 \text{ mA}$$

$$I_C = I_1 - I_L = 2 - 0.3 = 1.7 \text{ mA}$$

$$I_B = \frac{I_C}{h_{FE}} = \frac{1.7 \text{ mA}}{100} = 17 \text{ nA}$$

$$U_{BE} + R_B I_B - U_1 = 0 \Rightarrow$$

$$\underline{U_1 = U_{BE} + R_B I_B = 0.7 + 100 \cdot 10^3 \cdot 17 \cdot 10^{-9} = 2.4 \text{ V}}$$

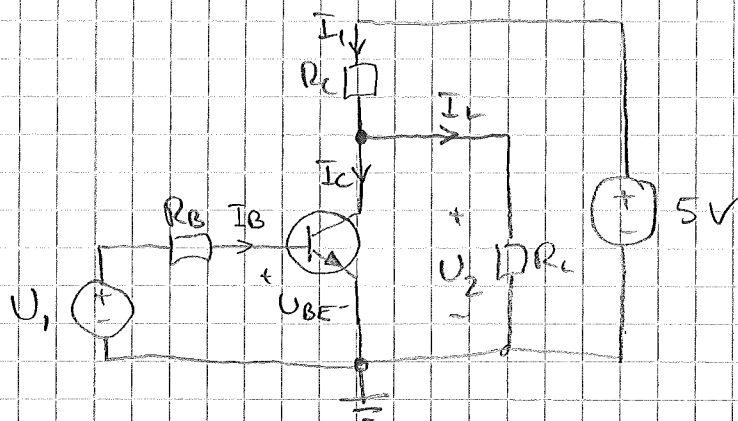K
⑥

$$R_C = 1k\Omega \quad R_L = 10k\Omega \quad U_1 = 5V \quad h_{FE} = 100 \quad U_{BE} = 0,7V$$

$$\text{Transistor bottenad} \Rightarrow U_2 = U_{CEsat} = 0,1V$$

$$I_L = \frac{U_2}{R_L} = \frac{0,1}{10000} = 10\mu A$$

$$U_2 + I_L R_C - 5 = 0 \Rightarrow$$

$$I_L = \frac{5 - U_2}{R_C} = \frac{5 - 0,1}{1000} = 4,90mA$$

$$I_C = I_L - I_L = 4,90mA - 10\mu A = 4,89mA$$

$$I_B = \frac{I_C}{h_{FE}} = \frac{4,89mA}{100} = 48,9\mu A$$


$$U_{BE} + R_B I_B - U_1 = 0 \Rightarrow$$

$$\underline{R_B} = \frac{U_1 - U_{BE}}{I_B} = \frac{5 - 0,7}{48,9 \cdot 10^{-6}} = \underline{87,9k\Omega}$$

Även lägre värde på R_B gör att transistor bottenar

K
⑦

36

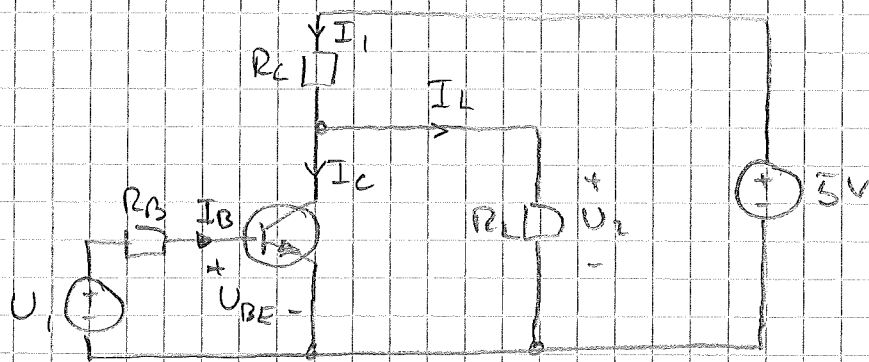

$$R_C = 1 \text{ k}\Omega \quad h_{FE} = 100 \quad U_{BE} = 0,7 \text{ V}$$

$$U_2 \geq 4,5 \text{ V} \quad \text{d.h.} \quad U_1 \leq 0,5 \text{ V}$$

$$U_1 \leq 0,7 \text{ V} \Rightarrow \text{Transistor stoppt} \Rightarrow I_B = 0 \Rightarrow I_C = 0$$

$$I_1 = \frac{5 - U_2}{R_C} = \frac{5 - 4,5}{1000} = 0,5 \text{ }\mu\text{A}$$

$$I_L = I_1 = 0,5 \text{ }\mu\text{A}$$

$$\underline{\underline{R_L = \frac{U_2}{I_L} = \frac{4,5}{0,5 \cdot 10^{-3}} = 9 \text{ k}\Omega}}$$

$$U_2 \leq 0,2 \text{ V} \quad \text{d.h.} \quad U_1 \geq 4,5 \text{ V}$$

$$U_1 > 0,7 \text{ V} \Rightarrow \text{Transistor leidet}$$


$$I_L = \frac{U_2}{R_L} = \frac{0,2}{9000} = 22,2 \text{ }\mu\text{A}$$

$$I_1 = \frac{5 - U_2}{R_C} = \frac{5 - 0,2}{1000} = 4,80 \text{ }\mu\text{A}$$

$$I_C = I_1 - I_L = 4,80 \text{ }\mu\text{A} - 22,2 \text{ }\mu\text{A} \approx 4,78 \text{ }\mu\text{A}$$

$$I_B = \frac{I_C}{h_{FE}} = \frac{4,78 \text{ }\mu\text{A}}{100} = 47,8 \text{ nA}$$

$$\underline{\underline{R_B = \frac{U_1 - U_{BE}}{I_B} = \frac{4,5 - 0,7}{47,8 \cdot 10^{-6}} = 79,5 \text{ k}\Omega}}$$

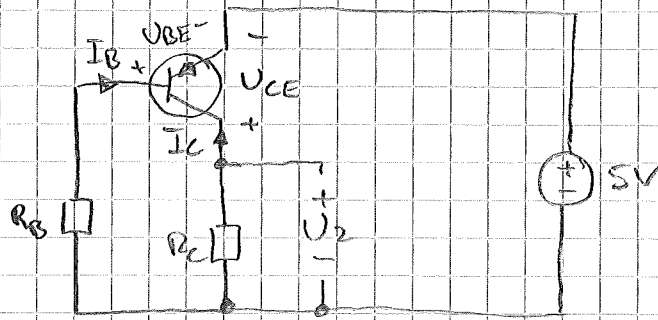K
8

$$R_C = 1 \text{ k}\Omega \quad h_{FE} = 100 \quad U_{BE} = -0,7 \text{ V} \quad U_{CEsat} = -0,1 \text{ V}$$

$$\text{Bottomed transistor} \Rightarrow U_{CE} = U_{CEsat} = -0,1 \text{ V}$$

$$5 + U_{CE} + I_C R_C = 0 \Rightarrow$$

$$I_C = \frac{-5 - U_{CE}}{R_C} = \frac{-5 - (-1)}{1000} = -4,9 \text{ mA}$$


$$I_B = \frac{I_C}{h_{FE}} = \frac{-4,9 \text{ mA}}{100} = -49 \mu\text{A}$$

$$5 + U_{BE} + R_B I_B = 0 \Rightarrow$$

$$\underline{\underline{R_B = \frac{-5 - U_{BE}}{I_B} = \frac{-5 - (-0,7)}{-49 \cdot 10^{-6}} = 87,7 \text{ k}\Omega}}$$

K
9

38

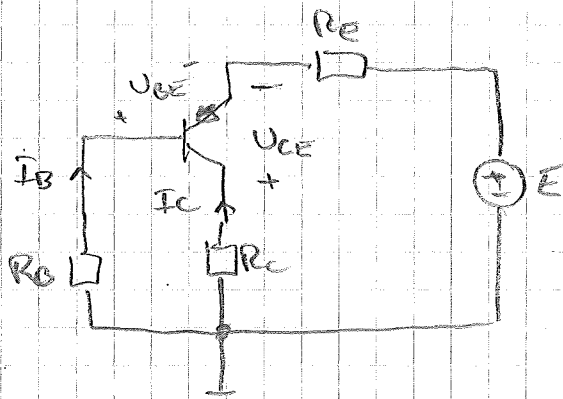

$$\begin{aligned} E &= 10V \\ R_E &= 1,2k\Omega \\ R_C &= 1,2k\Omega \\ h_{FE} &= 20 \\ U_{CE_{sat}} &= -0,1V \end{aligned}$$

a) $R_B = 0$

$$\begin{cases} -U_{BE} - (I_B + I_C)R_E - E = 0 & (1) \\ -I_C R_C - U_{CE} - (I_B + I_C)R_E - E = 0 & (2) \end{cases} \Rightarrow$$

$$U_{BE} = -0,7V$$

$$I_B = \frac{I_C}{h_{FE}}$$

$$\begin{aligned} (1) \quad I_C &= \frac{-U_{BE} - E}{R_E \left(1 + \frac{1}{h_{FE}}\right)} = \frac{0,7 - 10}{1200 \left(1 + \frac{1}{20}\right)} = -7,38 \mu A \\ (2) \quad U_{CE} &= -E - I_C \left\{ R_C + R_E \left(1 + \frac{1}{h_{FE}}\right) \right\} = 8,15V \end{aligned}$$

$U_{CE} > U_{CE_{sat}} \Rightarrow$ Transistor arbeitet

b)

$$\begin{cases} -R_B I_B - U_{BE} - (I_B + I_C)R_E - E = 0 & (1) \\ -I_C R_C - U_{CE} - (I_B + I_C)R_E - E = 0 & (2) \end{cases} \Rightarrow$$

$$U_{BE} = -0,7V$$

$$I_B = \frac{I_C}{h_{FE}} \quad \text{via both equations}$$

$$U_{CE} = -0,1V$$


$$(2) \quad I_C = \frac{-E - U_{CE}}{R_C + R_E \left(1 + \frac{1}{h_{FE}}\right)} = \frac{-10 + 0,1}{1200 + 1200 \left(1 + \frac{1}{20}\right)} = -4,02 \mu A$$

$$(1) \quad R_B = \frac{-E - U_{BE} - (I_B + I_C)R_E}{I_B} = \frac{-10 + 0,7 - 1200 \cdot (-4,1 \cdot 10^{-3}) \cdot \left(1 + \frac{1}{20}\right)}{\frac{-4,1 \cdot 10^{-3}}{20}} = 20,2 k\Omega$$

$\Rightarrow R_B < 20,2 k\Omega$

K
10

39

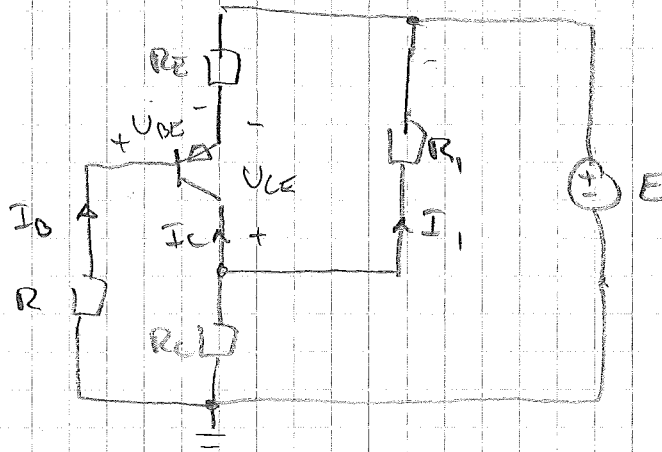

$$\begin{aligned} R_E &= 1 \text{ k}\Omega \\ R_E &= 200 \Omega \\ R_C &= 2 \text{ k}\Omega \\ h_{FE} &= 100 \\ E &= 12 \text{ V} \\ U_{BE} &= -0.7 \text{ V} \\ U_{CE_{sat}} &= -0.1 \text{ V} \\ U_{CE} &= -6 \text{ V} \end{aligned}$$

$$\begin{cases} -(I_C + I_B)R_C - U_{CE} - (I_C + I_B)R_E - E = 0 & (1) \\ -(I_C + I_B)R_C - I_B R_E - E = 0 & (2) \end{cases} \Rightarrow$$

$$(2) \quad \left\{ \begin{aligned} I_B &= \frac{-E - I_C R_C}{R_E + R_C} \quad \text{insatt. (1) ger:} \end{aligned} \right.$$

$$-I_C R_C + \frac{R_C}{R_E + R_C} \cdot E + \frac{R_C^2}{R_E + R_C} \cdot I_C - I_C \left(1 + \frac{1}{h_{FE}}\right) R_E - E - U_{CE} = 0$$

$$I_C = \frac{E \left(1 - \frac{R_C}{R_E + R_C}\right) + U_{CE}}{\frac{R_C^2}{R_E + R_C} - R_C - R_E \left(1 + \frac{1}{h_{FE}}\right)} = \frac{12 \cdot 0.667 + 6}{-869} = -2.31 \text{ mA}$$


$$-I_B R - U_{BE} - (I_B + I_C)R_E - E = 0$$

$$R = \frac{-U_{BE} - I_C \left(\frac{1}{h_{FE}} + 1\right) R_E - E}{\frac{I_C}{h_{FE}}} = \frac{0.7 + 2.31 \cdot 10^{-3} (1.01) \cdot 200 + 12}{- \frac{2.31 \cdot 10^{-3}}{100}} =$$

$$= 470 \text{ k}\Omega$$

K
111

(40)

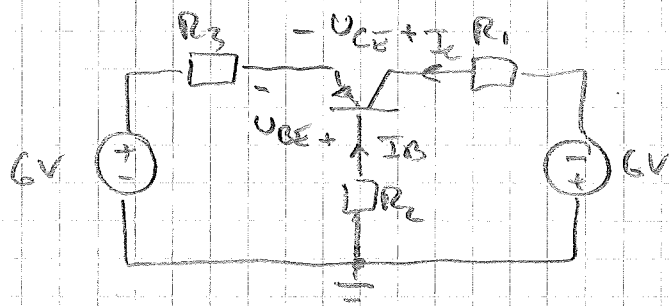

$$R_1 = R_2 = 1,8 \text{ k}\Omega$$

$$h_{FE} = 30$$

$$U_{CE} = -6 \text{ V}$$

$$U_{BE} = -0,7 \text{ V}$$


$$\begin{cases} 6 + (I_B + I_C)R_3 + U_{BE} + I_B R_2 = 0 & (1) \end{cases}$$

$$\begin{cases} 6 + (I_B + I_C)R_3 + U_{CE} + I_C R_1 + 6 = 0 & (2) \end{cases}$$

$$(2) \Rightarrow I_C = \frac{-12 - U_{CE}}{R_1 + R_3 \left(1 + \frac{1}{h_{FE}}\right)} = \frac{-12 + 6}{1800 + 1800 \left(1 + \frac{1}{30}\right)} = -1,658 \text{ mA}$$

$$(1) R_2 = \frac{-6 - U_{BE} - R_3 I_C \left(1 + \frac{1}{h_{FE}}\right)}{\frac{I_C}{h_{FE}}} = 411,4 \text{ k}\Omega$$

5.2

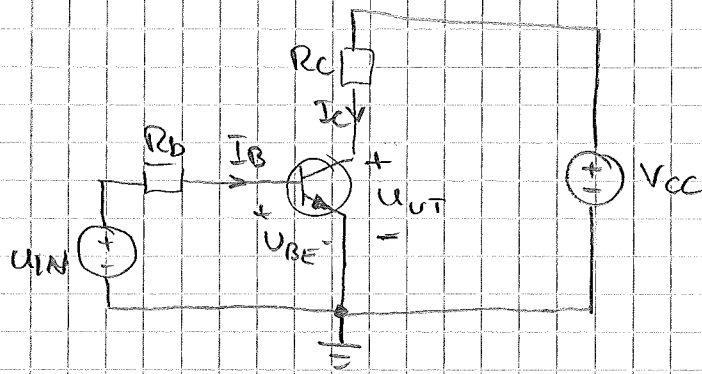

$$V_{CC} = 12V \quad u_{IN} = 1,0V \quad R_B = 22k\Omega \quad R_C = 1k\Omega$$

$$U_{BE} = 0,7V \quad h_{FE} = 250$$

$$U_{BE} + R_B I_B - u_{IN} = 0 \Rightarrow$$


$$I_B = \frac{u_{IN} - U_{BE}}{R_B} = \frac{1,0 - 0,7}{22 \cdot 10^3} = 13,6 \mu A$$

$$I_C = h_{FE} \cdot I_B = 250 \cdot 13,6 \mu A = 3,4 \text{ mA}$$


$$u_{UT} + R_C I_C - V_{CC} = 0 \Rightarrow$$

$$\underline{u_{UT}} = V_{CC} - R_C I_C = 12 - 1000 \cdot 3,4 \cdot 10^{-3} = \underline{8,6V}$$

5.3 | a) h_{FE} mkt stor. $\Rightarrow |I_C| = |I_E|$

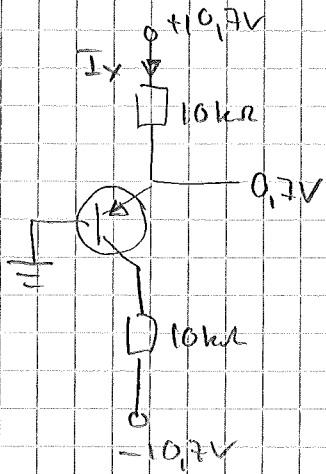

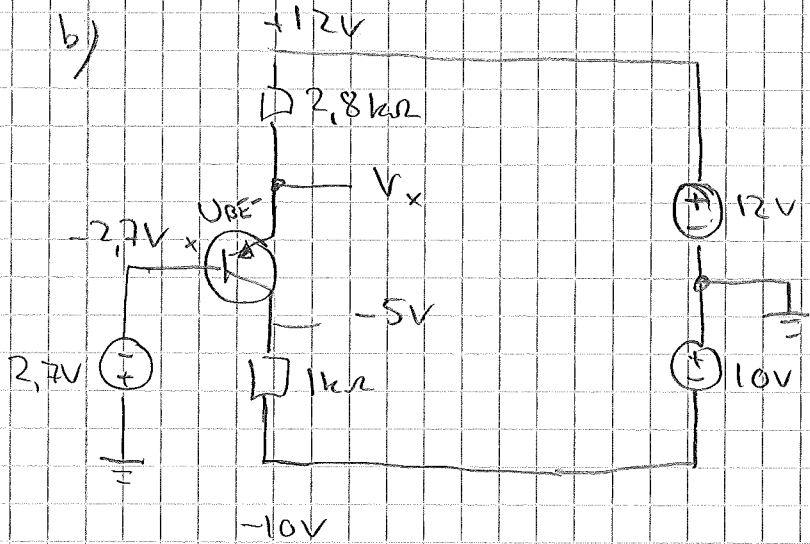
$$\underline{\underline{I_x = \frac{10.7 - 0.7}{10000} = 1 \mu A}}$$



Transistor leder $\Rightarrow \underline{\underline{V_x = -2.7 - U_{BE} = -2.7 - (-0.7) = -2.0V}}$

5.3 | c |

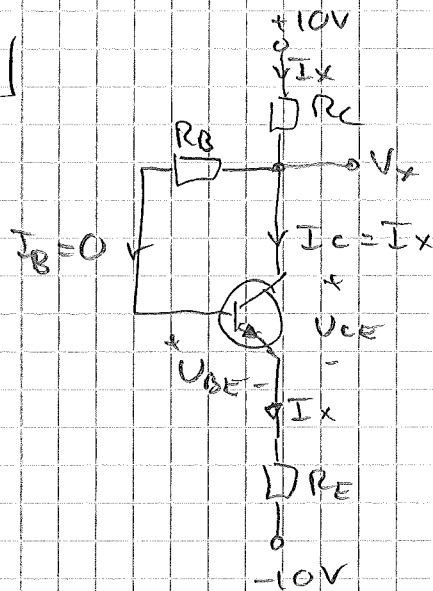

$$R_C = R_B = R_E = 10 \text{ k}\Omega$$

h_{FE} und β ster

$$V_{BE} = 0,7 \text{ V}$$


Ur. Folger $V_{CE} \geq V_{BE} \Rightarrow$ Transistor ej. bethead $\Rightarrow$

$$I_B = \frac{I_C}{h_{FE}} \approx 0 \text{ by } h_{FE} \text{ ster}$$

$$-10 + R_E I_x + V_{BE} + 0 \cdot R_B + R_C I_x = 10$$

$$\underline{I_x} = \frac{20 - V_{BE}}{R_E + R_C} = \frac{20 - 0,7}{20000} = \underline{0,965 \text{ mA}}$$
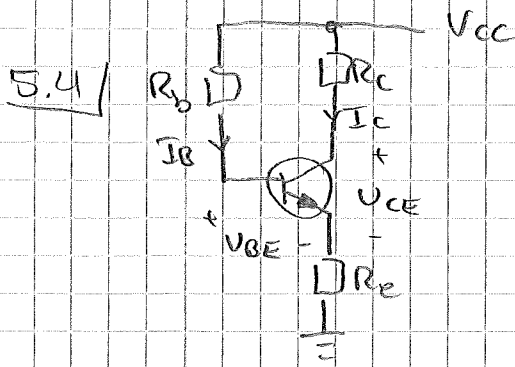
$$\underline{V_x} = 10 - R_C I_x = 10 - 10 \cdot 10^3 \cdot 0,965 \cdot 10^{-3} = \underline{0,35 \text{ V}}$$



$$V_{CC} = 6V$$

$$R_b = 200k\Omega$$

$$R_c = 1,5k\Omega$$

$$R_e = 1k\Omega$$

$$U_{BE} = 0,7V$$

$$U_{CEsat} = 0,2V$$

$$\begin{cases} R_e(I_B + I_C) + U_{CE} + R_c I_C = V_{CC} & (2) \\ R_e(I_B + I_C) + U_{BE} + R_b I_B = V_{CC} & (1) \end{cases} \quad \text{Byt ordering}$$

$$\begin{cases} I_B = \frac{I_C}{h_{FE}} \\ U_{BE} = 0,7V \end{cases}$$

$$\begin{cases} R_e I_C \left(1 + \frac{1}{h_{FE}}\right) + U_{CE} + R_c I_C = V_{CC} & (2) \\ R_e I_C \left(1 + \frac{1}{h_{FE}}\right) + U_{BE} + R_b \frac{I_C}{h_{FE}} = V_{CC} & (1) \end{cases} \quad \text{Byt ordering}$$

$$(1) \Rightarrow I_C = \frac{V_{CC} - U_{BE}}{R_e \left(1 + \frac{1}{h_{FE}}\right) + \frac{R_b}{h_{FE}}}$$

$$(2) \Rightarrow U_{CE} = V_{CC} - I_C \left(R_c + R_e \left(1 + \frac{1}{h_{FE}}\right) \right)$$

a) $h_{FE} = 100$

$$\underline{I_C} = \frac{6 - 0,7}{1000 \left(1 + \frac{1}{100}\right) + \frac{200 \cdot 10^3}{100}} = \underline{1,76 \mu A}$$

$$\underline{U_{CE}} = 6 - 1,76 \cdot 10^{-3} \left(1500 + 1000 \left(1 + \frac{1}{100}\right) \right) = \underline{1,58V}$$

b) $h_{FE} = 200$

$$I_C = \frac{6 - 0,7}{1000 \left(1 + \frac{1}{200}\right) + \frac{200 \cdot 10^3}{200}} = 2,64 \mu A$$

$$U_{CE} = 6 - 2,64 \cdot 10^{-3} \left(1500 + 1000 \left(1 + \frac{1}{200}\right) \right) = -0,61V$$

$U_{CE} < U_{CEsat} \Rightarrow$ Transistor bottomed
 (3) gatter es

5.4 Fertigkeiten | b |

Bipolar Transistor

$$\underline{U_{CE} = U_{CEsat} = 0,2V}$$

$$\begin{cases} R_e(I_B + I_C) + U_{CE} + R_c I_C = V_{CC} & (2) \\ R_e(I_B + I_C) + U_{BE} + R_b I_B = V_{CC} & (1) \\ U_{CE} = 0,2V \end{cases} \quad \uparrow \text{Byt}$$

Erlernen I_B

$$(1) \Rightarrow I_B = \frac{V_{CC} - U_{BE} - R_e I_C}{R_e + R_b} \quad \text{insert (2)}$$

$$\frac{R_e}{R_e + R_b} (V_{CC} - U_{BE} - R_e I_C) + R_e I_C + U_{CE} + R_c I_C = V_{CC}$$

$$I_C = \frac{V_{CC} - U_{CE} - \frac{R_e}{R_e + R_b} (V_{CC} - U_{BE})}{R_c + R_e - \frac{R_e^2}{R_e + R_b}} =$$

$$= \frac{6 - 0,2 - \frac{1k}{201k} (6 - 0,7)}{15 \cdot 10^3 + 10^3 - \frac{1000^2}{1500 + 200000}} = 2,3 \text{ mA}$$

5.5

$$a) I_B = - \frac{4,3}{450 \cdot 10^3} = -9,56 \mu A$$

$$I_C = - \frac{2}{2000} = -1 \text{ mA}$$

$$\underline{h_{FE}} = \frac{I_C}{I_B} = \underline{105}$$

$$b) I_B = - \frac{(4,3 - 2,3)}{20000} = 0,1 \text{ mA}$$

$$I_B + I_C = - \frac{2,3}{230} = -10 \text{ mA}$$

$$\Rightarrow I_C = -99 \text{ mA}$$

$$\underline{h_{FE}} = \frac{I_C}{I_B} = \underline{99}$$

$$c) \begin{cases} 8,3 + 150 \cdot 10^3 \cdot I_B + 1000 \cdot (I_B + I_C) = 0 \\ 9 - (I_C + I_B) 1000 = 10 \end{cases}$$

$$\Rightarrow I_C = \frac{-1 \pm 1000 I_B}{1000} = -I_B - 10^{-3}$$


$$8,3 + 150 \cdot 10^3 I_B + 1000 I_B - 1000 I_B - 1 = 0$$

$$I_B = \frac{-7,3}{150 \cdot 10^3} = -48,7 \mu A$$

$$I_C = -I_B - 10^{-3} = 48,7 \cdot 10^{-6} - 10^{-3} = -951 \mu A$$

$$\underline{h_{FE}} = \frac{I_C}{I_B} = \underline{19,5}$$

5.6

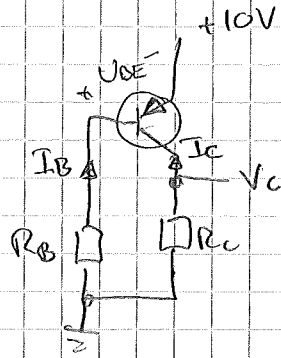

$$R_B = 100 \text{ k}\Omega$$

$$U_{BE} = -0,7 \text{ V}$$

$$-R_B I_B - U_{BE} = 10 \Rightarrow I_B = \frac{-U_{BE} - 10}{R_B} = \frac{0,7 - 10}{100 \cdot 10^3} = -93 \mu\text{A}$$


$$a) I_C = h_{FE} I_B = -50 \cdot 93 \mu\text{A} = -4,65 \text{ mA}$$

$$V_C = -R_C I_C \Rightarrow \underline{R_C} = -\frac{V_C}{I_C} = \frac{5}{4,65 \cdot 10^{-3}} = \underline{1075 \Omega}$$

$$b) I_C = h_{FE} \cdot I_B = -100 \cdot 93 \mu\text{A} = -9,3 \text{ mA}$$

$$\underline{V_C} = -R_C I_C = 1075 \cdot 9,3 \cdot 10^{-3} = \underline{10 \text{ V}} \text{ ca. transistor är } \text{bottnad.}$$

5.7

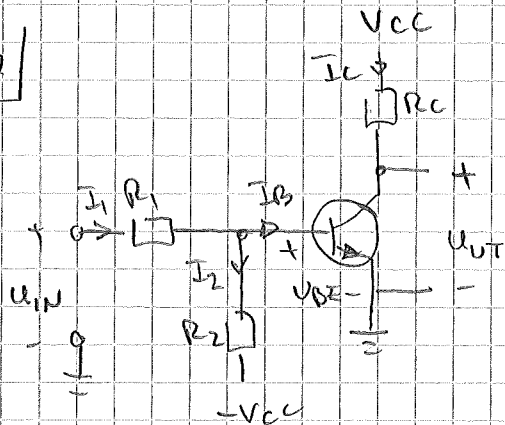

$$U_{BE} = 0,7 \text{ V}$$

$$U_{CEsat} = 0,2 \text{ V}$$

$$h_{FE} = 75$$

$$R_1 = 15 \text{ k}\Omega \quad R_2 = 100 \text{ k}\Omega \quad R_C = 2,2 \text{ k}\Omega$$

$$V_{CC} = 12 \text{ V}$$

$$U_{BE} - R_2 I_2 = -V_{CC} \Rightarrow$$

$$I_2 = \frac{V_{CC} + U_{BE}}{R_2} = \frac{12 + 0,7}{100 \cdot 10^3} = 127 \mu\text{A}$$

$$U_{BE} + R_1 I_1 = U_{IN} \Rightarrow$$

$$I_1 = \frac{U_{IN} - U_{BE}}{R_1} =$$

$$I_B = I_1 - I_2 = \frac{U_{IN}}{R_1} - \frac{0,7}{15000} - 127 \mu\text{A} = \frac{U_{IN}}{15000} - 174 \cdot 10^{-6}$$

5.7 Fort.


$$u_{UT} = V_{CC} - I_C R_C = V_{CC} - R_C h_{FE} \cdot I_B =$$

$$= 12 - R_C h_{FE} \left(\frac{u_{IN}}{15000} - 174 \cdot 10^{-6} \right) =$$


$$= 40,71 - 11 u_{IN} \quad \text{för } 0,2V \leq u_{UT} \leq 12V$$

$$12 = 40,71 - 11 u_{IN} \Rightarrow u_{IN} = 2,61V$$
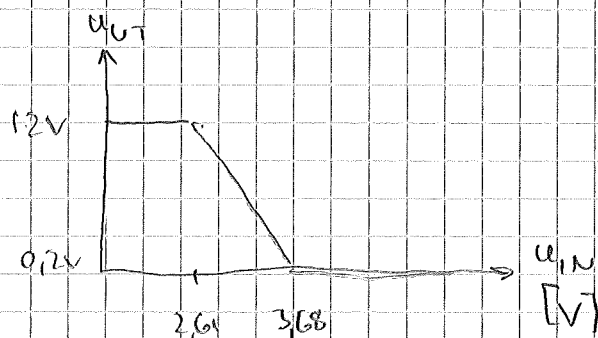
$$0,2 = 40,71 - 11 u_{IN} \Rightarrow u_{IN} = 3,68V$$



5.11

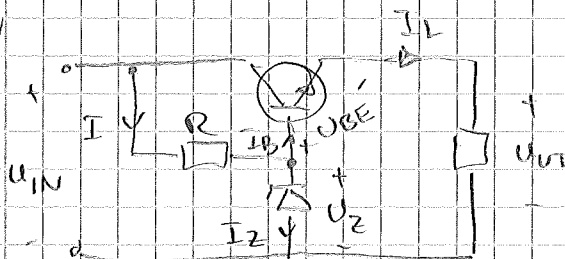

$$35 \leq u_{IN} \leq 45V$$

$$u_{UT} = 25V$$

$$0 \leq I_L \leq 500mA$$

$$U_{BE} = 0,6V \quad h_{FE} = 30$$

$$I_Z \geq 5mA$$

a) $\underline{U_Z = u_{UT} + U_{BE} = 25,6V}$

b) $I_{Bmax} = \frac{I_{Lmax}}{h_{FE}} = \frac{500mA}{30} = 16,7mA$

R ska alltid kunna ge strömen $I = I_{Bmax} + I_{Zmin} = 21,7mA$


$$\underline{R_{max} = \frac{u_{INmin} - U_Z}{I} = \frac{35 - 25,6}{21,7 \cdot 10^{-3}} = 433\Omega}$$

c) $\underline{P_{Lmax} = (u_{INmax} - u_{UT}) \cdot I_{Lmax} = (45 - 25,6) \cdot 0,5 = 9,7W}$

d) störst effekt i zener då I_L minimal och u_{IN} maximal

$$I_{Lmax} = \frac{u_{INmax} - u_Z}{R} = \frac{45 - 25,6}{433} = 44,8\mu A \quad P_{Zmax} = U_Z \cdot I_{Lmax} = 1,15W$$

5.12

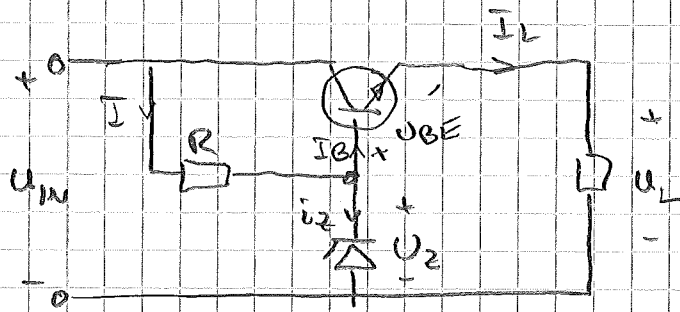

$$U_W = 20 \text{ V}$$

$$\text{Transistor: } U_{BE} = 0,7 \text{ V} \quad h_{FE} = 40 \quad P_{fmax} = 30 \text{ W}$$

$$\text{Zener: } U_Z = 11,0 \text{ V} \quad I_{Zmin} = 10 \text{ mA} \quad P_{Zmax} = 1,0 \text{ W}$$

$$R = 80 \, \Omega$$

$$U_L = U_Z - U_{BE} = 11,0 - 0,7 = \underline{\underline{10,3 \text{ V}}}$$

I_{Lmin} begränsas av hur mycket ström zenerdiad får

$$I_{Zmax} = \frac{P_{Zmax}}{U_Z} = \frac{1,0}{11,0} = 90,9 \text{ mA}$$

$$I = \frac{U_W - U_Z}{R} = \frac{20 - 11}{80} = 112,5 \text{ mA}$$

$$I_{Bmin} = I - I_{Zmax} = 112,5 - 90,9 = 21,6 \text{ mA}$$

$$\underline{\underline{I_{Lmin}}} = I_{Bmin} + I_C = I_{Bmin} (1 + h_{FE}) = 21,6 \cdot 10^{-3} (1 + 40) = \underline{\underline{0,886 \text{ A}}}$$

I_{Lmax} kan begränsas av P_{fmax} eller I_{Zmin}


$$P_{fmax} \approx (U_W - U_L) I_{Lmax} \Rightarrow \underline{\underline{I_{Lmax}}} = \frac{P_{fmax}}{U_W - U_L} = \frac{30}{9,7} = \underline{\underline{3,09 \text{ A}}}$$

$$I_{Bmax} = I - I_{Zmin} = 112,5 - 10 = 102,5 \text{ mA}$$

$$I_{Lmin} = I_{Bmax} (1 + h_{FE}) = 102,5 \cdot 10^{-3} (1 + 40) = 4,2 \text{ A}$$

$$P_{fmax} \text{ begränsar } \Rightarrow \underline{\underline{0,886 \text{ A} \leq I_L \leq 3,09 \text{ A}}}$$

5.17

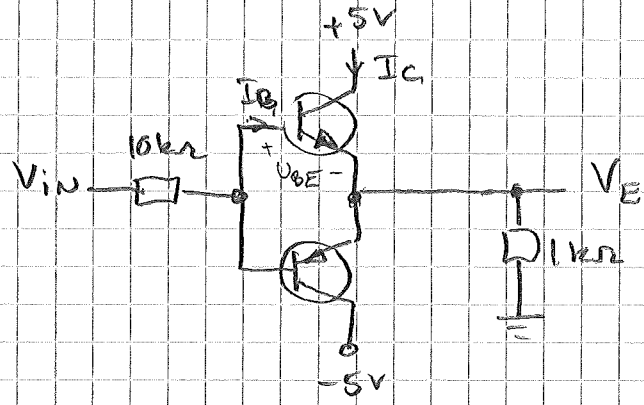

$$\beta = h_{FE} = 100$$

$$|U_{BE}| = 0,7V$$

a) $V_{IN} = 0 \Rightarrow$ Båda transistorer spärrar $\Rightarrow V_E = 0$

b) $V_{IN} = +3V \Rightarrow$ NPN leder PNP spärrar

$$\begin{cases} 3 - 10 \cdot 10^3 I_B - U_{BE} - (I_B + I_C) \cdot 10^3 = 0 \\ I_C = h_{FE} \cdot I_B \end{cases} \Rightarrow$$


$$3 - U_{BE} - 10 \cdot 10^3 I_B - I_B (1 + h_{FE}) \cdot 10^3 = 0$$

$$I_B = \frac{3 - U_{BE}}{10 \cdot 10^3 + (1 + h_{FE}) \cdot 10^3} = \frac{3 - 0,7}{10 \cdot 10^3 + 101 \cdot 10^3} = 20,72 \mu A$$

$$V_E = (I_B + I_C) \cdot 1k\Omega = I_B (1 + h_{FE}) \cdot 10^3 = 20,72 \cdot 10^{-6} \cdot (101) \cdot 10^3 = 2,09V$$

c)

S.18

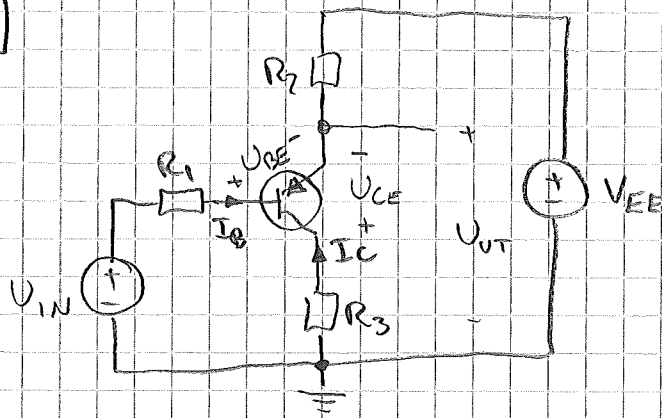

$$V_{EE} = 10V$$

$$R_1 = 15k\Omega$$

$$R_2 = R_3 = 1k\Omega$$

$$U_{BE} = -0,7V$$

$$U_{CEsat} = 0V$$

$$h_{FE} = 25$$

$$U_{IN} - R_1 I_B - U_{BE} - R_2 (I_B + I_C) - V_{EE} = 0 \quad (1)$$

$$V_{EE} + R_2 (I_B + I_C) + U_{CE} + R_3 I_C = 0 \quad (2)$$

$$\text{ur } (1) \quad U_{IN} - R_1 \frac{I_C}{h_{FE}} - U_{BE} - R_2 I_C \left(1 + \frac{1}{h_{FE}}\right) - V_{EE} = 0$$

$$I_C = \frac{U_{IN} - U_{BE} - V_{EE}}{\frac{R_1}{h_{FE}} + R_2 \left(1 + \frac{1}{h_{FE}}\right)} \quad (3)$$

$$\text{ur } (2) \quad U_{CE} = -V_{EE} - I_C \left(R_3 + R_2 \left(1 + \frac{1}{h_{FE}}\right)\right) \quad (4)$$

$$a) \quad U_{IN} = 7,5V$$

$$\text{ur } (3) \quad I_C = \frac{7,5 - (-0,7) - 10}{\frac{15000}{25} + 1000 \left(1 + \frac{1}{25}\right)} = -1,10 \text{ mA}$$

$$\underline{U_{UT}} = V_{EE} + R_2 (I_C + I_B) = V_{EE} + R_2 I_C \left(1 + \frac{1}{h_{FE}}\right) = 10 + 1000 \cdot (-1,10 \cdot 10^{-3}) \left(1 + \frac{1}{25}\right) = \underline{8,86V}$$

5.18b)

$$U_{CE} = 0$$

$$\begin{aligned} \text{Ur } \textcircled{1} \quad I_C &= \frac{-V_{EE} - U_{CE}}{R_3 + R_2 \left(1 + \frac{1}{h_{FE}}\right)} = \\ &= \frac{+10 - 0}{1000 + 1000 \left(1 + \frac{1}{25}\right)} = -4,90 \text{ mA} \end{aligned}$$

$$\begin{aligned} \text{Ur } \textcircled{1} \quad \underline{\underline{U_{IN}}} &= V_{EE} + U_{CE} + I_C \left(\frac{R_1}{h_{FE}} + R_2 \left(\frac{1}{h_{FE}} + 1 \right) \right) = \\ &= 10 - 0,7 - 4,90 \cdot 10^{-3} \left(\frac{15000}{25} + 1000 \left(\frac{1}{25} + 1 \right) \right) = \\ &= \underline{\underline{1,26 \text{ V}}} \end{aligned}$$


7.1 a) $A_p = \frac{P_{out}}{P_{in}} = \frac{230 \cdot 10^{-3}}{1,3 \cdot 10^{-6}} = 177\,000$

b) $A_p = \frac{P_{out}}{P_{in}} = \frac{600 \cdot 10^{-3}}{265 \cdot 10^{-9}} = 2,3 \cdot 10^6$

7.2 a) $|A_v| = \frac{|U_{out}|}{|U_{in}|} = \frac{50 \cdot 10^{-3}}{2 \cdot 10^{-3}} = 25$

b) $|A_v| = \frac{|U_{out}|}{|U_{in}|} = \frac{12 \cdot 10^{-3}}{15 \cdot 10^{-3}} = 0,8$

7.6

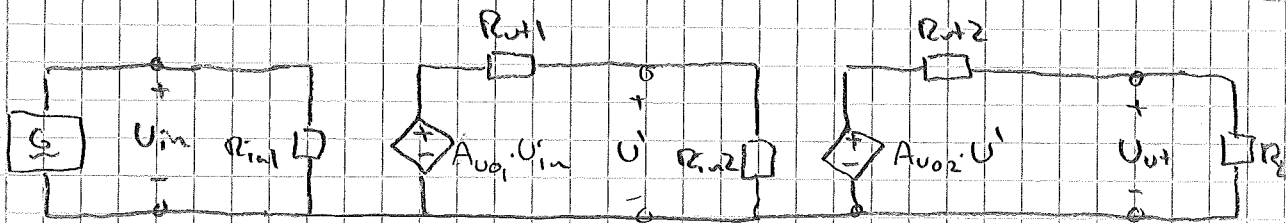

$R_{in1} = 800\,\Omega$ $A_{vo1} = 100$ $R_{out1} = 1,2\,k\Omega$ $R_{in2} = 350\,\Omega$ $A_{vo2} = 150$

$R_{out2} = 880\,\Omega$

a) $R_L = 1,3\,k\Omega$

$$\begin{cases} U_{out} = \frac{R_L}{R_L + R_{out2}} \cdot A_{vo2} \cdot U' \\ U' = \frac{R_{in2}}{R_{in2} + R_{out1}} \cdot A_{vo1} \cdot U_{in} \end{cases} \Rightarrow$$

$$U_{out} = \frac{R_L}{R_L + R_{out2}} \cdot A_{vo2} \cdot \frac{R_{in2}}{R_{in2} + R_{out1}} \cdot A_{vo1} \cdot U_{in}$$

$$\underline{\underline{A_v = \frac{U_{out}}{U_{in}} = \frac{R_L}{R_L + R_{out2}} \cdot A_{vo2} \cdot \frac{R_{in2}}{R_{in2} + R_{out1}} \cdot A_{vo1} = 1}} \quad (1)$$

$$= \frac{1300}{1300 + 880} \cdot 150 \cdot \frac{350}{350 + 1200} \cdot 100 = \underline{\underline{2020}}$$

7.6 b.) U_r ①

54

$$2500 = \frac{R_L}{R_L + 880} \cdot 150 \cdot \frac{350}{350 + 1200} \cdot 100$$

$$0,738 = \frac{R_L}{R_L + 880}$$

$$0,738 R_L + 649,5 = R_L$$

$$R_L = \frac{649,5}{1 - 0,738} = 2479$$

Da R_L eher eher $A_v \Rightarrow \underline{\underline{R_L \geq 2479 \Omega}}$

c) $A_P = \frac{P_{out}}{P_{in}} = \frac{\frac{U_{ute}^2}{R_L}}{\frac{U_{ine}^2}{R_{in}}} = \left(\frac{U_{ute}}{U_{ine}} \right)^2 \cdot \frac{R_{in}}{R_L} = A_v^2 \cdot \frac{R_{in}}{R_L}$

U_r ① $A_v = \frac{R_L}{R_L + 880} \cdot 150 \cdot \frac{350}{350 + 1200} \cdot 100 = \frac{R_L}{R_L + 880} \cdot 3387$

$$\begin{aligned} A_P &= A_v^2 \cdot \frac{R_{in}}{R_L} = \left(\frac{R_L}{R_L + 880} \right)^2 \cdot 3387^2 \cdot \frac{800}{R_L} = \\ &= \frac{R_L}{(R_L + 880)^2} \cdot 9,177 \cdot 10^9 \end{aligned}$$

Geht $A_P \geq 60 \text{ dB} = 10^{\frac{60}{10}} = \underline{\underline{10^6}}$ $\underline{\underline{A_P \geq 10^6}}$

Nahme grenen da $A_P = 10^6$

$$10^6 = \frac{R_L}{(R_L + 880)^2} \cdot 9,177 \cdot 10^9$$

$$(R_L + 880)^2 = R_L \cdot 9177$$

$$R_L^2 - 7417 R_L + 774400 = 0$$

7.6. c) Ants

55

$$R_L = \frac{7417}{2} \pm \sqrt{\left(\frac{7417}{2}\right)^2 - 774400} =$$

$$= \begin{cases} 7311 \Omega \\ 106 \Omega \end{cases}$$


Max effektförstärkning fås vid effektanpassning

d v s $R_L = R_{ut2} = 880 \Omega \Rightarrow$

$$A_p > 10^6 \quad \text{d s} \quad \underline{\underline{106 \Omega < R_L < 7311 \Omega}}$$

7.8

56

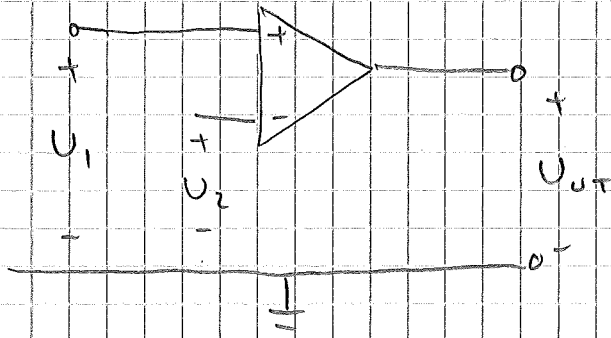

$$\textcircled{1} \quad U_{UT} = A_{UCM} \cdot U_{CM} + A_{UDM} \cdot U_{DM} \quad U_{CM} = \frac{U_1 + U_2}{2} \quad U_{DM} = U_1 - U_2$$

Messung 1 $U_{CM} = \frac{6,02 + 5,98}{2} = 6,0 \text{ V}$

$$U_{DM} = 6,02 - 5,98 = 0,04 \text{ V}$$

$$U_{UT} = 4,12 \text{ V}$$

Messung 2 $U_{CM} = \frac{0,03 - 0,03}{2} = 0$

$$U_{DM} = 0,03 - (-0,03) = 0,06 \text{ V}$$

$$U_{UT} = 6,00 \text{ V}$$

Messungen insatt i ① ger

$$\begin{cases} 6,0 A_{UCM} + 0,04 A_{UDM} = 4,12 \\ 0 \cdot A_{UCM} + 0,06 A_{UDM} = 6,00 \end{cases}$$

$$\Rightarrow \begin{cases} A_{UDM} = 100 \\ A_{UCM} = 0,02 \end{cases}$$


$$\underline{\underline{CMRR = 20 \log \left| \frac{A_{UDM}}{A_{UCM}} \right| = 20 \log \left| \frac{100}{0,02} \right| = \underline{\underline{74 \text{ dB}}}}}$$

9.1


Komparator

$$U_{UT} = +15V \quad \text{d\u00e4} \quad u_{in} < 2V$$
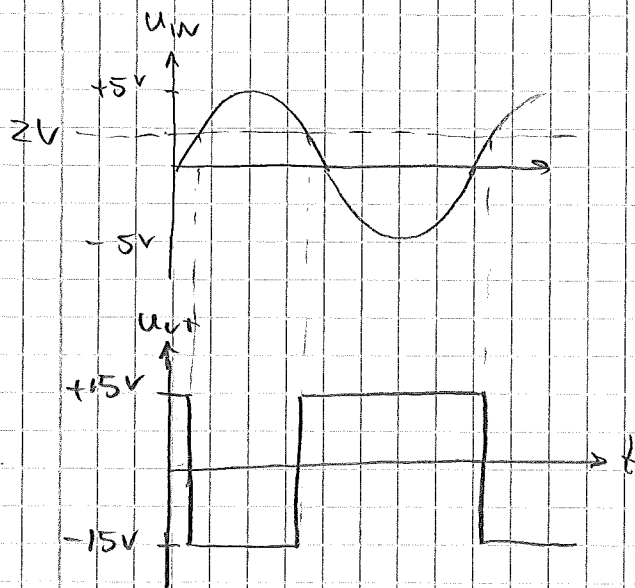
$$U_{UT} = -15V \quad \text{d\u00e4} \quad u_{in} > 2V$$



9.2

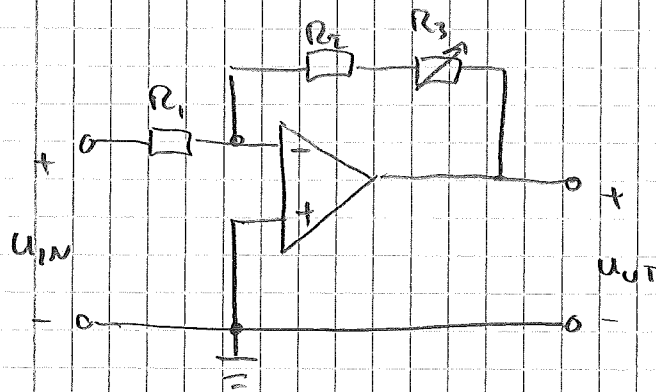

Invertierende Kopplung $\Rightarrow A_v = - \frac{R_2 + R_3}{R_1}$

$$|A_v| = \frac{R_2 + R_3}{R_1}$$

$$\underline{|A_v|_{\min}} = \frac{2200 + 0}{2200} = \underline{\underline{1}}$$

$$\underline{|A_v|_{\max}} = \frac{2200 + 100000}{2200} = \underline{\underline{46,5}}$$

9.3/


Iche - invertierende Kopplung

58

$$A_u = \frac{10R + R}{R} = 11$$

$$\underline{u_{UT}} = A_u \cdot u_{IN} = 11 \cdot 200 \text{ mV} = \underline{\underline{2,2 \text{ V}}}$$

9.4/

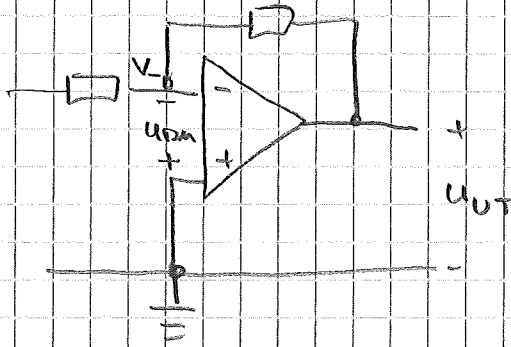

$$A_{uo} = 10000$$

$$u_{UT} = A_{uo} \cdot u_{DM} \Rightarrow$$

$$u_{DM} = \frac{u_{UT}}{A_{uo}}$$

$$V_- = -u_{DM} = -\frac{u_{UT}}{A_{uo}}$$

$$\text{Max } V_- \Rightarrow \underline{\underline{V_-}} = -\frac{u_{UT\text{min}}}{A_{uo}} = -\frac{-12}{10000} = \underline{\underline{1,2 \text{ mV}}}$$

9.5


Icke inverterande koppling

59


$$A_u = \frac{R_1 + R_2}{R_1} = \frac{1 + 30}{1} = 31$$

Förstärkaren överstyrs så

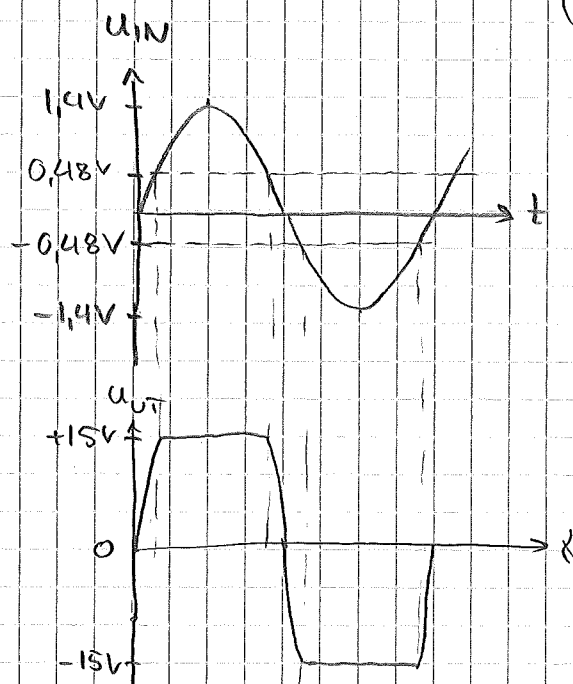
$$\left\{ \begin{aligned} u_{in} &= \frac{u_{outmax}}{A_u} = \frac{15}{31} = 0,48 \text{ V} \\ u_{in} &= \frac{u_{outmin}}{A_u} = \frac{-15}{31} = -0,48 \text{ V} \end{aligned} \right.$$



9.6 Icke Inverterande koppling

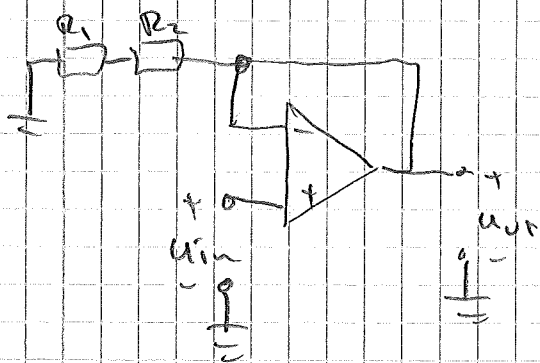
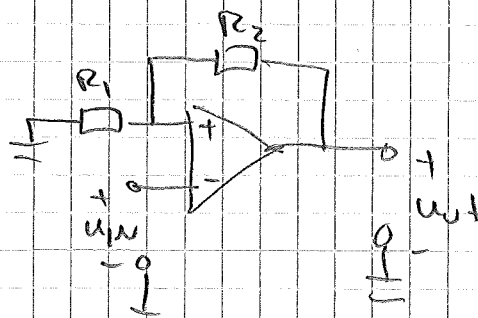
$$\underline{A_{u_{min}}} = \frac{0 + (R_1 + R_2)}{R_1 + R_2} = 1$$




$$R_1 = 100 \Omega$$

$$R_2 = 10 \text{ k}\Omega$$

$$\underline{A_{u_{max}}} = \frac{R_1 + R_2}{R_1} = \frac{100 + 10000}{100} = 101$$

9.10

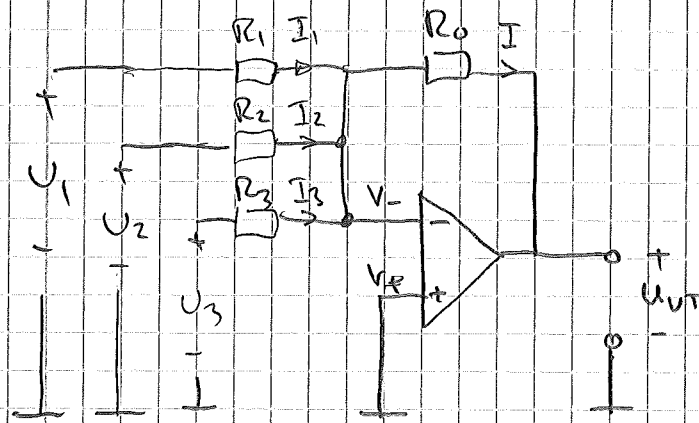

60


Idea OP negativt återkopplad: $V_- = V_+ = 0$

$$I = I_1 + I_2 + I_3 = \frac{U_1}{R_1} + \frac{U_2}{R_2} + \frac{U_3}{R_3}$$

$$\underline{U_{out}} = -R_0 \cdot I = -\left(\frac{R_0}{R_1} U_1 + \frac{R_0}{R_2} U_2 + \frac{R_0}{R_3} U_3\right) =$$

$$= -\left(\frac{10k}{5k} \cdot 1,2V + \frac{10k}{10k} \cdot (-3,5V) + \frac{10k}{20k} \cdot 2,8V\right) = \underline{\underline{-0,3V}}$$

9.11

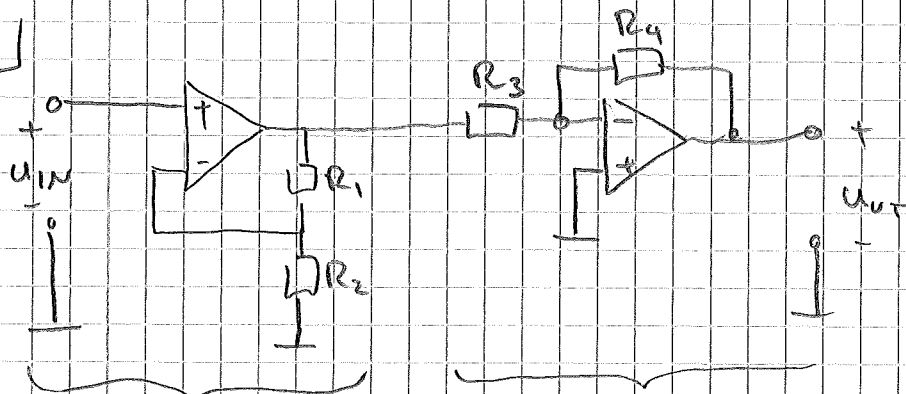

Icke invertande


$$A_{u1} = \frac{R_1 + R_2}{R_2}$$

Invertande

$$A_{u2} = -\frac{R_4}{R_3}$$

$$\text{Totalt } \underline{\underline{A_u}} = A_{u1} \cdot A_{u2} = -\frac{R_1 + R_2}{R_2} \cdot \frac{R_4}{R_3} = -\frac{39k + 22k}{2,2k} \cdot \frac{39k}{2,2k} = \underline{\underline{-332}}$$

9.14

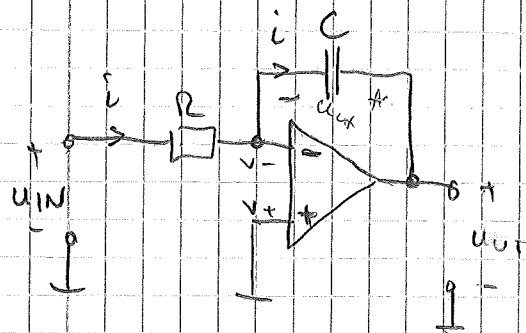

$$R = 1 \text{ k}\Omega$$

$$C = 1 \mu\text{F}$$

⑥

Ideal op. neg. återkopplad $\Rightarrow V_- = V_+ = 0$


$$i_+ \approx i_- = 0$$

$$i = \frac{u_{IN}}{R}$$

$$i = -C \frac{du_{UT}}{dt}$$

$$\Rightarrow \frac{du_{UT}}{dt} = -\frac{1}{RC} u_{IN} \Rightarrow$$
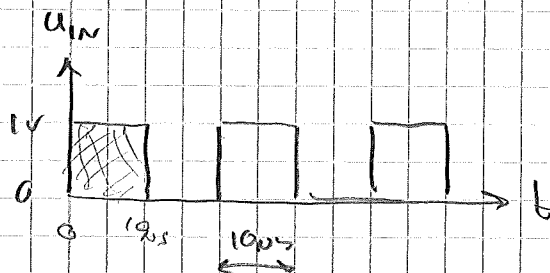
$$u_{UT} = -\frac{1}{RC} \int_{-\infty}^t u_{IN} dt$$



1 puls på $10 \mu\text{s}$ ändrar utsignalen

$$\Delta u_{UT} = -\frac{1}{RC} \int_0^{10 \mu\text{s}} 1 dt =$$

$$= -\frac{1}{RC} \cdot 10 \cdot 10^{-6} =$$


$$= -\frac{1}{10^3 \cdot 10^{-6}} \cdot 10 \cdot 10^{-6} = -0,01 \text{ V}$$

För att ändra utsignal 1 V

$$\text{krävs } \frac{1 \text{ V}}{0,01 \text{ V/puls}} = \underline{\underline{100 \text{ pulser}}}$$

9.17

62

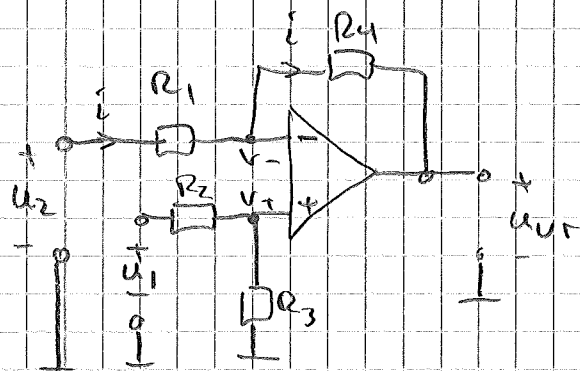

a) $R_1 = R_2 = 100 \Omega$
 $R_3 = R_4 = 100 \text{ k}\Omega$

FS $u_{UT} = \frac{R_4}{R_1} (u_2 - u_1)$

$A_{u_{DM}} = \frac{u_{UT}}{u_2 - u_1} = \frac{R_4}{R_1} = \frac{100 \cdot 10^3}{100} = \underline{\underline{1000}}$

b) $R_1 = 100 \Omega$ $R_2 = 98 \Omega$ $R_3 = 102 \text{ k}\Omega$ $R_4 = 100 \text{ k}\Omega$

Ideal OP neg. återkoppl. $V_+ = V_-$

$V_+ = \frac{R_3}{R_3 + R_2} \cdot u_1$ (1)

$\frac{u_2 - V_-}{R_1} = \frac{V_- + u_{UT}}{R_4} \Rightarrow V_- = \frac{R_4}{R_1 + R_4} u_2 + \frac{R_1}{R_1 + R_4} u_{UT}$ (2)

$V_+ = V_-$ ger

$\frac{R_3}{R_3 + R_2} \cdot u_1 - \frac{R_4}{R_1 + R_4} \cdot u_2 = \frac{R_1}{R_1 + R_4} u_{UT} \Rightarrow$

$0,99904 u_1 - 0,99900 u_2 = 0,000999 u_{UT}$

$u_{UT} = 1000,040 u_1 - 1000,000 u_2$

Or FS

$u_{UT} = A_{u_{DM}} u_{DM} + A_{u_{CM}} u_{CM} = A_{u_{DM}} (u_1 - u_2) + A_{u_{CM}} \frac{u_1 + u_2}{2}$
 $= \left(A_{u_{DM}} + \frac{A_{u_{CM}}}{2} \right) u_1 - \left(A_{u_{DM}} - \frac{A_{u_{CM}}}{2} \right) u_2$

9.12 parts 1

$$\text{ID} \begin{cases} A_{uom} + \frac{A_{ucm}}{2} = 1000,040 \\ A_{uom} - \frac{A_{ucm}}{2} = 1000,000 \end{cases}$$

(3)

(4)


$$(3) + (4) \Rightarrow A_{uom} = 1000,020$$

$$(3) - (4) \Rightarrow A_{ucm} = 0,040$$

$$\underline{\underline{CMRR}} = 20 \log \left| \frac{A_{uom}}{A_{ucm}} \right| = 20 \log \left| \frac{1000,020}{0,040} \right| = \underline{\underline{88 \text{ dB}}}$$

9.18

6A

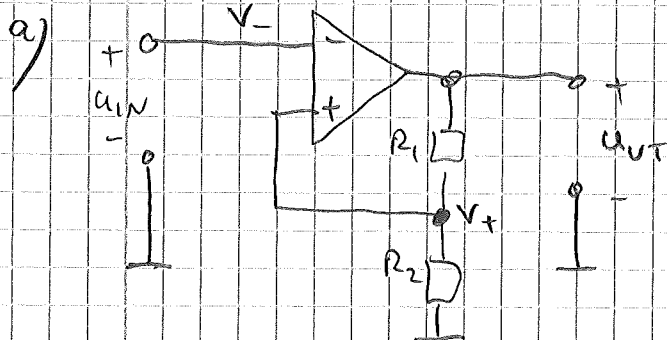

$$u_{UTmax} = +15V$$

$$u_{UTmin} = -15V$$

$$R_1 = 10k\Omega \quad R_2 = 1,5k\Omega$$

Anslag $u_{UT} = u_{UTmax} = +15V$

$$V_+ = \frac{R_2}{R_1 + R_2} \cdot u_{UTmax} = \frac{1,5k}{10k + 1,5k} \cdot 15V = \underline{\underline{1,96V}}$$


Övre
omslags
nivå

Anslag $u_{UT} = u_{UTmin} = -15V$

$$\underline{\underline{V_+ = \frac{R_2}{R_1 + R_2} \cdot u_{UTmin} = -1,96V}}$$

Undre
omslags
nivå

b)

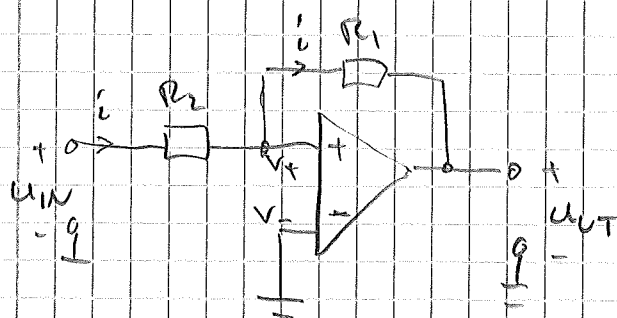

$$R_1 = 10k\Omega$$

$$R_2 = 1,5k\Omega$$

Slår om så $V_+ = V_-$. I följande $\underline{\underline{V_- = 0}}$

Undre omslagsnivå

Anslag $u_{UT} = u_{UTmax} = +15V$

$$u_{UT} = -R_1 \cdot i = -R_1 \cdot \frac{u_{in}}{R_2} \Rightarrow$$

$$\underline{\underline{u_{in} = -\frac{R_2}{R_1} u_{UT} = -\frac{R_2}{R_1} u_{UTmax} = -\frac{1,5}{10} \cdot 15 = -2,25V}}$$


Övre omslagsnivå

Anslag $u_{UT} = u_{UTmin} = -15V$

$$\underline{\underline{u_{in} = -\frac{R_2}{R_1} u_{UTmin} = \frac{1,5k}{10k} \cdot 15 = 2,25V}}$$

9.19

(5)

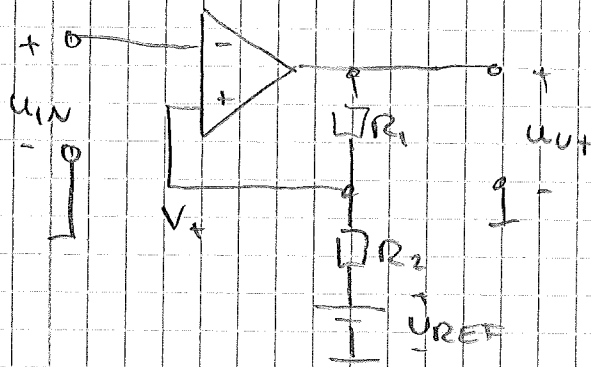

$$R_1 = 10 \text{ k}\Omega$$

$$u_{\text{OUTmax}} = 15 \text{ V}$$

$$u_{\text{OUTmin}} = -15 \text{ V}$$

Övre omslagssnivå +5V då $u_{\text{OUT}} = u_{\text{OUTmax}} = +15 \text{ V}$

$$V_+ = U_{\text{REF}} + (u_{\text{OUTmax}} - U_{\text{REF}}) \cdot \frac{R_2}{R_1 + R_2} \Rightarrow$$

$$5 = U_{\text{REF}} + (15 - U_{\text{REF}}) \cdot \frac{R_2}{R_1 + R_2} \quad (1)$$

Undre omslagssnivå +2V då $u_{\text{OUT}} = u_{\text{OUTmin}} = -15 \text{ V}$

$$V_+ = U_{\text{REF}} + (u_{\text{OUTmin}} - U_{\text{REF}}) \cdot \frac{R_2}{R_1 + R_2}$$

$$2 = U_{\text{REF}} + (-15 - U_{\text{REF}}) \cdot \frac{R_2}{R_1 + R_2} \quad (2)$$

Ur ① o ② lös ut $\begin{cases} U_{\text{REF}} = 3,89 \text{ V} \\ R_2 = 1,11 \text{ k}\Omega \end{cases}$