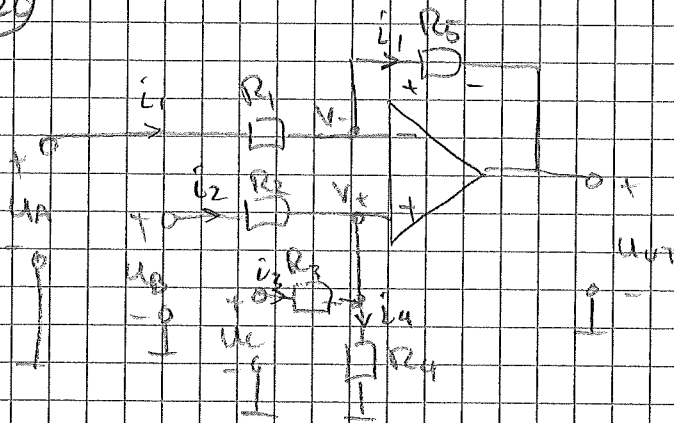


9.20

66



Bestimmen

Ideal OP negativt återkopplad $\Rightarrow V_- = V_+$

Bestimmen V_+

$$\text{KCL} \quad I_2 + I_3 = I_4 \quad \Rightarrow$$

$$\frac{U_B - V_+}{R_2} + \frac{U_C - V_+}{R_3} = \frac{V_+}{R_4} \quad \Rightarrow$$

$$\frac{U_B}{R_2} + \frac{U_C}{R_3} = \frac{V_+}{R_4} + \frac{V_+}{R_2} + \frac{V_+}{R_3} \quad \Rightarrow$$


$$V_+ = \frac{\frac{U_B}{R_2} + \frac{U_C}{R_3}}{\frac{1}{R_4} + \frac{1}{R_2} + \frac{1}{R_3}} = \frac{\frac{0,8}{10000} + \frac{1,2}{2200}}{\frac{1}{1500} + \frac{1}{10000} + \frac{1}{2200}} = 0,5122 \text{ V}$$

$$V_- = V_+ = 0,5122 \text{ V}$$

$$I_1 = \frac{4 \text{ A} - V_-}{R_1} = \frac{0,45 - 0,5122}{4700} = -13,23 \mu\text{A}$$


$$\underline{u_{U7}} = V_- - R_5 I_1 = 0,5122 - 8200 \cdot (-13,23 \cdot 10^{-6}) = \underline{0,62 \text{ V}}$$

9.22

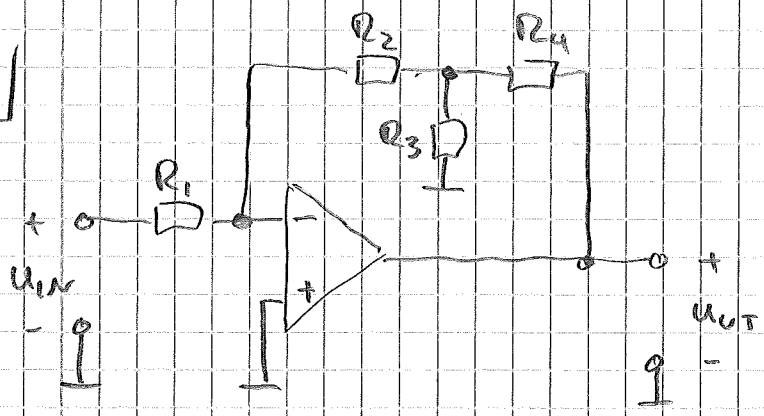

- $R_1 = 1 \text{ M}\Omega$
- $R_2 = 1 \text{ M}\Omega$
- $R_3 = 10 \text{ k}\Omega$
- $R_4 = 1 \text{ M}\Omega$

Stjärna-triangel transformering

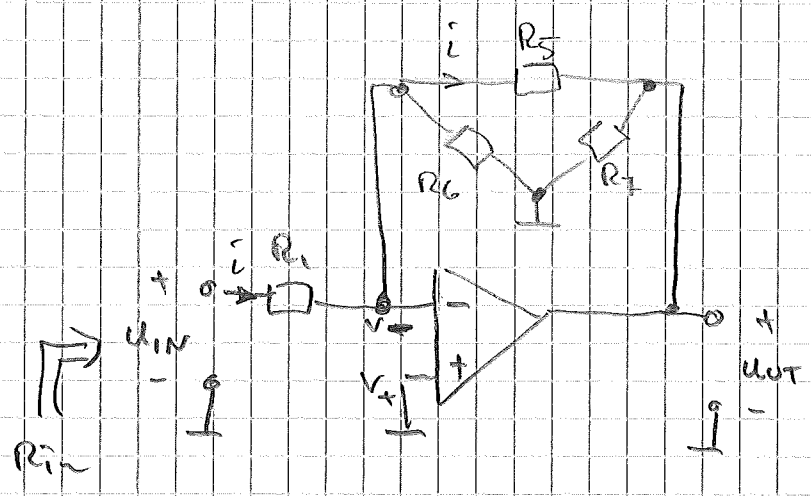

$$R_5 = R_2 + R_4 + \frac{R_2 \cdot R_4}{R_3} = 102 \text{ M}\Omega$$


Ideal OP neg återkopplad $V_- = V_+ = 0 \text{ V} \Rightarrow$
Ingen ström genom R_6 .

$$\begin{cases} i = \frac{u_{IN}}{R_1} \\ u_{OUT} = -R_5 \cdot i \end{cases} \Rightarrow u_{OUT} = -\frac{R_5}{R_1} \cdot u_{IN} \Rightarrow$$

a) $\underline{A_u} = \frac{u_{OUT}}{u_{IN}} = -\frac{R_5}{R_1} = -\frac{102 \text{ M}}{1 \text{ M}} = \underline{\underline{-102}}$

b) $\underline{R_{in}} = \frac{u_{IN}}{i} = \frac{u_{IN}}{\frac{u_{IN}}{R_1}} = R_1 = \underline{\underline{1 \text{ M}\Omega}}$

9.22

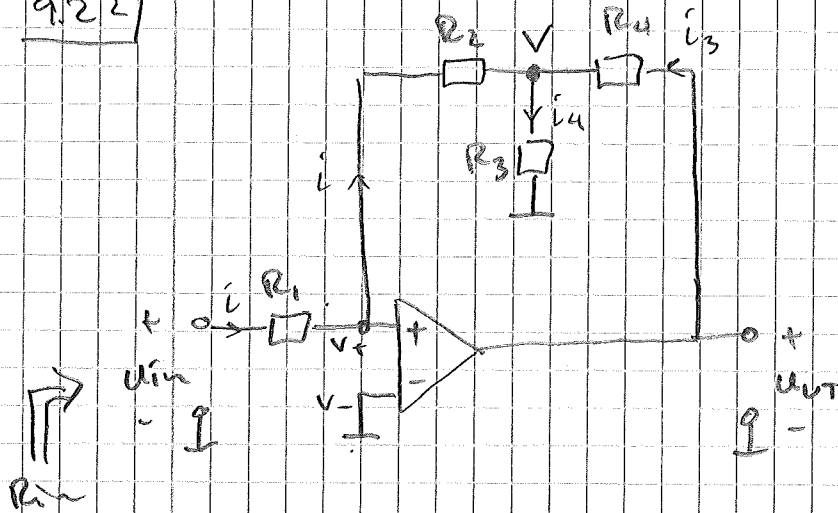

$$R_1 = R_2 = R_4 = 1\text{ M}\Omega$$

$$R_3 = 10\text{ k}\Omega$$

a) Ideal OP neg. återkoppl. $\Rightarrow V_+ = V_- = 0\text{ V}$

$$i = \frac{u_{in}}{R_1}$$

$$V = -R_2 \cdot i = -\frac{R_2}{R_1} \cdot u_{in}$$

KI $i + i_3 = i_4$

$$\frac{u_{in}}{R_1} + \frac{u_{out} - V}{R_4} = \frac{V}{R_3}$$

$$\frac{u_{out}}{R_4} = V \left(\frac{1}{R_4} + \frac{1}{R_3} \right) - \frac{u_{in}}{R_1}$$

$$\frac{u_{out}}{R_4} = \left\{ -\frac{R_2}{R_1} \left(\frac{1}{R_4} + \frac{1}{R_3} \right) - \frac{1}{R_1} \right\} \cdot u_{in}$$

$$\underline{\underline{A_u}} = \frac{u_{out}}{u_{in}} = -\frac{R_4}{R_1} \left(\frac{R_2}{R_4} + \frac{R_2}{R_3} + 1 \right) = -\frac{1\text{ M}}{1\text{ M}} \left(\frac{1\text{ M}}{1\text{ M}} + \frac{1\text{ M}}{10\text{ k}} + 1 \right) =$$

$$\underline{\underline{-102}}$$

b) $\underline{\underline{R_{in}}} = \frac{u_{in}}{i} = \frac{u_{in}}{\frac{u_{in}}{R_1}} = R_1 = \underline{\underline{1\text{ M}\Omega}}$

5.1 a)


$$I_1 - I_2 - I_3 - I_4 - J = 0$$

$$I_2 + I_5 - I_1 = 0$$

$$\hookrightarrow E_1 - R_1 I_1 - R_2 I_2 = 0$$

$$\hookrightarrow R_2 I_2 - R_3 I_3 + E_3 - R_5 I_5 = 0$$

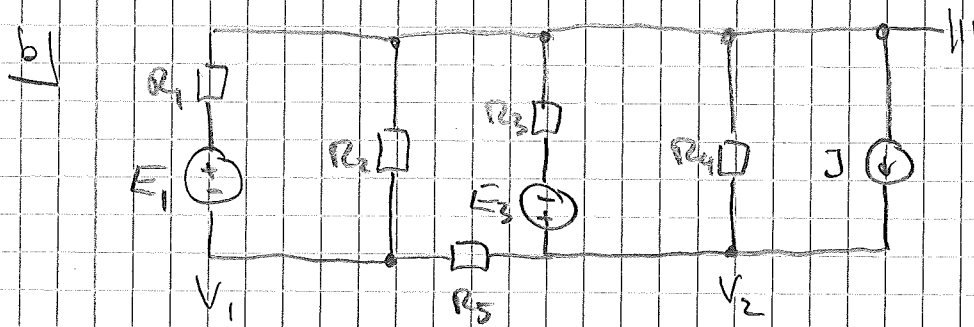
$$\hookrightarrow -E_3 + R_3 I_3 - R_4 I_4 = 0$$



$$\frac{V_1 + E_1}{R_1} + \frac{V_1}{R_2} + \frac{V_1 - V_2}{R_5} = 0$$


$$\frac{V_2 - V_1}{R_5} + \frac{V_2 - E_3}{R_3} + \frac{V_2}{R_4} - J = 0$$

5.1c

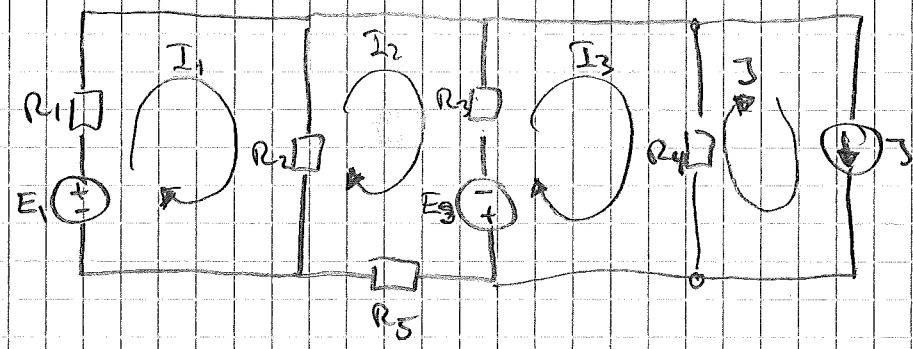

- 1) $E_1 - R_1 I_1 - R_2 (I_1 - I_2) = 0$
- 2) $-R_5 I_2 - R_2 (I_2 - I_1) - R_3 (I_2 - I_3) + E_3 = 0$
- 3) $-E_3 - R_3 (I_3 - I_2) - R_4 (I_3 - J) = 0$

5.3

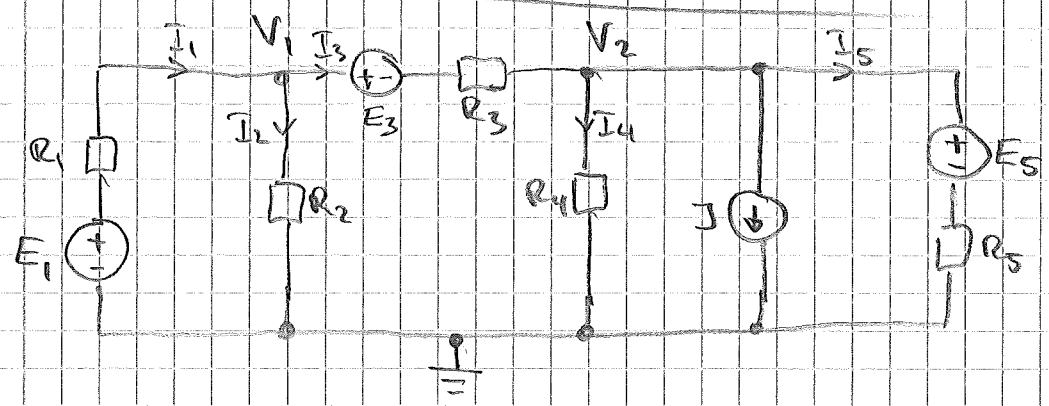

$$\begin{cases} \frac{V_1 - E_1}{R_1} + \frac{V_1}{R_2} + \frac{V_1 - E_3 - V_2}{R_3} = 0 \\ \frac{V_2 - (V_1 - E_3)}{R_3} + \frac{V_2}{R_4} + J + \frac{V_2 - E_5}{R_5} = 0 \end{cases} \Rightarrow$$

$$\begin{cases} V_1 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) + V_2 \left(-\frac{1}{R_3} \right) = \frac{E_3}{R_3} + \frac{E_1}{R_1} \\ -\frac{V_1}{R_3} + V_2 \left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} \right) = \frac{E_5}{R_5} - \frac{E_3}{R_3} - J \end{cases}$$

$$\begin{cases} 0,375 V_1 - 0,125 V_2 = 2,5 \\ -0,125 V_1 + 0,265 V_2 = -1,95 \end{cases} \quad \text{3x}$$

5.3) parts

70

$$0,67 V_2 = -3,35$$

$$\begin{cases} V_2 = -5,00 \text{ V} \\ V_1 = 5,00 \text{ V} \end{cases}$$

$$I_1 = \frac{E_1 - V_1}{R_1} = \frac{10 - 5}{5} = 1,00 \text{ A}$$


$$I_2 = \frac{V_1}{R_2} = \frac{5}{20} = 0,25 \text{ A}$$

$$I_3 = \frac{V_1 - E_3 - V_2}{R_3} = \frac{5 - 4 - (-5)}{8} = 0,75 \text{ A}$$

$$I_4 = \frac{V_2}{R_4} = \frac{-5}{25} = -0,2 \text{ A}$$

$$I_5 = \frac{V_2 - E_5}{R_5} = \frac{-5 - 4,5}{10} = -0,95 \text{ A}$$

5.6

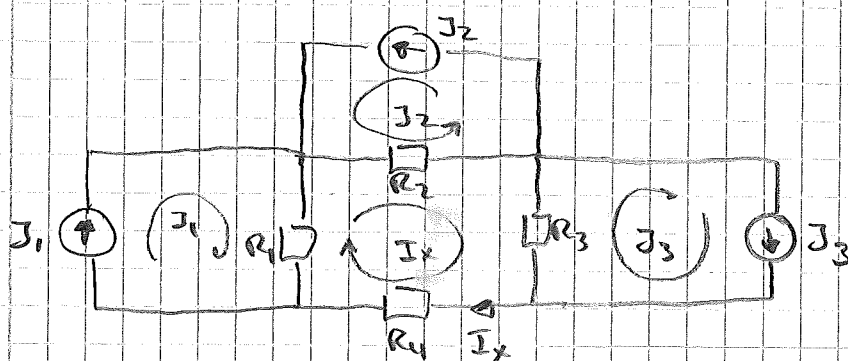


KV: $R_4 I_x + R_3 (I_x - J_3) + R_2 (I_x + J_2) + R_1 (I_x - J_1) = 0$

$$I_x (R_4 + R_3 + R_2 + R_1) = R_3 J_3 - R_2 J_2 + R_1 J_1$$

$$I_x = \frac{R_3 J_3 - R_2 J_2 + R_1 J_1}{R_1 + R_2 + R_3 + R_4} = \frac{3 \cdot 15 - 5 \cdot 11 + 2 \cdot 20}{(2 + 5 + 3 + 4) \cdot 10^3} =$$

$$= \underline{\underline{2,14 \text{ mA}}}$$

5.8

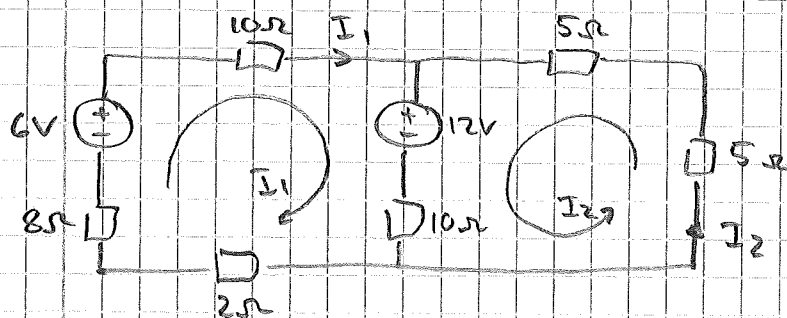

$\text{I} \quad \left\{ \begin{array}{l} 2I_1 + 10(I_1 + I_2) + 12 + 10I_1 - 6 + 8I_1 = 0 \end{array} \right.$

$\text{II} \quad \left\{ \begin{array}{l} 10(I_1 + I_2) + 12 + 5I_2 + 5I_2 = 0 \end{array} \right. \Rightarrow$


$$\left\{ \begin{array}{l} 30I_1 + 10I_2 = -6 \\ 10I_1 + 20I_2 = -12 \end{array} \right.$$

$$25I_1 = 0 \Rightarrow \underline{\underline{I_1 = 0}}$$

$$\underline{\underline{I_2 = \frac{-6}{10} = -0,6 \text{ A}}}$$

5.101

73

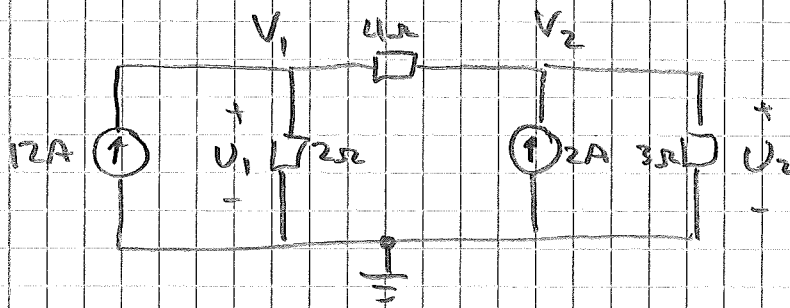

a)

$$\begin{cases} \frac{V_1}{2} - 12 + \frac{(V_1 - V_2)}{4} = 0 \\ \frac{V_2 - V_1}{4} - 2 + \frac{V_2}{3} = 0 \end{cases} \Rightarrow$$

$$\begin{cases} 0,75V_1 - 0,25V_2 = 12 \\ -0,25V_1 + 0,58333V_2 = 2 \end{cases} \begin{matrix} \times 3 \\ \times 3 \end{matrix}$$

$$1,5V_2 = 18$$


$$V_2 = 12V$$

$$\underline{V_1} = \frac{12 + 0,25V_2}{0,75} = \underline{20V}$$

$$\underline{U_1} = V_1 = \underline{20V}$$

$$\underline{U_2} = V_2 = \underline{12V}$$

b) Bidrag från 12A källa

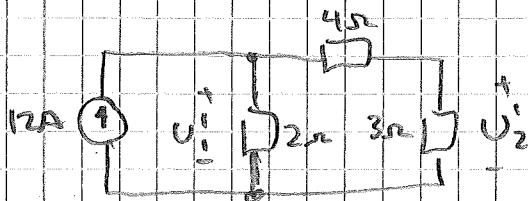

$$U_1' = 12 \cdot \left(\frac{2}{2+4} \right) = 12 \cdot 0,3333 = 4,0000V$$


$$U_2' = \frac{3}{3+4} \cdot U_1' = \frac{3}{7} \cdot 4,0000 = 1,7143V$$

5.10 b

fort

74

Bidrag från 2A källa

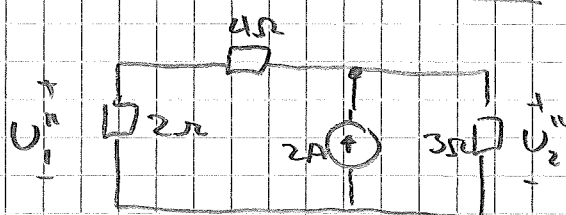

$$U_2'' = 2 \cdot (6 \parallel 3) = 2 \cdot 2 = 4,000 \text{ V}$$


$$U_1'' = \frac{2}{2+4} \cdot U_2'' = \frac{1}{3} \cdot 4 = 1,3333 \text{ V}$$

Totalt

$$U_1 = U_1' + U_1'' = 18,6667 + 1,3333 = \underline{\underline{20,0 \text{ V}}}$$

$$U_2 = U_2' + U_2'' = 8,0000 + 4,0000 = \underline{\underline{12,0 \text{ V}}}$$

5.11

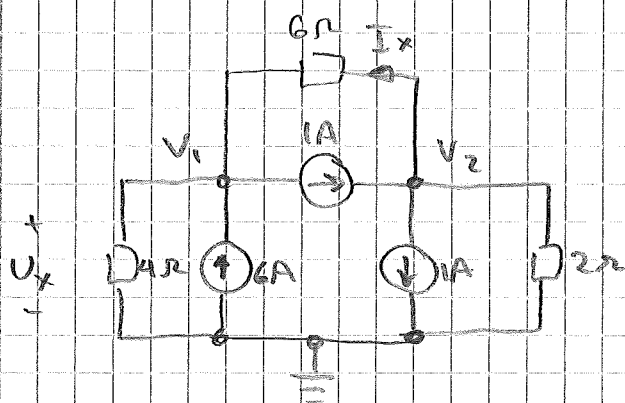

$$\begin{cases} \frac{V_1}{4} - 6 + 1 + \frac{(V_1 - V_2)}{6} = 0 \\ 1 - \frac{V_2}{2} - 1 + \frac{V_2 - V_1}{6} = 0 \end{cases} \Rightarrow \begin{cases} 2,5V_1 - V_2 = 30 \\ -V_1 + 4V_2 = 0 \end{cases} \quad (\times 4)$$

$$9V_1 = 120$$


$$V_1 = 13,33 \text{ V}$$

$$V_2 = \frac{V_1}{4} = 3,333 \text{ V}$$

$$U_x = V_1 = \underline{\underline{13,33 \text{ V}}}$$

$$I_x = \frac{V_2 - V_1}{6} = \frac{3,333 - 13,333}{6} = \underline{\underline{-1,67 \text{ A}}}$$

5.12/

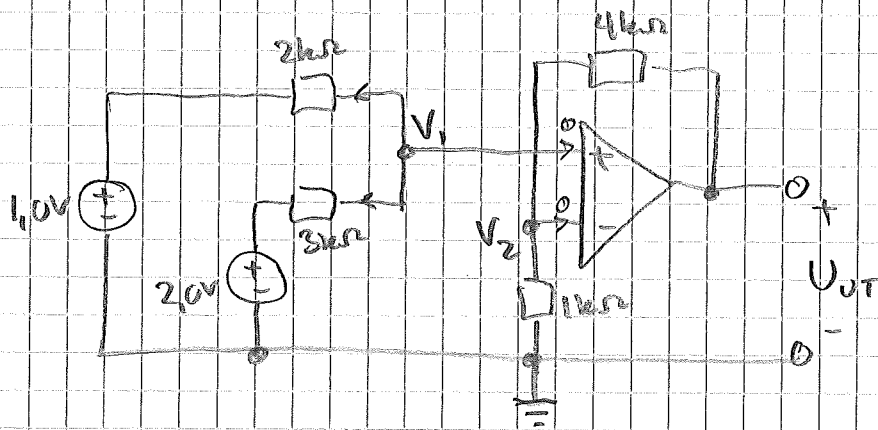

75

$$\left\{ \begin{array}{l} \frac{V_1 - 1}{2k} + \frac{V_1 - 2}{3k} = 0 \\ \frac{V_2 - U_{UT}}{4k} + \frac{V_2}{1k} = 0 \end{array} \right.$$



$$\left\{ \begin{array}{l} \frac{V_2 - U_{UT}}{4k} + \frac{V_2}{1k} = 0 \\ V_1 = V_2 \end{array} \right.$$


$V_1 = V_2$ Ideal OP negativ återkopplad

$$\left\{ \begin{array}{l} V_1 \left(\frac{1}{2k} + \frac{1}{3k} \right) = \frac{1}{2k} + \frac{2}{3k} \\ V_1 \left(\frac{1}{4k} + \frac{1}{1k} \right) = \frac{U_{UT}}{4k} \end{array} \right.$$

$$\Rightarrow \left\{ \begin{array}{l} 5V_1 = 7 \\ 5V_1 = U_{UT} \end{array} \right.$$

$$\Rightarrow \underline{\underline{U_{UT} = 7V}}$$

5.13/

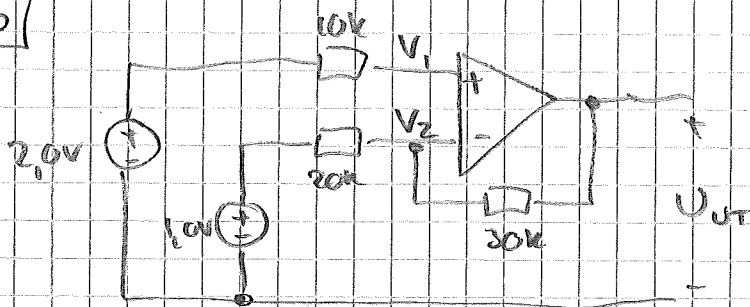

$$\left\{ \begin{array}{l} \frac{V_1 - 2}{10k} = 0 \\ \frac{V_2 - 1}{20k} + \frac{V_2 - U_{UT}}{30k} = 0 \end{array} \right. \Rightarrow V_1 = 2.0V$$

$$\left\{ \begin{array}{l} \frac{V_2 - 1}{20k} + \frac{V_2 - U_{UT}}{30k} = 0 \\ V_1 = V_2 \end{array} \right.$$


$V_1 = V_2$ Neg återkopplad ideal op

$$\Rightarrow \left\{ \begin{array}{l} V_1 = 2.0V \\ V_2 \left(\frac{1}{20k} + \frac{1}{30k} \right) = \frac{U_{UT}}{30k} + \frac{1}{20k} \\ V_2 = V_1 \end{array} \right.$$

$$\underline{\underline{U_{UT} = V_1 \left(\frac{30}{20} + \frac{30}{30} \right) - \frac{30}{20} = 2.0 (1.5 + 1) - 1.5 = 3.5V}}$$

5.14)

76

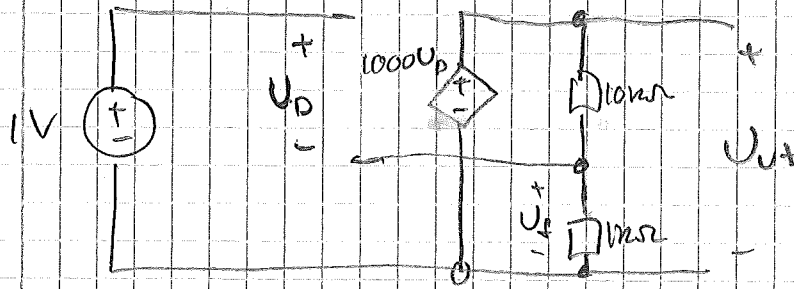

$$U_F = \frac{1k}{1k + 10k} \cdot U_{UT} = \frac{U_{UT}}{11}$$


$$U_{UT} = 1000 U_D$$

$$U_F + U_D = 1$$

$$\frac{U_{UT}}{11} + \frac{U_{UT}}{1000} = 1 \quad \Rightarrow \quad \underline{\underline{U_{UT} = \frac{1}{\frac{1}{11} + \frac{1}{1000}} = 10,28 \text{ V}}}$$

7.1

- a) $|I| = 4 \text{ A}$
 b) $T = 12 \text{ ms}$
 c) $f = \frac{1}{T} = 83 \text{ Hz}$
 d) $\omega = 2\pi f = 524 \text{ rad/s}$
 e) $\beta = \frac{2}{6} \cdot 180^\circ = 60^\circ$
 f) $i(t) = |I| \sin(\omega t + \beta) = 4 \sin(524t + 60^\circ) \text{ A}$

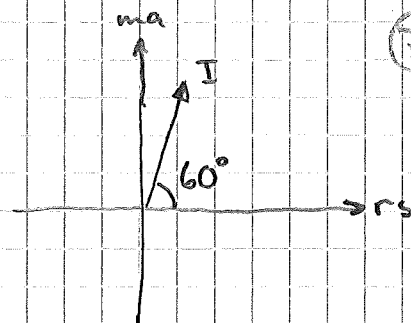7.2

$$u(t) = 128 \sin(\omega t - 1,17) \text{ V} \quad \text{für } \omega = 600 \text{ rad/s}$$

a) $f = \frac{\omega}{2\pi} = \frac{600}{2\pi} = 95,5 \text{ Hz}$

b) $\hat{u} = -128 \text{ V}$

c) $u(t=3 \text{ ms}) = 128 \sin(600 \cdot 3 \cdot 10^{-3} - 1,17) = 75,4 \text{ V}$

d) $100 = 128 \sin(600t - 1,17)$

$$\arcsin \frac{100}{128} = 600t - 1,17$$

$$t = 3,44 \text{ ms}$$

7.4

- a) $T = 6 \text{ ms}$
 $f = \frac{1}{T} = 170 \text{ Hz}$
 $\alpha_1 = -\frac{1}{3} \cdot 180^\circ = -60^\circ$
 $\alpha_2 = 0^\circ$

b) $u_1 = 7 \sin(\omega t - 60^\circ) \text{ V}$
 $u_2 = 4 \sin(\omega t) \text{ V}$

$$\omega = \frac{2\pi}{T} = 1,05 \text{ krad/s}$$

7.6)

$$|I| = 50 \text{ mA}$$

$$\Rightarrow I_e = \frac{|I|}{\sqrt{2}}$$

$$|U| = 30 \text{ V}$$

$$\Rightarrow U_e = \frac{|U|}{\sqrt{2}}$$

$$\varphi = -40^\circ$$

$$P = U_e \cdot I_e \cdot \cos \varphi = \frac{30}{\sqrt{2}} \cdot \frac{0,05}{\sqrt{2}} \cdot \cos(-40^\circ) = 0,58 \text{ W}$$

7.8)


$$|I| = 37 \text{ mA}$$

$$f = 14 \text{ kHz}$$

$$\beta = 113^\circ$$

$$a) i(t) = 37 \sin(2\pi f t + 113^\circ) \text{ mA}$$

b)

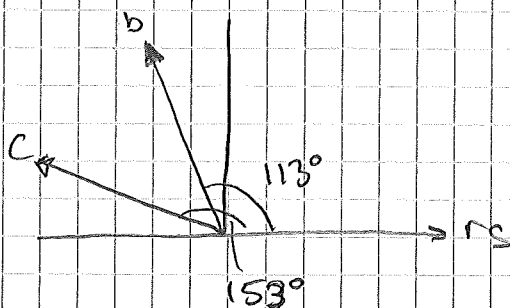

$$c) \text{ Tidvinkel } \omega t + \alpha = 2\pi \cdot 14 \cdot 10^3 \cdot 8 \cdot 10^{-6} \cdot \frac{180^\circ}{\pi} + 113^\circ = 153^\circ$$

vid $t = 8 \mu\text{s}$


7.10)

$$a) u = -1,8 \text{ V}$$

$$b) \text{ Tidvinkel } \omega t + \alpha = 216^\circ \text{ vid } t = 2 \text{ ms} \Rightarrow$$

$$\underline{\underline{\alpha}} = 216^\circ - \omega t \cdot \frac{180^\circ}{\pi} = 216^\circ - 2\pi \cdot 200 \cdot 2 \cdot 10^{-3} \cdot \frac{180^\circ}{\pi}$$

$$= \underline{\underline{72^\circ}}$$

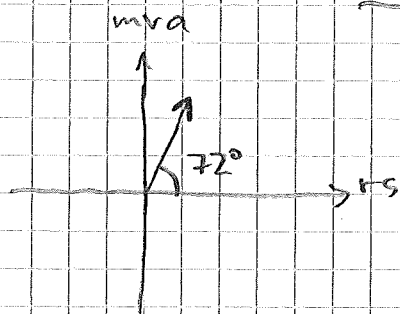

2.7)

$$\begin{cases} 200 \sin(\omega t + \alpha) = 155,7 \\ 4 \sin(\omega t + \beta) = \frac{p(t)}{u(t)} = \frac{212,5}{155,7} = 1,365 \end{cases}$$

$$\begin{cases} \sin(\omega t + \alpha) = 0,7785 \\ \sin(\omega t + \beta) = 0,3413 \end{cases}$$

$$\omega t + \alpha = \begin{cases} 0,892 \\ 2,250 \end{cases} \quad (1)$$

$$\omega t + \beta = \begin{cases} 0,348 \\ 2,794 \end{cases} \quad (2)$$

$$\varphi = \alpha - \beta = (1) - (2) = \begin{cases} 0,544 & \text{rad} \\ -1,902 & \text{"} \\ 1,902 & \text{"} \\ -0,544 & \text{"} \end{cases}$$

7.12

a) $\varphi = -30^\circ$

b) $|U| = 45 \text{ V}$

$|I| = 7,2 \text{ A}$


c) $\underline{P} = U_c \cdot I_c \cos \varphi = \frac{|U|}{\sqrt{2}} \cdot \frac{|I|}{\sqrt{2}} \cos \varphi = \frac{45}{\sqrt{2}} \cdot \frac{7,2}{\sqrt{2}} \cos(-30^\circ) = \underline{\underline{140 \text{ W}}}$

d) $P = u \cdot i = 20 \text{ V} \cdot 6 \text{ A} = 120 \text{ W}$

7.14

Ur f_5

KI $i_3 = i_1 + i_2$

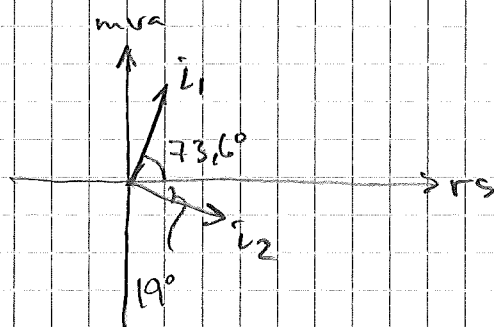

Koordinatenträgung: Horizontal led $i_{3h} = 473 \cos 73,6^\circ + 319 \cos 19^\circ = 435,2 \text{ mA}$

Vertikal led $i_{3v} = 473 \sin 73,6^\circ - 319 \sin 19^\circ = 349,9 \text{ mA}$

$$|I_3| = \sqrt{i_{3h}^2 + i_{3v}^2} = 558,4 \text{ mA}$$

$$\beta_3 = \arctan \frac{i_{3v}}{i_{3h}} = \arctan \frac{349,9}{435,2} = 38,8^\circ$$

$$i_3 = 558 \sin(\omega t + 38,8^\circ) \text{ mA}$$

8.1 | a) $C_{\text{tot}} = \frac{(C_2 + C_3) \cdot C_1}{C_1 + C_2 + C_3} = \frac{(2+3) \cdot 1}{1+2+3} = 0,83 \mu\text{F}$

b) $C_{\text{tot}} = \frac{C_1 \cdot C_2}{C_1 + C_2} + C_3 = \frac{1 \cdot 2}{1+2} + 3 = 3,67 \mu\text{F}$

c) $C_{\text{tot}} = C_1 + \frac{1}{\frac{1}{C_2} + \frac{1}{C_3} + \frac{1}{C_4}} = 1 + \frac{1}{\frac{1}{2} + \frac{1}{3} + \frac{1}{4}} = 1,92 \mu\text{F}$

8.2 | Forc anknappung

$$Q_{\text{tot}} = C_1 \cdot U = 4,7 \cdot 10^{-6} \cdot 24 = 1,128 \cdot 10^{-4} \text{ As}$$

After anknappung


$$C_{\text{tot}} = C_1 + C_2 + C_3 = 4,7 + 2,2 + 6,8 = 13,7 \mu\text{F}$$

a) $Q_{\text{tot}} = C_{\text{tot}} \cdot U_3 \Rightarrow U_3 = \frac{Q_{\text{tot}}}{C_{\text{tot}}} = \frac{1,128 \cdot 10^{-4}}{13,7 \cdot 10^{-6}} = \underline{\underline{8,23 \text{ V}}}$


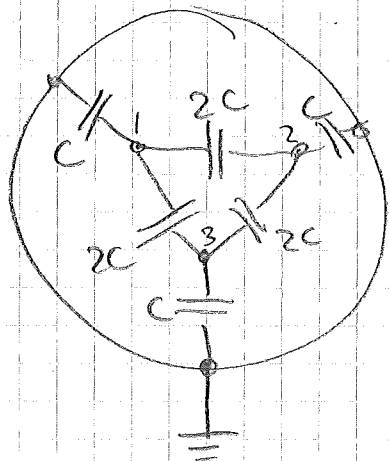
b) $Q_1 = C_1 \cdot U_3 = 4,7 \cdot 10^{-6} \cdot 8,23 = 38,7 \mu\text{As}$

$$Q_2 = C_2 \cdot U_3 = 2,2 \cdot 10^{-6} \cdot 8,23 = 18,1 \mu\text{As}$$

$$Q_3 = C_3 \cdot U_3 = 6,8 \cdot 10^{-6} \cdot 8,23 = 56,0 \mu\text{As}$$



Scheman där ③ jordas

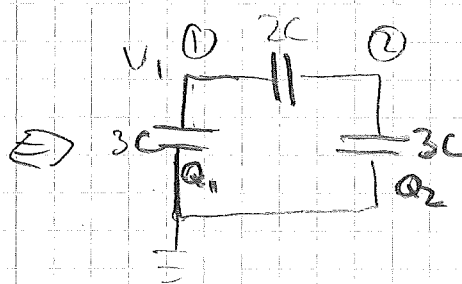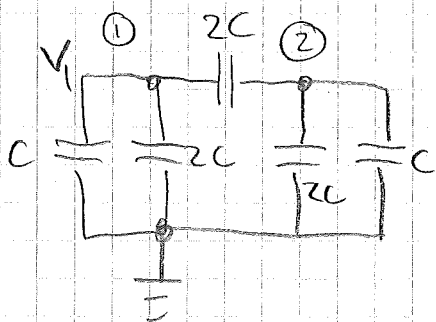



$$V_1 = 100 \text{ V}$$

Total kapacitans ① till jord: $C_{\text{jord}} = 3C + \frac{2C \cdot 3C}{2C + 3C} = 3C + 1,2C = 4,2C$

Laddning i vänster kond. $Q_1 = V_1 \cdot 3C = 300C$


u i Höger $Q_2 = V_1 \cdot 1,2C = 120C$

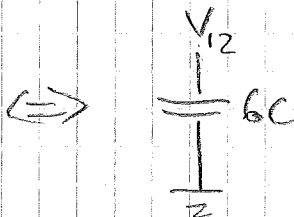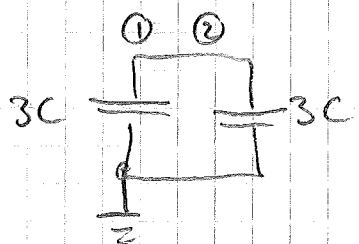Koppla samman ① = ② $\Rightarrow Q_{\text{tot}} = Q_1 + Q_2 = 420C$



$$V_{12} = \frac{Q_{\text{tot}}}{6C} = \frac{420C}{6C} = 70 \text{ V}$$

3.4)

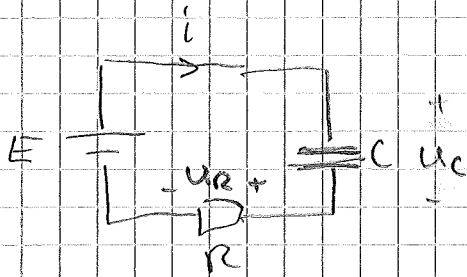Kondensator laddad vid $t=0 \Rightarrow$

a) Begynnelsevärde $\underline{i(0)} = \frac{E}{R} = \frac{120}{2 \cdot 10^6} = \underline{60 \mu A}$

b) KV: $u_R = E - u_C = 120 - 60 = 60 V$

$$\underline{i} = \frac{u_R}{R} = \frac{60}{2 \cdot 10^6} = \underline{30 \mu A}$$

c) $\underline{\tau} = RC = 2 \cdot 10^6 \cdot 5 \cdot 10^{-6} = \underline{10 s}$

d) $i(t) = i(0) e^{-\frac{t}{\tau}}$

$$\underline{i(2\tau)} = i(0) e^{-\frac{2\tau}{\tau}} = 60 \mu A \cdot e^{-2} = \underline{8,1 \mu A}$$

e) Slutvärde $u_C(\infty) = E = 120 V$

$$u_C(t) = u_C(\infty) \left(1 - e^{-\frac{t}{\tau}}\right) = 120 \left(1 - e^{-\frac{t}{10}}\right)$$

$$u_C(8) = 120 \left(1 - e^{-\frac{8}{10}}\right) = 66,1 V$$

8.5)


a) Begynnelsevärde $u_c(0) = \frac{R}{3R} \cdot E = 20 \text{ V}$

b) $i_c(0) = \frac{u_c(0)}{\frac{R}{2}} = \frac{20}{20 \cdot 10^3} = 1 \text{ mA}$

c) $\underline{u_c(t) = u_c(0) \cdot e^{-\frac{t}{\tau}}} \rightarrow \underline{0}$ då $t \rightarrow \infty$

d) $\underline{\tau = \frac{R}{2} \cdot C = 20 \cdot 10^3 \cdot 5 \cdot 10^{-6} = 0,1 \text{ s}}$

8.6)

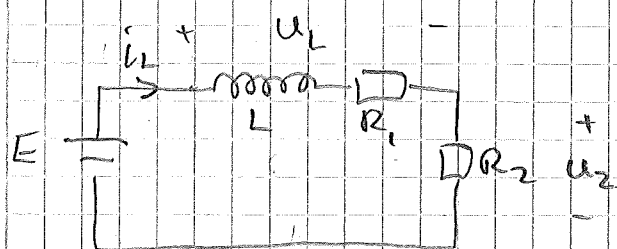

$$E = 4 \text{ V}$$

$$L = 2 \text{ mH}$$

$$R_1 = 2 \Omega$$

$$R_2 = 2 \text{ k}\Omega$$

a) Spole utan begynnelseenergi $\Rightarrow i_L(0) = 0 \Rightarrow$

$$u_2(0) = R_2 \cdot i_L(0) = 0 \Rightarrow$$

$$\underline{u_L(0) = E - u_2(0) = E = 4 \text{ V}}$$

b) Uppladdning $i_L(\infty) = \frac{E}{R_1 + R_2} = \frac{4}{2002} \approx 2,0 \text{ }\mu\text{A}$

$$i_L(t) = i_L(\infty) \left(1 - e^{-\frac{t}{\tau}}\right)$$


$$i_L(0) = 0$$

$$i_L(\infty) = 2,0 \text{ }\mu\text{A}$$

c) $\underline{\tau = \frac{L}{R} = \frac{2 \cdot 10^{-3}}{2002} \approx 1 \text{ }\mu\text{s}}$

d) $u_2 = R_2 \cdot i_L = R_2 i_L(\infty) \left(1 - e^{-\frac{t}{\tau}}\right) =$
 $= 2000 \cdot 2,0 \cdot 10^{-3} \left(1 - e^{-\frac{t}{10^{-6}}}\right) = 4 \left(1 - e^{-\frac{t}{10^{-6}}}\right) = 1$
 $\Rightarrow 0,75 = e^{-\frac{t}{10^{-6}}} \Rightarrow t = -10^{-6} \cdot \ln 0,75 = 0,29 \text{ }\mu\text{s}$

8.7)

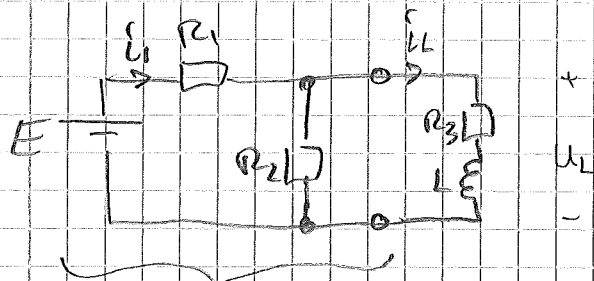


85

Träpöl

Tongångssp $U_T = \frac{R_2}{R_1 + R_2} \cdot E = \frac{60}{30 + 60} \cdot 60 = 40 \text{ V}$

Kortslutstr. str $I_K = \frac{E}{R_1} = \frac{60}{30} = 2 \text{ A}$

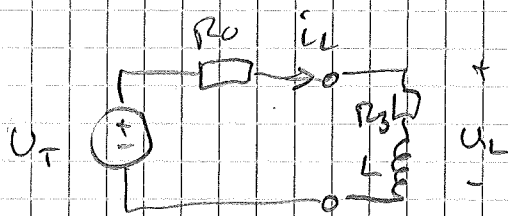Inre res $R_0 = \frac{U_T}{I_K} = \frac{40}{2} = 20 \Omega$



a) $t=0$ Spole utan lagringsenergi $\Rightarrow i_L(0) = 0 \Rightarrow$


$u_L(0) = U_T - R_0 i_L(0) = U_T = 40 \text{ V}$

b) $i_L(0) = 0 \Rightarrow \underline{\underline{i(0) = \frac{E}{R_1 + R_2} = \frac{60}{90} = 0,67 \text{ A}}}$

c) $u_L(\infty) = \frac{R_3}{R_0 + R_3} \cdot U_T = \frac{20}{40} \cdot 40 = 20 \text{ V}$

d) $\tau = \frac{L}{R_0 + R_3} = \frac{1}{40} = 25 \text{ ms}$

8.8

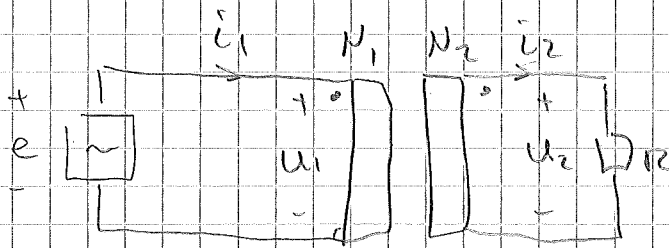


$$e = u_1 = 50 \sin \omega t \text{ [V]}$$

$$R = 100 \Omega \quad N_1 = 1000 \quad N_2 = 100$$

Ideal trafo: $\frac{u_1}{N_1} = \frac{u_2}{N_2} \Rightarrow \underline{u_2 = \frac{N_2}{N_1} \cdot u_1 = 5,0 \sin \omega t \text{ [V]}}$

$i_2 = \frac{u_2}{R} = 0,05 \sin \omega t \text{ [A]}$

8.9

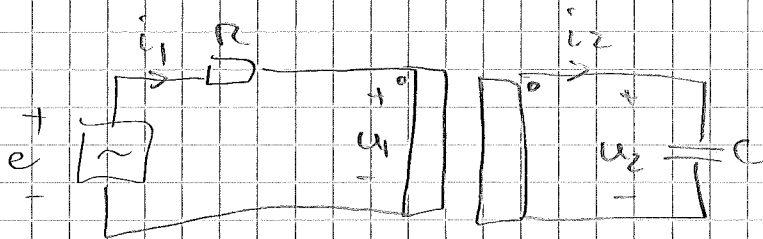

$$N_1 = 5000 \quad N_2 = 1000$$

$$C = 10 \mu\text{F}$$

$$u_2 = 2,0 \sin \omega t \text{ [V]}$$

$$R = 500 \Omega$$

$$f = 1000 \text{ Hz}$$

a) Ideal trafo $\frac{u_1}{N_1} = \frac{u_2}{N_2} \Rightarrow \underline{u_1 = \frac{N_1}{N_2} u_2 = 10 \sin \omega t \text{ [V]}}$


b) $i_2 = C \frac{du_2}{dt} = 10 \cdot 10^{-6} \cdot 2,0 \cdot \omega \cos \omega t \text{ [A]} = 0,126 \cos \omega t \text{ [A]}$

Ideal trafo $N_1 i_1 = N_2 i_2 \Rightarrow \underline{i_1 = \frac{N_2}{N_1} i_2 = 0,025 \cos \omega t \text{ [A]}}$

c) $e = u_1 + R \cdot i_1 = 10 \sin \omega t + 12,56 \cos \omega t = 16,0 \sin(\omega t + 51,5^\circ) \text{ V}$

8.10


(8)

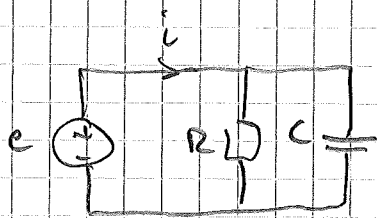

$$e = 35,6 \sin(\omega t + 13,8^\circ) \text{ V}$$

$$\omega = 80 \text{ rad/s}$$
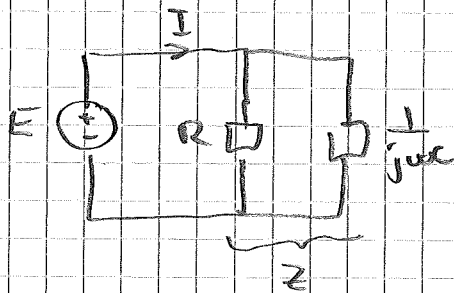
$$R = 1600 \Omega \quad C = 6,20 \mu\text{F}$$



$$E = 35,6 e^{j(\omega t + 13,8^\circ)} \text{ V}$$

$$Z = R // \frac{1}{j\omega C} = \frac{R \cdot \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{R}{1 + j\omega RC} = \frac{1600}{1 + j0,794}$$

$$= \frac{1600}{\sqrt{1 + 0,794^2}} e^{j \arctan \frac{0,794}{1}} = \frac{1600}{1,277} e^{j38,4^\circ}$$

$$= 1253 e^{-j38,4^\circ}$$

$$I = \frac{E}{Z} = \frac{35,6 e^{j(\omega t + 13,8^\circ)}}{1253 e^{-j38,4^\circ}} = 28,4 e^{j(\omega t + 55,2^\circ)} \text{ A}$$

$$i(t) = 28,4 \sin(\omega t + 55,2^\circ) \text{ A}$$