

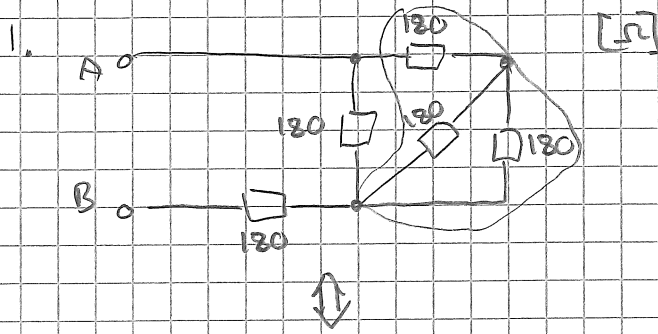


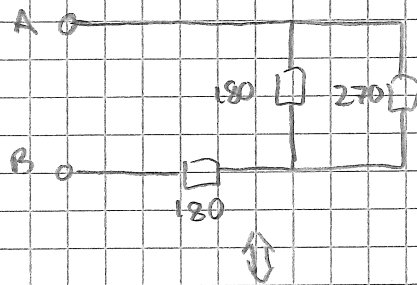







$$180 + 180 // 180 = 270 \Omega$$

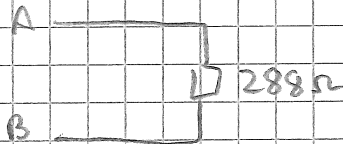


$$180 + 180 // 270 = 288 \Omega$$



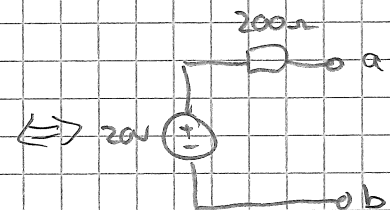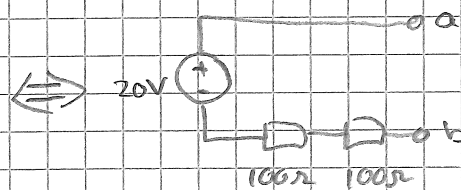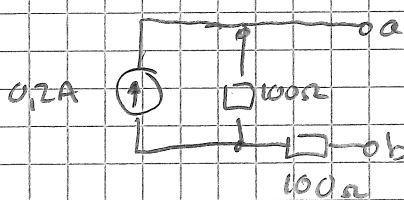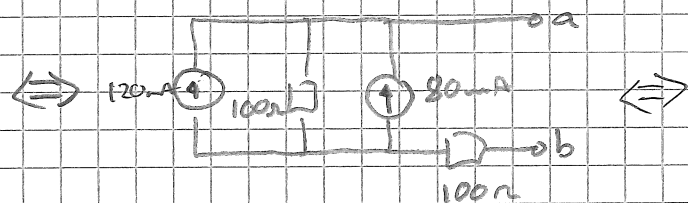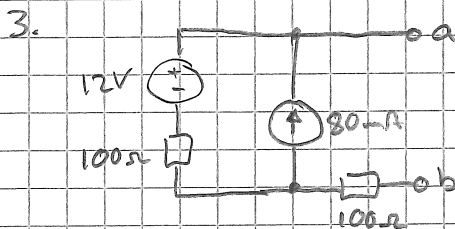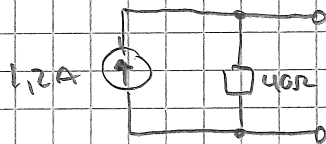2. U_r Figur $\begin{cases} U_T = 48V \\ I_k = 1,2A \end{cases} \Rightarrow \begin{cases} J = I_k = 1,2A \\ R_o = \frac{U_T}{I_k} = \frac{48}{1,2} = 40 \Omega \end{cases}$



4.

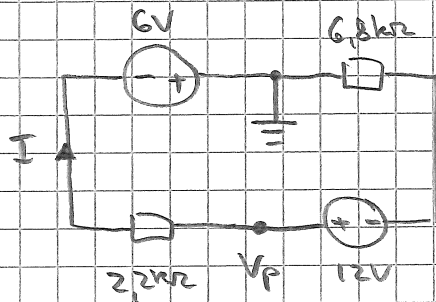


$$\text{KV} \quad -6V + 22k\Omega \cdot I - 12V + 6.8k\Omega \cdot I = 0 \Rightarrow$$

$$\underline{I} = \frac{6V + 12V}{22k\Omega + 6.8k\Omega} = \underline{2mA}$$

$$\underline{V_p} = -6V + 22k\Omega \cdot I = -6 + 2200 \cdot 2 \cdot 10^{-3} = \underline{-1.6V}$$

5.

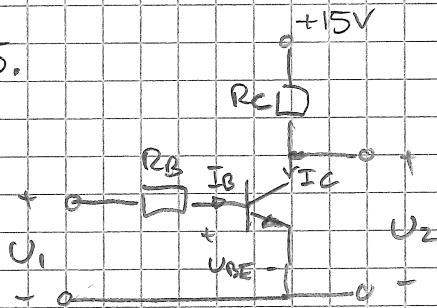

$$h_{FE} = 120$$

$$R_B = 100k\Omega$$

$$U_{CEsat} = 0.1V$$

a) $U_1 = 5V \quad R_C = 820\Omega$

$$\text{KV basbrekts} \quad U_1 - R_B I_B - U_{BE} = 0 \Rightarrow I_B = \frac{U_1 - U_{BE}}{R_B} = \frac{5 - 0.7}{100000} = 43\mu A$$

$$I_C = h_{FE} \cdot I_B = 120 \cdot 43\mu A = 5.16mA$$

$$\text{KV kollektorbräns} \quad U_2 + R_C I_C - 15V = 0 \Rightarrow \underline{U_2 = 15V - R_C I_C = 15 - 820 \cdot 5.16 \cdot 10^{-3} = \underline{10.8V}}$$

b) $U_1 = 2V \quad U_2 = U_{CEsat} = 0.1V$

$$\text{KV basbrekts} \Rightarrow I_B = \frac{U_1 - U_{BE}}{R_B} = \frac{2 - 0.7}{100000} = 13\mu A$$


$$I_C = h_{FE} \cdot I_B = 120 \cdot 13\mu A = 1.56mA$$

$$\text{KV kollektorbräns} \quad U_2 + R_C I_C - 15V = 0 \Rightarrow$$

$$R_C = \frac{15V - U_2}{I_C} = \frac{15 - 0.1}{1.56 \cdot 10^{-3}} = 9551\Omega$$

Detta är gränsfallet för botten.

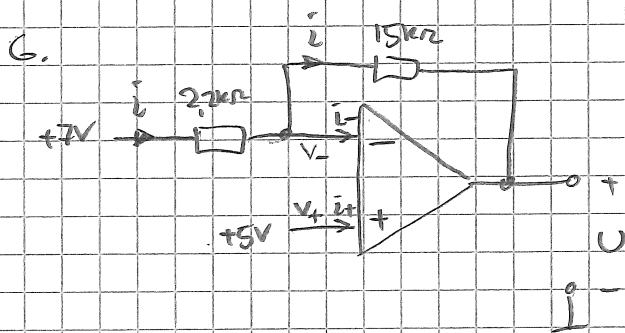Transistorn botten för $R_C \geq 9551\Omega$



Ideal OP $\Rightarrow i_+ = i_- = 0$

— " — negativt återkopplad $\Rightarrow v_- = v_+$

Från figur $v_+ = +5V \Rightarrow v_- = 5V$

$$i = \frac{7V - v_-}{2200\Omega} = \frac{7 - 5}{2200} = 0,909 \text{ mA}$$

$$\underline{\underline{U}} = v_- - 15k\Omega \cdot i = 5 - 15000 \cdot 0,909 \cdot 10^{-3} = \underline{\underline{-8,6 \text{ V}}}$$