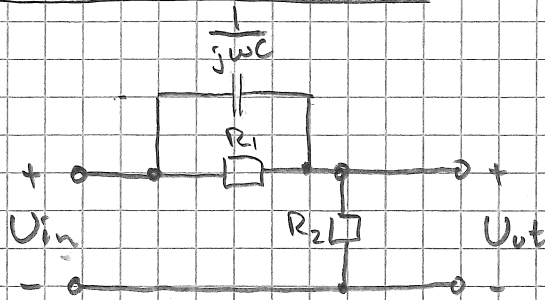


Ex 11.4 sid 218



$$Z_p = R_1 \parallel \frac{1}{j\omega C} = \frac{R_1 \cdot \frac{1}{j\omega C}}{R_1 + \frac{1}{j\omega C}} = \frac{R_1}{1 + j\omega C R_1}$$

$$U_{out} = \frac{R_2}{R_2 + Z_p} \cdot U_{in}$$

$$H(j\omega) = \frac{U_{out}}{U_{in}} = \frac{R_2}{R_2 + Z_p} = \frac{R_2}{R_2 + \frac{R_1}{1 + j\omega C R_1}} = \frac{R_2(1 + j\omega C R_1)}{R_2(1 + j\omega C R_1) + R_1}$$

$$= \frac{R_2(1 + j\omega C R_1)}{R_1 + R_2 + j\omega C R_1 R_2} = \frac{R_2(1 + j\omega C R_1)}{(R_1 + R_2)(1 + j\omega \frac{C R_1 R_2}{R_1 + R_2})}$$

$$= \underbrace{\left(\frac{R_2}{R_1 + R_2} \right)}_A \underbrace{\left(\frac{1 + j\omega \frac{C R_1 R_2}{R_1 + R_2}}{1 + j\omega \frac{C R_1 R_2}{R_1 + R_2}} \right)}_B$$

(C)

$$K = \frac{R_2}{R_1 + R_2} = \frac{4}{4+4} = 0,5 = -6 \text{ dB}$$

$$\omega_1 = \frac{1}{C R_1} = \frac{1}{100 \cdot 10^{-9} \cdot 4000} = 2500 \text{ rad/s}$$

$$\omega_2 = \frac{R_1 + R_2}{C R_1 R_2} = 5000 \text{ rad/s}$$

