
```

% Lab 2, uppgift 3
% Linjärisering av NTC-motstånd

% Konstanter
alpha = 3977; %kelvin
R25 = 2.2e3; %ohm
TA = 293; %kelvin
TB = 313; %kelvin
TC = 333; %kelvin
T = TA:TC; % Temp. intervallet vi vill linjärisera.

% NTC resistans vid TA, TB & TC.
R_TA = R25*exp(alpha * ((1 / TA) - (1 / 298)))
R_TB = R25*exp(alpha * ((1 / TB) - (1 / 298)))
R_TC = R25*exp(alpha * ((1 / TC) - (1 / 298)))

% Resistans R_lin som ger ett approx. linjärt område.
Rlin = (R_TA*R_TB + R_TB*R_TC - 2*R_TA*R_TC) / (R_TC + R_TA - 2*R_TB)

%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%

% Grafer
hold off

% Beräkna alla resistanser inom temp.intervallet
R_T = R25.*exp(alpha .* ((1 ./ T) - (1 ./ 298)));

hold on

subplot(2,1,1)
plot( T, R_T, 'k')
title('R_T vs. Temp')
grid on

subplot(2,1,2)
plot( T, (Rlin ./ (Rlin + R_T)), 'k')
title('U_R vs. Temp (efter linjärisering med R_{lin} = 860ohm)')
xlabel('20°C <= Temp. <= 60°C')
grid on

R_TA =

    2.7627e+003

R_TB =

    1.1605e+003


R_TC =

```

$541.0534e+000$

$R_{lin} =$

$859.5428e+000$

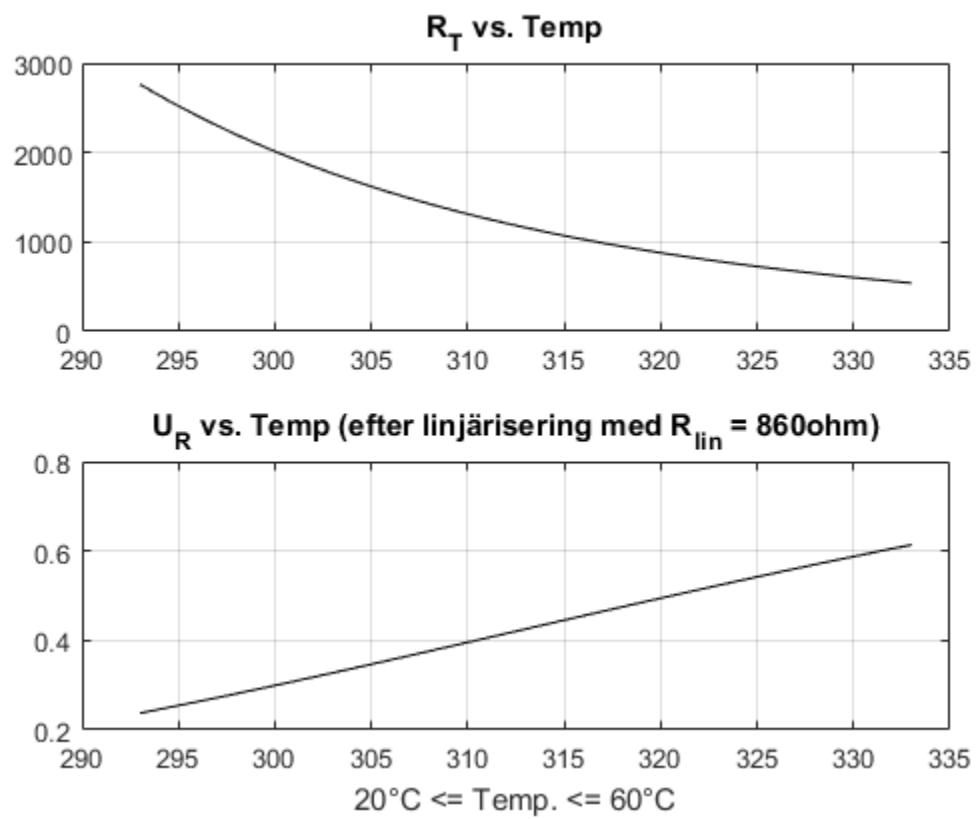

Published with MATLAB® R2016b