
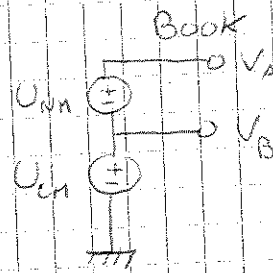


Signal model

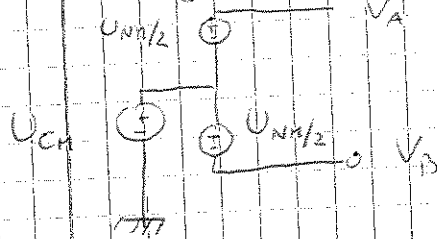

not correct!

$$\frac{V_A + V_B}{2} \neq U_{CM}$$

but quicker to draw, so we will use it

$$U_{out} = U_{out, NM} + U_{out, CM}$$

$$F_{NM} = \frac{U_{out, NM}}{U_{NM}}; \quad F_{CM} = \frac{U_{out, CM}}{U_{CM}}$$

Common mode rejection ratio (CMRR)

$$CMRR = 20 \log_{10} \frac{F_{NM}}{F_{CM}} \quad [dB]$$

Example

$$F_{NM} = 1000; \quad CMRR = 80 \text{ dB} \quad F_{CM} = ?$$

$$CMRR = 20 \log_{10} \frac{F_{NM}}{F_{CM}}$$

$$\Rightarrow 10^{CMRR/20} = \frac{F_{NM}}{F_{CM}} \Rightarrow F_{CM} = \frac{F_{NM}}{10^{CMRR/20}} = \frac{1000}{10^4} = 0,01$$

Interpretation

$$\text{"SNR"} = \frac{\text{useful signal}}{\text{disturbance}}$$

$$\text{"SNR}_{in} = \frac{U_{NM}}{U_{CM}}$$

$$\text{"SNR}_{out} = \frac{U_{out, NM}}{U_{out, CM}} = \frac{U_{NM} \cdot F_{NM}}{U_{CM} \cdot F_{CM}}$$


$$= \text{"SNR}_{in} \cdot CMRR$$

↑
linear scale

$$\Rightarrow \text{"SNR}_{out} [dB] = \text{"SNR}_{in} [dB] + CMRR [dB]$$

Example ECG


electrode disks

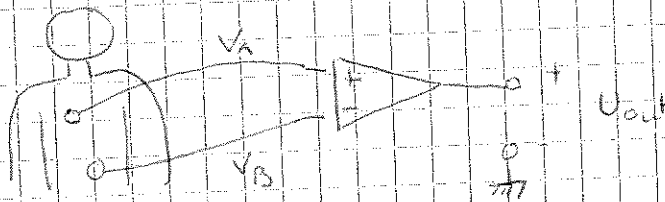


- 50 Hz interference from power line on the cables

$$U_{cn} = 4V$$

$$U_{nm} = 20mV$$

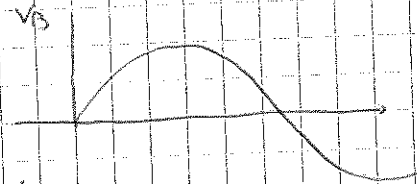

50 Hz noise

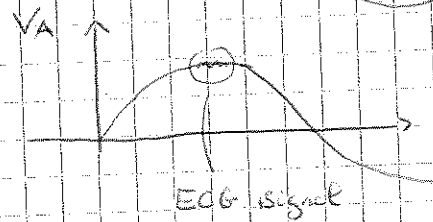

- instrumentation amplifier

$$F_{nm} = 100$$

$$CMRR = 80 dB$$


$$\Rightarrow U_{nm,out} = 100 \cdot 20mV = 2,0V$$

$$U_{cm,out}$$

$$CMRR = 20 \log_{10} \frac{F_{nm}}{F_{cn}}$$

$$\Rightarrow F_{cn} = 0.01$$
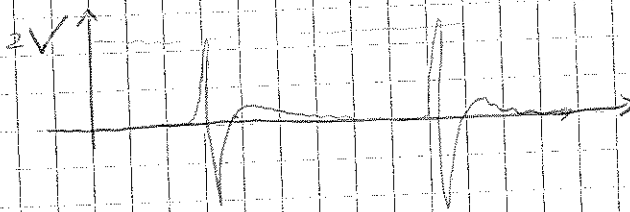
$$U_{cn,out} = F_{cn} \cdot U_{cn} = 0,04V$$




sampling and AD converters

[cheat sheet]

Slide $\rightarrow$ block diagram

analog $\xrightarrow{\text{sampling quantization}}$ digital

• Sampling (repetition)

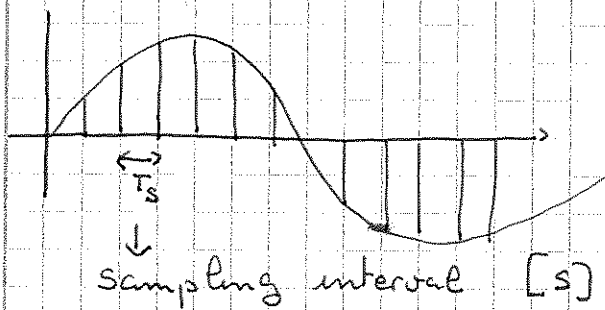

$$f_s = \frac{1}{T_s} \quad \text{sampling freq. [Hz]} \leftrightarrow \left[\frac{\text{samples}}{s} \right]$$

$$x[n] = x(nT_s) \quad \uparrow \text{nth sample}$$

• Sampling theorem for sin. functions


To recover a sin function at f Hz one has to sample at a frequency $f_s \geq 2f$

Equivalently, $f < f_s/2$.

• If we sample at $f_s < 2f$ we get **aliasing**! we reconstruct a sin of frequency lower than f !

- slide: aliasing;
- Recall $\Omega = 2\pi \frac{f}{f_s}$: normalized freq.

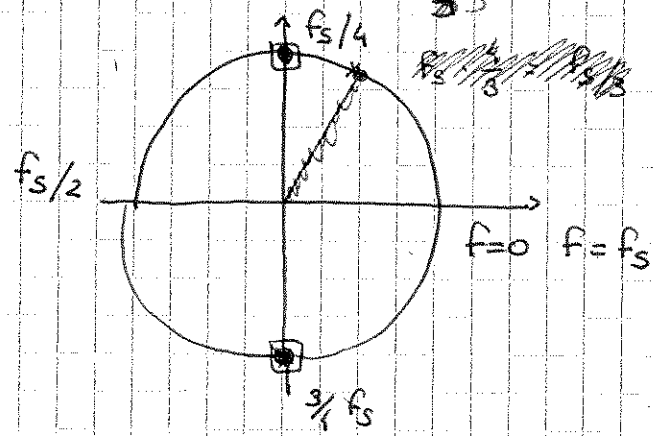• In our example: $f_s = \frac{4}{3}$, $f = 1 \Rightarrow \Omega = 2\pi \frac{3}{4} = 2\pi \frac{3}{4}$



$$f = \frac{3}{4} f_s \Rightarrow \frac{1}{4} f_s = \frac{1}{3} \text{ Hz}$$

$$\frac{3}{4} = -\frac{1}{4} = \frac{1}{4}$$

slide: second example

rule: all frequencies of the form

$$f = \pm f_1 + m f_s \quad m \in \mathbb{N}$$

are mapped to f_1 .

input signal

(In) Example: $f_1 = 1 \text{ kHz}$


$$f = 9 \text{ kHz} = -f_1 + f_s$$

That's why we get 1 kHz.

• Sampling theorem for bandlimited signals:

A bandlimited signal can be perfectly reconstructed by its
→ samples taken at twice the largest freq.

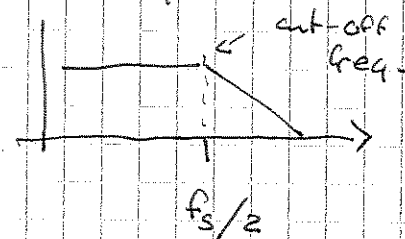
• To avoid aliasing: we use ~~LPF filter~~



Analog to digital converter

ADC

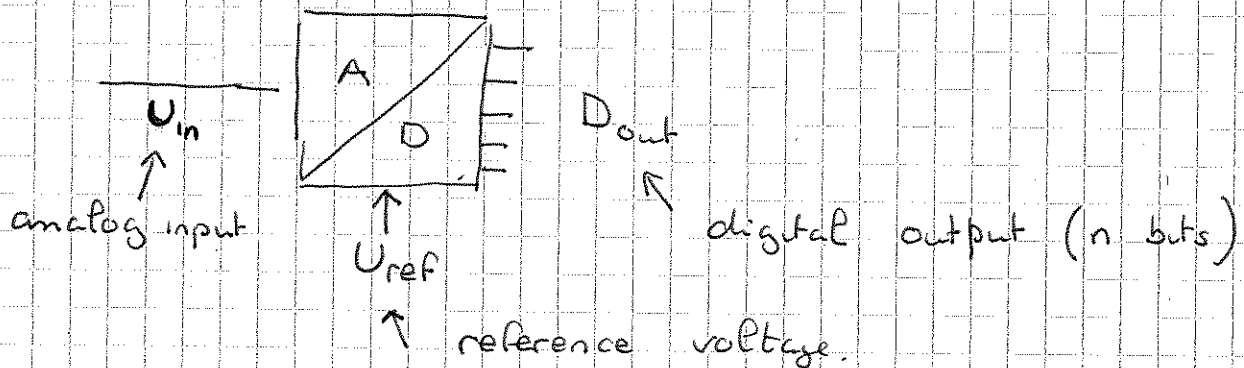• perform quantization: real-valued samples → integer-valued samples



• U_{ref} divided into 2^n levels
 $0, 1, \dots, 2^n - 1$; Compare U_{in} with levels

• Resolution $\Delta U = \frac{U_{ref}}{2^n}$: minimum variation of U_{in} that determines a variation in D

Example : slide

• $D_{out} = \left\lfloor \frac{U_{in}}{\Delta U} \right\rfloor \rightarrow \text{round to nearest integer.}$

• Given D_{out} , $U_{in} \in \left[D_{out} \cdot \Delta U - \frac{\Delta U}{2}, D_{out} \cdot \Delta U + \frac{\Delta U}{2} \right]$

• $\frac{\Delta U}{2}$: maximum quantization error.

• $U_Q = U_{in} - D_{out} \cdot \Delta U \rightarrow \text{quantization error}$

• Successive approximation : fast (200 MS/s)
accurate (24 bit)
cheap

• drift slope : slow (10 S/s)
very accurate

• Flash ADC : very fast (20 GS/s)
expensive
low resolution (8 bit)

• Successive approximation ADC

- SLIDE : SAR: Successive approximation register

EOC: end of conversion

DAC $\rightarrow$ resistive ladder

$\hat{=}$ dig-to-analog converter

- SLIDE : $n=4$ bit

$\Delta U = \frac{5}{2^4} = 0.3125 V$

$\rightarrow$ need n compar.
rison.

(TPS)

Y/N game
integer
number between 1 and 32


~~0.3125 V~~

Flash ADC

- slide: general $\rightarrow 2^n - 1$ comparators
- slide: 3 bits
- # bits limited by size, power consumption costs

Dual slope ADC

slide

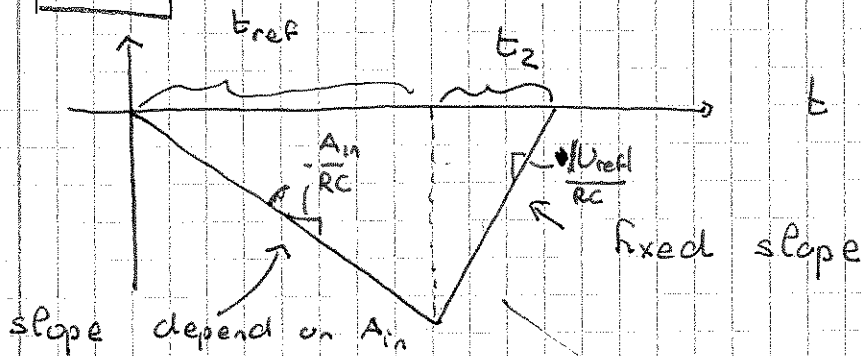

maybe skip!

$$U_1(t) = -\frac{1}{RC} A_{in} \cdot t$$

$$U_2(t) = U_1|_{t_{ref}} + \frac{1}{RC} |U_{ref}| \cdot t \quad t > t_{ref}$$

fixed slope.

$$\rightarrow A_{in} = \frac{t_2}{t_{ref}} |U_{ref}| \rightarrow [\text{see book for details}]$$

- accurate but slow
- used in digital voltmeters
- $t_{ref} = 100 \text{ ms}$



(5 periods @ 50 Hz

6 periods @ 60 Hz)


to avoid power-line disturbances.

Sample & hold

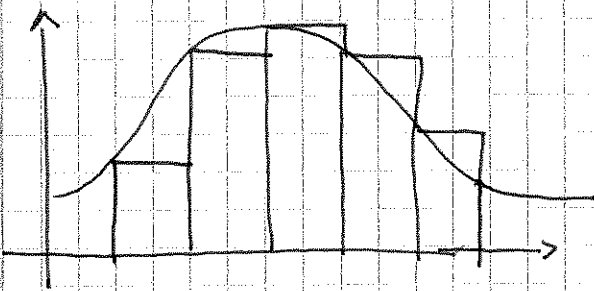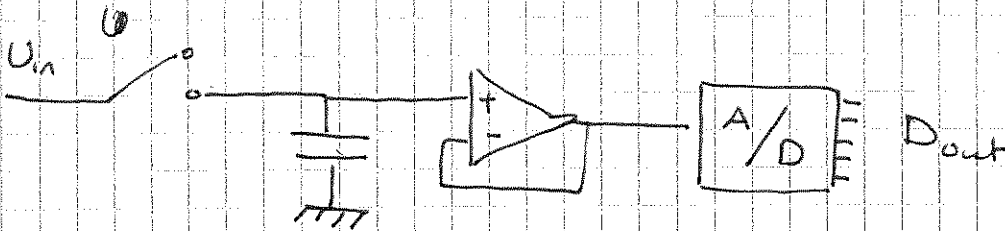- ADCs need constant signal over an interval
- SH circuitry



Block schema measurement system

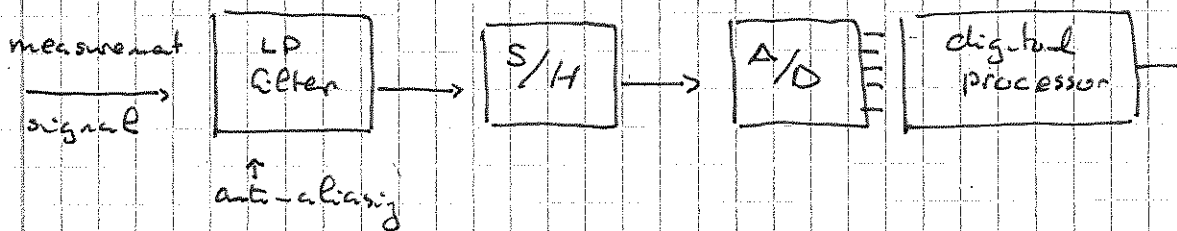

Oscilloscope

- voltmeter (digital)
- 8 bit vertical resolution, 1000 samples recorded
- max sampling rate: 500 MS/s $\Rightarrow f \leq 250$ MHz
- 3 basic settings
- vertical: attenuation / amplification of signal [V/div]
- horizontal: amount of time per division:
Note larger time/div $\Leftrightarrow$ lower sample rate

Noise and interference in electrical measurement systems

cheat sheet
lecture 5

- measurement signal superimposed to unwanted signal
- extractable with SIG. PROC. methods
- First: prevent disturbances from entering the system
- Related to EMC
 - ~~immune~~ → immune to EM fields
 - radiate limited amount of EM

our goal

Disturbances occur if

- ~~exists~~^a noise source exists
- noise freq. is within bandwidth of meas. sys.
- coupling between noise and meas. sys.

often the only thing we can work on


Coupling

- capacitive
- inductive
- conductive
- radiative
- via ground loops
- via internally generated noise

disturbances can be NM or CM


Thermal noise

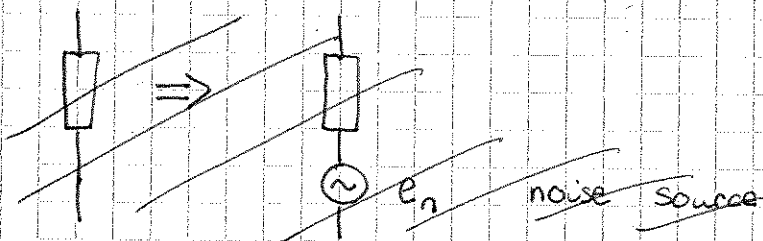- internally generated $\Rightarrow$ thermal agitation of electrons in conductor





$\Rightarrow$

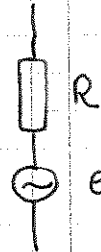

noise

Error in book (no π).

• RMS voltage

$$e_N = \sqrt{4k_B T R B}$$

Statistics:

- standard deviation of (Gaussian) random variable

$$k_B = 1,38 \cdot 10^{-23} \text{ J/K [Boltzmann constant]}$$

T = temperature $^{\circ}\text{K}$

B = bandwidth [Hz] over which noise is measured. or impedance


• $e_N \uparrow$ if $T \uparrow$, $R \uparrow$ or $B \uparrow$ Don't use larger bandwidth values than actually needed.

• independent noise add quadratically:

$$e_{N1}, e_{N2} \Rightarrow e_{\text{tot}} = \sqrt{e_{N1}^2 + e_{N2}^2}$$


• Think of noise as (Gaussian) n.v. with variance e_N^2 (more later)

Example

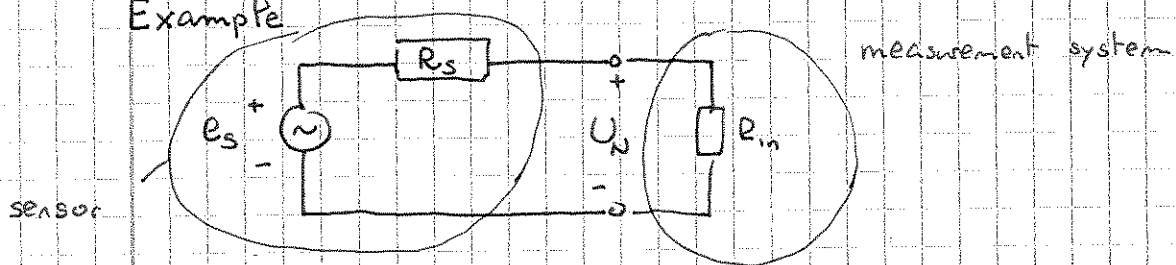

• map thermal noise impact on U_N ?
• Superposition: e_s off + noise sources on
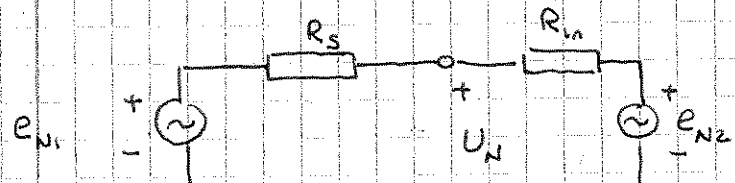
$$e_{N1} = \sqrt{4k_B T R_s B}; \quad e_{N2} = \sqrt{4k_B T R_m B}$$



- noise from R_s : $U_{N1} = \frac{R_{in}}{R_{in} + R_s} e_{N1}$

- noise from R_{in} : $U_{N2} = \frac{R_s}{R_{in} + R_s} e_{N2}$

Total noise

$$U_N^2 = U_{N1}^2 + U_{N2}^2 = \frac{R_{in}^2}{(R_{in} + R_s)^2} \{TBK_b e_s^2 + \frac{R_s^2}{(R_{in} + R_s)^2} \{TBK_b R_{in}^2$$

$$= \{TBK_b \frac{R_{in} R_s (R_{in} + R_s)}{(R_{in} + R_s)^2}$$

$$= \{TBK_b \underbrace{(R_{in} \parallel R_s)}_{R_p} \Rightarrow U_N = \sqrt{\{TBK_b R_p}$$

• Example

$$R_s = 100 \Omega, R_{in} = 1 \text{ M}\Omega, T = 300 \text{ K}, B = 50 \text{ MHz}$$

$$R_p = R_s \parallel R_{in} \approx 100 \Omega$$


$$U_N = \sqrt{\{K_b T R_p B} \approx 9,1 \mu\text{V}$$

• If $R_s = 1 \text{ M}\Omega$, however


$$\Rightarrow R_p = R_s \parallel R_{in} = 500 \text{ k}\Omega \Rightarrow U_N = 0,613 \text{ mV}$$

• Capacitive coupling

- two ~~wire~~ cables form a condenser!

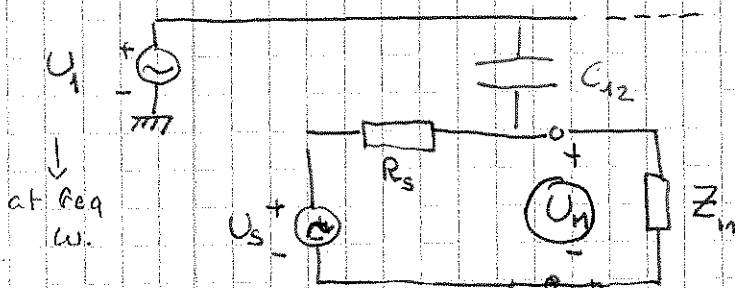

Impact on U_N

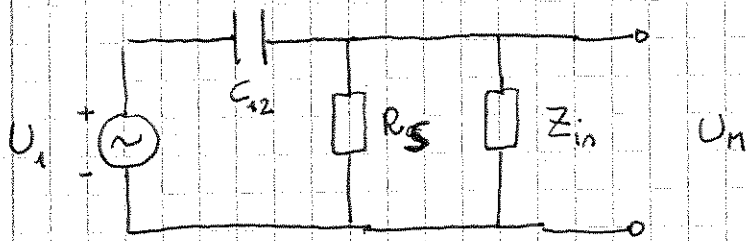




$$Z_p = R_S \parallel Z_{in} \Rightarrow U_n = \frac{Z_p}{Z_p + \frac{1}{j\omega C_{12}}} U_1 \approx j\omega C_{12} Z_p U_1$$

$$|Z_p| \ll \frac{1}{\omega C_{12}}$$

because R_S is small

• Countermeasures:


- reduce ω or U_1 (often not possible)
- make $|Z_p|$ small (choose R_S small)
- use ~~shielded~~ shielded cables that are grounded.

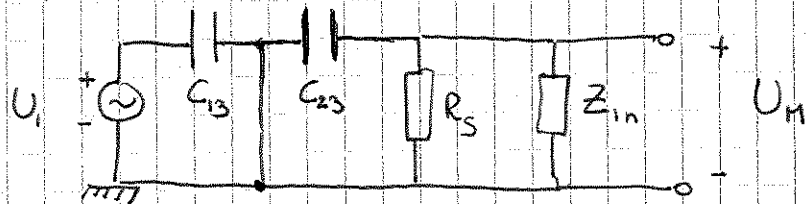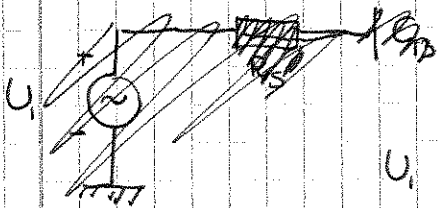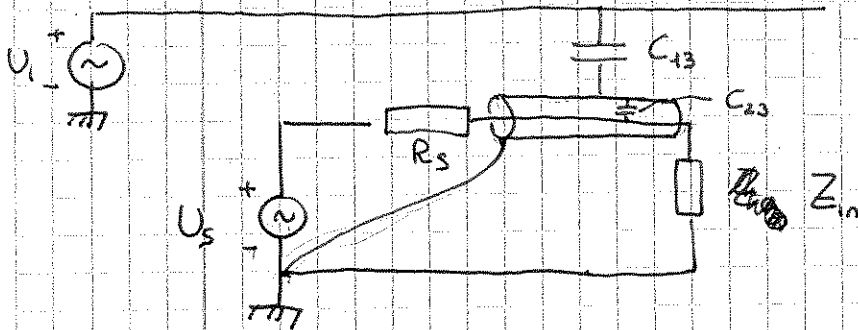

$U_n = 0$ if good connection to ground.

Inductive coupling

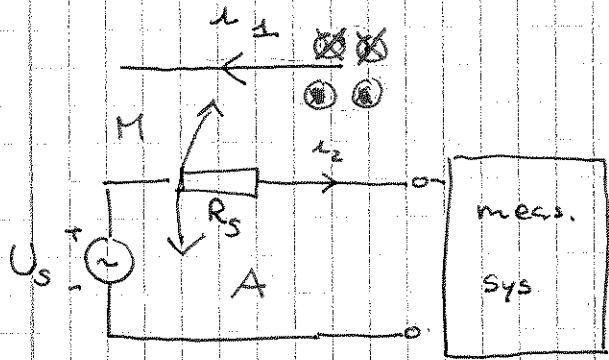- mutual inductance between two cables: they act as transformers




$I_1 \rightarrow$ magnetic field
 $\rightarrow$ tension

$$U_{ind} = A \frac{dB}{dt} = \underbrace{(\mu)}_{\text{mutual inductance}} \frac{dI_1}{dt}$$

• Countermeasures


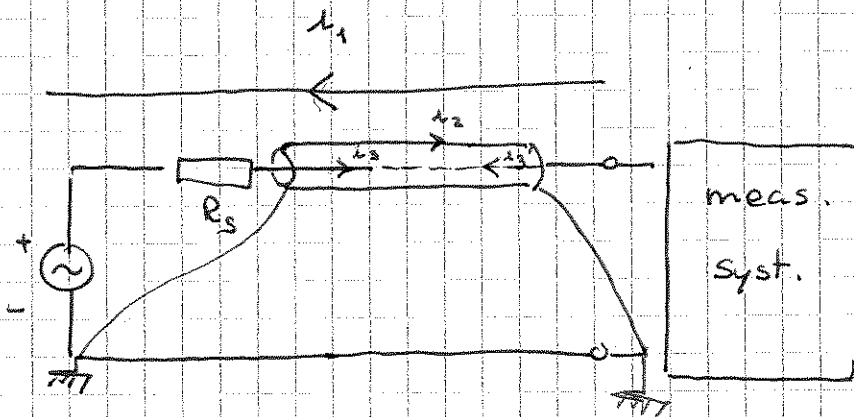
- reduce $\frac{dI_1}{dt} \Rightarrow$ amplitude $\downarrow$ freq. $\downarrow$
- reduce μ
- use shielded cable



ground at both end to
 $\Rightarrow$ close circuit!
 the

Conductive coupling

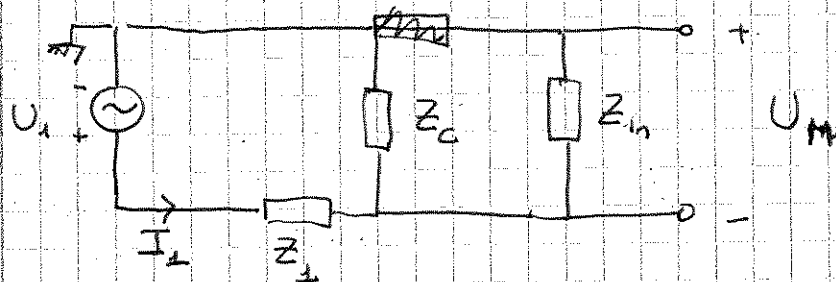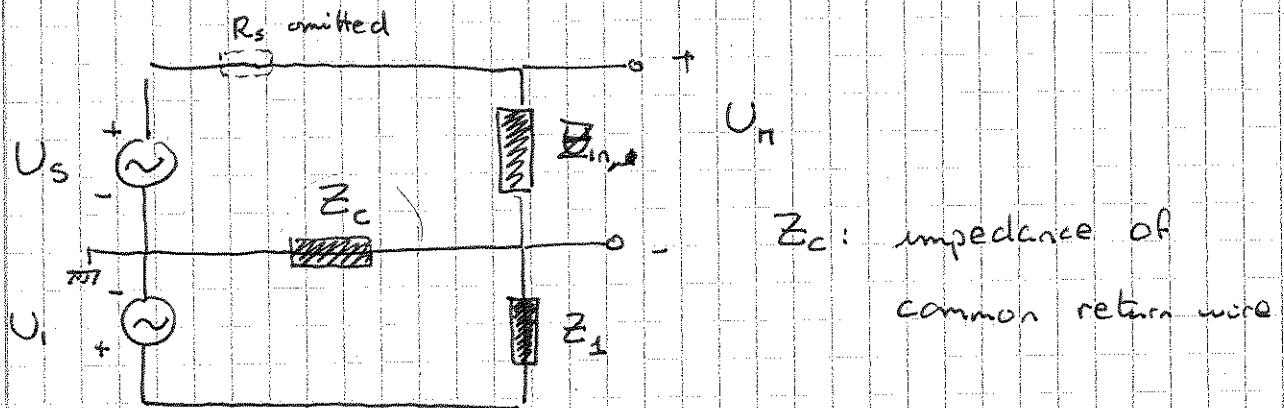- multewire cable with single return wire
- direct contact with conductive body



Typically $|Z_c| \ll |Z_L|$ and $|Z_c| \ll |Z_1|$


$$U_M \approx \frac{Z_c}{Z_c + Z_1} U_1 \approx - \frac{Z_c}{Z_1} U_1 = - Z_c I_1$$

Countermeasures

- reduce I_1 or Z_c
- use separate return wires
- dedicate one layer for ground only in ~~PBCs~~

PBCs
↑
printed circuit boards

Grounding

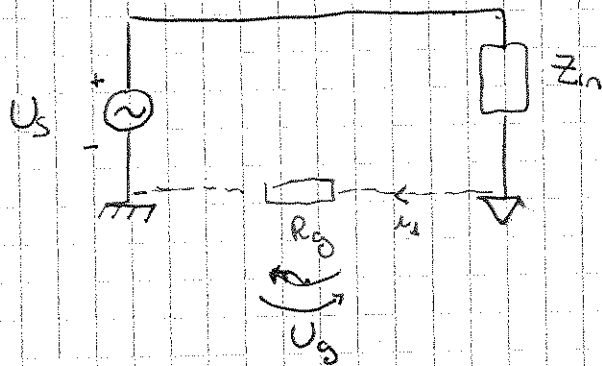

$$U_n + U_g$$

↑
problematic when U_n
is small

• ~~Do not use shield as return wire~~

SLIDE • Ground only at one end (inductive coupling)

SLIDE • do not use shield as return wire

⇒ need ^{sensor} output to be

differential ended (i.e.,
not relative to ground)

- active sensors ok

- passive sensors → make it independent of ground!

single-ended ⇒ differentially
- ended

SLIDES about this!



coax cable ⇒ shielded cable where the
shield is used as return wire

shielded-pair cable ⇒ shield is used as shield only!


Radiation coupling

• EM radiation sources:

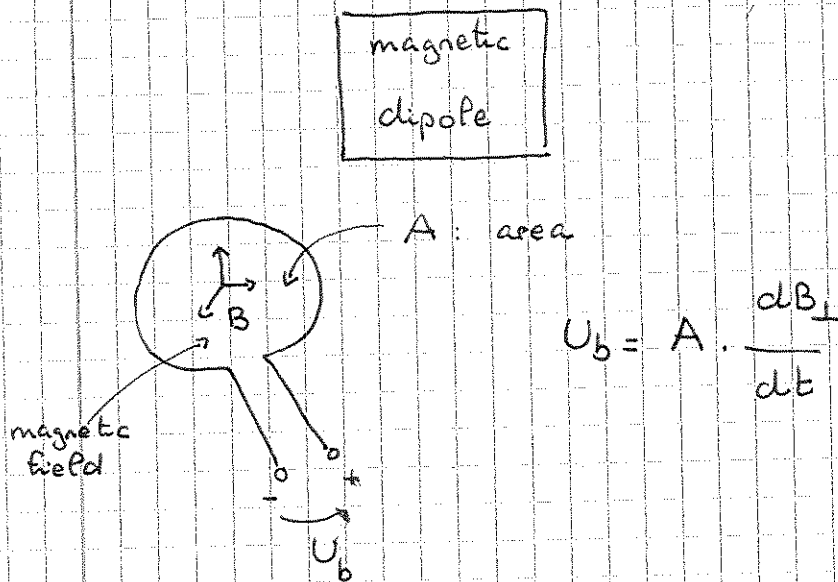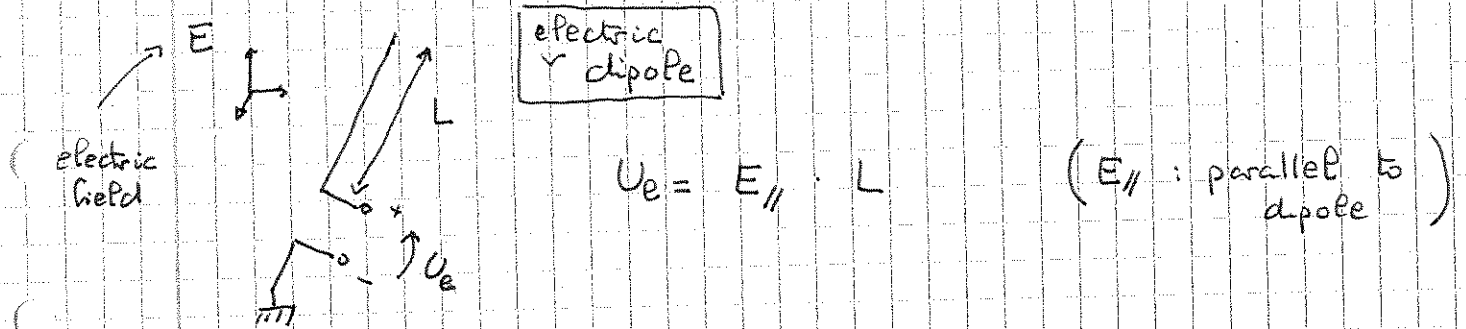- radio ~~mobile~~ + TV + wireless
- any electronic device containing AC circuit
- How EM enters a meas. system



• Countermeasures


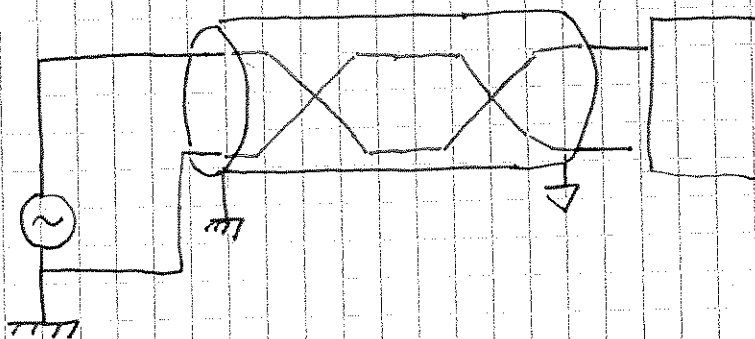


shield : protect against E-field
(Faraday cage)

twisted cable :
protect against M field.

Bandwidth of measurement systems

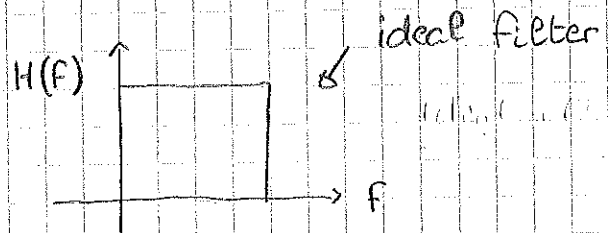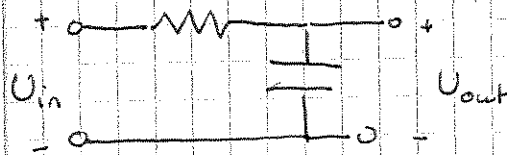- bandwidth of signal vs bandwidth of instrument
- Instrument: low-pass filter of first order;
cut-off freq $f_g = B$




- Transfer function filter

$$H(j\omega) = \frac{1}{j\omega C} = \frac{1}{\frac{1}{j\omega C} + R} = \frac{1}{1 + j\omega CR} = \frac{1}{1 + j2\pi f CR}$$

$$= \frac{1}{1 + j \frac{f}{f_g}}, \quad f_g = \frac{1}{2\pi CR}$$

- Amplitude

$$|H(j2\pi f)| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_g}\right)^2}}$$

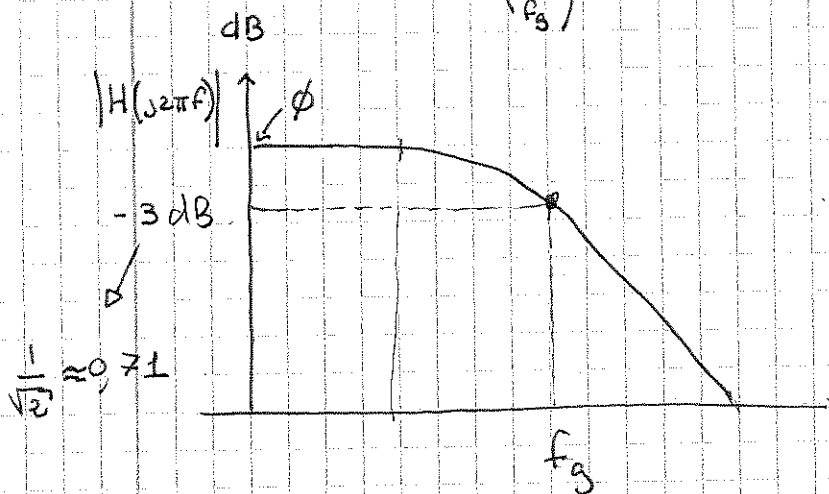

f	$ H(j2\pi f) $	amplitude error
f_g	0,71	29%
$f_g/2$	0,89	11%
$f_g/5$	0,98	2%
$f_g/10$	0,995	0,5%


- Bandwidth of a signal

⇒ Largest harmonic component present in the signal

Fast variations $\Leftrightarrow$ Large bandwidth




rise time

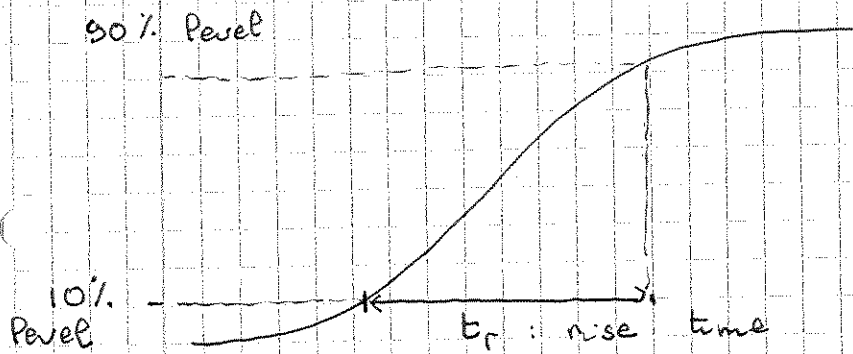

- Rule: if a signal has bandwidth B , its rise time cannot be smaller than

$$t_r \approx \frac{0,35}{B}$$

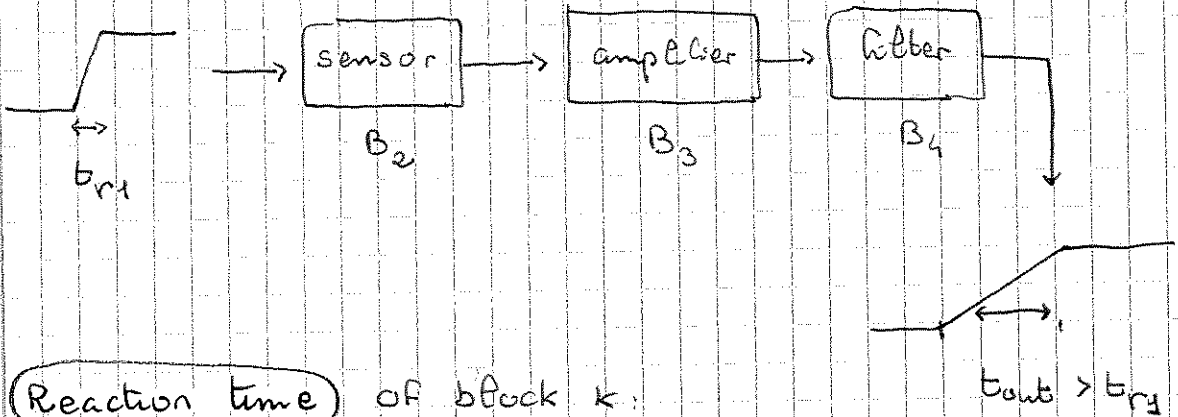

- Reaction time of block k :

$$t_k = \frac{0,35}{B_k}$$

- It can be shown that

$$t_{out} \approx \sqrt{t_{r1}^2 + t_{r2}^2 + t_{r3}^2 + t_{r4}^2}$$


Oscilloscope probes

$$R_2 = 1 \text{ M}\Omega$$

$$C_2 = 20 \text{ pF} + 80 \text{ pF}$$

↑
cables

$$= 100 \text{ pF}$$

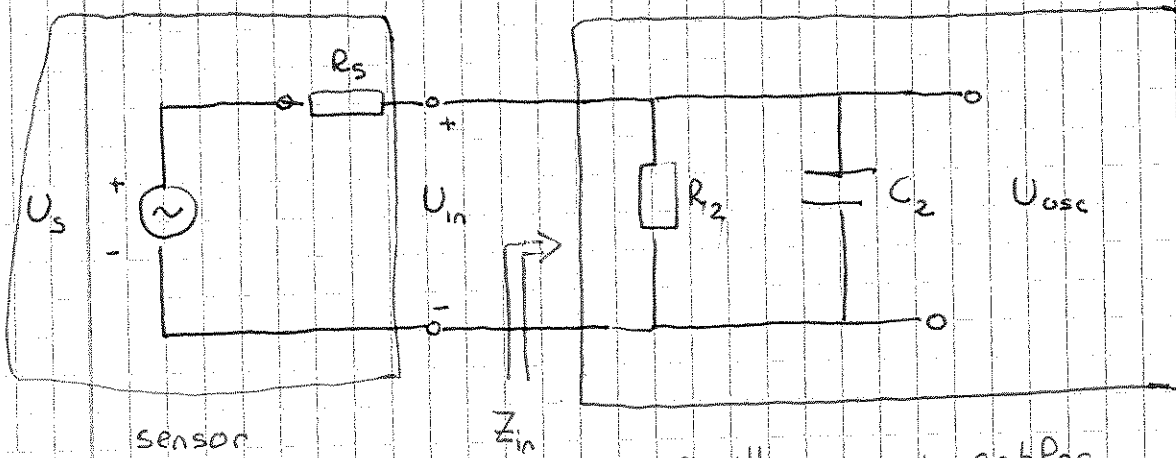

sensor

Oscilloscope + cables

• input impedance $Z_{in} = R_2 \parallel C_2 = \frac{R_2 \cdot \frac{1}{j\omega C_2}}{R_2 + \frac{1}{j\omega C_2}} = \frac{R_2}{j\omega C_2 R_2 + 1}$

• Want $U_{osc} \approx U_s$
 $\Rightarrow |Z_{in}| \gg R_s$

• Problems if

• $R_s \approx R_2$


[does not typically occur]

• or if ~~$\omega C_2 R_2 \gg 1$~~ ~~$\omega C_2 R_2 \gg 1$~~ ~~$\omega C_2 R_2 \gg 1$~~

$\omega C_2 R_2 \gg 1 \Rightarrow |Z_{in}| \approx \frac{1}{\omega C_2} \leftarrow \text{comparable with } R_s$

$\Rightarrow$ big freq. dep. attenuation.

• Solution: increase Z_{in} using probes

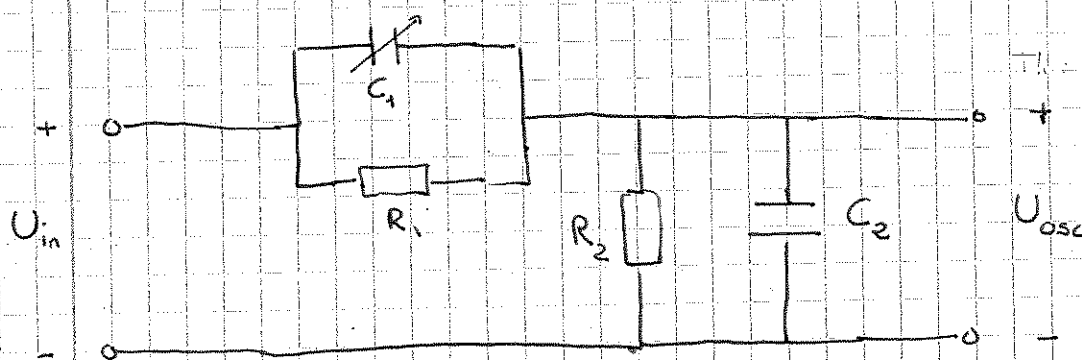

- Problem: gain reduction (may be frequency dependent)

$$\frac{U_{osc}}{U_{in}} = \frac{\frac{R_2}{j\omega R_2 C_2 + 1}}{\frac{R_1}{j\omega R_1 C_1 + 1} + \frac{R_2}{j\omega R_2 C_2 + 1}}$$

- at $\omega = 0$ (DC component)

$$\frac{U_{osc}}{U_{in}} = \frac{R_2}{R_1 + R_2}$$

TPS $\rightarrow$ how do I make gain reduction independent of ω and, hence, constant over frequency?

- Gain reduction independent of ω if

$$R_1 C_1 = R_2 C_2 \rightarrow \text{obtained by adjusting } C_1$$

$$\Rightarrow \frac{U_{osc}}{U_{in}} = \frac{R_2}{R_1 + R_2} \quad \text{for all } \omega \text{ if } R_1 C_1 = R_2 C_2$$

- New input impedance

$$Z'_{in} = R_1 \parallel C_1 + R_2 \parallel C_2 = \frac{R_1}{j\omega R_1 C_1 + 1} + \frac{R_2}{j\omega R_2 C_2 + 1}$$

$$\begin{aligned} R_1 C_1 = R_2 C_2 & \Rightarrow \frac{R_1 + R_2}{j\omega R_2 C_2 + 1} = \frac{R_1 + R_2}{R_2} Z'_{in} \end{aligned}$$

- Summary:

o amplitude reduction by $\frac{R_2}{R_1 + R_2}$

o input impedance increase by $\frac{R_1 + R_2}{R_2}$

Example: 10x probe oscilloscope

$\Rightarrow$ 10x impedance increase $\Rightarrow$ 10x gain reduction

$$\frac{R_2}{R_1 + R_2} = \frac{1}{10} \Rightarrow \frac{R_1}{R_2} + 1 = 10 \Rightarrow \frac{R_1}{R_2} = 9$$

Typically, $R_2 = 1 \text{ M}\Omega$


$$C_2 = 20 \text{ pF} + 80 \text{ pF} = 100 \text{ pF}$$

$$\Rightarrow R_1 = 9 \text{ M}\Omega$$

To choose C_1 ,

$$R_2 C_2 = R_1 C_1 \Rightarrow C_1 = \frac{R_2}{R_1} C_2 = 100 \frac{1}{9} \text{ pF} = 11,11 \text{ pF}$$
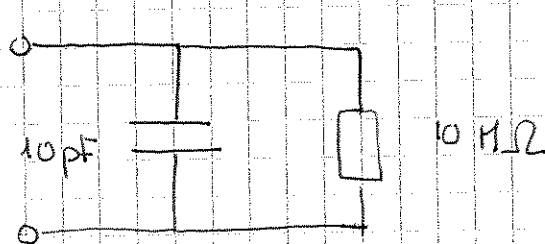
$$Z'_m \Rightarrow \begin{cases} R'_m = R_1 + R_2 = 10 \text{ M}\Omega \\ C'_m = C_1 \parallel C_2 = \frac{C_1 C_2}{C_1 + C_2} = \frac{C_2}{\frac{R_1}{R_2} + 1 + \frac{R_2}{R_1}} = 10 \text{ pF} \end{cases}$$



$$\frac{C_2}{C_1} = \frac{R_1}{R_2} = 9$$