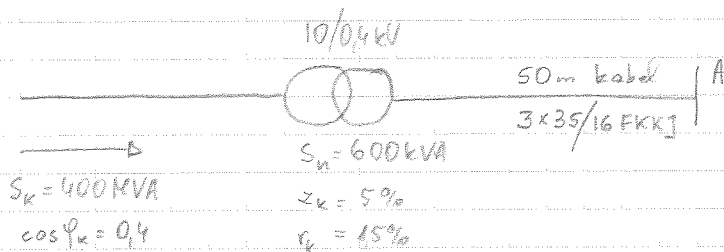


11.1/1

Impedanzsumming:

$$U_e = 0,4 \text{ kV}$$

Nähet:

$$S_k = \frac{U_e^2}{Z_k} \Rightarrow Z_k = \frac{U_e^2}{S_k} = \frac{0,4}{400} = 0,4 \cdot 10^{-3} \Omega/\text{fas}$$

$$R_k = Z_k \cdot \cos \varphi_k = 0,4 \cdot 10^{-3} \cdot 0,4 = 0,16 \cdot 10^{-3} \Omega/\text{fas}$$

$$X_k = Z_k \cdot \sin \varphi_k = 0,4 \cdot 10^{-3} \cdot 0,916 = 0,37 \cdot 10^{-3} \Omega/\text{fas}$$

Transformator:

$$R_k = r_k \cdot \frac{U_e^2}{S_n} = 0,015 \cdot \frac{0,4^2}{0,6} = 4 \cdot 10^{-3} \Omega/\text{fas}$$

! OBS!

$$X_k = x_k \cdot \frac{U_e^2}{S_n} = \sqrt{0,05^2 - 0,015^2} \cdot \frac{0,4^2}{0,6} = 12,7 \cdot 10^{-3} \Omega/\text{fas}$$

Kabel FKKJ (Cu-PE)

$$\text{Enl. fig 6.5 s 32} \Rightarrow R = 0,524 \Omega/\text{km}; X = 0,079 \Omega/\text{km} / \text{fas}$$

$$R_k = 0,05 \cdot 0,524 = 26,2 \cdot 10^{-3} \Omega/\text{fas}$$

$$X_k = 0,05 \cdot 0,079 = 3,95 \cdot 10^{-3} \Omega/\text{fas}$$

$$\Sigma R_k = (0,16 + 4,0 + 26,2) \cdot 10^{-3} = 30,36 \cdot 10^{-3} \Omega/\text{fas}$$

$$\Sigma X_k = (0,37 + 12,7 + 3,95) \cdot 10^{-3} = 17,02 \cdot 10^{-3} \Omega/\text{fas}$$

$$Z_{KA} = \sqrt{30,36^2 + 17,02^2} \cdot 10^{-3} = 34,8 \cdot 10^{-3} \Omega/\text{fas}$$

$$\underline{\underline{I_{KA}}} = \frac{U/\sqrt{3}}{Z_{KA}} = \frac{0,4}{\sqrt{3} \cdot 34,8 \cdot 10^{-3}} = \underline{\underline{6,64 \text{ kA}}}$$

$$\underline{\underline{S_{KA}}} = \sqrt{3} \cdot U \cdot I_{KA} = \sqrt{3} \cdot 0,4 \cdot 6,64 = \underline{\underline{4,6 \text{ MVA}}}$$

Delkortslutningseffekter:

11.1/2

Nätet : $S_k = 400 \text{ MVA}$

Trafo : $S_k = \frac{S_n}{z_k} = \frac{600 \cdot 10^3}{0,05} = 12 \text{ MVA}$

Kabel :

Enl. tidigare : $R_k = 26,2 \cdot 10^{-3} \Omega/\text{fas}$

$X_k = 3,95 \cdot 10^{-3} \Omega/\text{fas}$

$Z_k = \sqrt{26,2^2 + 3,95^2} \cdot 10^{-3} = 26,5 \cdot 10^{-3} \Omega/\text{fas}$

$S_k = \frac{U^2}{Z_k} = \frac{0,4^2}{26,5 \cdot 10^{-3}} = 6,04 \text{ MVA}$


$\frac{1}{S_{KA}} = \frac{1}{400} + \frac{1}{12} + \frac{1}{6,04}$

$\Rightarrow \underline{\underline{S_{KA} = 3,98 \text{ MVA}}} \Rightarrow I_{KA} = \frac{S_{KA}}{\sqrt{3}U} = \frac{3,98}{\sqrt{3} \cdot 0,4} = \underline{\underline{5,74 \text{ kA}}}$

Tänför och diskutera

$$S_{KA} = ? ; I_{KA} = ?$$

11.3

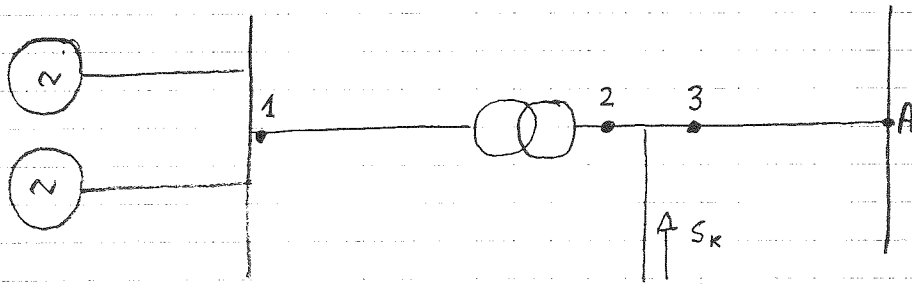

1) Generatorer: $S_n = 50 \text{ MVA}$; $S_k = 6 \times S_n$

$$S_{K1} = 2 \cdot 6 \cdot S_n = 2 \cdot 6 \cdot 50 = 600 \text{ MVA}$$

2) Trafo $S_{KT} = \frac{S_n}{x_k} = \frac{100}{0,1} = 1000 \text{ MVA}$

$$S_{K2} = \frac{S_{K1} \cdot S_{KT}}{S_{K1} + S_{KT}} = \frac{600 \cdot 1000}{1600} = 375 \text{ MVA}$$

3) $S_{K3} = S_{K2} + S_k = 375 + 120 = 495 \text{ MVA}$

Luftledning: $S_{KL} = \frac{U^2}{X} = \frac{130^2}{30} = 563,33 \text{ MVA}$

A) $\underline{\underline{S_{KA} = \frac{S_{K3} \cdot S_{KL}}{S_{K3} + S_{KL}} = \frac{495 \cdot 563,33}{1058,33} = 263,5 \text{ MVA}}}$

$\underline{\underline{I_{KA} = \frac{S_{KA}}{\sqrt{3} \cdot U} = \frac{263,5}{\sqrt{3} \cdot 130} = 1,17 \text{ kA}}}$

$$S_{KW2} = ? ; \varphi_{KW2} = ? ; I_{SQ1} = ? ; I_{SQ2} = ?$$

11.4/1

Räkna med impedanssummeringsmetoden då fasvinkeln skall anges.

1. Q1-sidan

Nätet: $S_K = 800 \text{ MVA}$ (räkna på 70 kV-sidan)

$$Z_N = \frac{U^2}{S_K} = \frac{70^2}{800} = 6,125 \Omega/\text{fas}$$

$$R_{KN} = Z_N \cos \varphi_K = 6,125 \cdot \cos 90^\circ = 0$$

$$X_{KN} = Z_N \sin \varphi_K = 6,125 \cdot \sin 90^\circ = 6,125 \Omega/\text{fas}$$

Träfa T1

$$R_{KT1} = r_K \frac{U^2}{S_n} = 0,02 \frac{70^2}{50} = 1,96 \Omega/\text{fas}$$

$$X_{KT1} = x_K \frac{U^2}{S_n} = \sqrt{0,1^2 - 0,02^2} \cdot \frac{70^2}{50} = 9,6 \Omega/\text{fas}$$

$$Z_{Q1} = 0 + 1,96 + j(6,125 + 9,6) = 1,96 + j15,725 = 15,85 / 82,9^\circ \Omega/\text{fas}$$

$$I_{Q1} = \frac{U}{\sqrt{3} Z_{Q1}} = \frac{70 \cdot 10^3}{\sqrt{3} \cdot 15,85} = 2550 \text{ A}$$

$$\underline{I_{SQ1}} = 2,5 \cdot 2550 = \underline{\underline{6375 \text{ A}}} \quad (\text{ca } 6400 \text{ A})$$

2. Q2-sidan

$$Z_{Q2} = \frac{U^2}{S_K} = \frac{70^2}{400} = 12,25 \Omega/\text{fas}$$

$$\cos \varphi_K = 0,342 \Rightarrow \varphi_K = 70^\circ$$

$$Z_{Q2} = 12,25 / 70^\circ = (4,19 + j11,51) \Omega/\text{fas}$$

$$I_{Q2} = \frac{U}{\sqrt{3} Z_{Q2}} = \frac{70 \cdot 10^3}{\sqrt{3} \cdot 12,25} = 3300 \text{ A}$$

$$\underline{I_{SQ2}} = 2,5 \cdot 3300 = \underline{\underline{8250 \text{ A}}}$$

3. Q1 - sidan // Q2 - sidan

11.4/2

$$\begin{aligned} Z_{W1} &= \frac{Z_{Q1} \cdot Z_{Q2}}{Z_{Q1} + Z_{Q2}} = \frac{15,85 \angle 82,9^\circ \cdot 12,25 \angle 70^\circ}{1,96 + j 15,725 + 4,19 + j 11,51} = \\ &= \frac{194,16 \angle 152,9^\circ}{27,92 \angle 77,28^\circ} = 6,95 \angle 75,62^\circ \Omega / \text{fas} = (1,73 + j 6,73) \Omega / \text{fas} \end{aligned}$$

4. Trafo T2 (vid 70 kV)

$$R_{KT2} = r_K \frac{U^2}{S_n} = 0,02 \frac{70^2}{15} = 6,53 \Omega / \text{fas}$$

$$X_{KT2} = x_K \frac{U^2}{S_n} = \sqrt{0,09^2 - 0,02^2} \frac{70^2}{15} = 28,66 \Omega / \text{fas}$$

$$\begin{aligned} 5. \quad Z_{W2} &= 6,53 + 1,73 + j(28,66 + 6,73) = 8,26 + j 35,39 = \\ &= 36,34 \angle 76,86^\circ \Omega / \text{fas} \quad (\text{vid } 70 \text{ kV}) \end{aligned}$$

$$\underline{\underline{\varphi_{KW2} = 76,86^\circ}}$$

$$\underline{\underline{S_{KW2} = \frac{U^2}{Z_{W2}} = \frac{70^2}{36,34} = 134,8 \text{ MVA}}}$$

$$\left(I_{KW2} = \frac{S_{KW2}}{\sqrt{3} \cdot U_{W2}} = \frac{134,8}{\sqrt{3} \cdot 20} = 3,89 \text{ kA} \right)$$