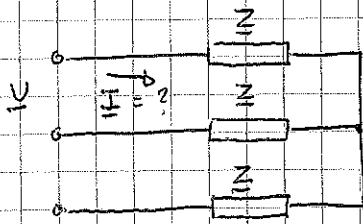


2.1

$$\underline{Z} = 12 + j6 \, \Omega ; \quad U = 380 \, \text{V};$$

2.1

a)




linjeström - fasström

$$\underline{Z} = 12 + j6 = 13,42 \angle 26,57^\circ \, \Omega/\text{fas}$$

$$R + jX$$

Ekvivalent Y-fas

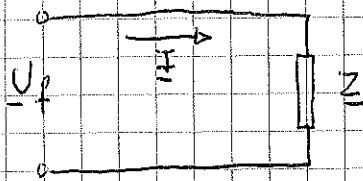

$$U_f = \frac{U}{\sqrt{3}} = \frac{380}{\sqrt{3}} = 220 \, \text{V}$$

$$\underline{I} = \frac{\underline{U}_f}{\underline{Z}} = \frac{220 \angle 0^\circ}{13,42 \angle 26,57^\circ} = 16,4 \angle -26,57^\circ \, \text{A}$$



$$P = 3 U_f I \cos \varphi = 3 \cdot 220 \cdot 16,4 \cdot \cos 26,57^\circ = 9681 \, \text{W} = 9,68 \, \text{kW}$$

$$\text{alt} \quad P = 3 R I^2 = 3 \cdot 12 \cdot (16,4)^2 = 9,68 \, \text{kW}$$

$$Q = 3 U_f I \sin \varphi = 3 \cdot 220 \cdot 16,4 \cdot \sin 26,57^\circ = 4841 \, \text{VAR} = 4,84 \, \text{kVAR}$$

$$\text{alt} \quad Q = 3 X I^2 = 3 \cdot 6 \cdot (16,4)^2 = 4,84 \, \text{kVAR}$$

b)

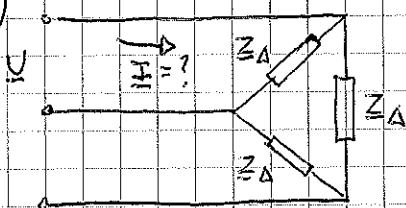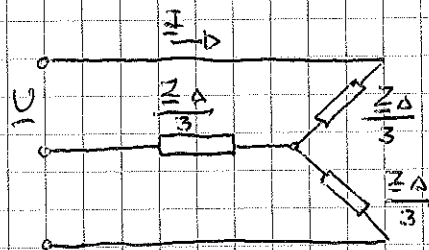 $\Rightarrow$ transformera
till ekvivalent
Y-kopplad krets

$$\underline{Z}_\Delta = 12 + j6 \, \Omega \Rightarrow \frac{\underline{Z}_\Delta}{3} = 4 + j2 = 4,47 \angle 26,57^\circ \, \Omega/\text{fas}$$

Ekv. Y-fas



$$\underline{I} = \frac{220 \angle 0^\circ}{4,47 \angle 26,57^\circ} = 49,2 \angle -26,57^\circ \, \text{A}$$

(x3)

$$P = 3 U_f I \cos \varphi = 3 \cdot 220 \cdot 49,2 \cdot \cos 26,57^\circ = 29053 \, \text{W} = 29,05 \, \text{kW}$$

$$Q = \sqrt{3} U I \sin \varphi = \sqrt{3} \cdot 380 \cdot 49,2 \sin 26,57^\circ = 14484 \, \text{VAR} = 14,48 \, \text{kVAR}$$


2.2

2.2


$$E_0 = 500 \text{ V} ; Z_i = 0,5 + j3 \Omega/\text{fas}$$

$$\text{Belastung: } \cos \varphi = 0,8 \text{ ind} ; Z_b = 9 \Omega/\text{fas}$$

a) $\underline{I} = ?$

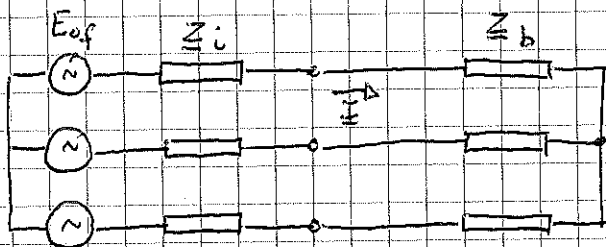

Ekv. Y-fas:

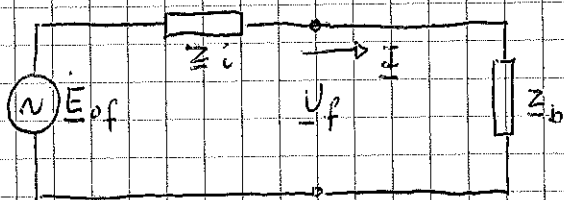

$$E_{0f} = \frac{E_0}{\sqrt{3}} \angle 0^\circ \text{ V referens}$$

$$Z_i = 0,5 + j3 = 3,04 \angle 80,54^\circ \Omega/\text{fas}$$

$$\cos \varphi = 0,8 \Rightarrow \varphi = 36,87^\circ \text{ ind}$$

$$Z_b = 9 \angle 36,87^\circ \Omega/\text{fas} = 7,2 + j5,4 \Omega/\text{fas}$$


$$\underline{I} = \frac{\underline{E}_{0f}}{\underline{Z}_i + \underline{Z}_b} = \frac{500/\sqrt{3} \angle 0^\circ}{0,5 + j3 + 7,2 + j5,4} = \frac{500\sqrt{3} \angle 0^\circ}{11,4 \angle 47,49^\circ} = 25,3 \angle -47,5^\circ \text{ A}$$

b) $\underline{U}_f = \underline{Z}_b \underline{I} = 9 \angle 36,87^\circ \cdot 25,3 \angle -47,5^\circ = 227,7 \angle -10,6^\circ \text{ V}$

$$U = \sqrt{3} \cdot 227,7 = 394,4 \text{ V}$$

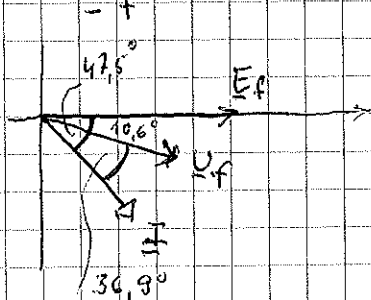c) $\underline{S}_f = \underline{U}_f \underline{I}^* = 227,7 \angle -10,6^\circ \cdot 25,3 \angle 47,5^\circ = 5761 \angle 36,9^\circ \text{ VA}$

$$\underline{S} = 3 \underline{S}_f = 17282 \angle 36,9^\circ = (13826 + j10369) \text{ VA}$$




$$\begin{matrix} \downarrow & \downarrow \\ P(\text{W}) & Q(\text{VAR}) \end{matrix}$$

$$\begin{matrix} 14787,8 \\ 14805 \end{matrix}$$


d) $P_g = 3 R_i I^2 = 3 \cdot 0,5 \cdot (25,3)^2 = 960 \text{ W}$

2.3

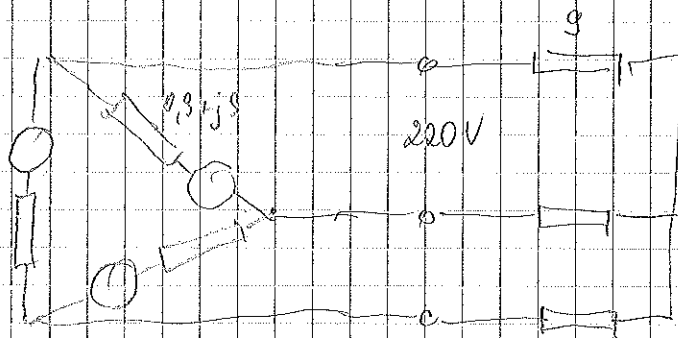

$$I = \frac{220}{\sqrt{3} \cdot 9} = 14,11 \text{ A}$$
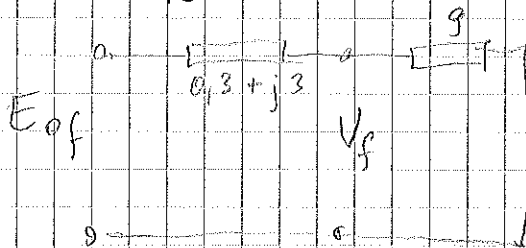
$$I_{\Delta} = \frac{14,1}{\sqrt{3}} = 8,15 \text{ A}$$



$$E_{of} = V_f + (0,3 + j3) \cdot 14,11 \angle 0$$

$$= 127 + 4,23 + j42,33$$

$$= 131,23 + j42,33 = 137,9 \text{ V} \angle 17,88^\circ$$

$$E_0 = 238,85 \text{ V}$$


2.4

$$U = 400 \text{ V} ; P = 10 \text{ kW} ;$$

2.4 / 1


Last - 3 lika motstånd (resistorer)

a) $R_{\Delta} = ? ; R_Y = ?$

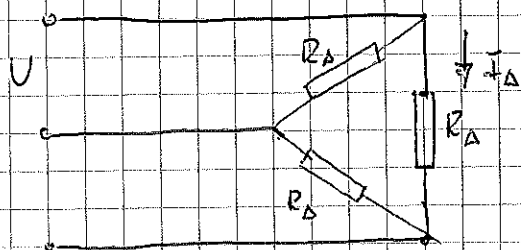

$$P = 3 R_{\Delta} I_{\Delta}^2 = 3 R_{\Delta} \left(\frac{U}{R_{\Delta}} \right)^2 = 3 \frac{U^2}{R_{\Delta}}$$
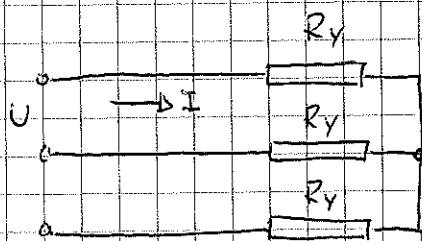
$$\Rightarrow \underline{\underline{R_{\Delta} = 3 \frac{U^2}{P} = 3 \frac{400^2}{10 \cdot 10^3} = 48 \, \Omega}}$$




$$P = 3 R_Y I^2 = 3 R_Y \left(\frac{U}{\sqrt{3} R_Y} \right)^2 = \frac{U^2}{R_Y}$$

$$\Rightarrow \underline{\underline{R_Y = \frac{U^2}{P} = \frac{R_{\Delta}}{3} = 16 \, \Omega}}$$

alt:

Ekv Y-fas

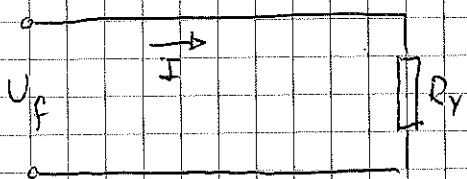


$$R_Y = \frac{U_f}{I} = \frac{U_f^2}{P_f} = \frac{\left(\frac{400}{\sqrt{3}} \right)^2}{\frac{10 \cdot 10^3}{3}} = 16 \, \Omega$$

$$P_f = U_f I = \frac{P}{3}$$

$$R_{\Delta} = 3 R_Y = 48 \, \Omega$$


2.4

2.4/2

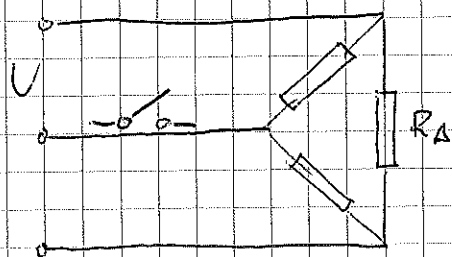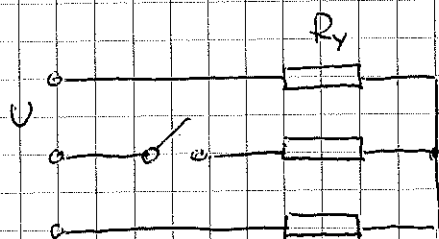b) $P = ?$ 


$$P_A = \frac{U^2}{R_{\text{ekv}}} = \frac{U^2}{\frac{R_A \cdot 2R_A}{3R_A}} = \frac{U^2}{\frac{2}{3}R_A} =$$

$$= \frac{400^2}{\frac{2}{3} \cdot 48} = \underline{\underline{5000 \text{ W}}}$$



$$P_Y = \frac{U^2}{R_{\text{ekv}}} = \frac{U^2}{2R_Y} = \frac{400^2}{2 \cdot 16} = \underline{\underline{5000 \text{ W}}}$$

med nollan:

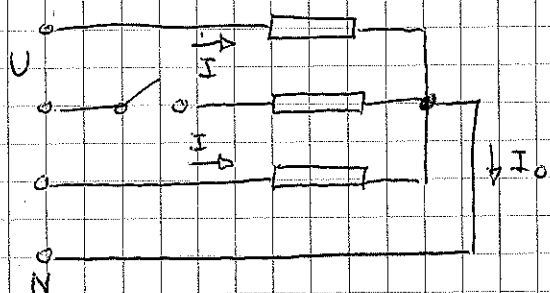


$$P_{Y0} = 2 \cdot \frac{U_f^2}{R_Y} = 2 \cdot \frac{\left(\frac{400}{\sqrt{3}}\right)^2}{16} = \underline{\underline{6666,7 \text{ W}}}$$

Extra! Hur stor är I_0 ?

$$I = \frac{U_f}{R_Y} = \frac{400}{\sqrt{3} \cdot 16} = 14,43 \text{ A}$$

$$\text{OBS! } \underline{I_0} = \underline{I_R} + \underline{I_T} \Rightarrow |I_0| = 14,43 \text{ A}$$

rita:

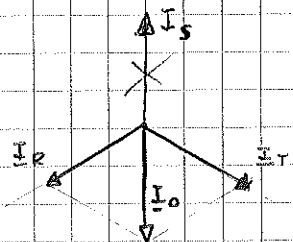


2.5

$$U = 3,2 \text{ kV}$$

$$P = 90 \text{ kW} \quad \cos \varphi = 0,85$$

2.5

Ekv. Y-fas :

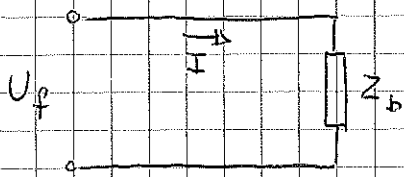

$$P = \sqrt{3} \cdot U \cdot I \cos \varphi \Rightarrow$$


$$I = \frac{P}{\sqrt{3} U \cos \varphi} = \frac{90 \cdot 10^3}{\sqrt{3} \cdot 3,2 \cdot 10^3 \cdot 0,85} = \underline{\underline{19,1 \text{ A}}}$$

$$Z = \frac{U_f}{I} = \frac{3,2 \cdot 10^3}{\sqrt{3} \cdot 19,1} = 98,7 \text{ } \Omega/\text{fas}$$

$$R = Z \cos \varphi = 82,2 \text{ } \Omega/\text{fas}$$

$$X_L = Z \sin \varphi = 50,9 \text{ } \Omega/\text{fas}$$
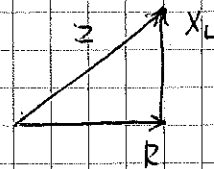
$$\underline{Z} = 82,2 + j 50,9 \text{ } \Omega/\text{fas}$$



2.6


$$U = 220 \text{ V}$$

$$Z = R + jX = 6 + j8 = 10 \angle 53,13^\circ \text{ } \Omega/\text{fas}$$

2.6

a) Y-kopplad last

Ekv Y-fas

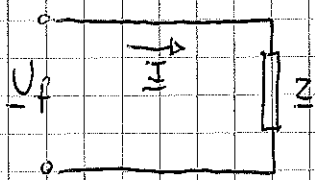


$$\underline{I} = \frac{\underline{U}_f}{Z} = \frac{220/\sqrt{3} \angle 0^\circ}{10 \angle 53,13^\circ} = \underline{12,7 \angle -53,13^\circ \text{ A}}$$

$$P = 3 R I^2 = 3 \cdot 6 \cdot (12,7)^2 = \underline{2,9 \text{ kW}}$$

$$\cos 53,13^\circ \Rightarrow \underline{\cos \varphi = 0,6}$$

b) Δ-kopplad last

Ekv Y-fas

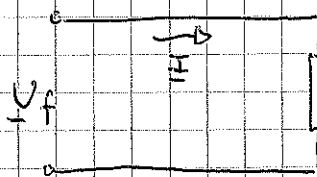

$$\underline{Z} = \frac{6 + j8}{3} = 2 + j2,67 = 3,33 \angle 53,13^\circ \text{ } \Omega/\text{fas}$$

$$\underline{I} = 3 \cdot 12,7 \angle -53,13^\circ = \underline{38,1 \angle -53,13^\circ \text{ A}}$$

$$P = 3 \cdot 2 \cdot (38,1)^2 = \underline{8,7 \text{ kW}}$$


$$\underline{\cos \varphi = 0,6}$$

2.7

$$U_f = 127 \text{ V}; \quad I = 40 \text{ A} \quad ; \quad P = 12 \text{ kW}$$

2.7

Ekv Y-fas.

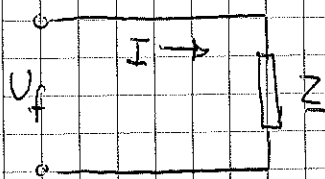

$$P = 3 U_f I \cos \varphi \Rightarrow$$


$$\Rightarrow \cos \varphi = \frac{P}{3 U_f I} = \frac{12000}{3 \cdot 127 \cdot 40} = \underline{\underline{0,987}}$$

$$\varphi = \pm 38,06^\circ \quad \text{ind eller kap last}$$

$$U = \sqrt{3} \cdot 127 = \underline{\underline{220 \text{ V}}}$$

$$P = 3 R I^2 \Rightarrow R = \frac{P}{3 I^2} = \frac{12000}{3 \cdot 40^2} = 2,5 \text{ } \Omega / \text{fas}$$
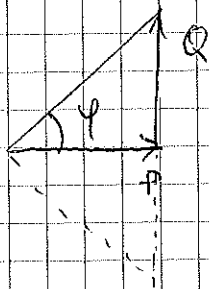
$$Q = P \cdot \tan \varphi = 12000 \cdot \tan \pm 38,06^\circ = \pm 9396 \text{ VAR}$$




$$X = \frac{Q}{3 I^2} = \frac{9396}{3 \cdot 40^2} = 1,96 \text{ } \Omega / \text{fas}$$


$$\underline{\underline{Z = 2,5 \pm j 1,96 \text{ } \Omega / \text{fas}}}$$

2.8

$$I_{\Delta} = 40 \text{ A}; \quad Z = 6 + j4 \quad \Omega/\text{fas}$$

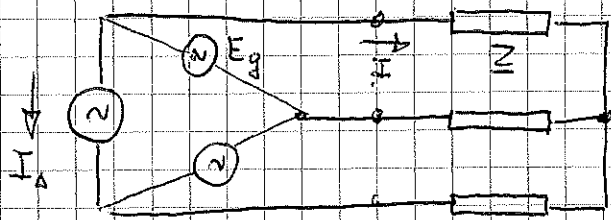2.8

Eku Y-fas:

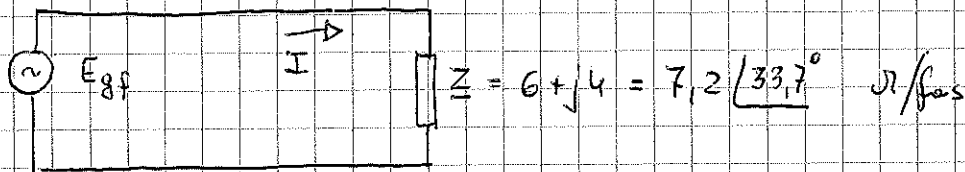

$$I = \sqrt{3} I_{\Delta} = \sqrt{3} \cdot 40 = \underline{\underline{69,3 \text{ A}}}$$


$$U_f = Z I = 7,2 \cdot 69,3 = \underline{\underline{499 \text{ V}}}$$

$$P = 3 R I^2 = 3 \cdot 6 \cdot (69,3)^2 = \underline{\underline{86,44 \text{ kW}}}$$

$$Q = 3 X I^2 = 3 \cdot 4 \cdot (69,3)^2 = \underline{\underline{57,63 \text{ kVAR}}}$$

2.9

2.9

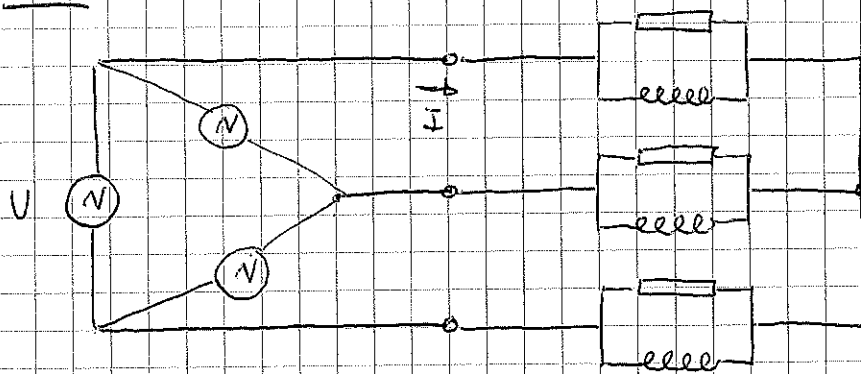



$$U = 500 \text{ V}$$

$$I = 30 \text{ A}$$

$$\cos \varphi = 0,8$$

$$\varphi = 36,87^\circ$$

Ekv. Y-fas:

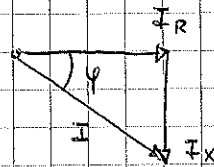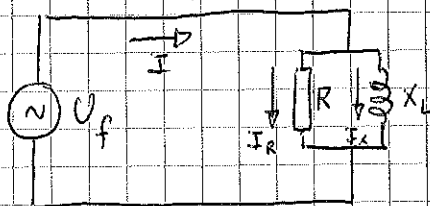

$$P = 3 U_f I \cos \varphi = 3 \frac{500}{\sqrt{3}} \cdot 30 \cdot 0,8 = 20,79 \text{ kW}$$

$$I_R = I \cos \varphi = 30 \cdot 0,8 = 24 \text{ A}$$

$$I_X = I \sin \varphi = 30 \cdot 0,6 = 18 \text{ A}$$

$$P = 3 R I_R^2 \Rightarrow R = \frac{20786}{3 \cdot (24)^2} = \underline{\underline{12 \text{ } \Omega / \text{fas}}}$$

$$Q = 3 U_f I \sin \varphi = 3 \frac{500}{\sqrt{3}} \cdot 30 \cdot 0,6 = 15,59 \text{ kVAR}$$

$$Q = 3 X_L I_X^2 \Rightarrow X_L = \frac{Q}{3 (I_X)^2} = \underline{\underline{16 \text{ } \Omega / \text{fas}}}$$

alt

$$P = 3 \frac{U_f^2}{R}$$

$$Q = 3 \frac{U_f^2}{X_L}$$


$$S = P + jQ$$

2.10


2.10

$$\underline{Z}_1 = (15 + j9) \Omega / \text{fas} - Y; U = 380V$$

$$X_c = 100 \Omega - \Delta$$

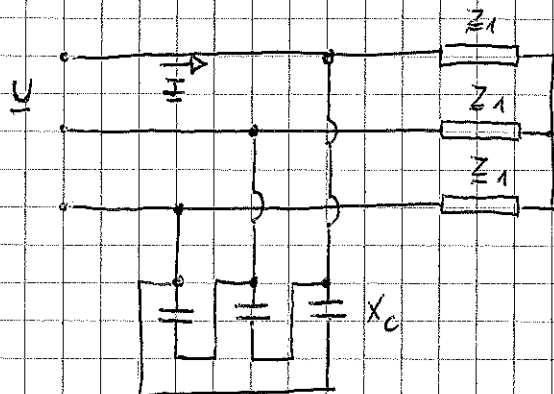


a) Ekv. Y-fas:

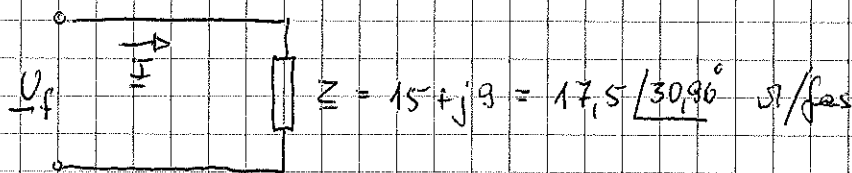

$$\underline{I} = \frac{\underline{U}_f}{\underline{Z}} = \frac{380/\sqrt{3} \angle 0^\circ}{17,5 \angle 30,96^\circ} = \underline{12,54 \angle -30,96^\circ} \text{ A}$$

$$\cos 30,96^\circ = 0,86 \text{ inel}$$

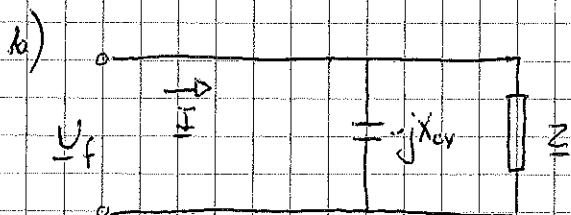

$$X_c = 100 \Omega$$

$$X_{cy} = \frac{1}{3} 100 = 33,3 \Omega / \text{fas}$$

$$\begin{aligned} \underline{Z}_{\text{tot}} &= \underline{Z} \parallel -jX_{cy} = \frac{(15 + j9)(-j33,3)}{15 + j9 - j33,3} = \frac{299,7 - j499,5}{15 - j24,3} \\ &= \frac{582,5 \angle -59,0^\circ}{28,6 \angle -58,4^\circ} = \underline{20,4 \angle -0,6^\circ} \Omega / \text{fas} \end{aligned}$$

$$\underline{I} = \frac{\underline{U}_f}{\underline{Z}_{\text{tot}}} = \frac{220 \angle 0^\circ}{20,4 \angle -0,6^\circ} = \underline{10,78 \angle 0^\circ} \text{ A}$$

I i fas med U_f
förklara faskomp

alt:



$$\begin{aligned} P &= 3U_p I \cos \varphi \\ Q &= 3U_p I \sin \varphi \\ Q_c &= 3 \frac{U^2}{X_c} \end{aligned}$$

$$Q_{\text{res}} = Q_L - Q_c \sim 0 \text{ VAR}$$

2.11

 $U = 220V$; Lampor - Δ - $3kW = P_L$

2.11

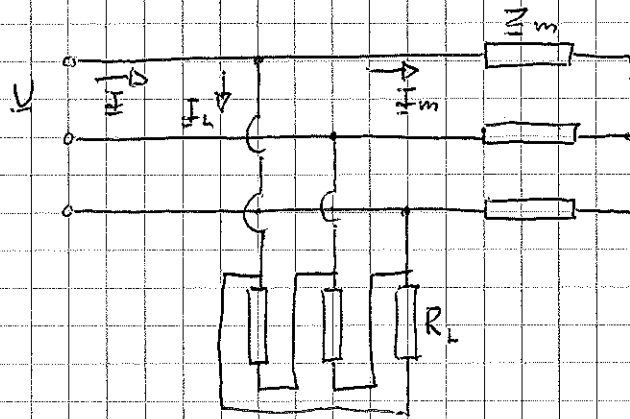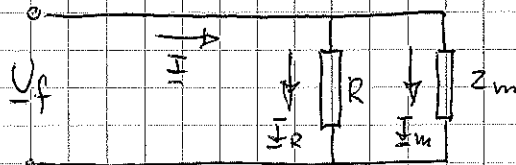Motor - Y - $10kW = P_m$; $\cos \varphi = 0,8$ Ekv Y -fas:

Motor:

$$P = 3 U_f I_m \cos \varphi \Rightarrow I_m = \frac{10 \cdot 10^3}{3 \cdot \frac{220}{\sqrt{3}} \cdot 0,8} = 32,8 A$$

$$\underline{I}_m = 32,8 (0,8 - j0,6) = (26,24 - j19,7) A$$

Lampor:

$$I_L = \frac{3 \cdot 10^3}{3 \cdot \frac{220}{\sqrt{3}}} = 7,87 A = \underline{I}_L$$

$$\underline{I} = \underline{I}_L + \underline{I}_m = 7,87 + 26,24 - j19,7 = 34,11 - j19,7 = \underline{\underline{39,4 \angle -30^\circ A}}$$

$$\underline{\underline{\cos \varphi = 0,866}}$$

Alt
visa!

P	Q	
10	7,5	
3	0	
13	7,5	

$$\Rightarrow S = 15,0 kVA \Rightarrow I = \frac{S}{\sqrt{3} U} = 39,4 A$$

$$\tan \varphi = \frac{7,5}{13} \Rightarrow \cos \varphi = 0,866$$

2.12

$$U = 500 \text{ V}$$

2.12

Träwattmetermetoden

$$P_1 = 0 \text{ W} \quad I = 15 \text{ A}$$

$$\cos \varphi = ? ; P_2 = ?$$

$$1. P_1 = U_{12} I_1 \cos \varphi' ; P_2 = U_{32} I_3 \cos \varphi''$$

$$P_1 = 0 = U_{12} I_1 \cos \varphi' \Rightarrow \cos \varphi' = 0$$

$$\varphi + 30^\circ = \pm 90^\circ$$

$$\cos \varphi = 0,5$$

$$\varphi = 60^\circ$$

 $(-120^\circ \text{ orimligt})$

$$P_2 = U_{32} I_3 \cos(\varphi - 30^\circ) = 500 \cdot 15 \cdot \cos 30^\circ = \underline{\underline{6495 \text{ W}}}$$

$$2. P_2 = 0 \text{ W} = U_{32} I_3 \cos \varphi'' \Rightarrow \varphi'' = \pm 90^\circ \rightarrow \varphi - 30^\circ = \pm 90^\circ$$

$$\varphi = -60^\circ$$

$$\Rightarrow \varphi' = -60^\circ + 30^\circ = -30^\circ$$


$$P_1 = 500 \cdot 15 \cdot \cos(-30^\circ) = \underline{\underline{6495 \text{ W}}}$$

$$\cos(-60^\circ) = 0,5$$

 $\varphi - \text{pos} \rightarrow \text{ind}$ $\varphi - \text{neg} \rightarrow \text{kap}$

2.13

2.13

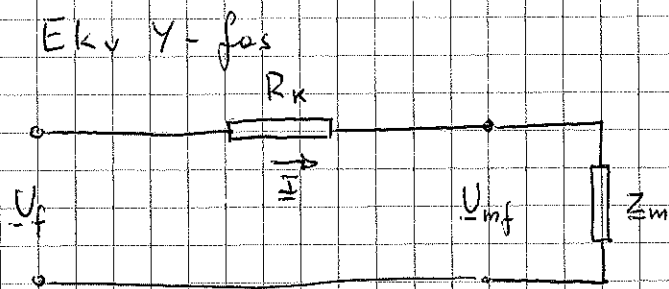

$$U_m = 365 \text{ V}$$

$$P = 8,1 \text{ kW}$$

$$I = 16 \text{ A}$$

$$R_k = \rho \frac{l}{A} = 0,017 \frac{80}{2,5} = 0,54 \text{ } \Omega/\text{fas}$$

$$1 \Omega_m = 10^6 \frac{\Omega \text{ mm}^2}{\text{m}}$$

$$1 \mu \Omega_m = 1 \frac{\text{mm}^2}{\text{m}} \Omega$$

$$P = \sqrt{3} U_m I \cos \varphi \Rightarrow \cos \varphi = \frac{P}{\sqrt{3} U_m I} = \frac{8100}{\sqrt{3} \cdot 365 \cdot 16} = 0,8$$

$$\underline{I} = 16 (0,8 - j0,6) = 12,8 - j9,6 = 16 \angle -36,87^\circ \text{ A}$$

$$\underline{Z}_m = \frac{U_{mf}}{\underline{I}} = \frac{365/\sqrt{3} \angle 0^\circ}{16 \angle -36,87^\circ} = 13,17 \angle 36,87^\circ = (10,54 + j7,9) \Omega/\text{fas}$$

$$\underline{Z}_{tot} = R_k + \underline{Z}_m = (11,08 + j7,9) \Omega/\text{fas} = 13,6 \angle 35,5^\circ \Omega/\text{fas}$$

$$\underline{U}_f = \underline{Z}_{tot} \cdot \underline{I} = 13,6 \angle 35,5^\circ \cdot 16 \angle -36,87^\circ = 217,6 \angle -1,37^\circ \text{ V}$$

$$U = \sqrt{3} U_f = \underline{\underline{377 \text{ V}}}$$

2.14


$$U = 400 \text{ V} ; f = 50 \text{ Hz}$$

2.14

AM

$$P_{2m} = 7 \text{ kW} ; \cos \varphi = 0,8 ; \eta = 87,5\%$$
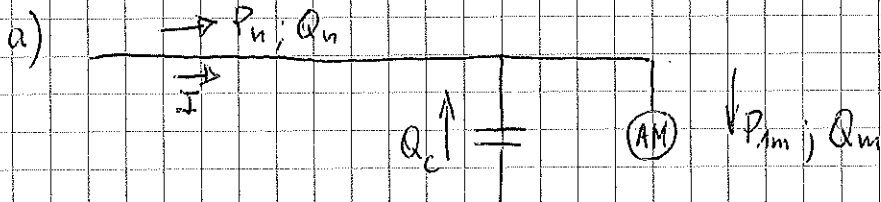
$$\text{Kond. bat. } Q_c = 4 \text{ kVAR}$$



$$\eta = \frac{P_{2m}}{P_{1m}} \Rightarrow P_{1m} = \frac{P_{2m}}{\eta} = \frac{7}{0,875} = 8 \text{ kW} \quad (\text{AM-förbrukar } 8 \text{ kW})$$

$$Q_m = P_{1m} \tan \varphi = 8 \cdot 0,75 = 6 \text{ kVAR}$$

$$\underline{\underline{P_n = P_{1m}}}$$

$$Q_n = Q_m - Q_c = \underline{\underline{2 \text{ kVAR}}}$$

$$\tan \varphi_n = \frac{Q_n}{P_n} = \frac{2}{8} = 0,25 \Rightarrow \underline{\underline{\cos \varphi_n = 0,97}}$$

$$I = \frac{P_n}{\sqrt{3} \cdot U \cos \varphi_n} = \frac{8000}{\sqrt{3} \cdot 400 \cdot 0,97} = \underline{\underline{11,9 \text{ A}}}$$

b)

$$\text{Allmänt } Q_c = 3 \frac{U_c^2}{X_c} = 3 \omega C U_c^2 \quad 3 U_c I \sin \varphi$$

Y-koppling

$$U_c = \frac{400}{\sqrt{3}} \text{ V} \quad C_Y = \frac{Q_c}{3 \omega U_c^2} = \frac{4000}{2\pi \cdot 50 \cdot 400^2} = 79,6 \mu\text{F}$$

 Δ -koppling

$$U_c = 400 \text{ V} \quad C_A = \frac{Q_c}{3 \omega U_c^2} = \frac{4000}{3 \cdot 2\pi \cdot 50 \cdot 400^2} = 26,5 \mu\text{F}$$


(x3)

*
2.15

$$U = 400 \text{ V} ; f = 50 \text{ Hz}$$

2.15

Före:

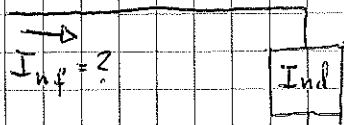


$$P_i = 140 \text{ kW} ; \cos \varphi_i = 0,707$$

$$\varphi_i = 45^\circ$$

$$Q_i = P_i \tan \varphi_i = 140 \text{ kVAR}$$

$$S_i = \sqrt{2} \cdot 140 \text{ kVA} \Rightarrow I_{nf} = \frac{S_i}{\sqrt{3} U} = \frac{\sqrt{2} \cdot 140 \cdot 10^3}{\sqrt{3} \cdot 400} = 285,5 \text{ A}$$

Efter:

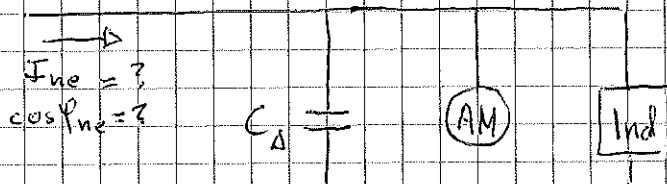

$$C_d = 1 \text{ mF}$$

$$P_m = 15 \text{ kW} ; P_i = 140 \text{ kW}$$

$$I_m = 28,5 \text{ A} ; Q_i = 140 \text{ kVAR}$$

AM

$$\begin{cases} S_m = \sqrt{3} \cdot 400 \cdot 28,5 = 19745 \text{ VA} \\ Q_m = \sqrt{S_m^2 - P_m^2} = \sqrt{19745^2 - 15000^2} = 12840 \text{ VAR} \end{cases}$$

Δ - koppl. kond

$$U_c = 400 \text{ V} ; Q_c = 3 \omega C_d U_c^2 = 3 \cdot 100\pi \cdot 1 \cdot 10^{-3} \cdot 400^2 = 150,8 \text{ kVAR}$$

$$Q_{ne} = Q_i + Q_m - Q_c = 140 + 12,84 - 150,8 = 2,04 \text{ kVAR}$$

$$P_{ne} = P_i + P_m = 140 + 15 = 155 \text{ kW}$$

$$\tan \varphi_{ne} = \frac{2,04}{155} \Rightarrow \cos \varphi_{ne} = 0,999$$

$$I_{ne} = \frac{P_{ne}}{\sqrt{3} U \cos \varphi_{ne}} = \frac{155 \cdot 10^3}{\sqrt{3} \cdot 400 \cdot 0,99} = 223,7 \text{ A} \angle -0,75^\circ$$

diskutera

$$U = 400 \text{ V}, f = 50 \text{ Hz}$$

före: $P_i = 140 \text{ kW}; \cos \varphi_i = 0,707 \quad \underline{I} = ?$

$$Q_i = P_i \tan \varphi_i = 140 \text{ kVar} \quad \varphi_i = 45^\circ$$

$$S_i = \sqrt{2} \cdot 140 \text{ kVA} \Rightarrow I = \frac{S_i}{\sqrt{3} U} = \frac{\sqrt{2} \cdot 140 \cdot 10^3}{\sqrt{3} \cdot 400} = 285,8 \text{ A}$$

$$\underline{I = 285,8 \angle -45^\circ \text{ [A]}}$$

efter: $P_i = 140 \text{ kW}; \cos \varphi_i = 0,707 \Rightarrow Q_i = 140 \text{ kVar}$

AM $P_m = 15 \text{ kW}; I_m = 28,5 \text{ A}$

$$C_\Delta = 1 \text{ mF}$$

AM: $S_m = \sqrt{3} \cdot 400 \cdot 28,5 = 19745 \text{ VA}$

$$Q_m = \sqrt{S_m^2 - P_m^2} = \sqrt{19745^2 - 15000^2} = 12840 \text{ Var}$$

Δ - koppl. kondensatorer

$$U_c = 400 \text{ V}; Q_c = 3 \omega C_\Delta U_c^2 = 3 \cdot 100\pi \cdot 1 \cdot 10^{-3} \cdot 400^2 = 150,8 \text{ kVar}$$

Effekt som skall tillföras från nätet:

$$Q = Q_i + Q_m - Q_c = 140 + 12,84 - 150,8 = 2,04 \text{ kVar}$$

$$P = P_i + P_m = 140 + 15 = 155 \text{ kW}$$

Hela lastens $\cos \varphi$:

$$\tan \varphi = \frac{Q}{P} = \frac{2,04}{155} \Rightarrow \cos \varphi = 0,999$$

$$I = \frac{P}{\sqrt{3} U \cos \varphi} = \frac{155 \cdot 10^3}{\sqrt{3} \cdot 400 \cdot 0,999} = 223,7 \text{ A}$$

$$\underline{I = 223,7 \angle -0,8^\circ \text{ [A]}}$$

Obs! $I_{\text{efter}} < I_{\text{före}}$