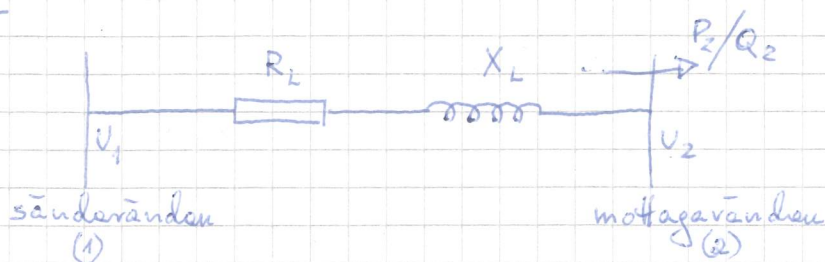


3.1

3.1



$$l = 40 \text{ km} ; r = 0,25 \Omega/\text{km, fas} ; x = 0,4 \Omega/\text{km, fas}$$

$$P_2 = 4,15 \text{ MW} ; \cos \varphi_2 = 0,8 ; U_2 = 30 \text{ kV}$$

$$U_{\text{längsf}} = a = R_L I \cos \varphi_2 + X_L I \sin \varphi_2 \quad / \cdot \sqrt{3} U_2$$

$$U_{\text{tvärf}} = b = X_L I \cos \varphi_2 - R_L I \sin \varphi_2 \quad / \cdot \sqrt{3} U_2$$

$$U_{\text{längs}} = \frac{R_L P_2 + X_L Q_2}{U_2} \quad (\text{som huvudsp})$$

$$U_{\text{tvär}} = \frac{X_L P_2 - R_L Q_2}{U_2} \quad "$$

a) med tvärspänningsfallet: $X_L = 0,4 \cdot 40 = 16 \Omega/\text{fas}$
 $Q_2 = P_2 \tan \varphi_2 = 3,11 \text{ MVar} ; R_L = 0,25 \cdot 40 = 10 \Omega/\text{fas}$

$$U_{\text{längs}} = \frac{10 \cdot 4,15 + 16 \cdot 3,11}{30} \approx 3,04 \text{ kV}$$

$$U_{\text{tvär}} = \frac{16 \cdot 4,15 - 10 \cdot 3,11}{30} \approx 1,18 \text{ kV}$$


$$U_1 = \sqrt{(U_2 + U_{\text{längs}})^2 + U_{\text{tvär}}^2} = 33,06 \text{ kV}$$

vita
visar diegr.

b) Utan tvärspänningsfallet:

$$U_1 = U_2 + U_{\text{längs}} = 33,04 \text{ kV}$$

3.2

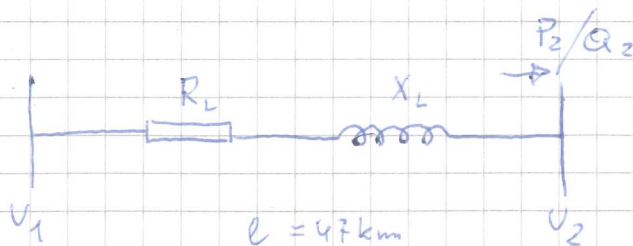

3.2

$$U_2 = ? \text{ om } U_1 = 51 \text{ kV}$$

Linjen:

$$R_L = r \cdot l = 0,18 \cdot 47 = 8,46 \text{ } \Omega/\text{fas}$$

$$X_L = x \cdot l = 0,30 \cdot 47 = 14,10 \text{ } \Omega/\text{fas}$$

försumma
tvärs.p.f.

Belastningen:

P MW	$\cos \varphi$	Q MVar
2,2	0,9	1,07
1,7	0,8	1,28
0,6	0,6 kap	-0,8

$$P_2 = 4,5 \text{ MW}$$

$$Q_2 = 1,55 \text{ MVar}$$

$$U_1 = U_2 + \frac{R_L P_2 + X_L Q_2}{U_2} ; \quad U_2^2 - U_1 U_2 + R_L P_2 + X_L Q_2 = 0$$

$$R_L P_2 + X_L Q_2 = 8,46 \cdot 4,5 + 14,1 \cdot 1,55 = 59,9$$


$$U_2^2 - 51 U_2 + 59,9 = 0$$

$$U_2 = 25,5 \pm \sqrt{25,5^2 - 59,9} = 25,5 \pm 24,3$$

$$\underline{\underline{U_2 = 49,8 \text{ kV}}}$$

$$\left(\Delta U = 25,5 - 24,3 = 1,2 \text{ kV} \right)$$

3.3

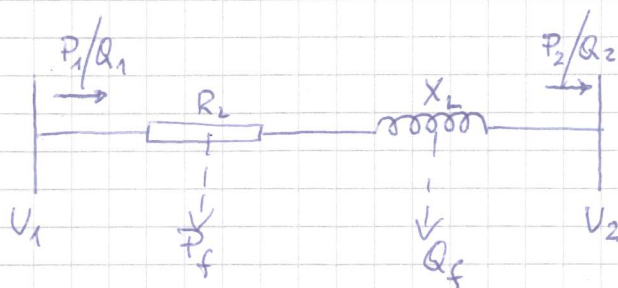

3.3

$$(1 \text{ } \Omega \text{ m} = 10^6 \text{ } \Omega \text{ mm}^2/\text{m})$$

Linje: $R_L = \rho \frac{l}{A} = 17,5 \cdot \frac{40}{120} = 5,8 \text{ } \Omega/\text{fas}$

$$\rho = 17,5 \text{ } \Omega \text{ mm}^2/\text{km}$$

$$X_L = 0,4 \cdot 40 = 16 \text{ } \Omega/\text{fas}$$

Lasten:

$$P_2 = 12 \text{ MW}; \cos \varphi_2 \approx 0,8 \Rightarrow Q_2 = 9 \text{ MVar} \Rightarrow S_2 = 15 \text{ MVA}$$

$$U_2 = 54 \text{ kV}$$

a) Visardiagram:

Försumma tvärs p-fallet

$$U_{\text{längs}} = \frac{R_L P_2 + X_L Q_2}{U_2} = \frac{5,8 \cdot 12 + 16 \cdot 9}{54} = 3,96 \text{ kV}$$

$$\underline{U_1} = U_2 + U_{\text{längs}} \approx \underline{58 \text{ kV}}$$

$$P_f = 3 R_L I^2; \quad Q_f = 3 X_L I^2$$

$$I = \frac{S_2}{\sqrt{3} U_2} = \frac{15}{\sqrt{3} \cdot 54} = 0,16 \text{ kA}$$

$$\underline{P_f} = 3 \cdot 5,8 \cdot 0,16^2 = \underline{0,45 \text{ MW}}$$

$$\underline{Q_f} = 3 \cdot 16 \cdot 0,16^2 = \underline{1,23 \text{ MVar}}$$

b) Förlustsummeringsmetoden:

$$P_1 = P_2 + P_f = 12 + 0,45 = 12,45 \text{ MW}$$


$$Q_2 = Q_2 + Q_f = 9 + 1,23 = 10,23 \text{ MVar}$$

$$S_1 = \sqrt{12,45^2 + 10,23^2} = 16,1 \text{ MVA}; \quad S_1 = \sqrt{3} U_1 I \quad \text{där } I = 0,16 \text{ kA}$$

$$\underline{U_1} = \frac{16,1}{\sqrt{3} \cdot 0,16} = \underline{58,1 \text{ kV}}$$

3.4

Före:

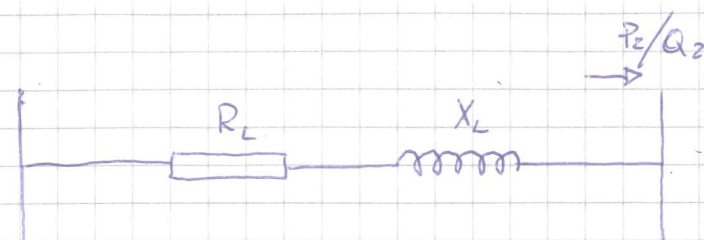

$$U_1 = 21 \text{ kV}$$

$$U_2 = ?$$

3.4

$$R_L = 5 \Omega / \text{fas}$$

$$X_L = 8 \Omega / \text{fas}$$

$$S_2 = 5 \text{ MVA}; \cos \varphi_2 = 0,8 \Rightarrow P_2 = 0,8 \cdot 5 = 4 \text{ MW}$$


$$Q_2 = 0,6 \cdot 5 = 3 \text{ MVar}$$

$$U_{\text{längs}} = \frac{R_L P_2 + X_L Q_2}{U_2} = \frac{5 \cdot 4 + 8 \cdot 3}{U_2} = \frac{44}{U_2} \text{ kV}$$

$$U_1 \approx U_2 + U_{\text{längs}} \Rightarrow 21 = U_2 + \frac{44}{U_2} \Rightarrow U_2^2 - 21U_2 + 44 = 0$$

$$U_2 = 10,5 \pm 8,1 \Rightarrow U_2 = 18,6 \text{ kV} \quad (U_{\text{längs}} = 2,4 \text{ kV})$$


Efter:

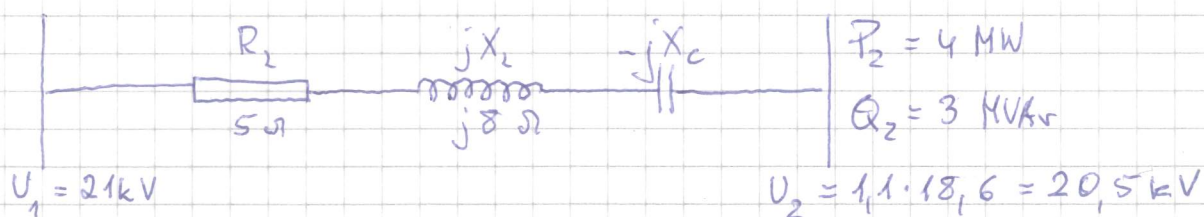

$$U_{\text{längs}} = 21 - 20,5 = 0,5 \text{ kV}$$

$$0,5 = \frac{R_L P_2 + (X_L - X_C) Q_2}{U_2} \Rightarrow 10,25 = 20 + 24 - 3X_C$$

$$3X_C = 33,75 \Rightarrow X_C = 11,25 \Omega / \text{fas}$$

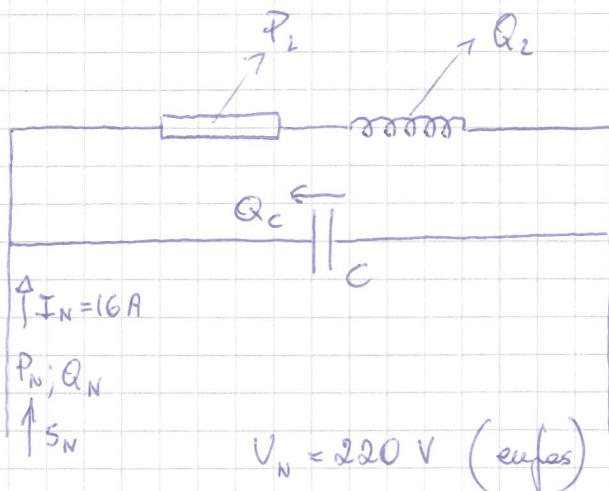3.53.5

$$f = 50 \text{ Hz}$$

$$I = 22,73 \text{ A}$$

1. Lysröven:

$$P_L = 3 \text{ kW} ; \cos \varphi_L = 0,6 \Rightarrow Q_L = 4 \text{ kVAR}$$

$$\Rightarrow \text{Behov: } P_L = 3 \text{ kW} ; Q_L = 4 \text{ kVAR}$$

2. Nätet:

$$S_N = U_N I_N = 220 \cdot 16 = 3,52 \text{ kVA}$$

$$P_N = P_L = 3 \text{ kW}$$


$$Q_N = \sqrt{S_N^2 - P_N^2} = \sqrt{3,52^2 - 3^2} = 1,84 \text{ kVAR}$$

$$\text{Från nätet: } \begin{cases} P_N = 3 \text{ kW} \\ Q_N = 1,84 \text{ kVAR} \end{cases}$$

$$Q_N + Q_C = Q_L \Rightarrow Q_C = Q_L - Q_N = 4 - 1,84 = 2,16 \text{ kVAR}$$

$$Q_C = \omega C U_C^2 \text{ där } U_C = 220 \text{ V}$$

$$C = \frac{2160}{100\pi \cdot 220^2} \approx 142 \mu\text{F}$$

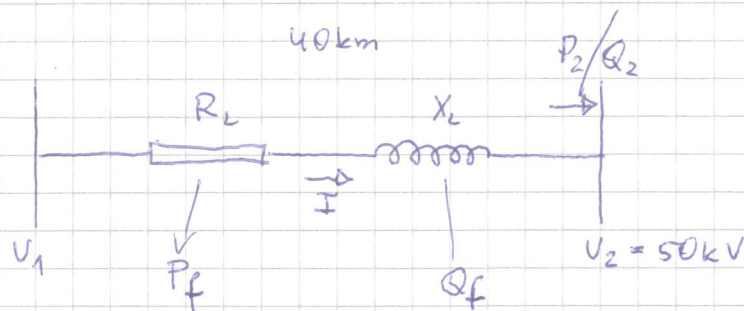3.63.6

$$a) \quad R_L = \rho \frac{l}{A} = 17,5 \cdot \frac{40}{70} = 10 \, \Omega/\text{fas}$$

$$X_L = x l = 0,4 \cdot 40 = 16 \, \Omega/\text{fas}$$

$$P_2 = 8 \text{ MW}; \cos \varphi_2 = 0,8 \Rightarrow Q_2 = 6 \text{ MVar} \Rightarrow S_2 = 10 \text{ MVA}$$


$$U_{\text{l\ddot{a}ngs}} = \frac{R_L P_2 + X_L Q_2}{U_2} = \frac{10 \cdot 8 + 16 \cdot 6}{50} = 3,52 \text{ kV}$$

$$U_1 = 50 + 3,52 = 53,52 \text{ kV}$$

$$P_f = 3 R_L I^2; \quad Q_f = 3 X_L I^2; \quad I = \frac{S_2}{\sqrt{3} U_2} = \frac{10}{\sqrt{3} \cdot 50} = \frac{1}{5\sqrt{3}} \text{ kA} \quad (115,5 \text{ A})$$

$$P_f = 3 \cdot 10 \cdot \frac{1}{25 \cdot 3} = 0,4 \text{ MW}$$
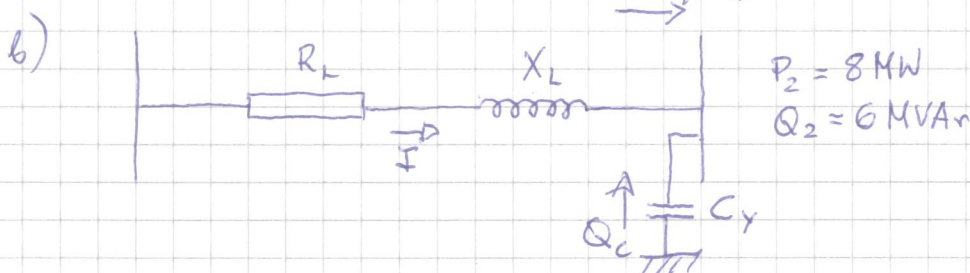
$$Q_f = 16 \cdot 0,4 = 0,64 \text{ MVar}$$



$$P_{\text{f\ddot{a}rl}} = 3 R_L I^2 = 0,3 \text{ MW} \Rightarrow I = 0,1 \text{ kA}$$

$$S_2 = \sqrt{3} U_2 \cdot I \Rightarrow S_{2N} = \sqrt{3} \cdot 50 \cdot 0,1 = 5\sqrt{3} \text{ MVA}$$

$$P_{2N} = P_2 = 8 \text{ MW}$$

$$Q_{2N} = \sqrt{S_{2N}^2 - P_{2N}^2} = \sqrt{(5\sqrt{3})^2 - 8^2} = 3,32 \text{ MVar}$$

$$Q_{2N} + Q_c = Q_2 \Rightarrow Q_c = 6 - 3,32 = 2,68 \text{ MVar}$$

$$Q_c = 3 \omega C_y U_c^2 = 3 \omega C_y \left(\frac{U_2}{\sqrt{3}} \right)^2 = \omega C_y U_2^2 \Rightarrow C_y = \frac{Q_c}{\omega U_2^2}$$

$$C_y = \frac{2,68 \cdot 10^6}{100\pi \cdot (50 \cdot 10^3)^2} = 3,41 \, \mu\text{F}/\text{fas}$$