

4.1

$$U_1 = 220V$$

$$U_2 = 15V$$

$$A_{Fe} = (0,02 \cdot 0,03) \text{ m}^2$$

$$k_f = 0,9$$

$$\hat{B} = 1,2T ; S_{cu} = 2,5 \text{ A/mm}^2 ; \Delta U = 5\%$$

4.1

$$S = 75 \text{ VA}$$

$$f = 50 \text{ Hz}$$

$$N_1 ; N_2 = ?$$

a) Transf. formel

$$U_1 = 4,44 f N_1 A_{Fe} \cdot \hat{B} \quad A_{Fenetto} = k_f A_{Fe}$$

$$N_1 = \frac{220}{4,44 \cdot 50 \cdot 0,02 \cdot 0,03 \cdot 0,9 \cdot 1,2} = \underline{\underline{1530 \text{ varv}}}$$

Vid fällgång är $U_2 = 15 \cdot 1,05 = 15,75V$

$$\frac{U_1}{U_2} = \frac{N_1}{N_2} \Rightarrow N_2 = \frac{U_2}{U_1} N_1 = \frac{15,75}{220} \cdot 1530 = \underline{\underline{110 \text{ varv}}}$$

$$I_2 = \frac{S}{U_2} = \frac{75}{15} = 5A \Rightarrow A_{2cu} = \frac{I_2}{S_{cu}} = \frac{5}{2,5} = \underline{\underline{2 \text{ mm}^2}}$$

$$I_1 = I_2 \frac{N_2}{N_1} = 5 \frac{110}{1530} = 0,359A \Rightarrow A_{1cu} = \frac{0,359}{2,5} = \underline{\underline{0,144 \text{ mm}^2}}$$

laminerad plåt 0,3-0,6 mm

ev. orienterad magnetiskt - goda magn. egenskaper
valvriktn.

legerad med 5-6% kisel

$$E = 4,44 f N A \hat{B}$$


netto area

$$V = \frac{1}{3} \cdot m \cdot \frac{1}{\rho}$$

4.2

en ideal trafo

4.2/1

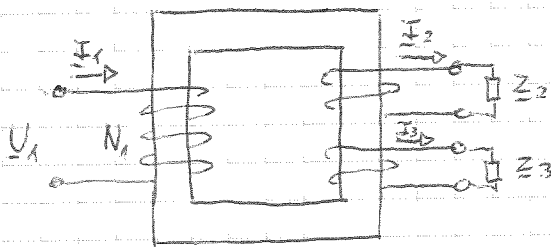

$$N_1 = 500 \quad U_1 = 150 \text{ V}$$

$$I_1 = ?$$

$$N_2 = 300 \quad Z_2 = 30 + j40 \, \Omega$$

$$I_2 = ?$$

$$N_3 = 200 \quad Z_3 \rightarrow R_3 // X_3$$

$$I_3 = ?$$

$$\frac{U_1}{U_2} = \frac{N_1}{N_2} \Rightarrow U_2 = U_1 \frac{N_2}{N_1} = 150 \cdot \frac{300}{500} = 90 \text{ V}$$

$$U_3 = U_1 \frac{N_3}{N_1} = 150 \cdot \frac{200}{500} = 60 \text{ V}$$

$$Z_2 = 30 + j40 = 50 \angle 53,13^\circ \, \Omega$$

$$I_2 = \frac{U_2}{Z_2} = \frac{90 \angle 0^\circ}{50 \angle 53,13^\circ} = 1,8 \angle -53,13^\circ \text{ A}$$

$$Z_3 = \frac{12 \cdot (-j15)}{12 - j15} = \frac{-j180}{12 - j15} = \frac{180 \angle -90^\circ}{19,2 \angle -56,34^\circ} = 9,4 \angle -38,66^\circ \, \Omega$$


$$I_3 = \frac{60 \angle 0^\circ}{9,4 \angle -38,66^\circ} = 6,4 \angle 38,66^\circ \text{ A}$$

$$I_1 = I_2' + I_3' = (1,8 \angle -53,13^\circ) \frac{N_2}{N_1} + \frac{N_3}{N_1} 6,4 \angle 38,66^\circ =$$

$$= 1,08 \angle -53,13^\circ + 2,56 \angle 38,66^\circ = 0,65 - j0,86 + 2 + j1,6 =$$

$$= 2,65 + j0,74 = 2,75 \angle 15,6^\circ \text{ A}$$

b)

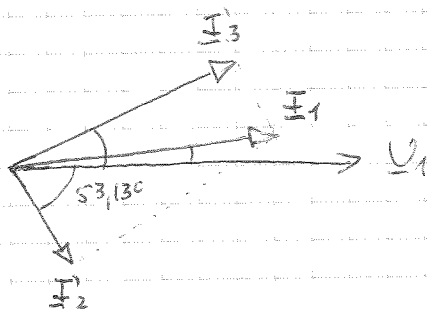

$$\cos 15,6^\circ = 0,963 \text{ kap}$$

4.2

4.2/2

Akt:

Leistung 2: $Z_2 = 30 + j40 \Rightarrow |Z_2| = 50 \Omega$

$$\underline{I_2 = \frac{90}{50} = 1,8 A} \Rightarrow P_2 = R_2 I_2^2 = 30 \cdot 1,8^2 = 97,2 \text{ W}$$

$$Q_2 = X_2 I_2^2 = 40 \cdot 1,8^2 = 129,6 \text{ VAR}$$

Leistung 3:

$$P_3 = \frac{U_3^2}{R_3} = \frac{60^2}{12} = 300 \text{ W} ; \quad Q_3 = \frac{60^2}{15} = 240 \text{ VAR}$$

$$S_3 = \sqrt{300^2 + 240^2} = 384,2 \text{ VA}$$

$$I_3 = \frac{S_3}{U_3} = \frac{384,2}{60} = \underline{\underline{6,4 A}}$$

Leistung 1:

$$P_1 = P_2 + P_3 = 97,2 + 300 = 397,2 \text{ W}$$

$$Q_1 = Q_2 - Q_3 = 129,6 - 240 = -110,4 \text{ VAR}$$


:" kapazitiv

$$S_1 = \sqrt{(397,2)^2 + (110,4)^2} = 412,26 \text{ VA}$$

$$\cos \varphi = \frac{P_1}{S_1} = 0,963 \quad \text{kap}$$

$$I_1 = \frac{S_1}{U_1} = 2,75 \text{ A}$$

4.3

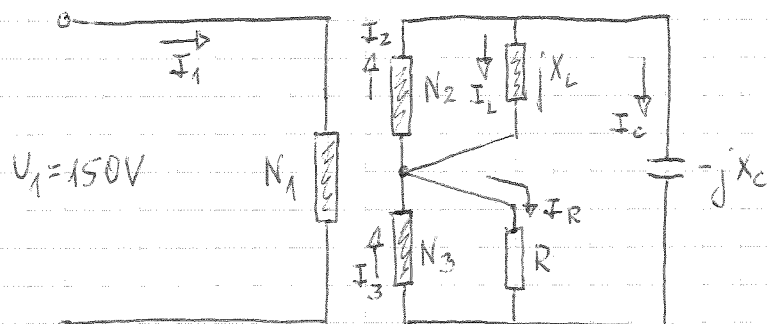

4.3

$$U_2 = 90V$$

$$U_3 = 60V$$

$$N_2 = 300$$

$$N_3 = 200$$

a) F_m balans $N_1 I_1 = N_2 I_2 + N_3 I_3$

$$I_2 = I_L + I_c = \frac{U_2}{jX_L} + \frac{U_2 + U_3}{-jX_c}$$

$$I_3 = I_R + I_c = \frac{U_3}{R} + \frac{U_2 + U_3}{-jX_c}$$

$$N_1 I_1 = j \frac{(U_2 + U_3) N_2}{X_c} - j \frac{U_2 N_2}{X_L} + j \frac{(U_2 + U_3) N_3}{X_c} + \frac{U_3 N_3}{R}$$

$$I_1 \rightarrow \min \rightarrow = 0$$

kan inte
göra något åt

$$\Rightarrow \frac{U_2 + U_3}{X_c} N_2 + \frac{U_2 + U_3}{X_c} N_3 = \frac{U_2}{X_L} N_2$$

$$\frac{(U_2 + U_3)(N_2 + N_3)}{X_c} = \frac{U_2}{X_L} N_2 \Rightarrow X_c = \frac{(U_2 + U_3)(N_2 + N_3)}{U_2 N_2} X_L =$$

$$= \frac{150 \cdot 500}{90 \cdot 300} \cdot 10 = \underline{\underline{27,78 \Omega}}$$

b) $I_2 = -j \frac{90}{10} + j \frac{150}{27,8} = -j 9 + j 5,4 = -j 3,6 A \quad |I_2| = \underline{\underline{3,6 A}}$


$$I_3 = \frac{60}{4,5} + j 5,4 = 13,3 + j 5,4 = 14,4 \angle 22,1^\circ A \quad |I_3| = \underline{\underline{14,4 A}}$$

$$I_1 = I_2' + I_3' = -j 3,6 \frac{300}{500} + (13,3 + j 5,4) \frac{200}{500} = -j 2,16 + 5,32 + j 2,16 = \underline{\underline{5,32 A}}$$

4.4

 $S_n = 25 \text{ kVA}$; $400/230 \text{ V}$; en rufes frefo

4.4

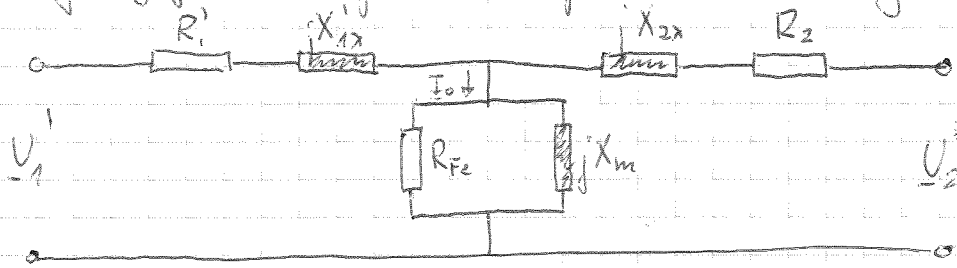Tomgångsprövet från nedsp. sida $\rightarrow$ börja med b)

$$U_2 = U_0 \Rightarrow P_0 = \frac{U_0^2}{R_{Fe}} \Rightarrow R_{Fe} = \frac{U_0^2}{P_0} = \frac{230^2}{275} = 192,4 \, \Omega$$

$$S_0 = U_0 I_0 = 230 \cdot 7,8 = 1794 \text{ VA}$$

$$Q_0 = \sqrt{S_0^2 - P_0^2} = \sqrt{1794^2 - 275^2} = 1772,8 \text{ VAR}$$

$$X_m = \frac{U_0^2}{Q_0} = \frac{230^2}{1772,8} = 29,84 \, \Omega$$

$$R_1' = \left(\frac{U_2}{U_1} \right)^2 \cdot R_1 = \left(\frac{230}{400} \right)^2 \cdot 0,031 = 0,010 \, \Omega$$

$$X_{12}' = \left(\frac{U_2}{U_1} \right)^2 \cdot X_{12} = \left(\frac{230}{400} \right)^2 \cdot 0,15 = 0,05 \, \Omega \quad X_{c1}$$

$$R_1' = 0,010 \, \Omega \quad R_2 = 0,011 \, \Omega \quad R_{Fe} = 192,4 \, \Omega$$

$$X_{12}' = 0,05 \, \Omega \quad X_{21} = 0,05 \, \Omega \quad X_m = 29,84 \, \Omega$$

a) 400 V-sidan

$$R_2' = \left(\frac{U_1}{U_2} \right)^2 \cdot R_2 = \left(\frac{400}{230} \right)^2 \cdot 0,011 = 0,033 \, \Omega \quad R_1 = 0,031 \, \Omega$$

$$X_{21}' = \left(\frac{U_1}{U_2} \right)^2 \cdot X_{21} = \left(\frac{400}{230} \right)^2 \cdot 0,05 = 0,15 \, \Omega \quad X_{12} = 0,15 \, \Omega$$

$$R_{Fe}' = \left(\frac{U_1}{U_2} \right)^2 \cdot R_{Fe} = \left(\frac{400}{230} \right)^2 \cdot 192,4 = 581,9 \, \Omega \quad R_2' = 0,033 \, \Omega$$

$$X_m' = \left(\frac{U_1}{U_2} \right)^2 \cdot X_m = \left(\frac{400}{230} \right)^2 \cdot 29,84 = 90,25 \, \Omega \quad X_{21}' = 0,15 \, \Omega$$

$$R_{Fe}' = 581,9 \, \Omega$$


$$X_m' = 90,25 \, \Omega$$

4.5

$$U_1 = 400 \text{ V} ; R_b = 2,3 \Omega$$

4.5/1

Trafos förenklade ekv. schema:

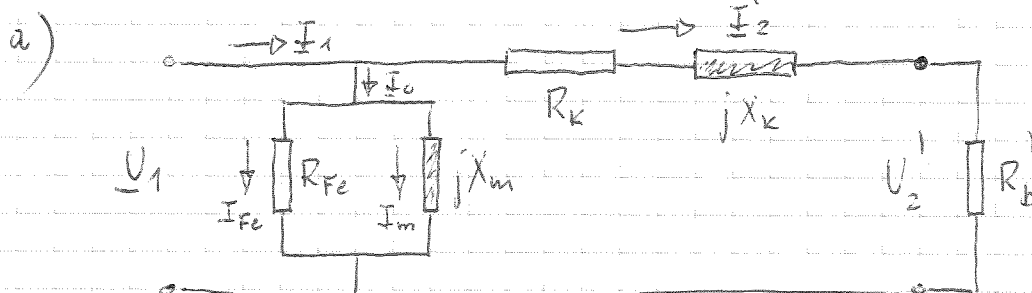

enl. 4.4:

$$R_{Fe} = 581,9 \Omega$$

$$X_m = 90,25 \Omega$$

$$R_k = R_1 + R_2' = 0,031 + 0,033 = 0,064 \Omega$$

$$X_k = X_{1\sigma} + X_{2\sigma}' = 0,15 + 0,15 = 0,3 \Omega$$

$$Z_k = 0,064 + j0,3 \Omega$$

$$Z_b' = R_b' = R_b \left(\frac{400}{230} \right)^2 = 6,96 \Omega$$

$$\underline{I}_2' = \frac{U_1}{Z_k + Z_b'} = \frac{400 \angle 0^\circ}{0,064 + j0,3 + 6,96} = \frac{400 \angle 0^\circ}{7,02 + j0,3} = \frac{400 \angle 0^\circ}{7,03 \angle 2,45^\circ} = 56,9 \angle -2,45^\circ = (56,85 + j2,43) \text{ A}$$

$$\underline{I}_2 = \underline{I}_2' \frac{U_1}{U_2} = 56,9 \frac{400}{230} = \underline{98,95 \text{ A}}$$

$$\underline{I}_1 = \underline{I}_2' + \underline{I}_0$$

$$\underline{I}_{Fe} = \frac{U_1}{R_{Fe}} = 0,69 \text{ A} ; \underline{I}_m = \frac{U_1}{X_m} = 4,43 \text{ A}$$

$$\underline{I}_0 = (0,69 - j4,43) \text{ A} \quad 4,48 \text{ A}$$

$$\underline{I}_1 = 56,85 - j2,43 + 0,69 - j4,43 = 57,54 - j6,86 = 57,95 \angle -6,8^\circ \text{ A}$$

$$\underline{I}_1 = 57,95 \text{ A}$$

liten $I_0 \rightarrow$ försummas ofta

7,7%

Visa 2012 2012

4.54.5/2

$$b) \quad U_2 = I_2 \cdot R_b = 98,95 \cdot 2,3 = \underline{\underline{227,6 \text{ V}}}$$

$$c) \quad P_2 = R_b I_2^2 = 2,3 (98,95)^2 = 22520 \text{ W}$$

$$P_0 = 275 \text{ W}$$

$$P_{cu} = R_k (I_2')^2 = 0,064 \cdot (56,9)^2 = 207,2 \text{ W}$$

$$P_{\text{förl}} = 275 + 207,2 = 482,2 \text{ W}$$

$$\eta = \frac{P_2}{P_1} = \frac{P_2}{P_2 + P_f} = \frac{22520}{22520 + 482,2} = 0,979$$

$$\underline{\underline{\eta = 97,9 \%}}$$

4.6

$$I_2 = 99 \text{ A} ; \cos \varphi_2 = 0,7 ; U_1 = 400 \text{ V}$$

$$\left. \begin{array}{l} a) R_k = 0,064 \, \Omega \\ X_k = 0,3 \, \Omega \end{array} \right\} \text{eul. 4.5}$$

$$I_2' = I_2 \frac{U_2}{U_1} = 99 \frac{230}{400} = 56,93 \text{ A}$$

$$\begin{aligned} \Delta U &= I_2' (R_k \cos \varphi_2 + X_k \sin \varphi_2) = \\ &= 56,93 (0,064 \cdot 0,7 + 0,3 \cdot 0,71) = 14,75 \text{ V} \end{aligned}$$

$$U_2' = 400 - 14,75 = 385,25 \text{ V}$$

$$\underline{U_2 = 385,25 \frac{230}{400} = 221,5 \text{ V}}$$

$$b) \underline{P_{\text{förl}} = 482,2 \text{ W}} \quad \text{eul. 4.5 (samma } U_1 \text{ och } I_2)$$

$$P_2 = U_2 I_2 \cos \varphi_2 = 221,5 \cdot 99 \cdot 0,7 = \underline{\underline{15351 \text{ W}}}$$

$$P_1 = P_2 + P_{\text{förl}} = 15351 + 482 = \underline{\underline{15833 \text{ W}}}$$

$$\eta = \frac{P_2}{P_1} = 0,969 \approx \underline{\underline{96,9\%}}$$

Om 3-fas värmare med en Y-fas ev. A kopplad last
 R_k ... anges gSV om till Y

Om last provat $\rightarrow$

4.7

Enfasterfo

4.7/1


- a) Ksl. prov utförs med märkström från högsp. sidan med nedsp. sidan kortsluten

$$U_{1n} = 3300 \text{ V} ; S_n = 50 \text{ kVA}$$

$$I_{1n} = \frac{S_n}{U_{1n}} = \frac{50 \cdot 10^3}{3,3 \cdot 10^3} = 15,15 \text{ A}$$

$$I_k = I_{1n}$$

Mha ksl. prov får vi fram R_k och X_k :

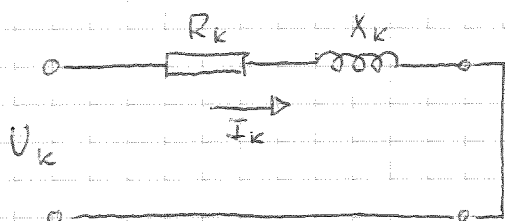

$$U_k = 155 \text{ V} ; P_k = 587 \text{ W}$$

$$P_k = R_k I_k^2 \Rightarrow$$

$$R_k = \frac{P_k}{I_k^2} = \frac{587}{15,15^2} = 2,56 \, \Omega ; Z_k = \frac{U_k}{I_k} = \frac{155}{15,15} = 10,23 \, \Omega$$

$$X_k = \sqrt{Z_k^2 - R_k^2} = 9,91 \, \Omega \Rightarrow \underline{Z_k} = (2,56 + j 9,91) \, \Omega$$

$$I_{2n} = \frac{S_n}{U_{2n}} = \frac{50 \cdot 10^3}{0,4 \cdot 10^3} = 125 \text{ A} ; I_2 = 0,8 \cdot I_{2n} = 100 \text{ A}$$

$$I_2' = I_2 \frac{U_{2n}}{U_{1n}} = 100 \frac{400}{3300} = 12,12 \text{ A} \quad \text{se } * \rightarrow$$

$$\Delta U = I_2' (R_k \cos \varphi_2 + X_k \sin \varphi_2) = 12,12 (2,56 \cdot 0,75 + 9,91 \cdot 0,66) = 102,7 \text{ V}$$

$$U_2' = U_1 - \Delta U = 3300 - 102,7 = 3197,3 \text{ V}$$

$$\underline{U_2} = U_2' \frac{U_{2n}}{U_{1n}} = 3197,3 \frac{0,4}{3,3} = \underline{\underline{387,5 \text{ V}}}$$

4,7

4.7/2

$$P_0 = 450 \text{ W}$$


$$b) P_1 = P_2 + P_{\text{förl}}$$

$$P_{\text{förl}} = P_0 + P_{\text{cu}} = P_0 + R_k (I_2')^2 = 450 + 2,56 (12,12)^2 = 826 \text{ W}$$

$$P_2 = U_2 I_2 \cos \varphi_2 = 387,5 \cdot 100 \cdot 0,75 = 29063 \text{ W}$$

$$P_1 = 29063 + 826 = 29889 \text{ W} \approx 29,9 \text{ kW}$$
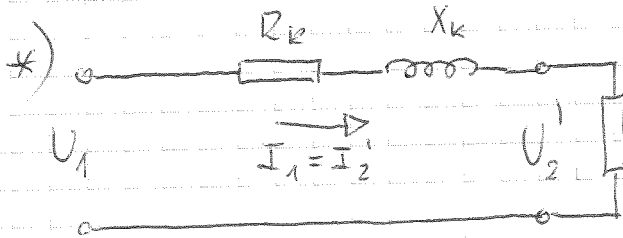
$$\eta = \frac{P_2}{P_1} = \frac{29063}{29889} = 0,972 \Rightarrow \eta = 97,2 \%$$



4.8 ej oblig.

4.8/1

Enfastrafo

$$S_n = 40 \text{ kVA} ; 1,5 / 0,23 \text{ kV}$$

$$U_k = 125 \text{ V} ; P_k = 550 \text{ W} ; P_o = 385 \text{ W}$$

$$S_2 = 30 \text{ kVA} ; \cos \varphi_2 = 0,72$$

a) Ksl. prov från 1,5 kV sidan:

$$I_{1n} = \frac{S_n}{U_{1n}} = \frac{40 \cdot 10^3}{1,5 \cdot 10^3} = 26,7 \text{ A} \Rightarrow I_k = I_{1n}$$

$$R_k = \frac{P_k}{I_k^2} = \frac{550}{26,7^2} = 0,77 \Omega$$

$$Z_k = \frac{U_k}{I_k} = \frac{125}{26,7} = 4,68 \Omega ; X_k = \sqrt{Z_k^2 - R_k^2} = 4,62 \Omega$$

$$Z_k = (0,77 + j 4,62) \Omega$$

$$P_2 = 30 \cdot 0,72 = 21,6 \text{ kW} ; Q_2 = 30 \cdot 0,69 = 20,7 \text{ kVAR}$$

$$\Delta U = R_k I_2' \cos \varphi_2 + X_k I_2' \sin \varphi_2$$

Vi vet ej I_2' och inte heller U_2' , förkläng ΔU med U_2'

$$\Delta U \cdot U_2' = R_k U_2' I_2' \cos \varphi_2 + X_k U_2' I_2' \sin \varphi_2$$

$$\Delta U \cdot U_2' = R_k P_2 + X_k Q_2 \Rightarrow \Delta U = \frac{R_k P_2 + X_k Q_2}{U_2'} =$$

$$= \frac{0,77 \cdot 21,6 + 4,62 \cdot 20,7}{U_2'} \cdot 10^3 = \frac{112,3}{U_2'} \cdot 10^3 \text{ V}$$

$$\text{om } U_2' \text{ i kV} \Rightarrow \Delta U = \frac{112,3}{U_2'} \text{ V} \Rightarrow \Delta U = \frac{0,112}{U_2'} \text{ kV}$$

$$U_1 = U_2' + \Delta U = U_2' + \frac{0,112}{U_2'} = 1,5$$

$$(U_2')^2 - 1,5 U_2' + 0,112 = 0$$

$$U_2' = 0,75 \pm \sqrt{0,75^2 - 0,112} = 0,75 \pm 0,67 \Rightarrow 1,42 \text{ kV}$$

$$\underline{U_2 = 1,42 \frac{0,23}{1,5} = 217,9 \text{ V}} ; \underline{I_2 = \frac{S_2}{U_2} = \frac{30}{0,218} = 137,7 \text{ A}}$$

4.8

4.8/2

b)

$$P_{cu} = R_k(I_2')^2 = 0,77 \left(137,7 \cdot \frac{0,23}{1,5} \right)^2 = 343 \text{ W}$$

$$P_0 = 385 \text{ W}$$

$$P_{\text{fore}} = P_0 + P_{cu} = 728 \text{ W}$$

$$P_2 = 21600 \text{ W}$$

$$P_1 = 21600 + 728 = 22328 \text{ W}$$



$$\eta = \frac{21600}{22328} = 0,967 \approx \underline{\underline{96,7\%}}$$

4.9

$$S_n = 25 \text{ kVA}$$

4.9/1

1. Δ/Δ

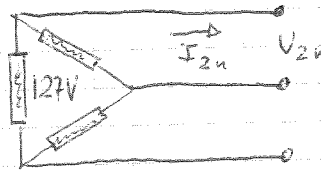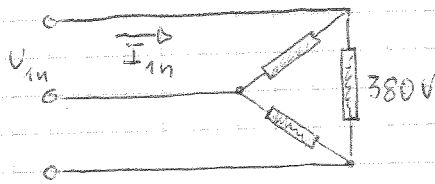



$$\underline{\underline{380/127 \text{ V}}}$$

$$S_n = \sqrt{3} U_{1n} I_{1n} \Rightarrow I_{1n} = \frac{25 \cdot 10^3}{\sqrt{3} \cdot 380} = \underline{\underline{38 \text{ A}}}$$

$$I_{2n} = I_{1n} \frac{U_{1n}}{U_{2n}} = 38 \cdot \frac{380}{127} = \underline{\underline{113,7 \text{ A}}}$$

$$(S_n = \sqrt{3} U_{2n} I_{2n} \Rightarrow I_{2n} = 113,7 \text{ A})$$

2. Δ/Y

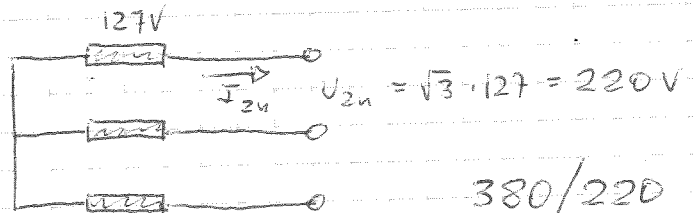
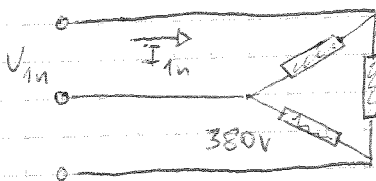


$$\underline{\underline{380/220 \text{ V}}}$$

$$I_{2n} = \frac{380}{220} \cdot 38 = \sqrt{3} \cdot 38 = \underline{\underline{65,6 \text{ A}}}$$

$$I_{1n} = \underline{\underline{38 \text{ A}}}$$



3. Y/Δ

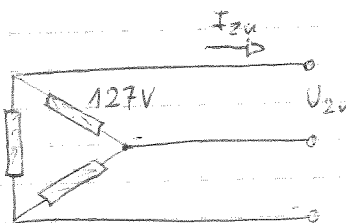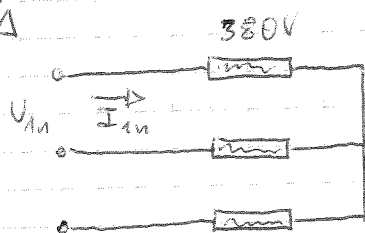

$$\underline{\underline{658/127 \text{ V}}}$$

$$U_{1n} = 380 \cdot \sqrt{3} = \underline{\underline{658 \text{ V}}}; I_{1n} = \frac{S_n}{\sqrt{3} U_{1n}} = \frac{25 \cdot 10^3}{\sqrt{3} \cdot 658} = \underline{\underline{21,9 \text{ A}}}$$
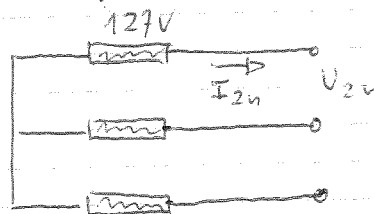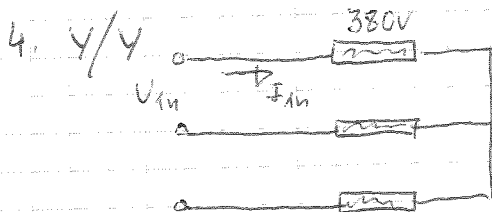
$$I_{2n} = \underline{\underline{113,7 \text{ A}}} \text{ som 1}$$



$$\underline{\underline{658/220 \text{ V}}}$$

$$I_{1n} = \underline{\underline{21,9 \text{ A}}} \text{ som 3}$$

$$I_{2n} = \underline{\underline{65,6 \text{ A}}} \text{ som 2}$$

4.94.9/2

L_1	L_2	U_{1n} (V)	I_{1n} (A)	U_{2n} (V)	I_{2n} (A)
Δ	Δ	380	38	127	113,7
Δ	Y	380	38	220	65,6
Y	Δ	658	21,9	127	113,7
Y	Y	658	21,9	220	65,6

4.10 $S_b = 20 \text{ kVA}$ vid 220V matas från ett nät med 380V

Alla förluster försummas

$$\text{Enl. 4.9} \rightarrow 380/220 \text{ V} \rightarrow \Delta/Y$$



$$S_1 = S_2 = S_b = 20 \text{ kVA}$$

$$I_1 = \frac{20 \cdot 10^3}{\sqrt{3} \cdot 380} = 30,4 \text{ A} \Rightarrow I_{\Delta} = \frac{I_1}{\sqrt{3}} = \frac{30,4}{\sqrt{3}} = 17,5 \text{ A}$$

$$I_2 = \frac{20 \cdot 10^3}{\sqrt{3} \cdot 220} = 52,5 \text{ A} \quad \left(I_2 = I_1 \frac{U_{1n}}{U_{2n}} \right)$$

4.11

4.11/1

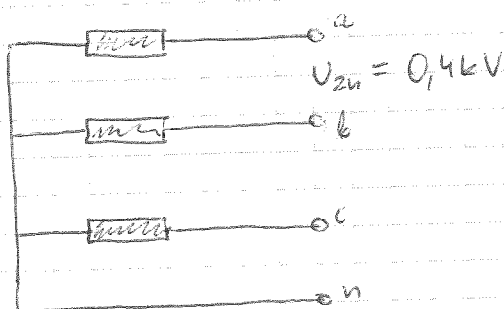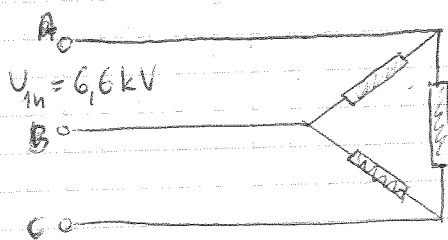3-fas trafo $S_n = 125 \text{ kVA}$; $6,6/0,4 \text{ kV}$ $\Delta/Y-0$ 

Ksl prov:

från $6,6 \text{ kV}$ sidan


$$I_{1n} = \frac{S_n}{\sqrt{3} U_{1n}} = \frac{125 \cdot 10^3}{\sqrt{3} \cdot 6,6 \cdot 10^3} = 10,93 \text{ A}$$

$$I_k = I_{1n}$$

$$U_{kf} = I_k \cdot Z_k \Rightarrow Z_k = \frac{U_{kf}}{I_k} = \frac{310}{\sqrt{3} \cdot 10,93} = 16,37 \, \Omega / \text{fas}$$

$$\cos \varphi_k = \frac{P_k}{\sqrt{3} U_k I_k} = \frac{1330}{\sqrt{3} \cdot 310 \cdot 10,93} = 0,23 ; \sin \varphi_k = 0,97$$



$$\underline{Z}_k = Z_k (\cos \varphi_k + j \sin \varphi_k) = 16,37 (0,23 + j 0,97) = (3,77 + j 15,88) \, \Omega / \text{fas}$$

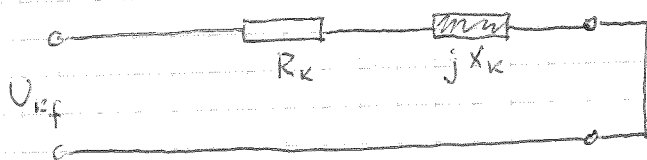Ekv. Y-fas
vid ksl.

alt.:


$$P_k = 3 R_k I_k^2 \Rightarrow R_k$$
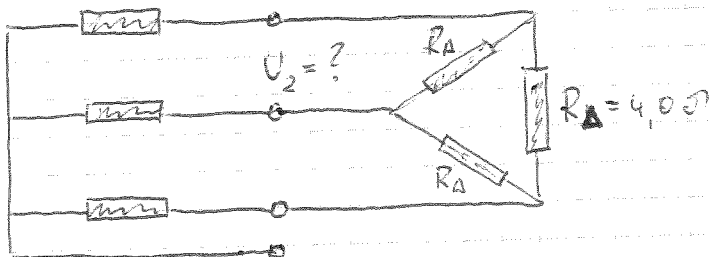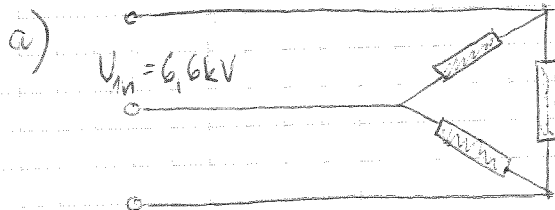
$$Q_k = P_k \tan \varphi_k \Rightarrow X_k = \frac{Q_k}{3 I_k^2} \quad \left(\text{alt } Q_k = \sqrt{S_k^2 - P_k^2} \right)$$



4.11

4.11/2

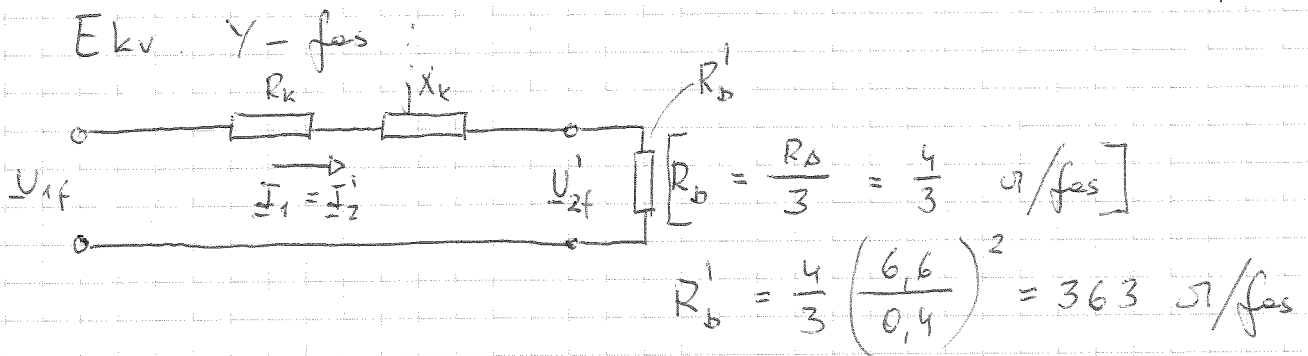

$$\underline{I_2} = \frac{U_{1f}}{Z_{tot}} = \frac{6600/\sqrt{3} \angle 0^\circ}{3,77 + j15,88 + 363} = \frac{6600/\sqrt{3} \angle 0^\circ}{367 \angle 2,48^\circ} = 10,38 \angle -2,48^\circ \text{ A} \quad |\underline{I_2}| = 10,38 \text{ A}$$

$$\underline{I_2} = \underline{I_2}' \frac{U_{1n}}{V_{2n}} = 10,38 \frac{6,6}{0,4} = \underline{171,3 \text{ A}}$$

$$U_{2f} = R_b \cdot I_2 = \frac{4}{3} \cdot 171,3 = 228,4 \text{ V}$$

$$\underline{U_2} = \sqrt{3} \cdot U_{2f} = \underline{395,6 \text{ V}}$$

b) $I_1 = I_2$ om I_0 försummas

$$I_\Delta = \frac{I_1}{\sqrt{3}} = \underline{5,99 \text{ A}}$$

extra Räkna fram z_k ; r_k ; x_k

$$Z_{bas} = \frac{U_n^2}{S_n} = \frac{6,6^2}{125} = 348,5 \text{ } \Omega$$

$$\underline{r_k} = \frac{3,77}{348,5} = 0,011 \hat{=} 1,1\%$$

$$\underline{x_k} = \frac{15,88}{348,5} = 0,0456 \hat{=} 4,56\%$$

$$x_k = \sqrt{z_k^2 - r_k^2} = \sqrt{4,7^2 - 1,1^2} = 4,57\%$$

4.12

$$P_0 = 1,05 \text{ kW} ; P_1 = ? ; \eta = ?$$

Belastungsverluste:

$$P_{cu} = 3 R_k (I_2)^2 = 3 \cdot 3,77 \cdot (10,38)^2 = 1218,6 \text{ W}$$

$$P_{förl} = 1218,6 + 1050 = 2268,6 \text{ W}$$

$$P_1 = P_2 + P_{förl} = \sqrt{3} U_2 I_2 + P_{förl} = \sqrt{3} \cdot 395,6 \cdot 17,13 + 2268,6 =$$

$$= 119643 \text{ W}$$

$$\eta = \frac{117375}{119643} = 0,981 \approx 98,1\%$$

4.13


4.13

$$S_n = 500 \text{ kVA} ; 6,0/0,4 \text{ kV}$$

$$P_2 = 300 \text{ kW} ; \cos \varphi_2 = 0,8$$

$$\Delta P = ?$$
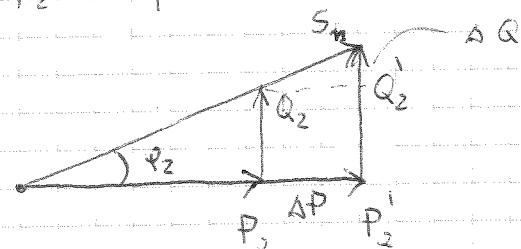
$$a) \cos \varphi_2 = 0,8 - \text{konst}$$




$$P'_2 = S_n \cos \varphi_2 = 500 \cdot 0,8 = 400 \text{ kW}$$

$$\Delta P = 400 - 300 = 100 \text{ kW}$$

b)

$$Q_2 = \text{konst}$$
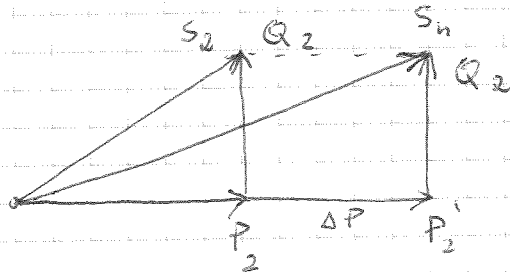
$$Q_2 = P_2 \tan \varphi_2 = 300 \cdot 0,75 = 225 \text{ kVar}$$



$$S_n^2 = (P_2 + \Delta P)^2 + Q_2^2$$

$$(300 + \Delta P)^2 = 500^2 - 225^2 = 199375$$

$$300 + \Delta P = 446,5$$

$$\Delta P = 146,5 \text{ kW}$$

4.14

$$S_n = 1 \text{ MVA} ; 6,6 / 0,4 \text{ kV} ; 50 \text{ Hz} ; r_k = 3\% ; z_k = 8\%$$

$$P_2 = 650 \text{ kW} ; \cos \varphi_2 = 0,8 ; U_2 = 350 \text{ V}$$

a) Uttagbar aktiv effekt vid $U_{2n} = 400 \text{ V}$ och $\cos \varphi_2 = 0,8$

$$P_2 = 1000 \cdot 0,8 = 800 \text{ kW}$$

$$\text{ motsvarar } P_2' = 800 \cdot \frac{350}{400} = 700 \text{ kW}$$

$$\Delta P = 700 - 650 = \underline{\underline{50 \text{ kW}}}$$

alt.

$$\text{Närkedrift : } S_n = \sqrt{3} U_{n1} I_{n1} = \sqrt{3} U_{n2} I_{n2} \Rightarrow$$

$$\Rightarrow I_{2n} = \frac{1000}{\sqrt{3} \cdot 0,4} = 1443 \text{ A}$$

$$U_2 = 350 \text{ V} ; I_2 = I_{2n} = 1443 \text{ A} ; \cos \varphi_2 = 0,8$$

$$\text{möjlig } P_2 = \sqrt{3} \cdot U_2 I_{2n} \cos \varphi_2 = \sqrt{3} \cdot 350 \cdot 1443 \cdot 0,8 = 700 \text{ kW}$$

$$\underline{\Delta P = 50 \text{ kW}}$$

$$b) P_{cu} = 3 R_k I_2^2 \Rightarrow \text{min om } I_2 \text{ min} \rightarrow \text{om } Q_2 = Q_c \text{ (} \cos \varphi = 1 \text{)}$$

$$Q_2 = P_2 \tan \varphi_2 = 650 \cdot 0,75 = 487,5 \text{ kVAR}$$

$$Q_c = 3 \omega C U_c^2 = 3 \omega C \left(\frac{U_2}{\sqrt{3}} \right)^2 = \omega C U_2^2$$

$$C = \frac{Q_c}{\omega U_2^2} = \frac{487,5 \cdot 10^3}{2\pi \cdot 50 \cdot 350^2} = 12,67 \text{ mF/fas}$$

$$I_{2c} = \frac{P_2}{\sqrt{3} \cdot 350 \cdot 1} = 1072 \text{ A} ; R_k = r_k \frac{U_n^2}{S_n} = 0,03 \frac{0,4^2}{1} = 4,8 \cdot 10^{-3} \Omega/\text{fas}$$

$$\underline{\underline{P_{cu} = 3 \cdot 4,8 \cdot 10^{-3} \cdot 1072^2 = 16548 \text{ W} \approx 16,55 \text{ kW}}}$$

4.15

Ingår ej kursen

4.15

$$S_n = 125 \text{ MVA} ; 6,6/0,4 \text{ kV} ; \Delta/Y-0$$

$$U_k = 310 \text{ V} ; P_k = 1,33 \text{ kW}$$

$$P_0 = 1,05 \text{ kW}$$

$$\eta - \max ; \cos \varphi_2 = 0,8 \quad - P_2 = ?$$

$$\eta = \frac{P_2}{P_2 + P_0 + \alpha^2 P_{\text{cun}}}$$

$$\eta = \frac{\alpha S_n \cos \varphi}{\alpha S_n \cos \varphi + P_0 + \alpha^2 P_{\text{cun}}} = \frac{\alpha A}{\alpha A + P_0 + \alpha^2 P_{\text{cun}}}$$

$$\frac{d\eta}{d\alpha} = 0$$

$$\frac{(\alpha A^2 + P_0 + \alpha^2 P_{\text{cun}}) \cdot A - (A + 2\alpha P_{\text{cun}}) \alpha A}{[\quad]^2} = 0$$

$$\alpha A^2 + P_0 A + \alpha^2 A P_{\text{cun}} - \alpha A^2 - 2\alpha^2 A P_{\text{cun}} = 0$$

$$P_0 A = \alpha^2 P_{\text{cun}} A \quad \alpha^2 = \frac{P_0}{P_{\text{cun}}} \quad P_{\text{cun}} = P_k$$

$$\alpha = \sqrt{\frac{1,05}{1,33}} = 0,889$$

$$\underline{P_2 = \alpha S_n \cos \varphi_2 = 0,889 \cdot 125 \cdot 0,8 = 88,85 \text{ kW}}$$

$$\eta_{\max} = \frac{P_2}{P_2 + P_0 + \alpha^2 P_k} = \frac{88,85}{88,85 + 1,05 + 0,889^2 \cdot 1,33} = 0,977$$

$$\underline{\eta_{\max} = 97,7 \%}$$

4.16/1

$$S_n = 125 \text{ kVA} ; 6,6 / 0,4 \text{ kV} ; \Delta / Y$$

$$z_k = 4,7 \% ; r_k = 1,1 \%$$

$$z_k = \frac{Z_k}{Z_{bas}} ; r_k = \frac{R_k}{Z_{bas}} ; X_k = \sqrt{Z_k^2 - R_k^2}$$

Räkna på 0,4 kV sidan:

$$Z_{bas} = \frac{U_{n2}^2}{S_n} = \frac{400^2}{125 \cdot 10^3} = 1,28 \Omega / \text{fas}$$


$$Z_k = 0,047 \cdot 1,28 = 60,2 \cdot 10^{-3} \Omega / \text{fas}$$

$$R_k = 0,011 \cdot 1,28 = 14,1 \cdot 10^{-3} \Omega / \text{fas}$$

$$X_k = 58,53 \cdot 10^{-3} \Omega / \text{fas}$$

a) Y-kopplad last - $Z_L = (0,6 + j1,0) \Omega / \text{fas} = 1,17 / 59,04^\circ \Omega / \text{fas}$

Ekv. Y-fas:

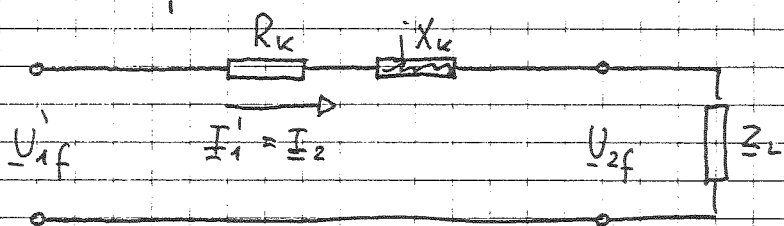

$$I_2 ; U_2 = ?$$

$$P_L ; Q_L = ?$$

$$U'_{1f} = \frac{400}{\sqrt{3}} \text{ V} ; U'_{1f} = Z_{tot} I_2$$

$$Z_{tot} = Z_k + Z_L = 14,1 \cdot 10^{-3} + j58,53 \cdot 10^{-3} + 0,6 + j1,0 = 0,614 + j1,059 = 1,22 / 59,9^\circ \Omega / \text{fas}$$

$$I_2 = \frac{400 / 0^\circ}{\sqrt{3} \cdot 1,22 / 59,9^\circ} = 189,3 / -59,9^\circ \text{ A}$$

$$I_2 = 189,3 \text{ A}$$

$$U'_{2f} = Z_L I_2 = 1,17 / 59,04^\circ \cdot 189,3 / -59,9^\circ = 221,5 / -0,86^\circ \text{ V}$$

$$U_2 = \sqrt{3} U'_{2f} = \sqrt{3} \cdot 221,5 = 383,65 \text{ V}$$

$$P_L = \sqrt{3} U_2 I_2 \cos \varphi_L = \sqrt{3} \cdot 383,65 \cdot 189,3 \cdot \cos 59,04 = 64,7 \text{ kW}$$

$$Q_L = \sqrt{3} U_2 I_2 \sin \varphi_L = \sqrt{3} \cdot 383,65 \cdot 189,3 \cdot \sin 59,04 = 107,9 \text{ kVAR}$$

b) ej då $I_2 > I_{n2} (180,4 \text{ A})$ transformatorn är överbelastad
 eller $S_2 > S_n$


$$c) \underline{\underline{P_{cu} = 3 R_k I_2^2 = 3 \cdot 14,1 \cdot 10^{-3} \cdot 189,3^2 = 1,52 \text{ kW}}}}$$

$$d) I_1 = I_2 \frac{U_{n2}}{U_{n1}} = 189,3 \cdot \frac{0,4}{6,6} = 11,47 \text{ A}$$

$$\underline{\underline{I_\Delta = \frac{I_1}{\sqrt{3}} = 6,6 \text{ A}}}}$$

4.164.16

a)

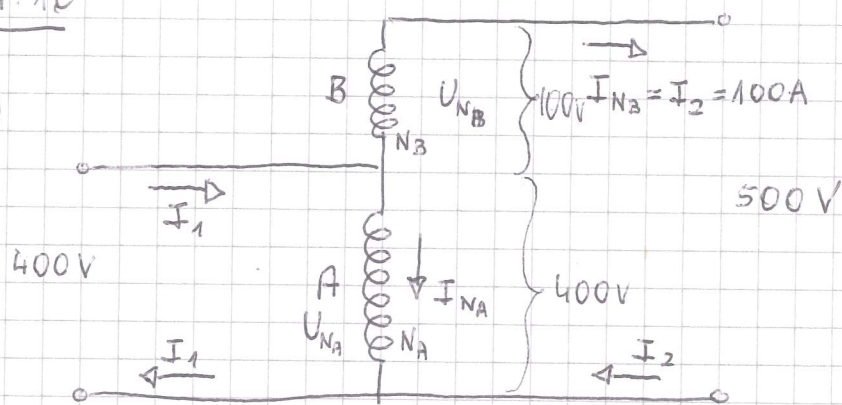

$$I_2 + I_{NA} = I_1 \Rightarrow I_{NA} = I_1 - I_2$$

$$b) \frac{U_{NA} = 400V}{U_{NB} = 100V}$$

$$\frac{U_{NB}}{U_{NA}} = \frac{N_B}{N_A} = \frac{100}{400}$$

c)

$$I_{NB} = I_2 = 100A \quad \text{mmk lika} \rightarrow$$

$$I_{NB} \cdot N_B = I_{NA} \cdot N_A \quad ; \quad I_{NA} = I_{NB} \cdot \frac{N_B}{N_A} = 100 \cdot \frac{1}{4} = 25A$$

$$\underline{I_{NA} = 25A} \quad ; \quad \underline{I_{NB} = 100A} \quad (I_1 = I_{NA} + I_2 = 125A)$$

$$d) \underline{S_{NA} = U_{NA} \cdot I_{NA} = 400 \cdot 25 = 10kVA}$$


$$\underline{S_{NB} = U_{NB} \cdot I_{NB} = 100 \cdot 100 = 10kVA}$$

Diskutera lindningsdimensionering

4.17

4.18

1. Fulltransformator (förlustfri; enfas)

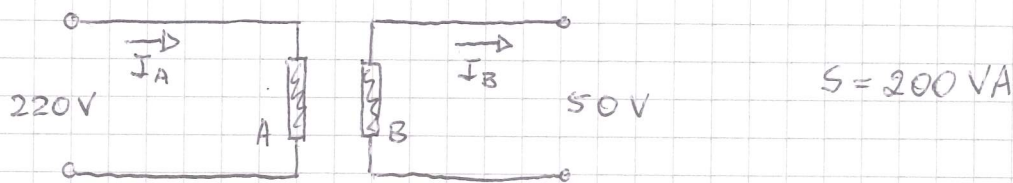


$$\therefore S = U_1 I_A = U_2 I_B$$

$$I_A = \frac{200}{220} = \frac{10}{11} \text{ A} ; \text{ Linding A klarar } \frac{10}{11} \text{ A}$$

$$I_B = \frac{200}{50} = 4 \text{ A} ; \text{ - " - B - " - 4 A}$$

2. Spartransformator


a)

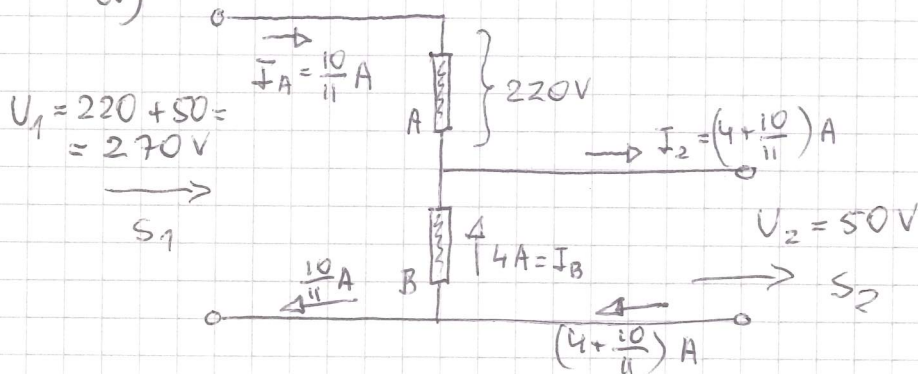

$$\underline{\underline{270/50 \text{ V}}}$$

$$\underline{\underline{S_1 = 270 \cdot \frac{10}{11} = 245 \text{ VA}}} \text{ eller } \underline{\underline{S_2 = 50 \left(4 + \frac{10}{11}\right) = 245 \text{ VA}}}$$

b)

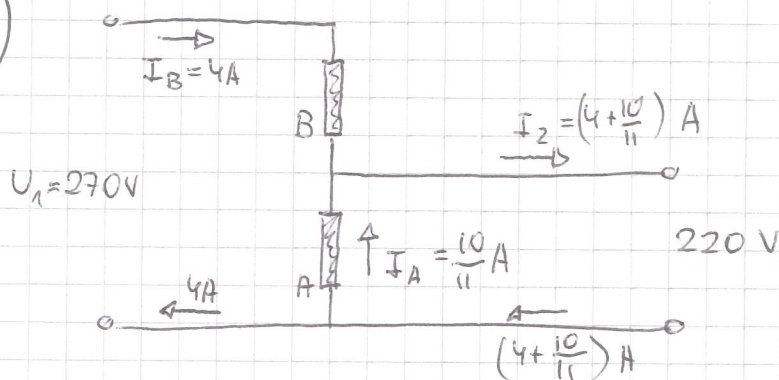

$$\underline{\underline{270/220 \text{ V}}}$$

$$\underline{\underline{S_1 = 270 \cdot 4 = 1080 \text{ VA}}} \text{ eller } \underline{\underline{S_2 = 220 \left(4 + \frac{10}{11}\right) = 1080 \text{ VA}}}$$

jämför !