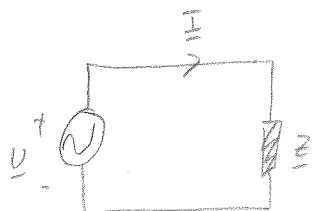


III)



$$\underline{U} = 380 \angle 0^\circ \text{ V}$$

$$\underline{Z} = (16 + j12) \Omega = 20 \angle 36,87^\circ \Omega$$

a) Bestäm S , P och Q .

$$\underline{I} = \frac{\underline{U}}{\underline{Z}} = \frac{380 \angle 0^\circ}{20 \angle 36,87^\circ} = 19 \angle -36,87^\circ \text{ A} = 15,20 - j11,40 \text{ A}$$

$$\underline{S} = \underline{U} \cdot \underline{I}^* = 380 \angle 0^\circ \cdot 19 \angle 36,87^\circ = 7220 \angle 36,87^\circ = 5776 + j4332 \text{ VA}$$


svår:

$$S = 7,22 \text{ kVA}$$

$$P = 5,78 \text{ kW}$$

$$Q = 4,33 \text{ kVAR}$$

b)

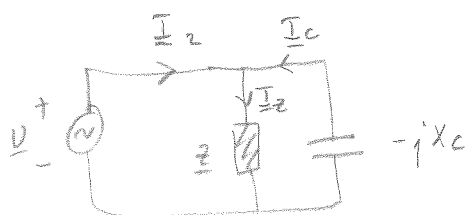

Strömmen är minimal
om bara aktiv effekt överförs,
dä är kompenseringen optimal,
 $S = \sqrt{P^2 + Q^2}$, $S = \underline{U} \cdot \underline{I}^*$

$$\underline{I}_2 = \frac{\underline{U}}{\underline{Z}} = \left\{ \text{ samma som tidigare } \right\} = 19 \angle -36,87^\circ \text{ A} = 15,20 - j11,40 \text{ A}$$

$$\underline{I}_2 = \underline{I}_2 + \underline{I}_c, \quad \underline{I}_2 = \left\{ \text{ rent reell } \right\} = 15,2 \text{ A}$$

$$\underline{I}_c = \left\{ \text{ rent imaginär } \right\} = -j11,40 \text{ A} \text{ (kondensatorn bidrar bara med reaktiv effekt)}$$

$$U = jX_c \cdot I_c$$

$$\Rightarrow jX_c = \frac{U}{I_c} = \frac{380 \angle 0^\circ}{11,40 \angle -90^\circ} = 33 \angle 90^\circ = j33 \Omega$$

$$\Rightarrow X_c = 33 \Omega$$

Från generatorns sida: $\underline{S}_g = \underline{U} \cdot \underline{I}_2^* = 380 \angle 0^\circ \cdot 15,20 \angle 0^\circ = 5776 \text{ VA}$ (rent aktiv)

$$\Rightarrow P_g = 5,78 \text{ kW}$$

$$Q_g = 0 \text{ kVAR}$$

c) kondensatorn minskas med 25%

$$X_{C2} = 0,75 \cdot X_C = 25 \, \Omega$$

$$\underline{Z}_{\text{par}} = \underline{Z} // -jX_C = \frac{20 \angle 36,87^\circ \cdot 25 \angle -90^\circ}{16 + j12 - j25} = \frac{500 \angle -53,13^\circ}{20,62 \angle -39,09^\circ} = 24,25 \angle -14,04^\circ \, \Omega$$

$$\Rightarrow \underline{I} = \frac{\underline{U}}{\underline{Z}_{\text{par}}} = \frac{380 \angle 0^\circ}{24,25 \angle -14,04^\circ} = 15,67 \angle 14,04^\circ$$


$$\underline{S} = \underline{U} \cdot \underline{I}^* = 380 \angle 0^\circ \cdot 15,67 \angle -14,04^\circ = 5955 \angle -14,04^\circ = 5777 - j1445 \, \text{VA}$$

Svar: $S = 5,96 \, \text{kVA}$

$$P = 5,78 \, \text{kW}$$

$$Q = -1,45 \, \text{kVAR} \quad (\text{generatoren upptar reaktiv effekt})$$

d)

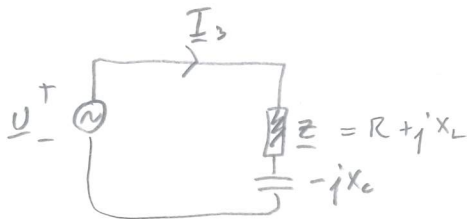

$$\underline{Z}_{\text{tot}} = \underline{Z} + (-jX_C) = R + j(X_L - X_C)$$


Den aktiva effekt blir maximal om $X_C = X_L = 12 \, \Omega$

$$\Rightarrow \underline{Z}_{\text{tot}} = R = 16 \, \Omega$$

$$\underline{I}_3 = \frac{\underline{U}}{\underline{Z}_{\text{tot}}} = \frac{380 \angle 0^\circ}{16 \angle 0^\circ} = 23,75 \angle 0^\circ \, \text{A}$$


$$\underline{U}_{X_C} = \underline{I}_3 \cdot (-jX_C) = 23,75 \angle 0^\circ \cdot 12 \angle -90^\circ = 285 \angle -90^\circ \, \text{V}$$

Svar: spänningen över kondensatorn blir 285 V

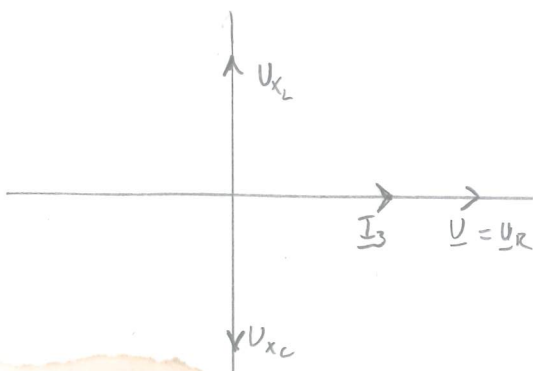

Övning 2-1

2.9)

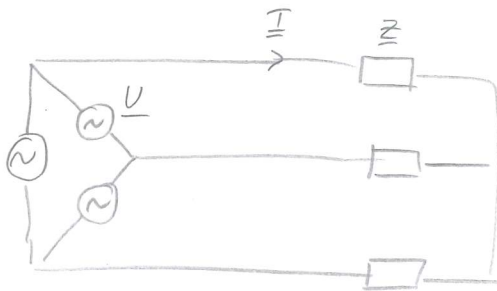


$$U = 500 \text{ V}$$

$$I = 30 \text{ A}$$


$$\cos \varphi = 0,8$$

$$\Rightarrow \varphi = 36,87^\circ$$

$$Z = R // jX_L$$

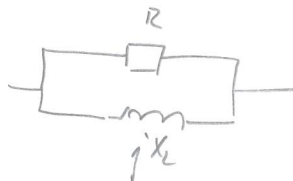

Ekvivalent Y-fas

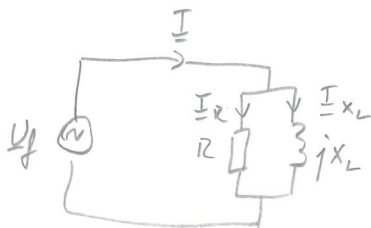

$$P = 3 \cdot U_f \cdot I \cos \varphi = 3 \cdot \frac{500}{\sqrt{3}} \cdot 30 \cdot 0,8 = \underline{\underline{20,78 \text{ kW}}}$$

$$I_R = I \cdot \cos \varphi = 30 \cdot 0,8 = 24 \text{ A}$$

$$I_{X_L} = I \cdot \sin \varphi = 18 \text{ A}$$

$$P = 3 \cdot R \cdot I_R^2 \Rightarrow R = \frac{P}{3 I_R^2} = \underline{\underline{12 \Omega/\text{fas}}}$$

$$Q = 3 \cdot U_f \cdot I \sin \varphi = 15,59 \text{ kVAR}$$

$$Q = 3 \cdot X_L I_{X_L}^2 \Rightarrow X_L = \frac{Q}{3 \cdot I_{X_L}^2} = \underline{\underline{16 \Omega/\text{fas}}}$$

Oving 2-4