

ENM061 - Power Electronic Converters 7.5 ECTS, 2017

Mebtu Beza

mebtu.beza@chalmers.se

Chalmers University of Technology
Department of Electrical Engineering
Division of Electric Power Engineering

Lecture outline


The Full-bridge, half-bridge and Push-Pull DC/DC converters



- The non-isolated full-bridge converter – bipolar vs unipolar switching
- The isolated full-bridge DC/DC converter
- The isolated half-bridge DC/DC converter
- The push-pull DC/DC converter
- How to select a suitable converter topology
 - ❖ Core excitation and isolation
 - ❖ Power rating and efficiency
 - ❖ Switch utilization
- Summary

Learning outcomes


- Fourier components and total harmonic distortion (THD) for basic waveforms.
- Operating principles of the most common active components (e.g. diode, thyristor, IGBT, and MOSFET) and passive components (e.g. capacitors, transformers and inductors).
- Operation of a pulse width modulation (PWM), the purpose of controlling the desired quantity and the need for a controller circuit within the power electronic converter.
- **Analysis of ideal DC/DC converters (e.g. buck, boost, buck-boost, flyback, the forward, the half-bridge, the full-bridge and the push-pull converters) in CCM and DCM operation.**
- Operating principles of single-phase and three-phase AC/DC inverters with different modulation strategies (e.g. PWM and square wave operation).
- Operation of multilevel converters (e.g. NPC, flying capacitor and MMC topologies) using current and voltage waveform analysis. Pros and Cons of the converter in terms of harmonics and losses.
- Operation of single- and three-phase diode rectifiers operating with voltage-stiff and current-stiff DC-side. Investigating the impact of line impedance within the converter circuit for current commutation.
- Operation of single- and three-phase thyristor rectifiers operating with a current-stiff DC-side and the impact of line impedance for current commutation. Investigating the use of 6/12-pulse configurations.
- Identify simple power electronic converter schematics. Recognizing the different parts in a physical circuit on which basic wave-shape and efficiency measurements is performed.
- Loss calculation in passive and active components. Evaluating the temperature rise in the active components and choosing an appropriate heat-sink. Gaining a basic understanding of component life time.
- Utilizing the software Cadence PSpice to simulate basic power electronic circuits and the practical labs to have a firsthand experience of how real DC/DC converters operate.

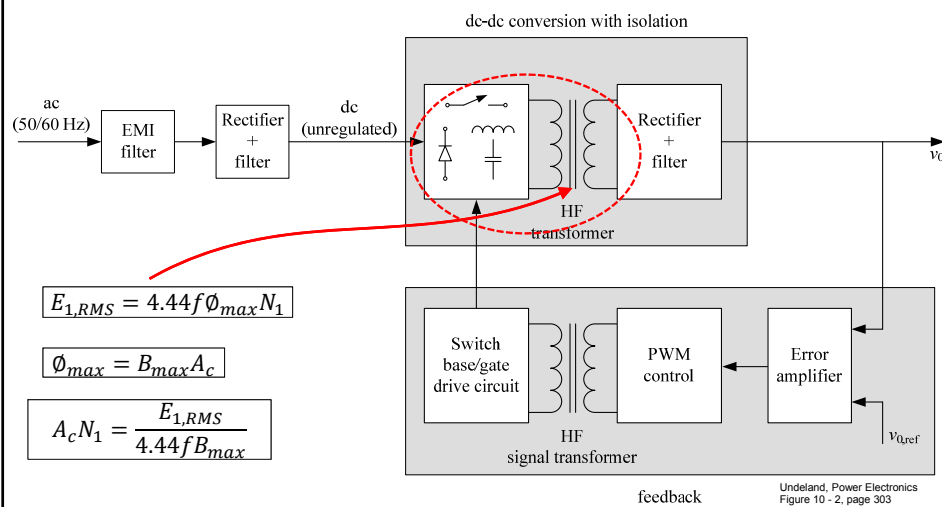Switch-mode power supply with electrical Isolation



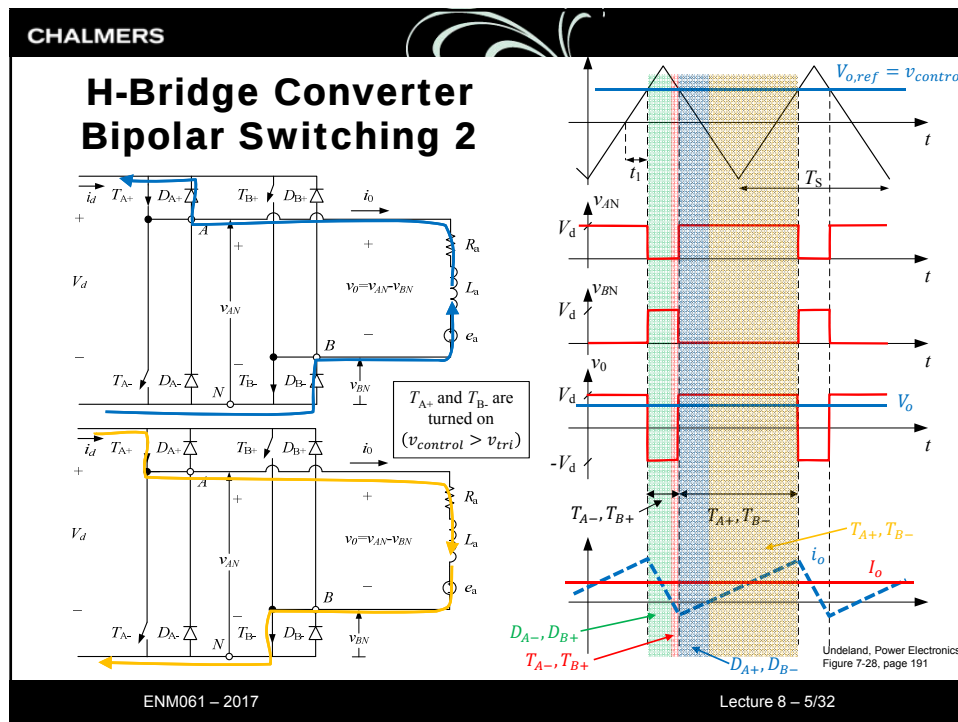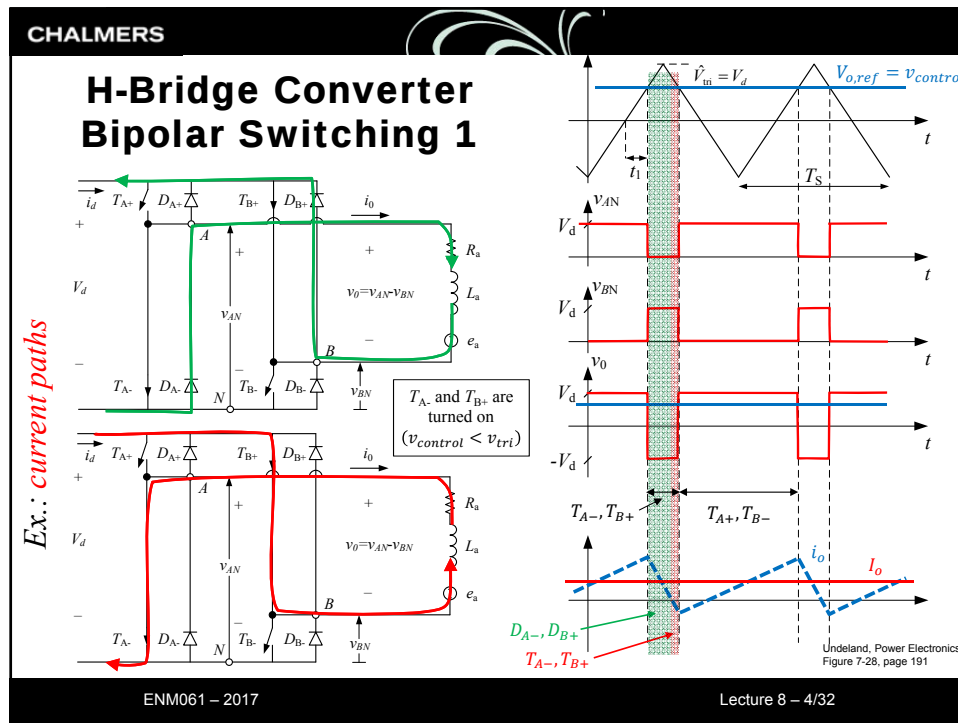


H-Bridge Converter Unipolar Switching 1

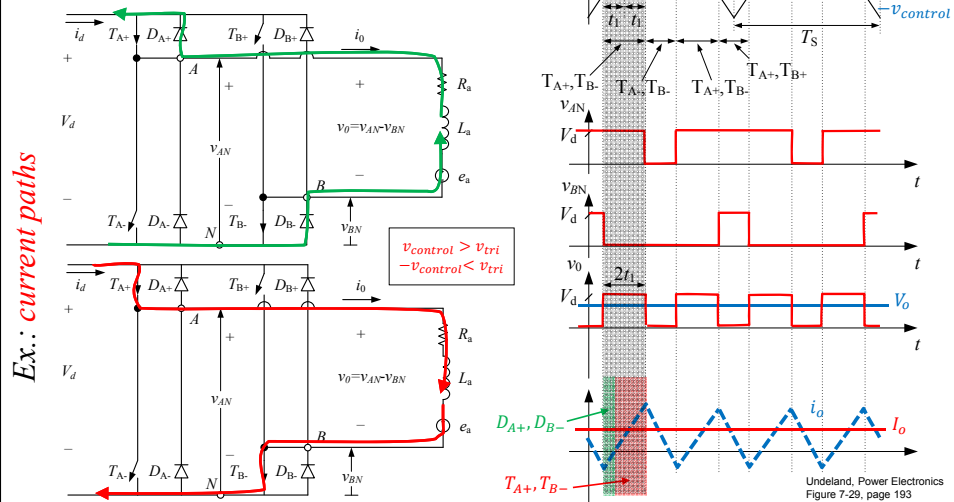

ENM061 – 2017

Lecture 8 – 6/32



H-Bridge Converter Unipolar Switching 2

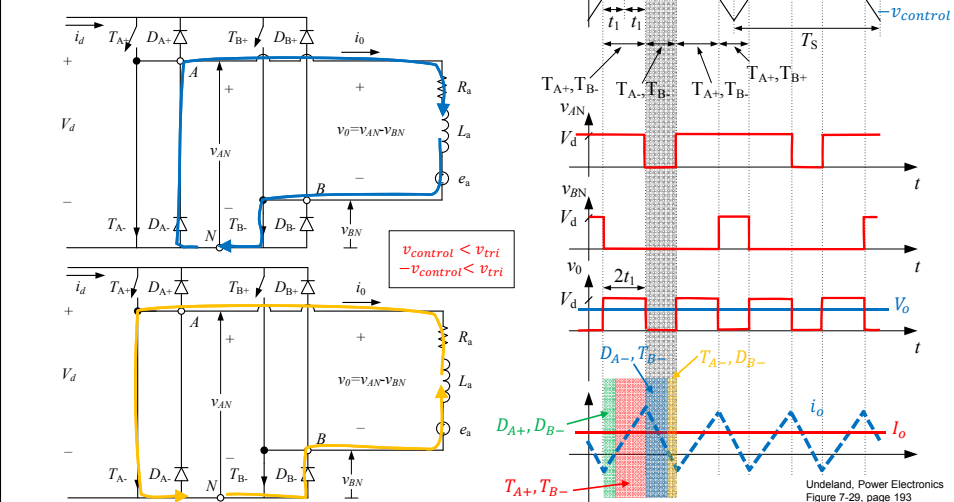

ENM061 – 2017

Lecture 8 – 7/32



H-Bridge Converter Unipolar Switching 3

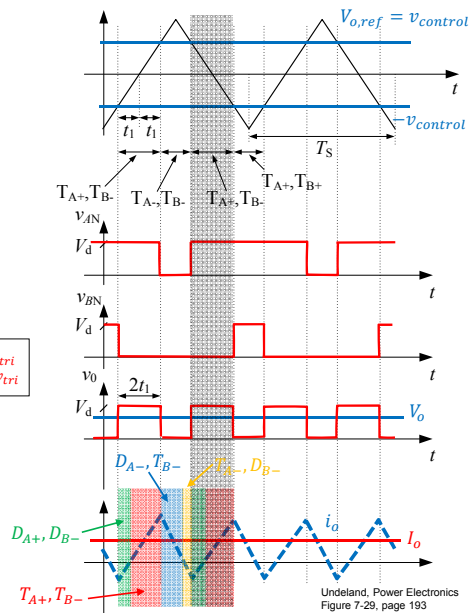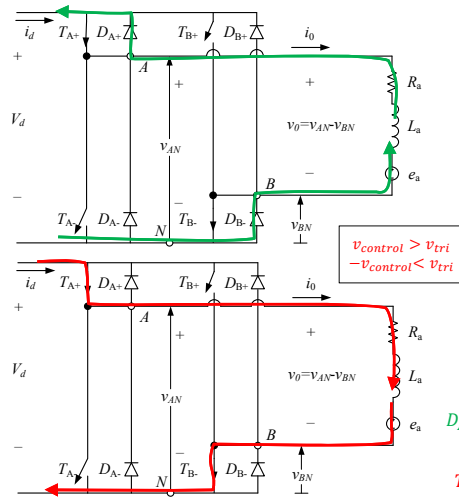

ENM061 – 2017

Lecture 8 – 8/32


H-Bridge Converter Unipolar Switching 4

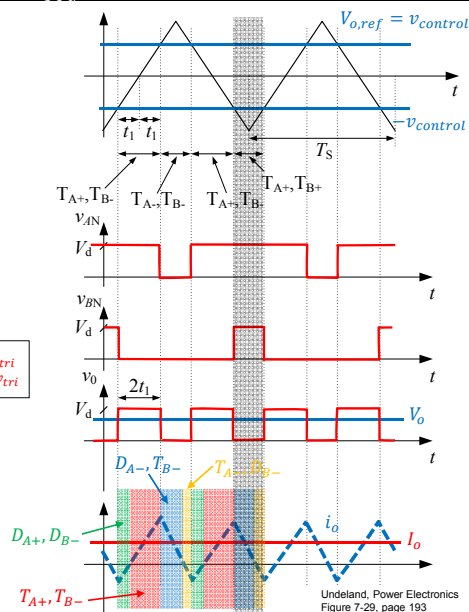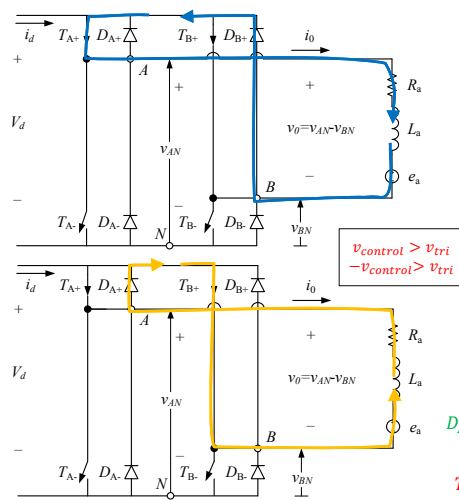

ENM061 – 2017

Lecture 8 – 9/32

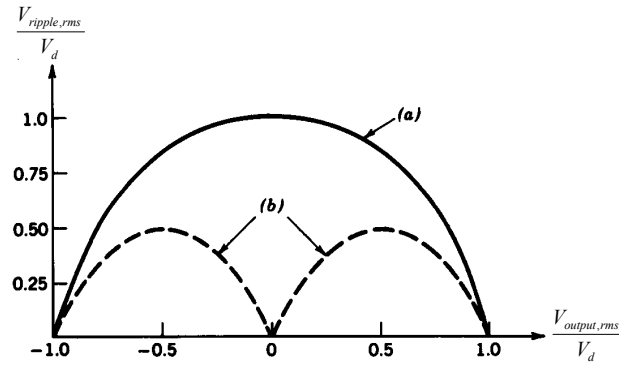Bipolar vs unipolar switching Output Voltage Comparison




(a) bipolar switching, (b) unipolar switching


Undeland, Power Electronics
Figure 7 - 30, page 194

Bipolar vs unipolar switching Output current comparison

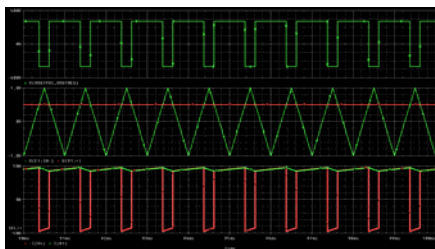- With the same switching frequency, PWM with unipolar switching results in a lower RMS ripple component in the output voltage.




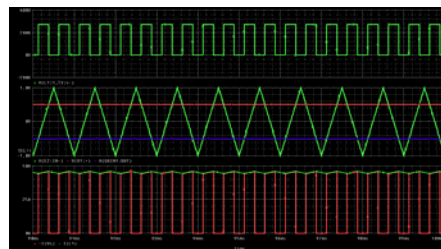Bipolar: $v_c=0.5$
 $V_{out}=135V$ ($-V_d$ to $+V_d$)
 Current ripple: 5.3A (RL load)
 Current ripple freq: 1kHz



Unipolar: $v_c=0.5$
 $V_{out}=135V$ (0 to $+V_d$)
 Current Ripple: 1.6A (RL load)
 Current ripple freq: 2kHz

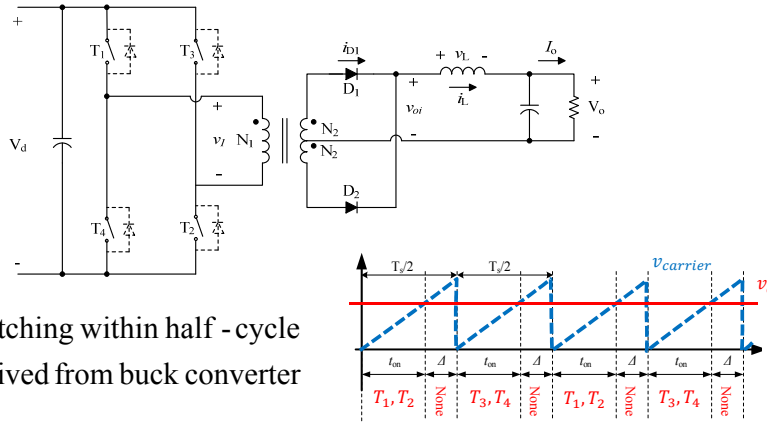
The Isolated Full-Bridge DC/DC Converter – Ideal Waveforms 1



Switching within half - cycle
Derived from buck converter

Undeland, Power Electronics
Figure 10-15, page 318

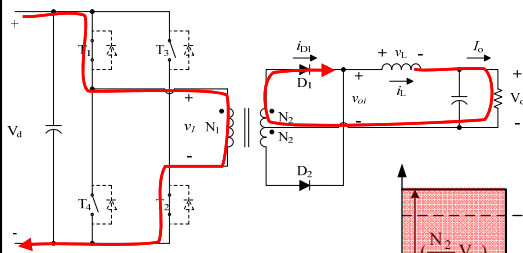The Isolated Full-Bridge DC/DC Converter – Ideal Waveforms 1




Ex.: *current paths and plots*

$$\text{Ex.: } \frac{V_o}{V_d} = ?$$

Switching within half - cycle
Derived from buck converter


$$\frac{V_o}{V_d} = 2 \frac{N_2}{N_1} D \quad (D \leq 0.5)$$

$$D = \frac{t_{on}}{T_s}$$

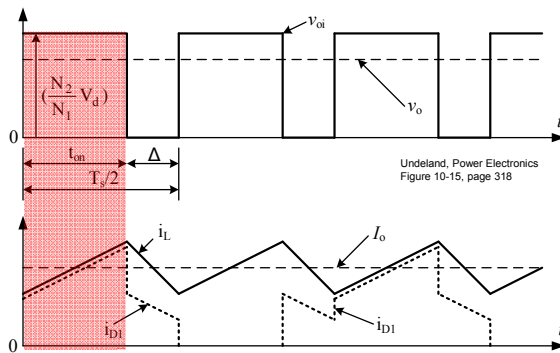

Undeland, Power Electronics
Figure 10-15, page 318


The Isolated Full-Bridge DC/DC Converter – Ideal Waveforms 2

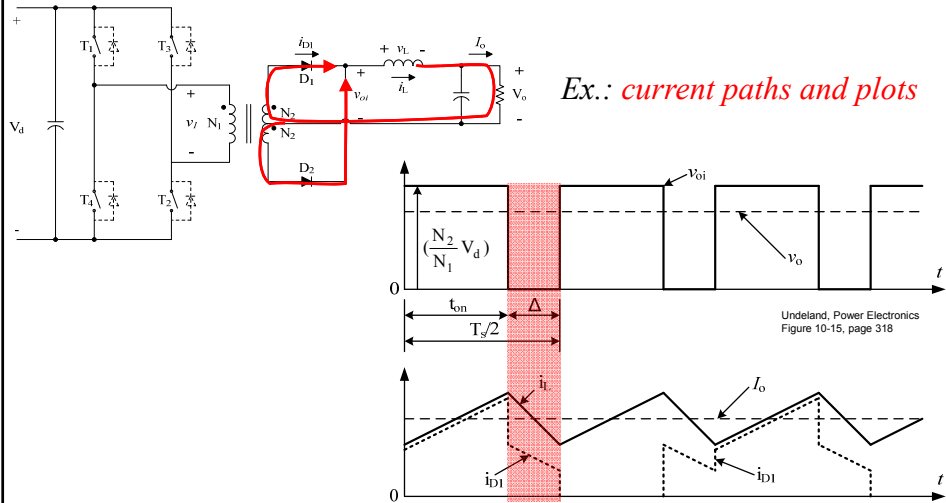

ENM061 – 2017

Lecture 8 – 14/32


Isolated Full-Bridge DC/DC Converter – Nonideal Waveforms 2

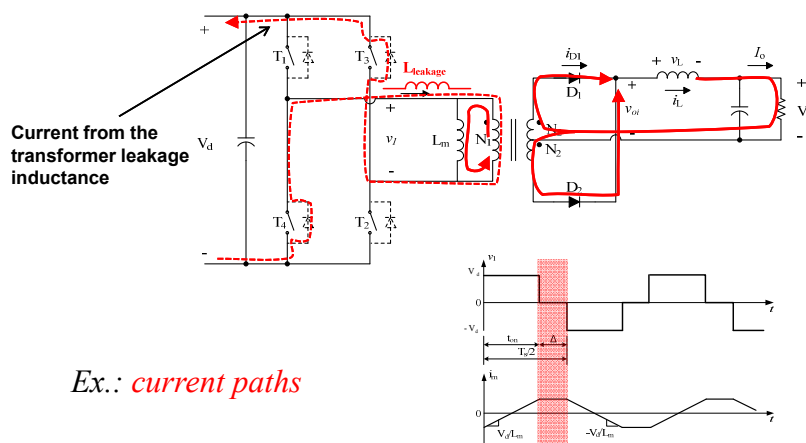

ENM061 – 2017

Lecture 8 – 15/32


The Isolated Full-Bridge DC/DC Converter - ideal Waveforms 3

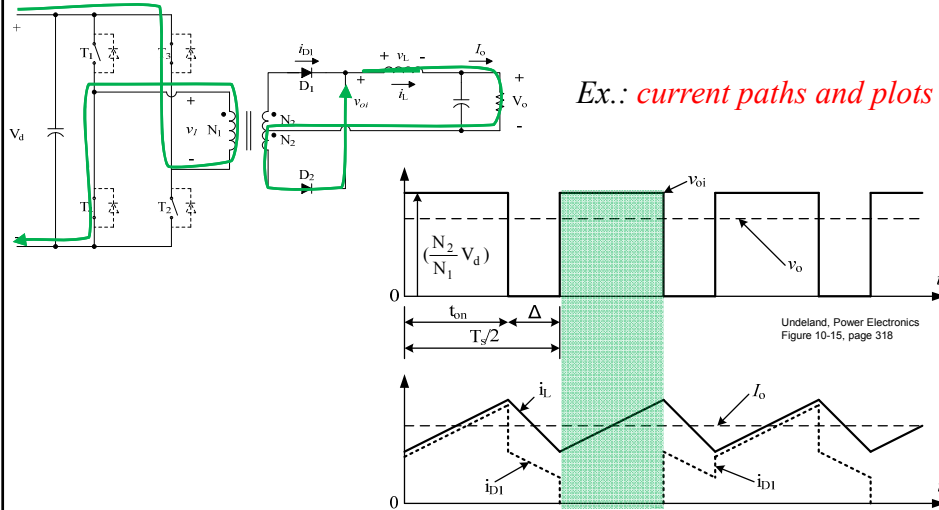

ENM061 – 2017

Lecture 8 – 16/32


The Isolated Full-Bridge DC/DC Converter – Ideal Waveforms 4

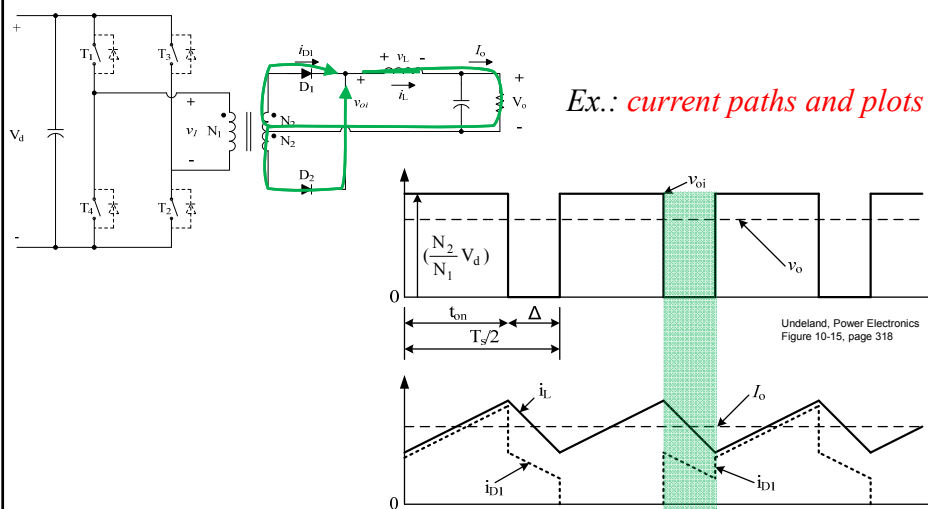

ENM061 – 2017

Lecture 8 – 17/32

Isolated Full-Bridge DC/DC Converter – Nonideal Waveforms 4

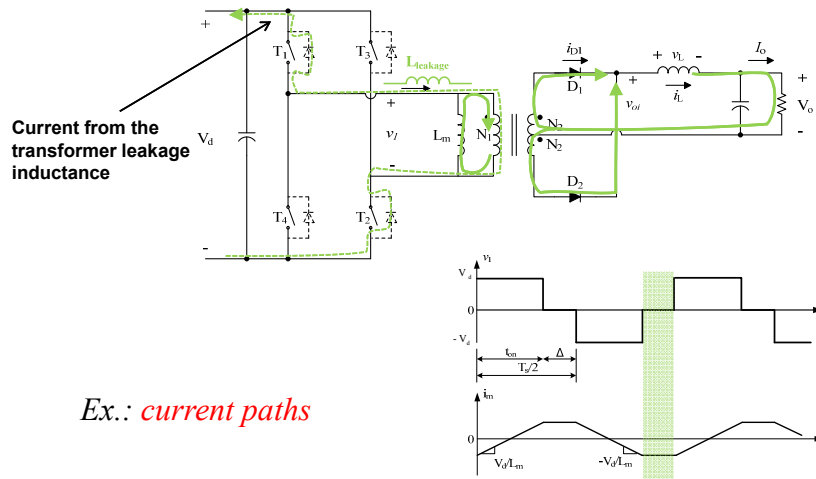


ENM061 – 2017

Lecture 8 – 18/32

The Half-Bridge Converter


- The two switches from the full-bridge are replaced with two capacitors

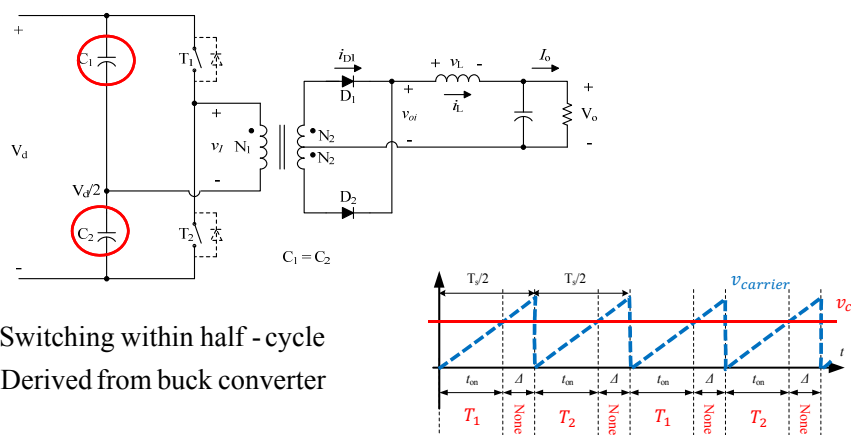

ENM061 – 2017

Lecture 8 – 19/32


Half-Bridge Converter – Waveforms 1

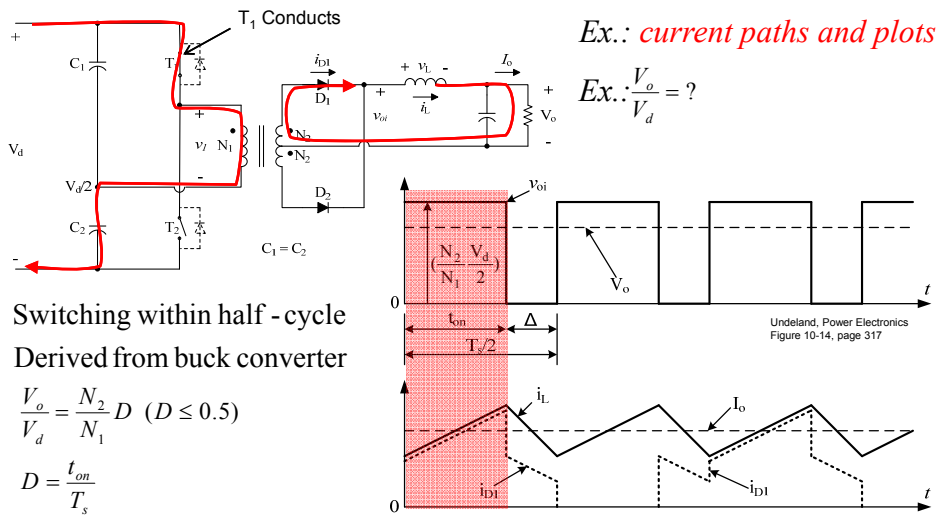

ENM061 – 2017

Lecture 8 – 20/32

Half-Bridge Converter – Waveforms 2

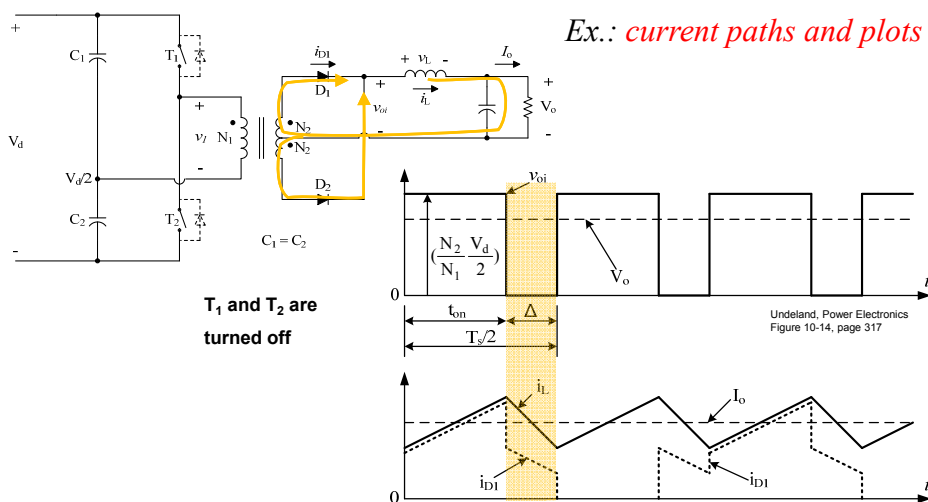


ENM061 – 2017

Lecture 8 – 21/32

Half-Bridge Converter – Waveforms 3

Ex.: *current paths and plots*

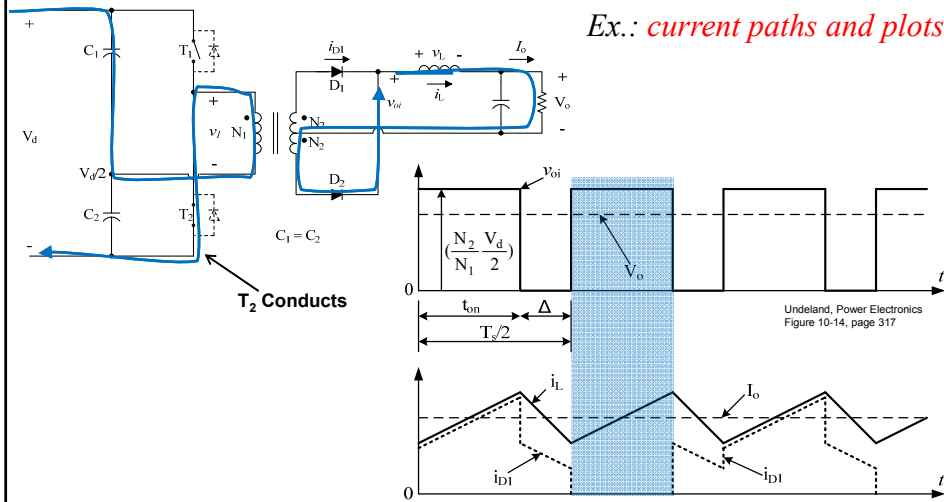


ENM061 – 2017

Lecture 8 – 22/32

Half-Bridge Converter – Waveforms 4

Ex.: *current paths and plots*

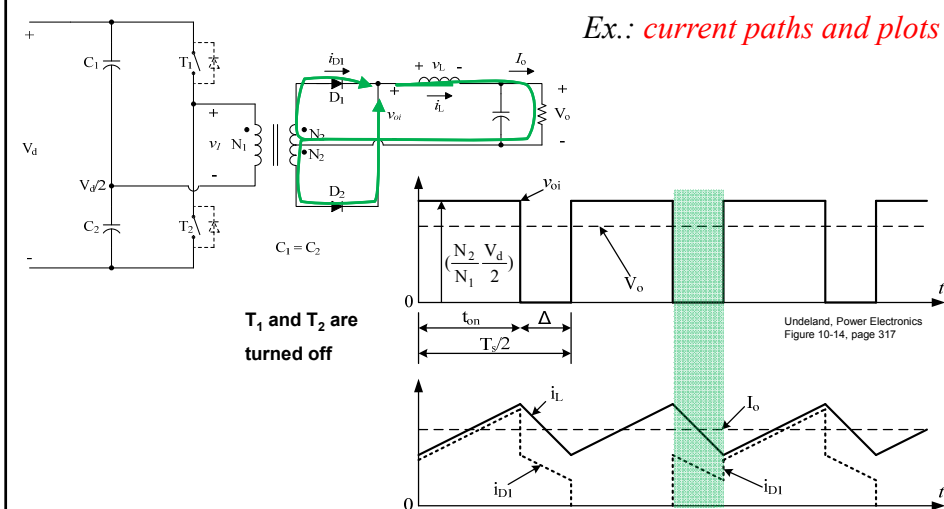


ENM061 – 2017


Lecture 8 – 23/32

The Push-Pull Converter

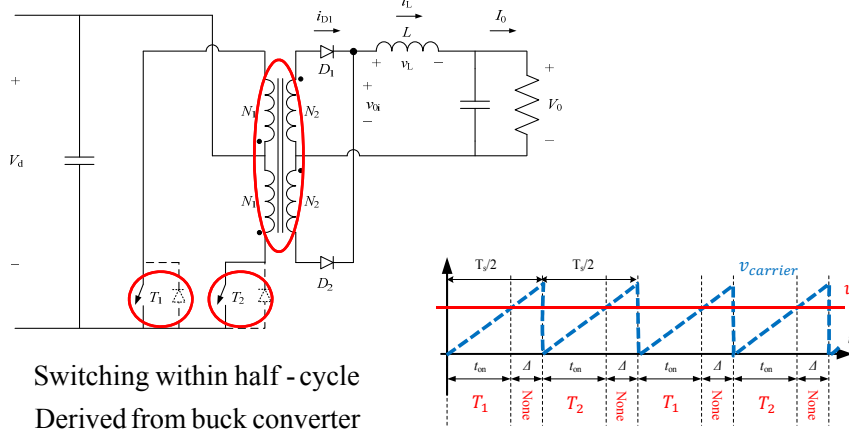
- Same output stage – two switches and two primary windings



Push-Pull Converter – Waveforms 1

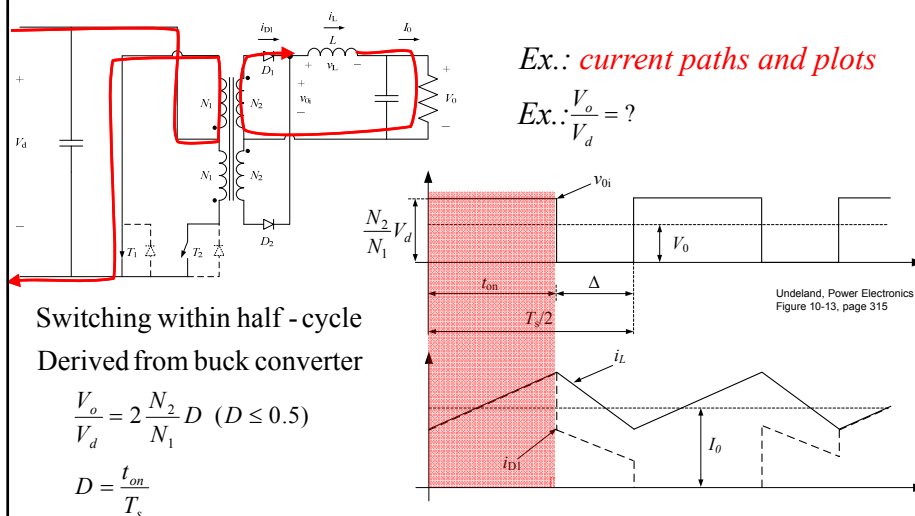


Push-Pull Converter – Waveforms 2

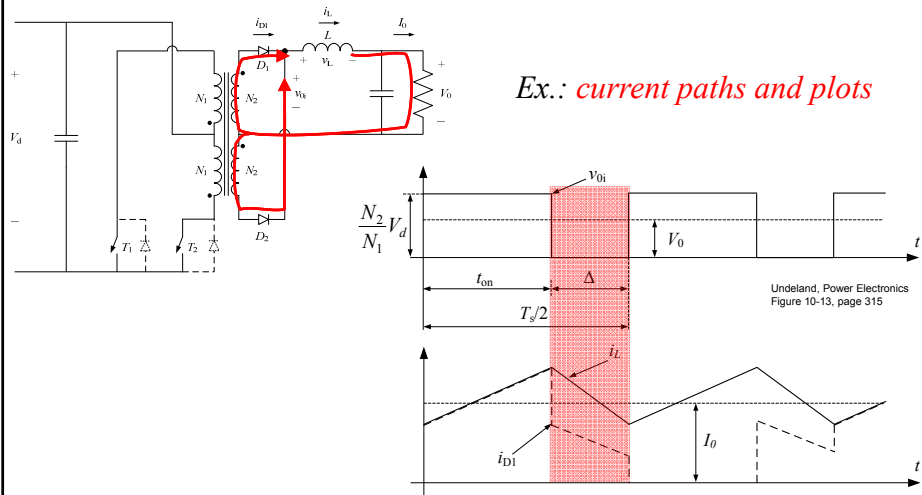

ENM061 – 2017

Lecture 8 – 26/32


Push-Pull Converter – Waveforms 3

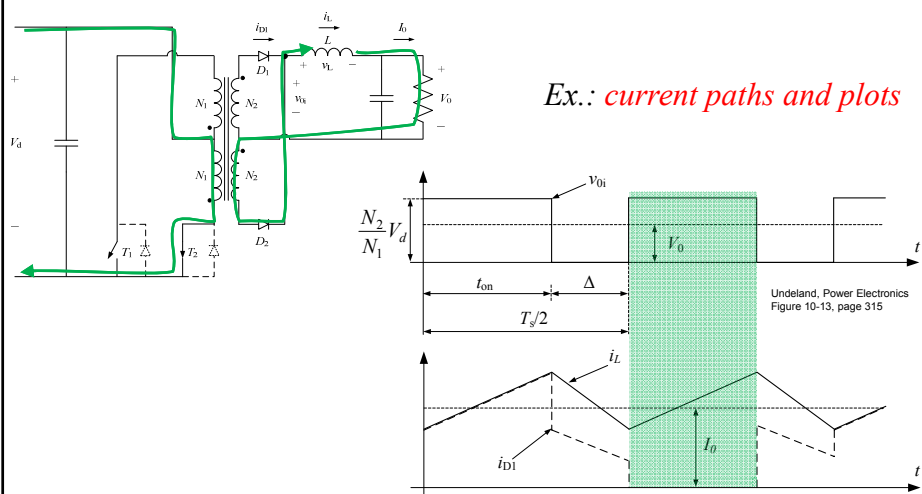

ENM061 – 2017

Lecture 8 – 27/32

Push-Pull Converter – Waveforms 4


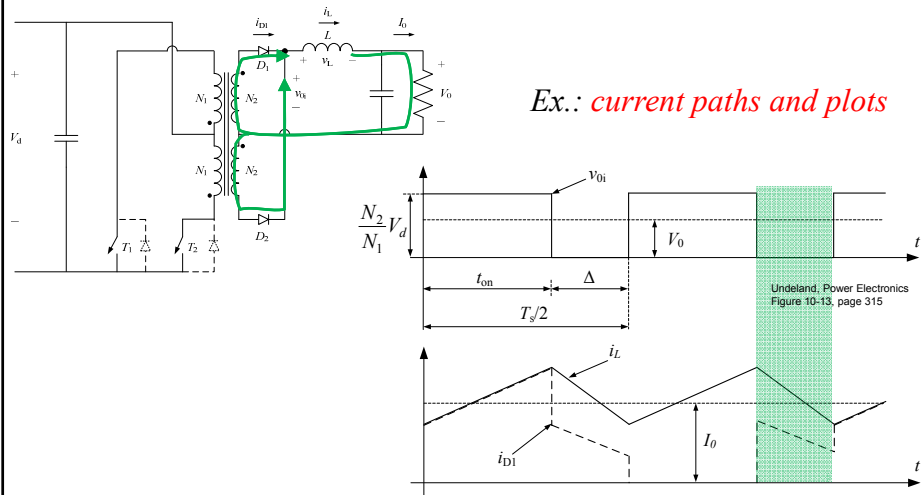


ENM061 – 2017

Lecture 8 – 28/32

Isolated DC/DC Converters transformer core excitation

- Unidirectional, $\Delta B = B_{\max}$ (Flyback, forward) vs bidirectional, $\Delta B = 2B_{\max}$ (Push-pull, HB, FB). **ΔB prioritized for smaller core size or low core loss!!!**
- Usually no air gap for higher mutual inductance but in flyback is necessary for energy storage
- The core is chosen based on the switching frequency and excitation type

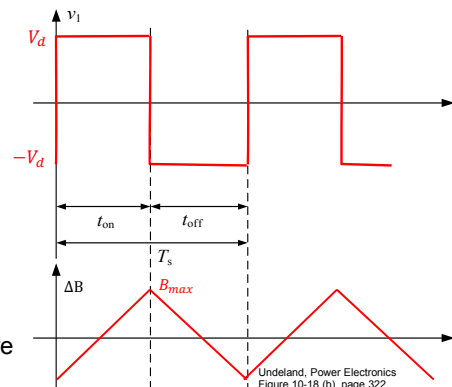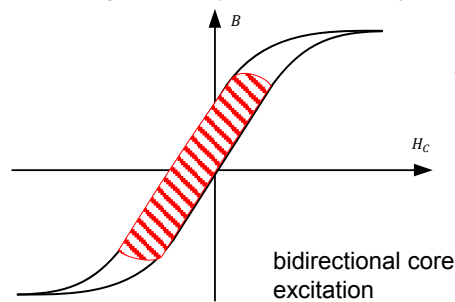

ENM061 – 2017

Lecture 8 – 29/32

Isolated DC/DC Converters Power rating and efficiency

Converter Topology	Typical max output power
Flyback	200W
Forward	300W
Two transistor forward / flyback	400W
Push-pull	500W
Half-Bridge	1000W
Full-Bridge	>1000W

Table 1. Converter output power range.

© Philips

Topology	Max. Power (Watts)	Typical Efficiency (%)
Flyback	30	75
1 Transistor Forward	150	80
2 Transistor Forward	200	83
Push-Pull	350	80
Full Bridge	500	85

Table 1: Comparison of various switching regulator topologies.

Topology	Maximum Drain Voltage	Average Drain Current
Flyback	1.5Vin(max)	75I _{SPout} /Vin(max)
1 Transistor Forward	2.5 to 3.0 Vin(max)	1.3Pout/Vin(max)
2 Transistor Forward	Vin(max)	1.2Pout/Vin(max)
Push-Pull	352.5 to 3.0 Vin(max)	0.65Pout/Vin(max)
Full Bridge	Vin(max)	0.60Pout/Vin(max)

Table 2: Power MOSFET voltage and current ratings versus power supply topology.

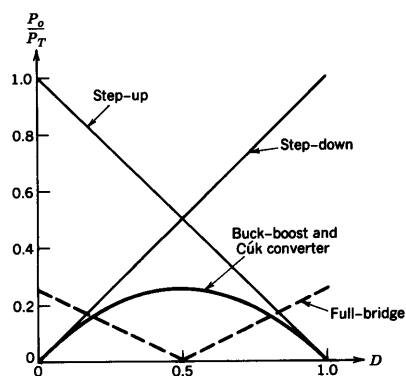
© Fairchild

TABLE 4: SMPS TOPOLOGY SELECTION GUIDELINES

Input voltage	Output power	Preferred Topology
Universal input (90-264) VAC	Po < 150 watt, Load current < 10A	Flyback, Forward
Universal input (90-264) VAC	Po < 150 watt, Load current > 10A	Forward
Universal input (90-264) VAC	150 watt < Po < 350	Two-Switch Forward, Half-Bridge, Push-Pull
Universal input (90-264) VAC	Po < 500 watt	Half-Bridge, Push-Pull
Vin > 350 VDC	Po < 750 watt	Half-Bridge
Vin < 200 VDC	Po < 500 watt	Push-Pull
Vin > 350 VDC	500 < Po < 1000 watt	Full-Bridge
Vin > 350 VDC	Po > 1000 watt	ZVT Full-Bridge
Vin > 350 VDC	Po > 2000 watt	More than one ZVT full-bridge in parallel, interleaved with more than one ZVT full-bridge

© Microchip

non-isolated DC/DC converters Switch utilization

Undeland, Power Electronics
Figure 7 - 31, page 195

- Use step-up or Step-down if possible for a switch utilization point of view
- Use buck-boost if higher or lower output voltage than the input is required
- Use full-bridge, If 4-quadrant operation or DC/AC conversion is required
- Other factors can be power rating, cost and efficiency



Summary

- Show current paths for a non-isolated H-bridge converter with bipolar and unipolar switching.
- Explain the operating principle of isolated full-bridge DC/DC converter with and without a non-ideal transformer.
- Explain the operating principle of isolated half-bridge DC/DC converter.
- Explain the operating principle a push-pull converter.
- Compare the different DC/DC converters in terms of power rating, efficiency, isolation and core excitation.
- Learning outcome:
 - ❖ Analysis of operation of isolated full-bridge, half-bridge and the push-pull converters.