



ENM061 - Power Electronic Converters

7.5 ECTS, 2017

Mebtu Beza

mebtu.beza@chalmers.se

Chalmers University of Technology
Department of Electrical Engineering
Division of Electric Power Engineering



Lecture outline


The single-phase inverter

- Power flow direction and definition of inverter/rectifier stage
- Revisiting the H-bridge converter
- The single-phase inverter in square-wave operating mode
- The single-phase inverter in bipolar-PWM operating mode
- The single-phase inverter in unipolar-PWM operating mode
- Output voltage and current ripple with a back-EMF load
- Summary

Learning outcomes

- Fourier components and total harmonic distortion (THD) for basic waveforms.
- Operating principles of the most common active components (e.g. diode, thyristor, IGBT, and MOSFET) and passive components (e.g. capacitors, transformers and inductors).
- Operation of a pulse width modulation (PWM), the purpose of controlling the desired quantity and the need for a controller circuit within the power electronic converter.
- Analysis of ideal DC/DC converters (e.g. buck, boost, buck-boost, flyback, the forward, the push-pull, half-bridge and full-bridge converters) in CCM and DCM operation.
- Operating principles of single-phase and three-phase DC/AC inverters with different modulation strategies (e.g. PWM and square wave operation).**
- Operation of multilevel converters (e.g. NPC, flying capacitor and MMC topologies) using current and voltage waveform analysis. Pros and Cons of the converter in terms of harmonics and losses.
- Operation of single- and three-phase diode rectifiers operating with voltage-stiff and current-stiff DC-side. Investigating the impact of line impedance within the converter circuit for current commutation.
- Operation of single- and three-phase thyristor rectifiers operating with a current-stiff DC-side and the impact of line impedance for current commutation. Investigating the use of 6/12-pulse configurations.
- Identify simple power electronic converter schematics. Recognizing the different parts in a physical circuit on which basic wave-shape and efficiency measurements is performed.
- Loss calculation in passive and active components. Evaluating the temperature rise in the active components and choosing an appropriate heat-sink. Gaining a basic understanding of component life time.
- Utilizing the software Cadence PSpice to simulate basic power electronic circuits and the practical labs to have a firsthand experience of how real DC/DC converters operate.

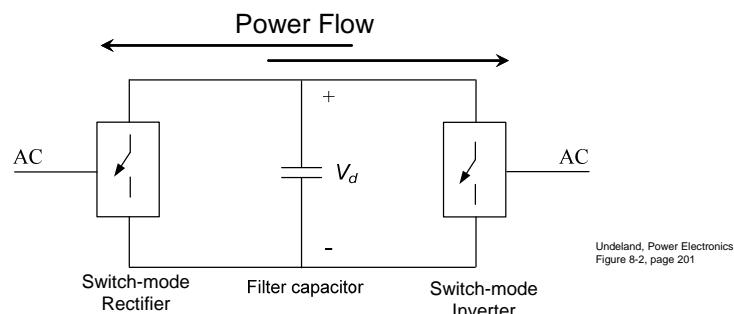
Power Flow direction Rectifier vs Inverter stage



- AC-AC converter as a whole
- The inverter transforms DC to AC with a controllable voltage and/or frequency
- A rectifier transforms AC of any frequency to DC
- Examples: motor drives, uninterruptible power supplies (UPS), grid-connected converters (active filters, FACTS, HVDC)

Power Flow direction the inverter stage



- Consider a motor drive system where the load can typically be represented with a large inductance and a back-EMF as $e_0 = \sqrt{2}E_0 \sin(\omega t)$
- Due to the phase difference between the current and voltage, the inverter has to be able to operate in all four quadrants.

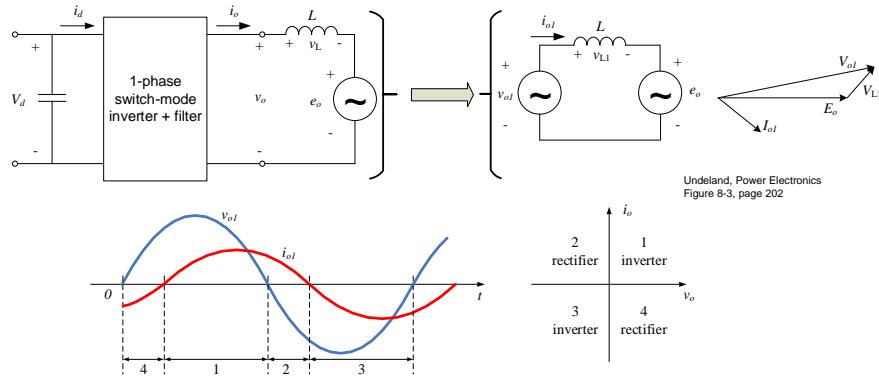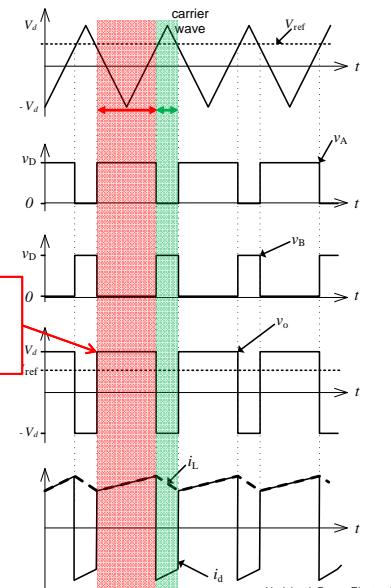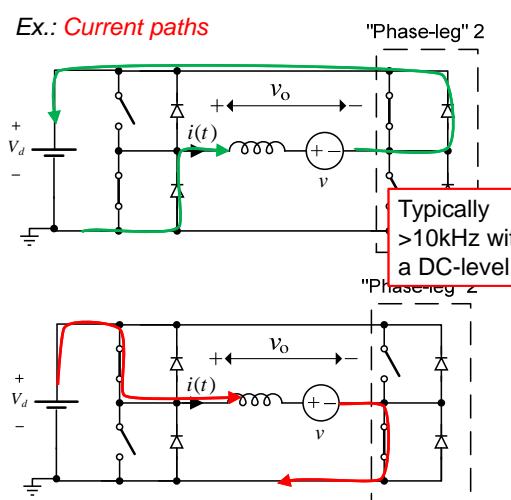

ENM061 – 2017

Lecture 9 – 4/30


Revisiting the H-Bridge DC/DC Converter

Ex.: *Current paths*

ENM061 – 2017



Lecture 9 – 5/30


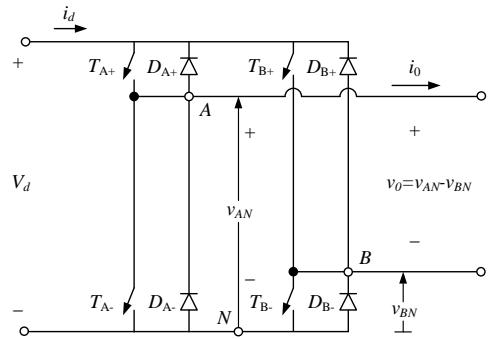
Single-Phase Inverter Different Operating Modes




Single-Phase Inverter Square-Wave Mode

Ex.: Current paths

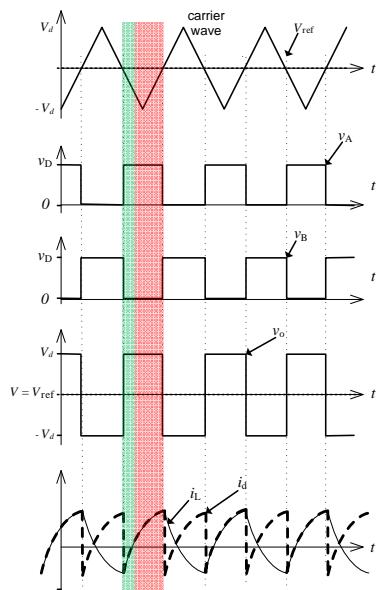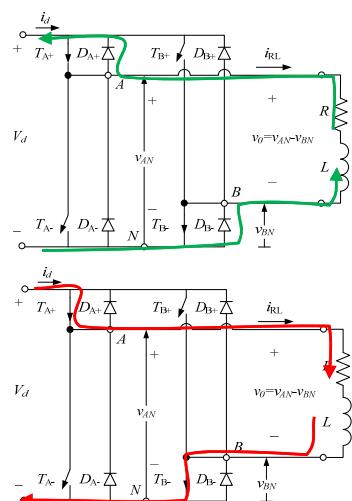

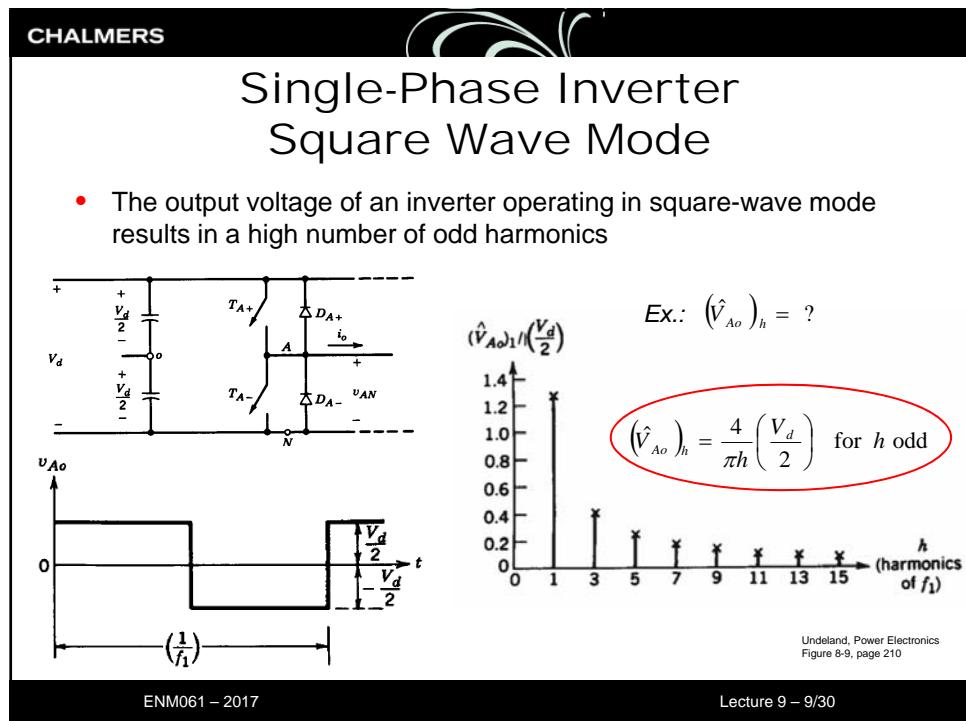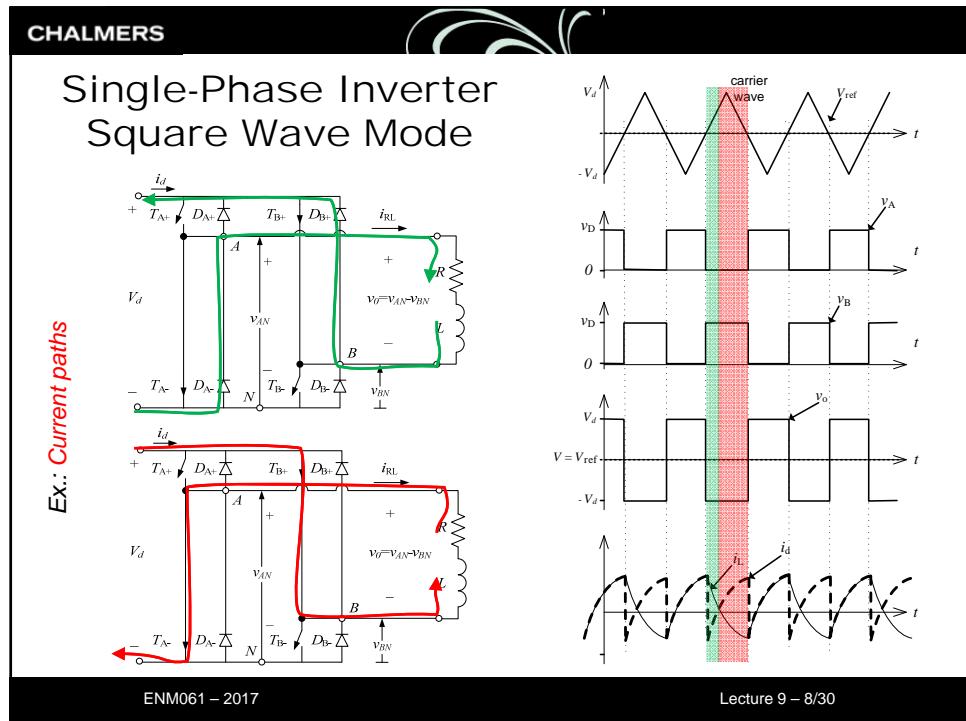

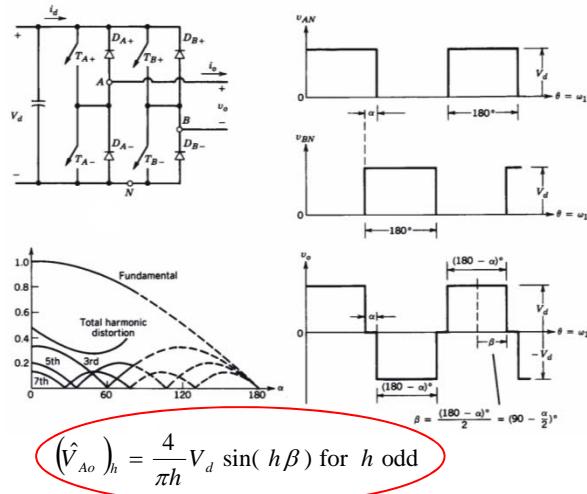Single-Phase Full-bridge Inverter Square-Wave + Unipolar Switching




Undeland, Power Electronics
Figure 8-17, page 219

ENM061 – 2017

Lecture 9 – 10/30

Single-Phase Inverter Bipolar Switching and Voltage Control

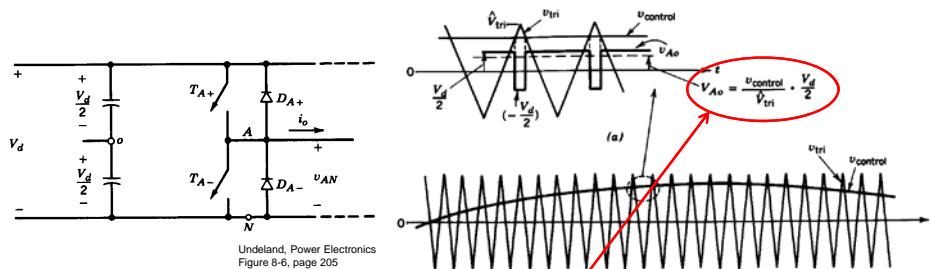- Compare the reference voltage with a triangular voltage with much higher frequency – bipolar switching




Valid in the linear range ($m_a \leq 1$) for the half-bridge phase leg!

ENM061 – 2017

Lecture 9 – 11/30

Single-Phase Inverter Bipolar Switching and Voltage Control


- Compare the reference voltage with a triangular voltage with much higher frequency – bipolar switching as for a H-bridge DC/DC-converter

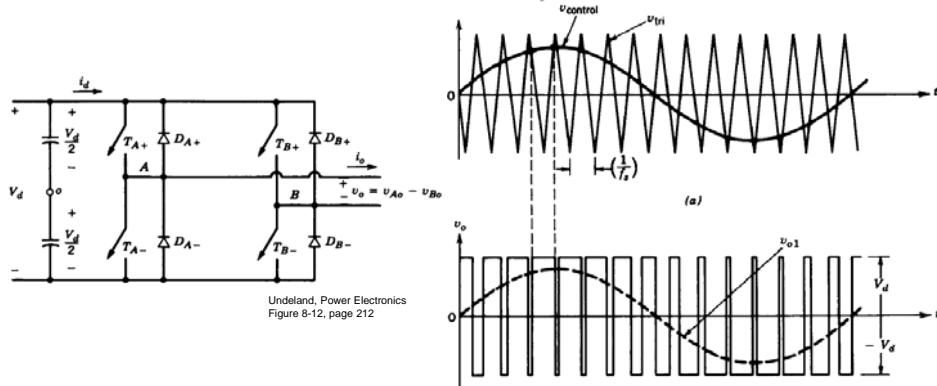

ENM061 – 2017

Lecture 9 – 12/30

Single-Phase Inverter Bipolar Switching and Current Paths

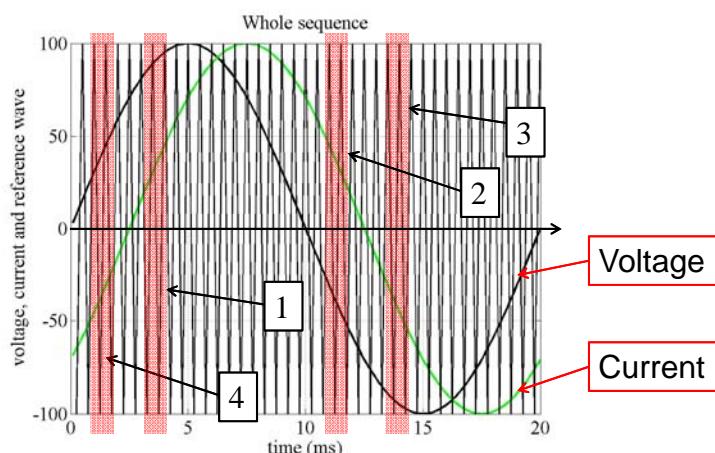


ENM061 – 2017


Lecture 9 – 13/30

Bipolar Switching Current Path 1

Ex.: Current paths

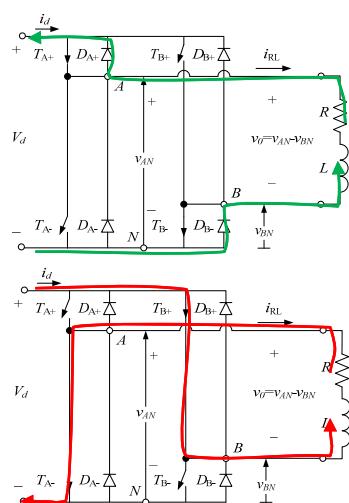


ENM061 – 2017

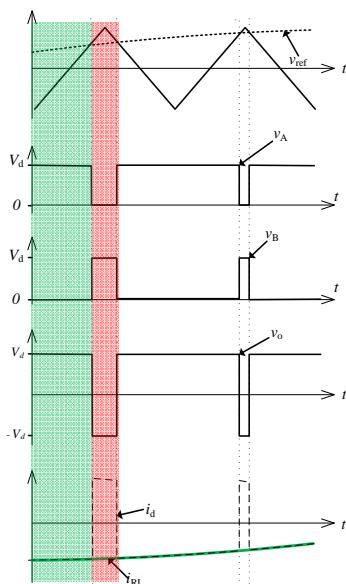


Lecture 9 – 14/30

Bipolar Switching Current Path 2



Ex.: Current paths

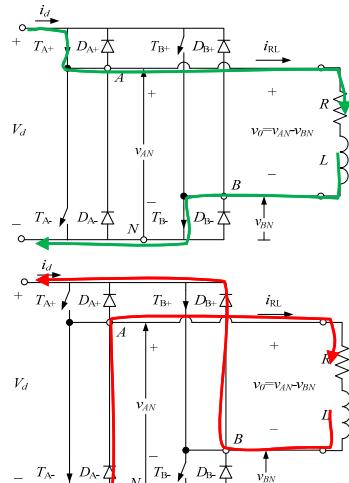

ENM061 – 2017

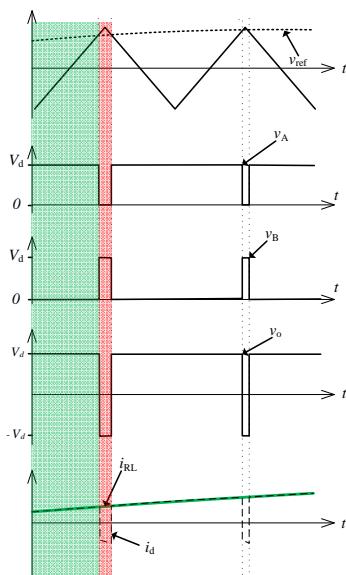


Lecture 9 – 15/30

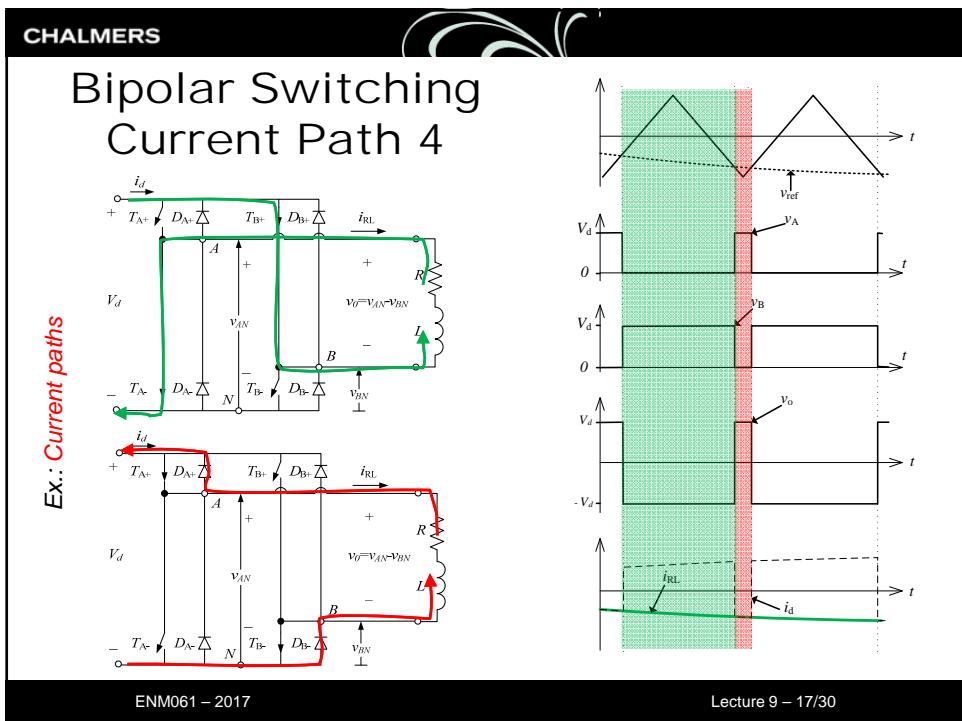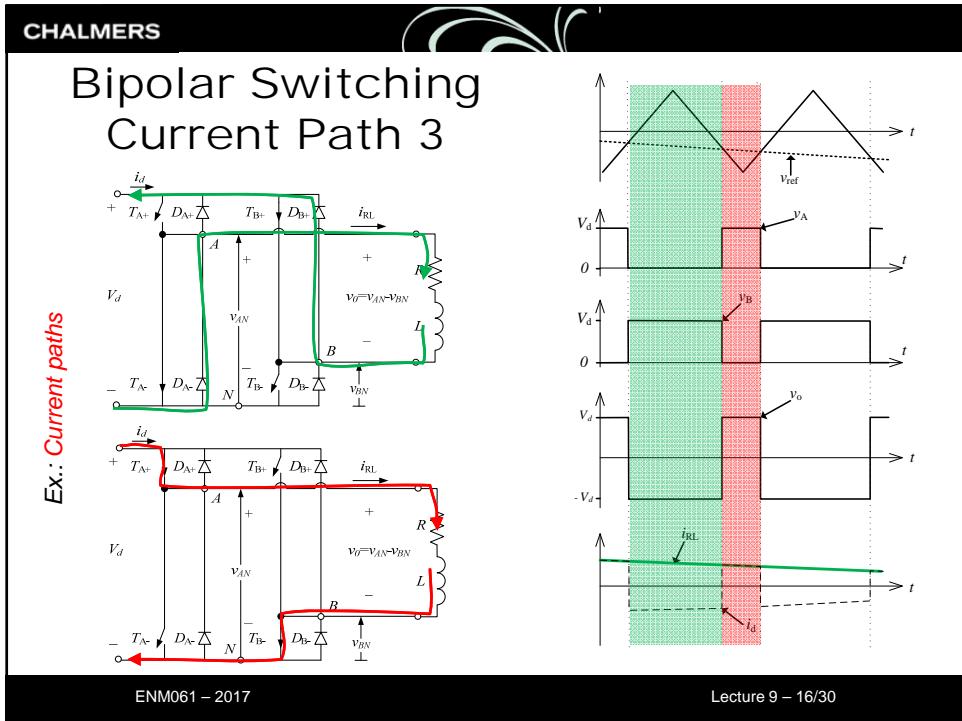

Single-Phase Inverter Harmonics in Bipolar Switching

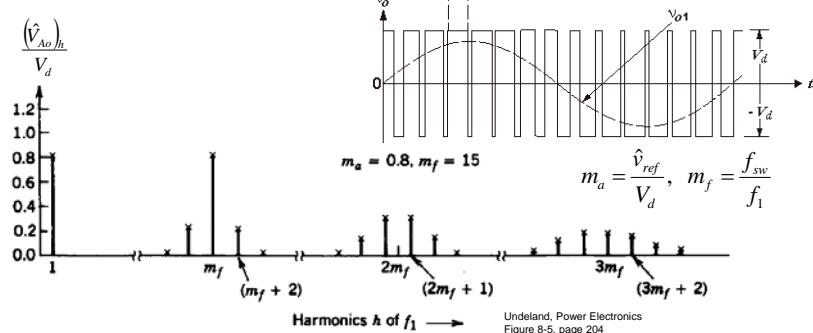- High content of harmonics – shifted high up in frequency



Undeland, Power Electronics

Figure 8-5, page 204

- Synchronous PWM: when the control voltage and the carrier are synched (when $m_f \leq 21$).
- Asynchronous PWM: when m_f is not an integer. Creates unwanted subharmonics of the fundamental frequency component (OK when $m_f \geq 21$)

Single-Phase Inverter Harmonics in Bipolar Switching

Table 8-1 Generalized Harmonics of v_{Ao} for a Large m_f


h	m_a	0.2	0.4	0.6	0.8	1.0
<i>Fundamental</i>	<i>I</i>	0.2	0.4	0.6	0.8	1.0
<i>m_f</i>						
m_f		1.242	1.15	1.006	0.818	0.601
$m_f \pm 2$		0.016	0.061	0.131	0.220	0.318
$m_f \pm 4$						0.018
$2m_f \pm 1$		0.190	0.326	0.370	0.314	0.181
$2m_f \pm 3$			0.024	0.071	0.139	0.212
$2m_f \pm 5$					0.013	0.033
$3m_f$		0.335	0.123	0.083	0.171	0.113
$3m_f \pm 2$		0.044	0.139	0.203	0.176	0.062
$3m_f \pm 4$			0.012	0.047	0.104	0.157
$3m_f \pm 6$					0.016	0.044
$4m_f \pm 1$		0.163	0.157	0.008	0.105	0.068
$4m_f \pm 3$		0.012	0.070	0.132	0.115	0.009
$4m_f \pm 5$				0.034	0.084	0.119
$4m_f \pm 7$					0.017	0.050

Note: $(\hat{v}_{Ao})_h / \frac{1}{2}V_d$ [$= (\hat{v}_{AN})_h / \frac{1}{2}V_d$] is tabulated as a function of m_a .Undeland, Power Electronics
Table 8-1, page 207

- Harmonics appear as side bands at multiples of the switching frequency

Single-Phase Inverter – Modulation Index with Bipolar Switching


- An increased modulation index gives over modulation – the linear relationship between m_a and V_d is no longer valid

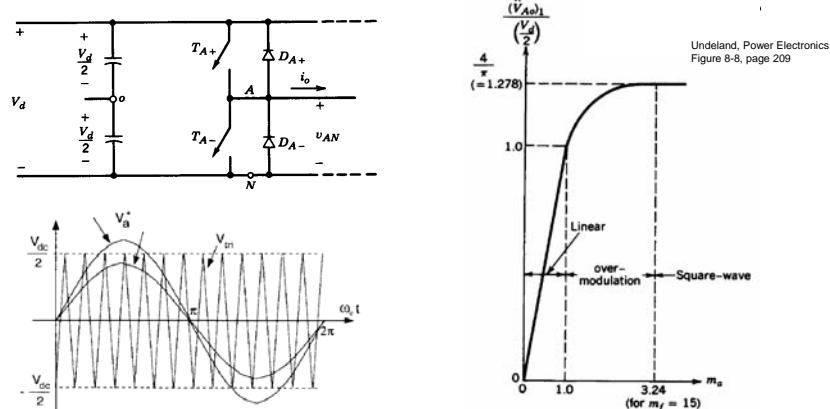

ENM061 – 2017

Lecture 9 – 20/30

Single-Phase Inverter – Harmonics and Over-Modulation

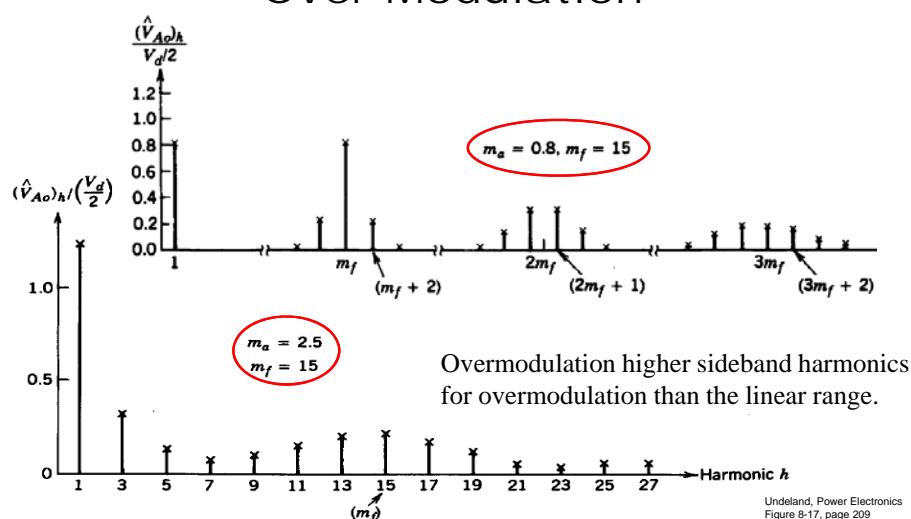


ENM061 – 2017

Lecture 9 – 21/30

Single-Phase Inverter – DC-Side Current Ripple in Bipolar Switching

- The inverter input current (i_d) consists of i_d^* and the high frequency components due to the inverter switchings

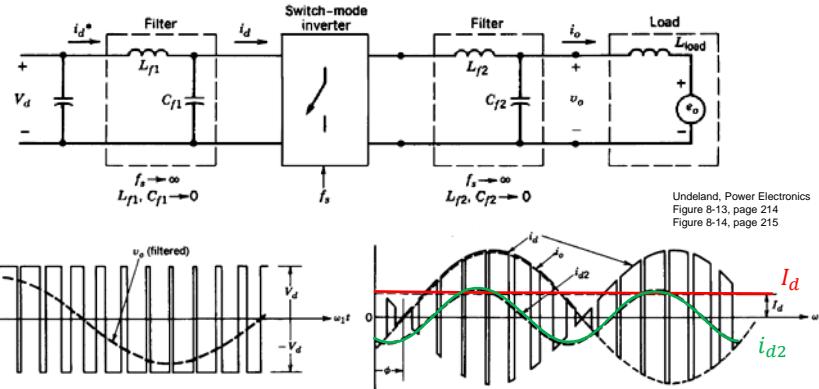


ENM061 – 2017

Lecture 9 – 22/30

Undeland, Power Electronics
Figure 8-13, page 214
Figure 8-14, page 215

Single-Phase Inverter Unipolar Switching

- Legs A and B are controlled by comparing v_{tri} with $v_{control}$ and $-v_{control}$ respectively.

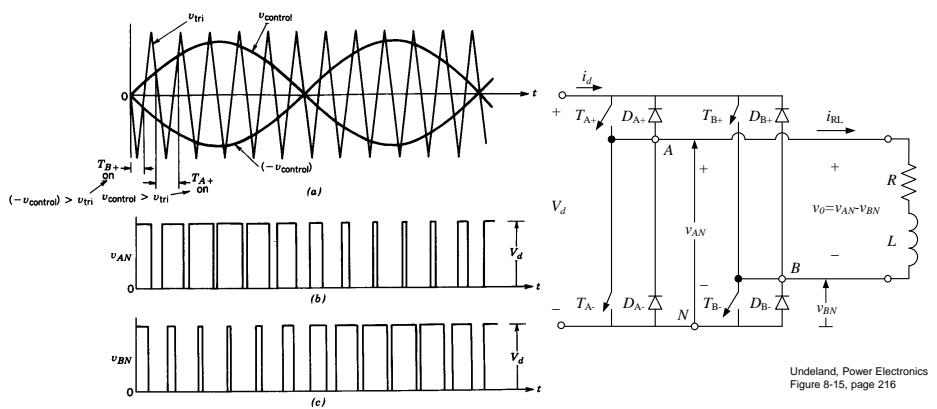


ENM061 – 2017

Lecture 9 – 23/30

Undeland, Power Electronics
Figure 8-15, page 216

Single-Phase Inverter Unipolar Switching

- The load experiences a doubled switching frequency with lower harmonic content

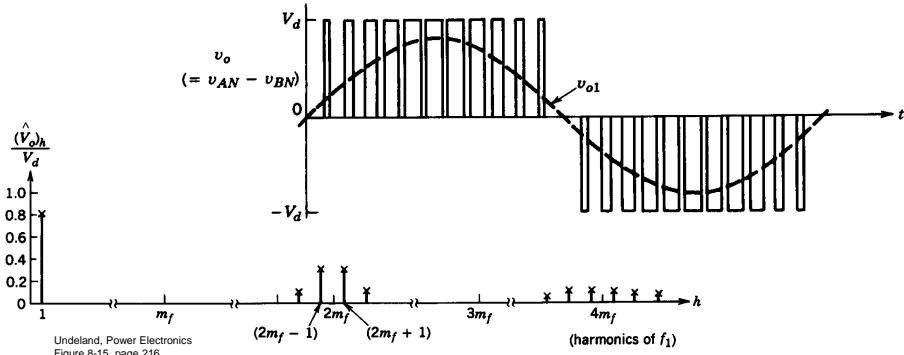


ENM061 – 2017

Lecture 9 – 24/30

Single-Phase Inverter DC-Side Current in Unipolar Switching

- PWM with unipolar switching results in lower ripple on the DC-side current compared with bipolar switching

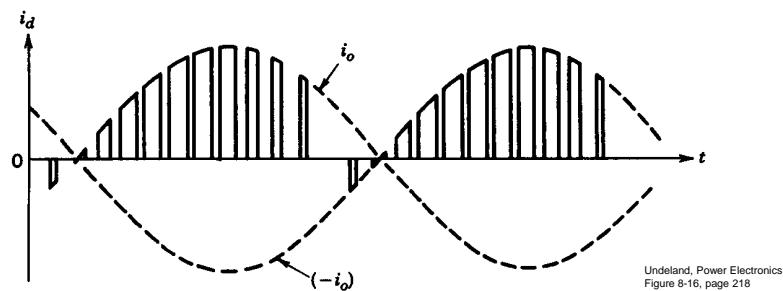


ENM061 – 2017

Lecture 9 – 25/30

Single-Phase Inverter Output Ripple Current

- The inverter supplies an induction motor represented by a back-emf
- Only the fundamental frequency sinusoidal component transfer real power
- Fundamental and higher frequency ripple components can be separated – the current ripple is formed by the voltage over the inductor

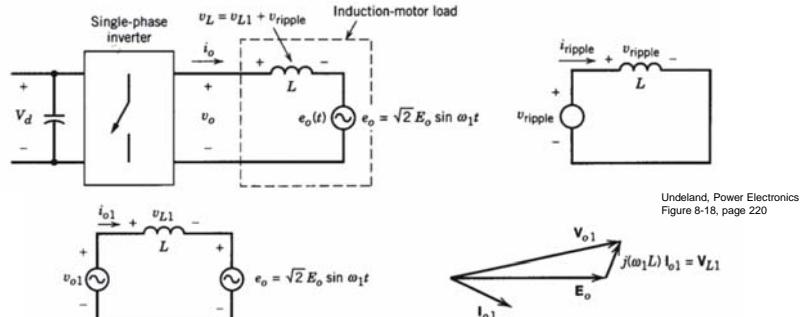


ENM061 – 2017


Lecture 9 – 26/30

Single Phase Inverter Output Ripple Current

Square-wave Switching

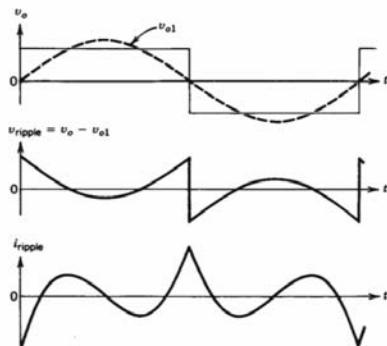

Bipolar Switching

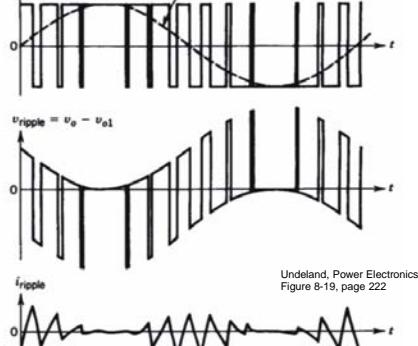


- PWM switching gives lower current ripple for the same load

ENM061 – 2017


Lecture 9 – 27/30

Tutorial 7

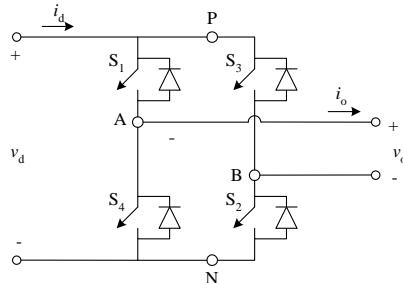

- PWM: $295 \leq V_{dc} \leq 325$, $m_a \leq 1.0$ for low distortion, $\max(V_{o(1)})$ on nameplate?
- Square: $V_{dc} = 300$; purely inductive load with back-emf e_o ; $v_{o(1)} = e_o$;
Calculate $V_{o(1)}$, sketch the current ripple and find its peak value
- Square: purely inductive load, plot output voltage and current waveforms

PSpice 4

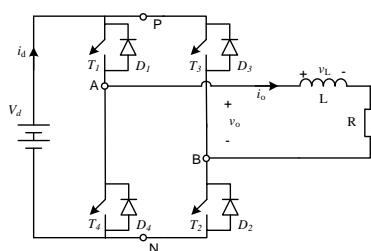

Square-wave vs PWM (bi- and uni-polar switching) for the same v_o

- Load voltage and current waveforms
- Calculate and compare the load voltage and current harmonic components
- Impact of unipolar switching over bipolar switching



Summary

- Power flow direction and definition of an inverter/rectifier stage
- Pros and cons of square wave vs. PWM operating mode
- Pros and cons of bipolar vs. unipolar PWM operating mode
- Estimation of harmonics in the output current and voltage of inverters
- Learning outcome:
 - ❖ Operating principles of a single-phase DC/AC inverter with different modulation strategies (e.g. PWM and square wave operation).