



# ENM061 - Power Electronic Converters

## 7.5 ECTS, 2017

Mebtu Beza

[mebtu.beza@chalmers.se](mailto:mebtu.beza@chalmers.se)

Chalmers University of Technology  
Department of Electrical Engineering  
Division of Electric Power Engineering



## Lecture outline

### **The single-phase diode rectifier**


- Prerequisites for today's lecture
- The concept of rectification
- The effect of inductance on diode currents
- Single-phase diode rectifier with resistive and inductive load
- Single-phase diode rectifier with source inductance
- Single-phase diode rectifier with voltage and current stiff loads
- Practical single-phase diode rectifiers
- Impact of non-linear rectifier loads and the power factor corrector (PFC)
- Summary

## Learning outcomes

- Fourier components and total harmonic distortion (THD) for basic waveforms.
- Operating principles of the most common active components (e.g. diode, thyristor, IGBT, and MOSFET) and passive components (e.g. capacitors, transformers and inductors).
- Operation of a pulse width modulation (PWM), the purpose of controlling the desired quantity and the need for a controller circuit within the power electronic converter.
- Analysis of ideal DC/DC converters (e.g. buck, boost, buck-boost, flyback, the forward, the push-pull, half-bridge and full-bridge converters) in CCM and DCM operation.
- Operating principles of single-phase and three-phase AC/DC inverters with different modulation strategies (e.g. PWM and square wave operation).
- Operation of multilevel converters (e.g. NPC, flying capacitor and MMC topologies) using current and voltage waveform analysis. Pros and Cons of the converter in terms of harmonics and losses.
- Operation of single- and three-phase diode rectifiers operating with voltage-stiff and current-stiff DC-side. Investigating the impact of line impedance within the converter circuit for current commutation.**
- Operation of single- and three-phase thyristor rectifiers operating with a current-stiff DC-side and the impact of line impedance for current commutation. Investigating the use of 6/12-pulse configurations.
- Identify simple power electronic converter schematics. Recognizing the different parts in a physical circuit on which basic wave-shape and efficiency measurements is performed.
- Loss calculation in passive and active components. Evaluating the temperature rise in the active components and choosing an appropriate heat-sink. Gaining a basic understanding of component life time.
- Utilizing the software Cadence PSpice to simulate basic power electronic circuits and the practical labs to have a firsthand experience of how real DC/DC converters operate.
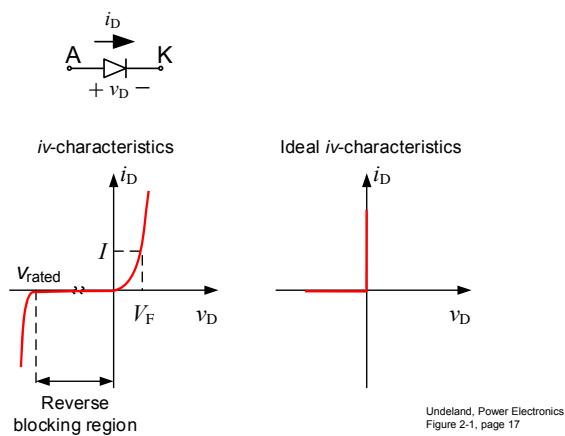
## The Diode

- On and off states controlled by the power circuit







## Inductors and Capacitors

$$v_L = L \frac{di_L}{dt}$$

$$i_C = C \frac{dv_C}{dt}$$

$$i_L = i_L(t_1) + \frac{1}{L} \int v_L dt$$
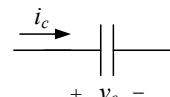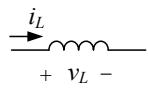
$$v_C = v_C(t_1) + \frac{1}{C} \int i_C dt$$



Average and RMS current and voltage?

Current stiff component


Average and RMS current and voltage?

Voltage stiff component


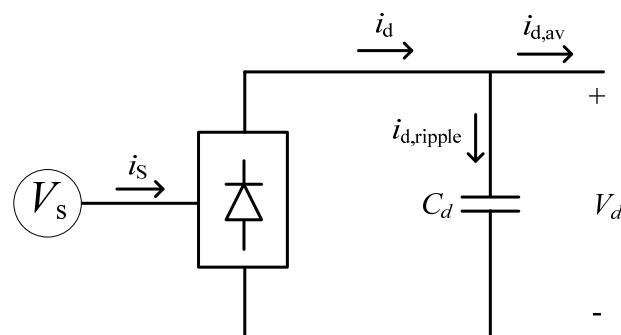
## The Concept of Rectification Diode Rectifier Block Diagram


- Generates uncontrolled DC voltage for low or high power application




Undeland, Power Electronics  
Figure 5-1, page 79
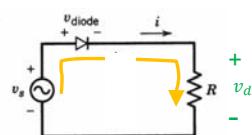
## The Effect of Inductance on Diode Currents – Resistive Load

- A diode in series prevents the current flow in one direction when the source voltage becomes negative



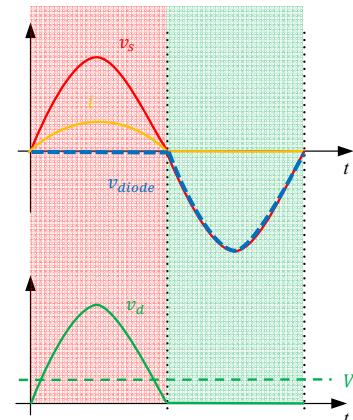Undeland, Power Electronics  
Figure 5-2, page 80




Ex: plot  $i$ ,  $v_d$  and  $v_{diode}$

ENM061 – 2017

Lecture 12– 6/29
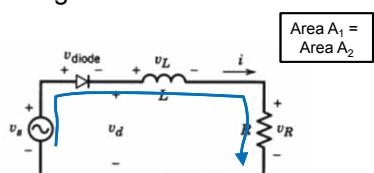
## The Effect of Inductance on Diode Currents – Inductive Load

- An inductor in series keeps the current flowing in the same direction for some time – even when the source voltage becomes negative




Undeland, Power Electronics  
Figure 5-3, page 81

Ex: plot  $i$ ,  $v_L$ ,  $v_d$ ,  $v_R$  and  $v_{diode}$



ENM061 – 2017

Lecture 12– 7/29

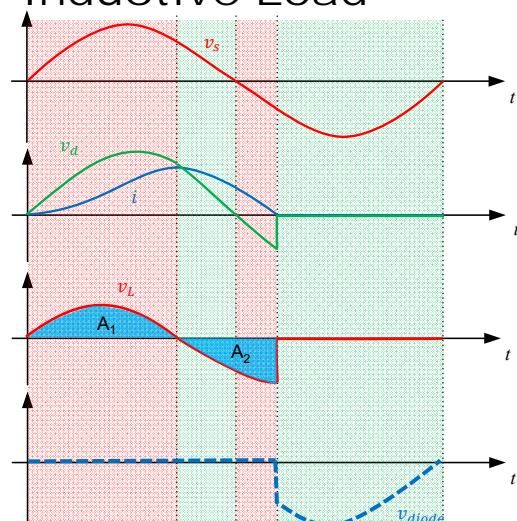

## The Effect of Inductance on Diode Currents – Inductive Load and EMF

- An inductor in series keeps the current flowing in the same direction – even when the source voltage becomes negative

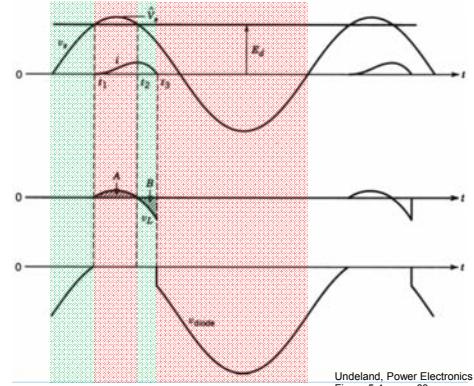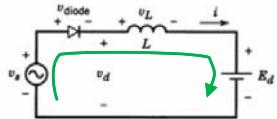


ENM061 – 2017


Lecture 12– 8/29

## Single-phase Diode Rectifier


- Resistive Load

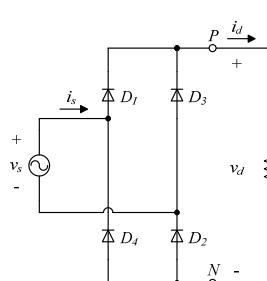

- Current stiff load series inductance

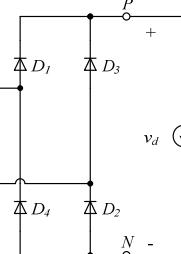

- Voltage stiff load shunt capacitor

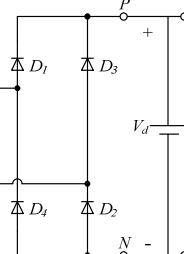


ENM061 – 2017

Lecture 12– 9/29

## Diode Rectifier with Resistive Load

- The voltage over the resistor is a full-wave rectified sinusoidal wave

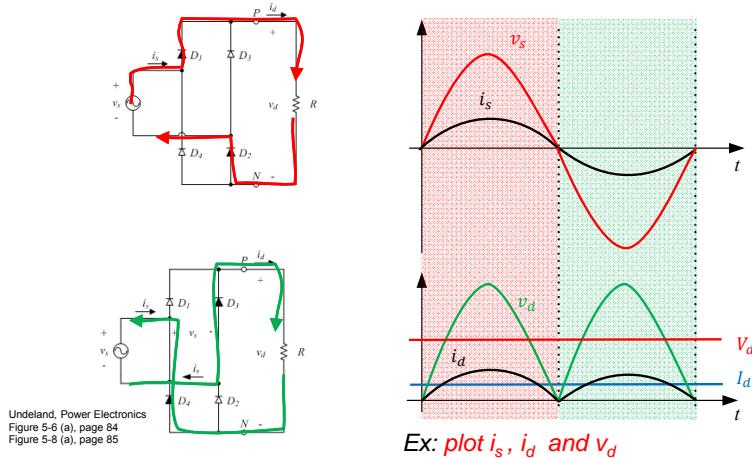


ENM061 – 2017

Lecture 12– 10/29

## Diode Rectifier with Inductive Load

- The output current is a constant DC-current (assume large  $L$ )
- With no source inductance, the source current is square-wave shaped

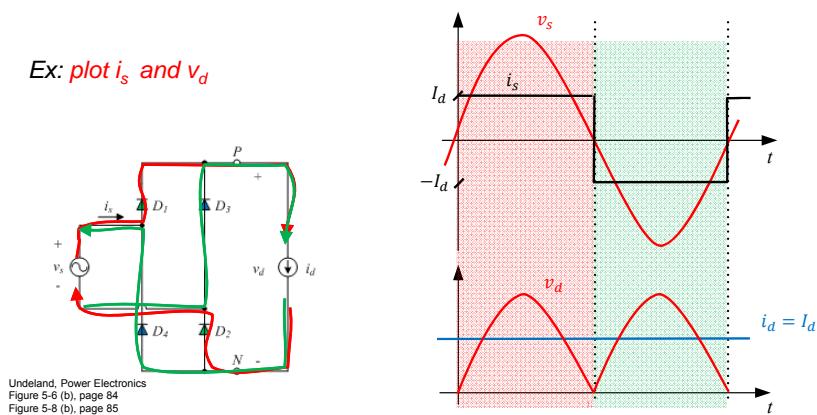


ENM061 – 2017

Lecture 12– 11/29

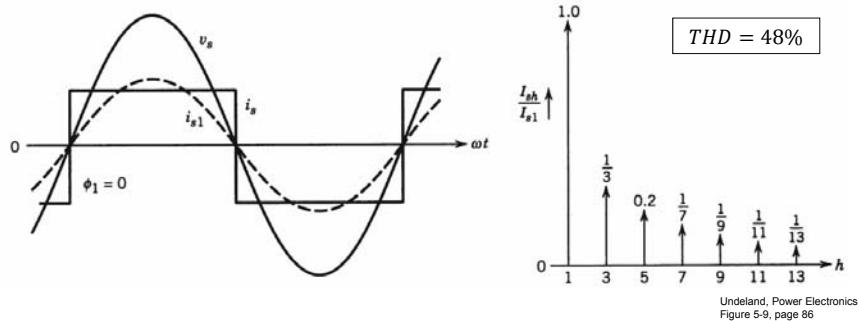
## Diode Rectifier with Inductive Load Input Current

- The source current has a high harmonic content




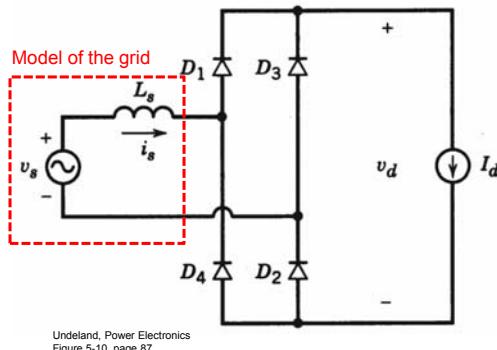
## Diode Rectifier with Inductive Load and AC-side inductance

- The source inductance in the grid will influence the operation of the rectifier – the commutation will not be instantaneous


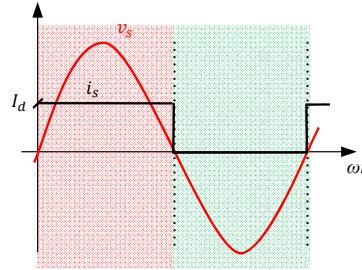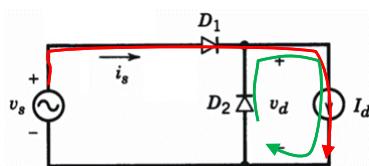
## Diode Rectifier with Inductive Load Current Commutation

- Half-rectification with one current path without source inductance ( $L_s=0$ )



Ex: show current paths for one cycle


Undeland, Power Electronics  
Figure 5-11, page 87

Ex: what happens during current commutation between  $D_1$  to  $D_2$


ENM061 – 2017

Lecture 12– 14/29

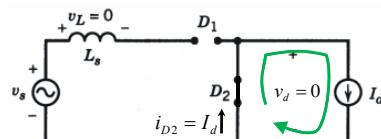
## Diode Rectifier with Inductive Load Current Commutation



Before,  $\omega t < 0$

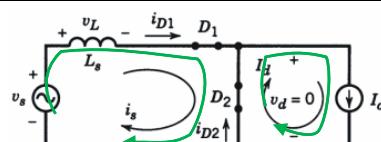

During,  $0 \leq \omega t \leq u$

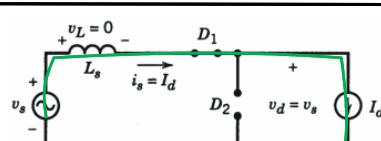

After,  $\omega t > u$

Undeland, Power Electronics  
Figure 5-12, page 88

ENM061 – 2017

Lecture 12– 15/29


## Diode Rectifier with Inductive Load Current Commutation

- Half-rectification with one current path and with source inductance ( $L_s \neq 0$ )


Ex: plot  $i_s$ ,  $v_L$  and  $v_d$

Ex: calculate the voltage reduction
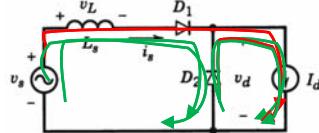
$$\Delta V_d = \frac{A_u}{2\pi} = \frac{\omega L_s I_d}{2\pi}$$



Undeland, Power Electronics  
Figure 5-13, page 88

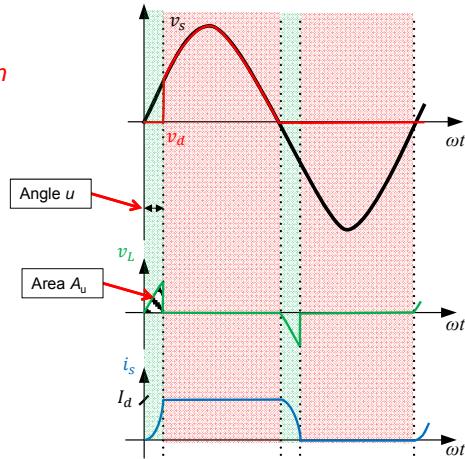

ENM061 – 2017

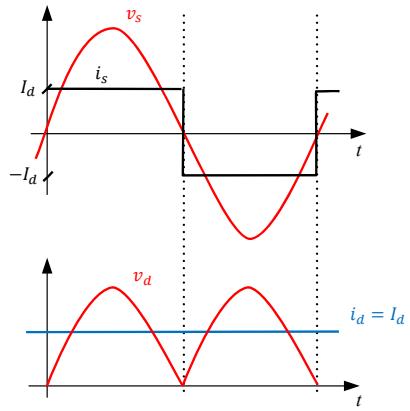
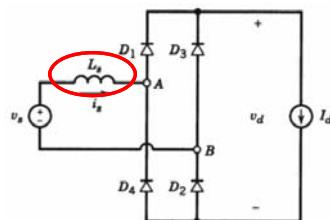
Lecture 12– 16/29

ENM061 – 2017

Lecture 12– 17/29

## Diode Rectifier with Inductive Load

- Full-rectification without source inductance ( $L_s=0$ )

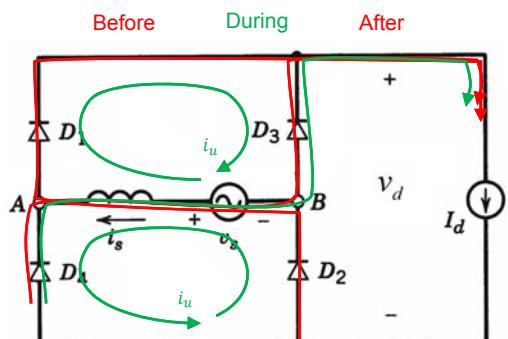
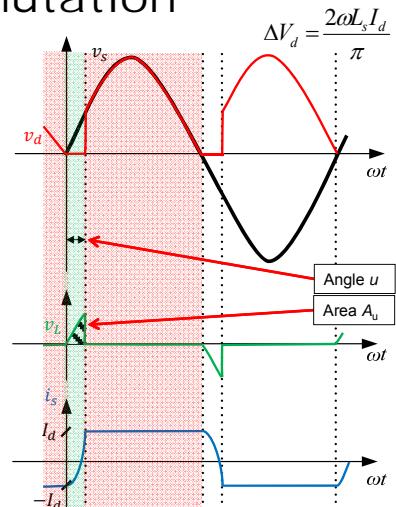


ENM061 – 2017

Lecture 12– 18/29

## Diode Rectifier with Inductive Load Current Commutation

- Full rectifier (slightly redrawn) with source inductance ( $L_s \neq 0$ )



Ex: plot  $i_s$ ,  $v_L$  and  $v_d$ Undeland, Power Electronics  
Figure 5-15, page 91

ENM061 – 2017

Lecture 12– 19/29

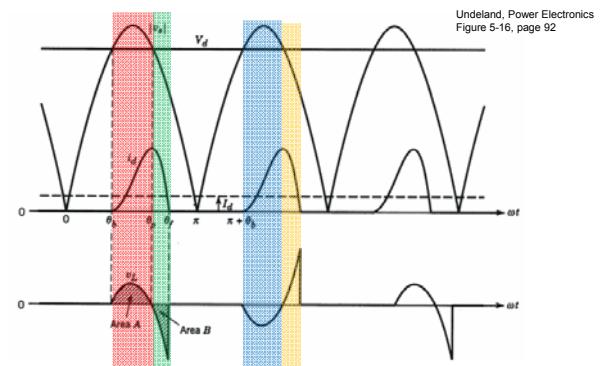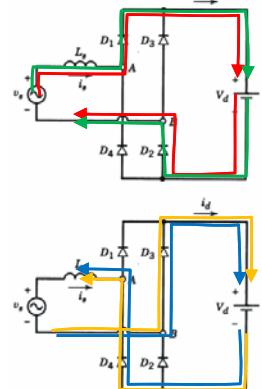
## Diode Rectifier With DC-Side Voltage

- Full rectifier with source inductance ( $L_s \neq 0$ )



- No current commutation since the current is zero when the polarity changes!


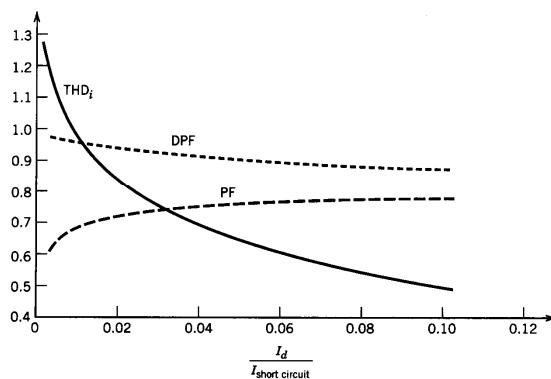
## Diode Rectifier With DC-Side Voltage THD, PF and DPF



$$I_{\text{short circuit}} = \frac{V_s}{\omega L_s}$$

- Very high THD at low currents
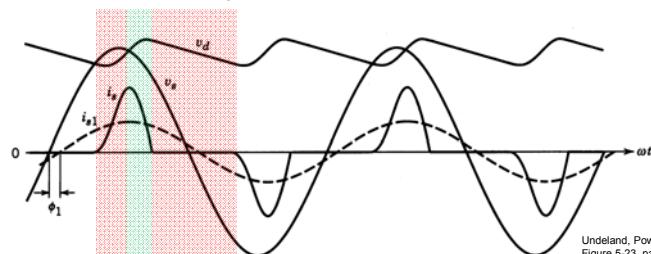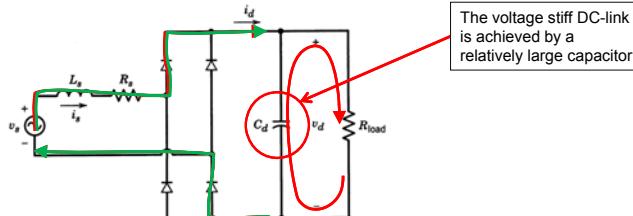
## Diode Rectifier – Practical Implementation and Power Factor




Undeland, Power Electronics  
Figure 5-23, page 98

ENM061 – 2017

Lecture 12– 22/29

## Impact of Diode Rectifier loads Distorted voltage for other loads

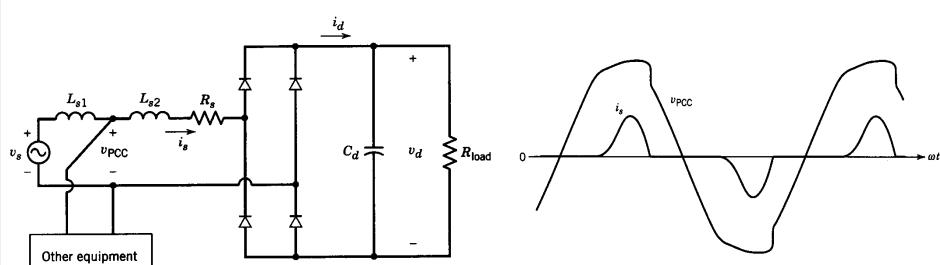


ENM061 – 2017

Lecture 12– 23/29

# Impact of Diode Rectifier loads
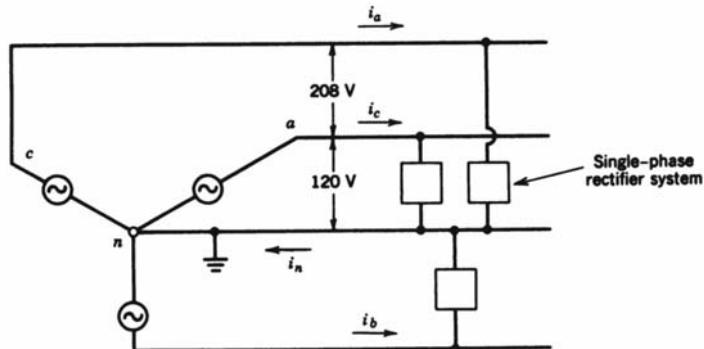
## High current in the neutral conductor

- A typical application of a 3-phase utility source with several 1-phase loads connected on each phase




Undeland, Power Electronics  
Figure 5-28, page101

ENM061 – 2017

Lecture 12– 24/29

# Diode Rectifier – Practical Implementation and Power Factor

- For non-sinusoidal quantities, DPF and PF will differ depending on the harmonic content.
- DPF only takes the angle between the fundamental components into consideration
- PF accounts for the angle between the fundamental components as well as the ratio between the fundamental current component and the total RMS-current (including harmonics)

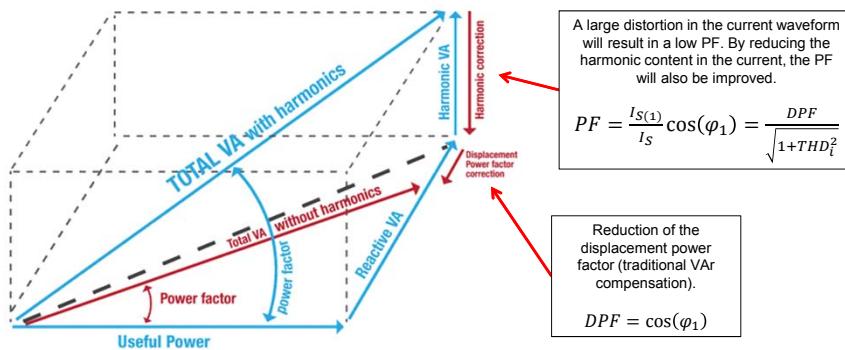


ENM061 – 2017

Lecture 12– 25/29

## Power Factor Correction (PFC) Unit


- Active (switched) unit that makes the input current more sinusoidal

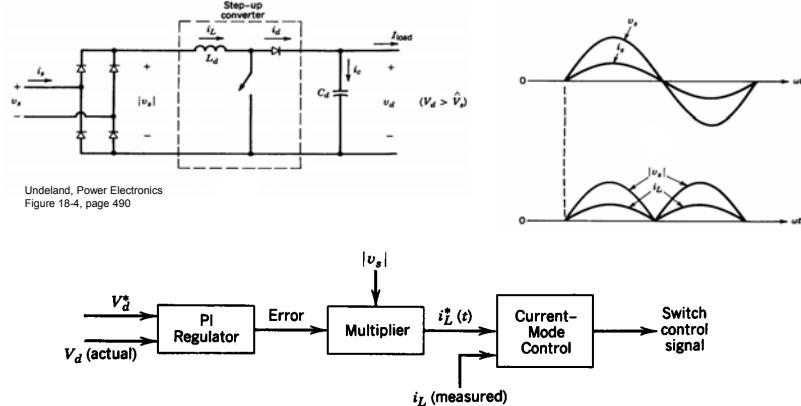

ENM061 – 2017


Lecture 12 – 26/29

## Tutorial 10

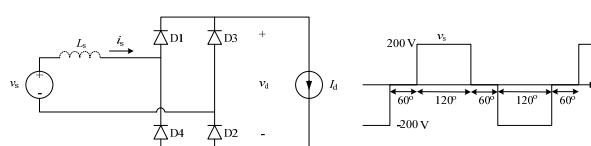

- With  $L_s = 0$  and  $I_d = 10 A$ , calculate the average power supplied to the load if the input voltage is sinusoidal with RMS value of 120 V, frequency 60 Hz.
- With  $L_s = 0$  and  $I_d = 10 A$ , calculate the average power supplied to the load if the input voltage is the pulsed waveform above with frequency of 60 Hz.


- For  $L_s = 10 \text{ mH}$  and  $v_d = 160 \text{ V}$ , plot  $i_d$  and  $i_s$  waveforms

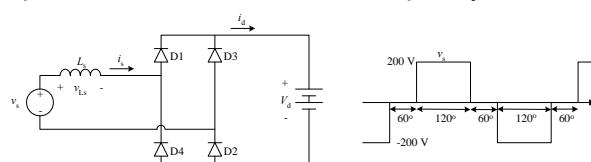

ENM061 – 2017

Lecture 12 – 27/29

## PSpice 6

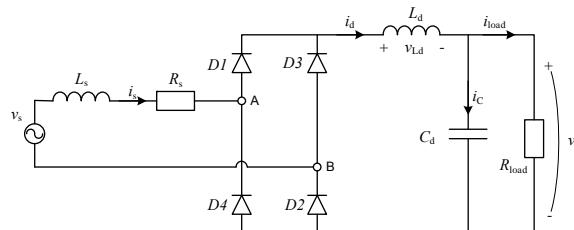

$L_d$  and  $C_d$  decides if the load is of voltage or current stiff type

- Plot current and voltage waveforms
- Input PF, DPF, THD and output voltage ripple
- Impact of source inductance on commutation angle and output voltage for the two types of loads

## Summary

- Single-phase diode rectifier with resistive and inductive loads
- Single-phase diode rectifier with a voltage and current stiff loads
- Half- vs full-wave rectification
- Current commutation
- Impact of non-linear rectifier loads on THD, DPF and PF
- The concept of active PFCs
- Learning outcome:
  - ❖ Operation of single-phase diode rectifiers operating with voltage-stiff and current-stiff DC-side. Investigating the impact of line impedance within the converter circuit for current commutation.