



ENM061 - Power Electronic Converters

7.5 ECTS, 2017

Mebtu Beza

mebtu.beza@chalmers.se

Chalmers University of Technology
Department of Electrical Engineering
Division of Electric Power Engineering



Lecture outline

The single-phase thyristor rectifier


- The operation principle of thyristors
- Single-phase thyristor rectifiers without source inductance
- Single-phase thyristor rectifiers with source inductance and current commutation
- Single-phase thyristor rectifier – the delay angle and inverter mode
- Summary

Learning outcomes


- Fourier components and total harmonic distortion (THD) for basic waveforms.
- Operating principles of the most common active components (e.g. diode, thyristor, IGBT, and MOSFET) and passive components (e.g. capacitors, transformers and inductors).
- Operation of a pulse width modulation (PWM), the purpose of controlling the desired quantity and the need for a controller circuit within the power electronic converter.
- Analysis of ideal DC/DC converters (e.g. buck, boost, buck-boost, flyback, the forward, the push-pull, half-bridge and full-bridge converters) in CCM and DCM operation.
- Operating principles of single-phase and three-phase AC/DC inverters with different modulation strategies (e.g. PWM and square wave operation).
- Operation of multilevel converters (e.g. NPC, flying capacitor and MMC topologies) using current and voltage waveform analysis. Pros and Cons of the converter in terms of harmonics and losses.
- Operation of single- and three-phase diode rectifiers operating with voltage-stiff and current-stiff DC-side. Investigating the impact of line impedance within the converter circuit for current commutation.
- Operation of single- and three-phase thyristor rectifiers operating with a current-stiff DC-side and the impact of line impedance for current commutation. Investigating the use of 6/12-pulse configurations.**
- Identify simple power electronic converter schematics. Recognizing the different parts in a physical circuit on which basic wave-shape and efficiency measurements is performed.
- Loss calculation in passive and active components. Evaluating the temperature rise in the active components and choosing an appropriate heat-sink. Gaining a basic understanding of component life time.
- Utilizing the software Cadence PSpice to simulate basic power electronic circuits and the practical labs to have a firsthand experience of how real DC/DC converters operate.

Simple Thyristor Circuits

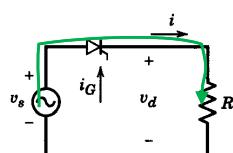- The thyristor can be described as a diode that you can turn on
- The current keeps on flowing until it reaches zero where the thyristor turns off




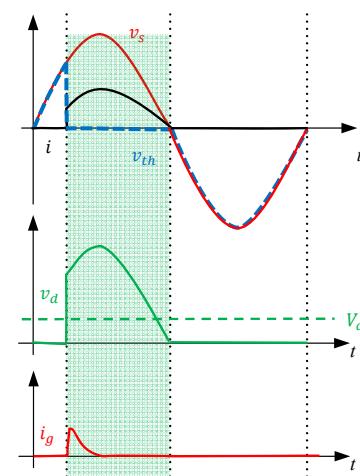Undeland, Power Electronics
Figure 6-2, page 123




Simple Thyristor Circuits

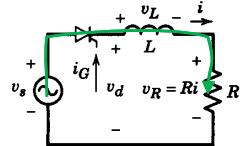- If the source inductance is included, the current keeps on flowing even after the source voltage becomes negative



Undeland, Power Electronics
Figure 6-2, page 123

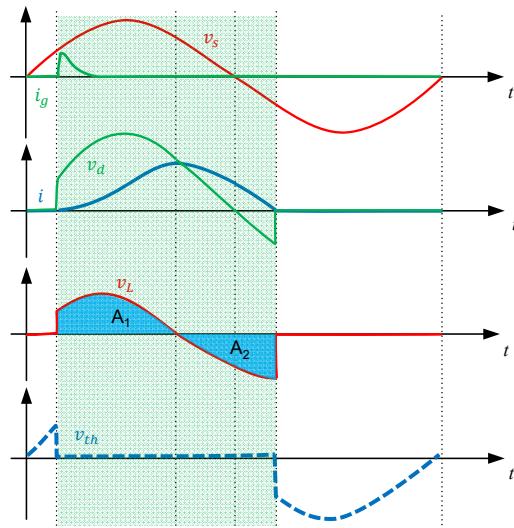


ENM061 – 2017


Lecture 14 – 4/18

Simple Thyristor Circuits

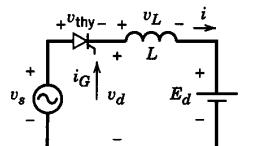- If a DC-source is added in series, the current will start to flow once the source voltage exceeds the DC-level and the thyristor is turned on.



Undeland, Power Electronics
Figure 6-2, page 123

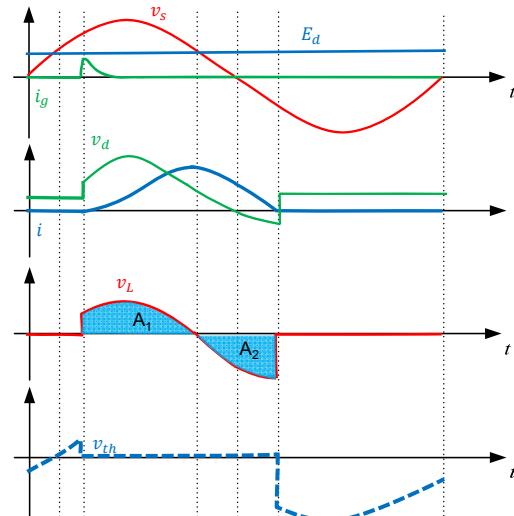


ENM061 – 2017

Lecture 14 – 5/18

Thyristor Rectifiers Basic Configurations

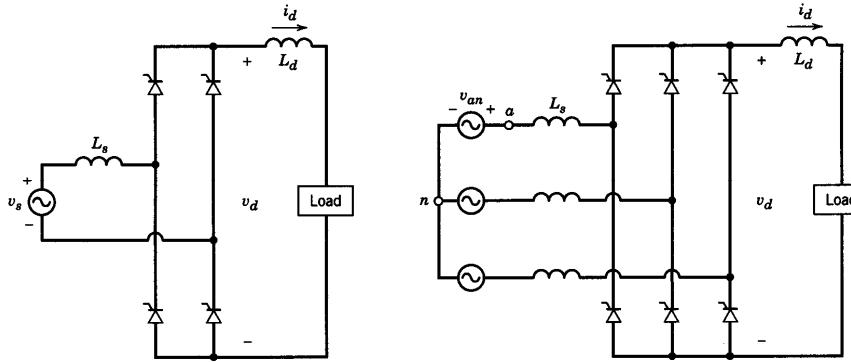- Practical area application of the thyristor – a rectifier in which you can control the output voltage level




Undeland, Power Electronics
Figure 6-4, page 126

ENM061 – 2017

Lecture 14 – 6/18

Thyristor Rectifiers Operating Conditions

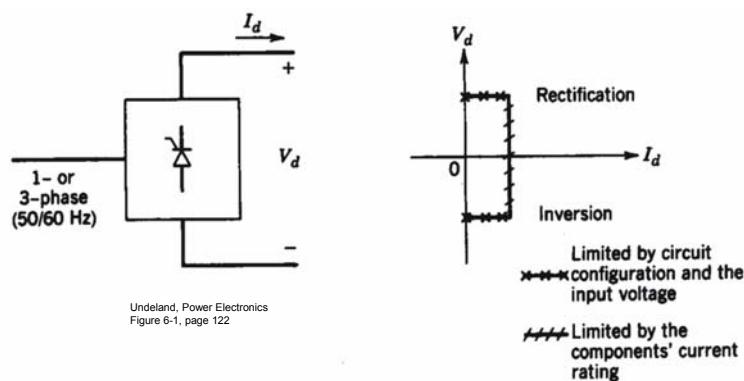- The thyristor rectifier can invert the output voltage





Undeland, Power Electronics
Figure 6-1, page 122

ENM061 – 2017

Lecture 14 – 7/18



Single-Phase Thyristor with Constant DC-Side Current ($\alpha=0^\circ$)

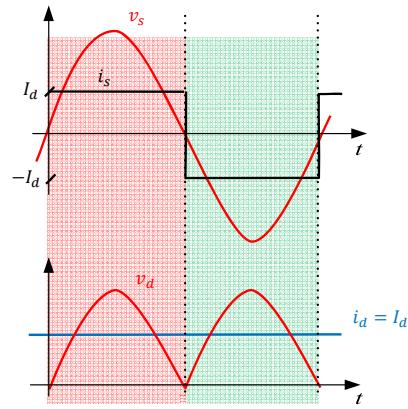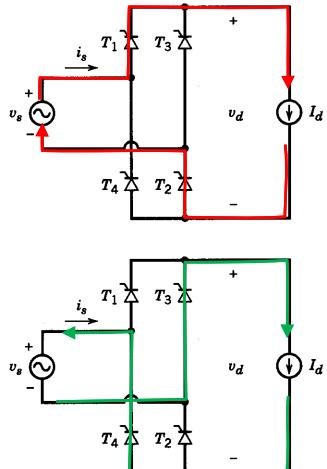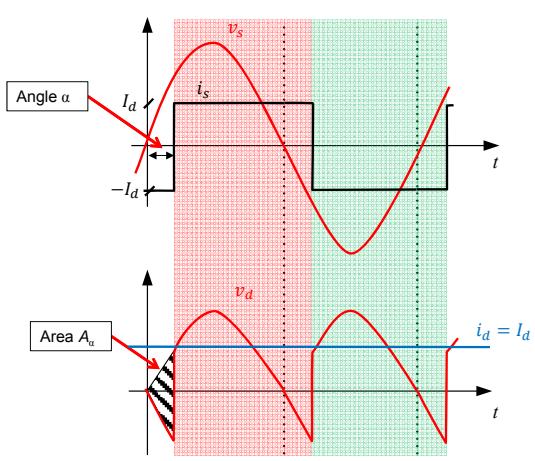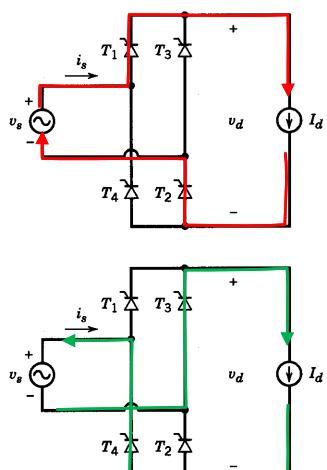

ENM061 – 2017

Lecture 14 – 8/18

Single-Phase Thyristor with Constant DC-Side Current ($\alpha=30^\circ$)


Undeland, Power Electronics
Figure 6-6, page 127

ENM061 – 2017

Lecture 14 – 9/18

Single-Phase Thyristor Rectifier Input Line Current Harmonics

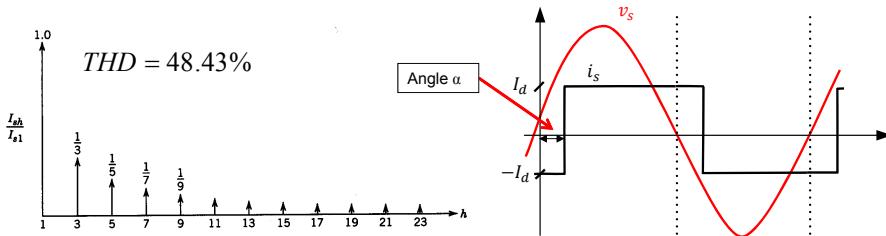- The source current (i_s) is square-wave shaped and consists of odd harmonics





Undeland, Power Electronics
Figure 6-8, page 129

ENM061 – 2017

Lecture 14 – 10/18

Single-Phase Thyristor Rectifier Input Line Current Harmonics




- As the delay angle increases, the phase shift of the fundamental frequency component in the source current ($i_{s(1)}$) also increases. This reduces the active power transfer.

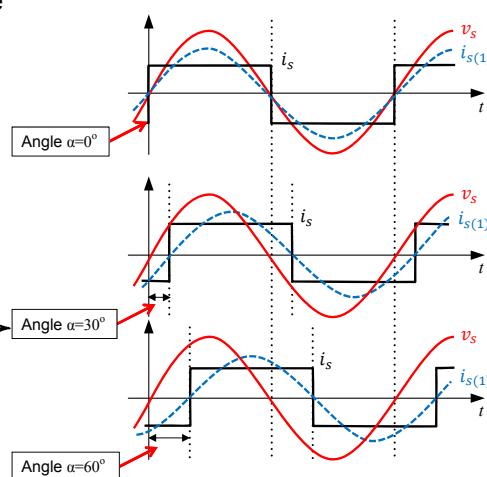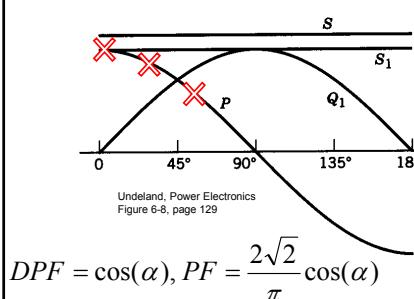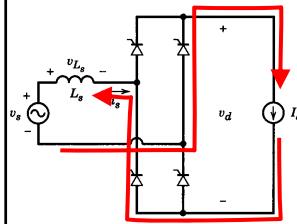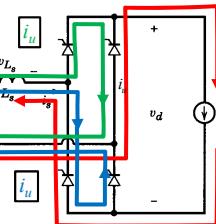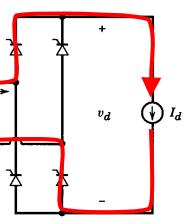

ENM061 – 2017

Lecture 14 – 11/18

Single-Phase Thyristor Rectifier AC-Side Inductance

Before: $(\omega t < \alpha)$ During: $(\alpha \leq \omega t \leq \alpha + u)$ After: $(\omega t > \alpha + u)$ 


Undeland, Power Electronics
Figure 6-9, page 130

ENM061 – 2017

Lecture 14 – 12/18

Single-Phase Thyristor Rectifier AC-Side Inductance

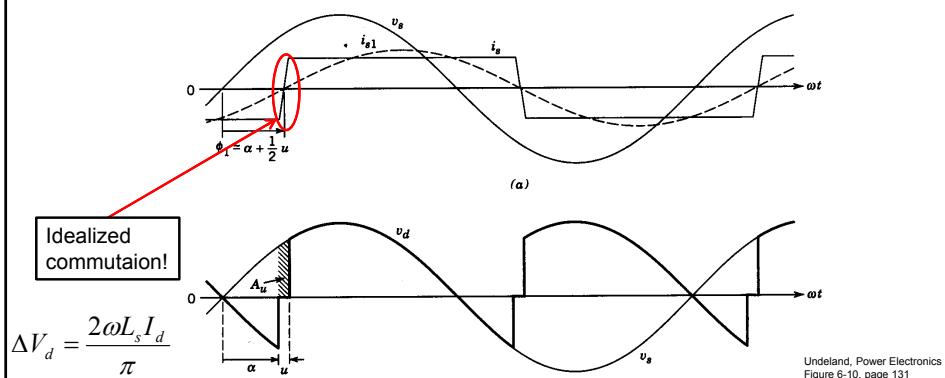- The commutation of the input current takes a certain time known as the commutation angle (u)
- The output voltage reduced due to the commutation




Undeland, Power Electronics
Figure 6-10, page 131

ENM061 – 2017

Lecture 14 – 13/18

Delay Angle in the Thyristor Rectifier



- The variation of V_d as a function of α shows that the average output voltage becomes negative when $\alpha > 90^\circ$

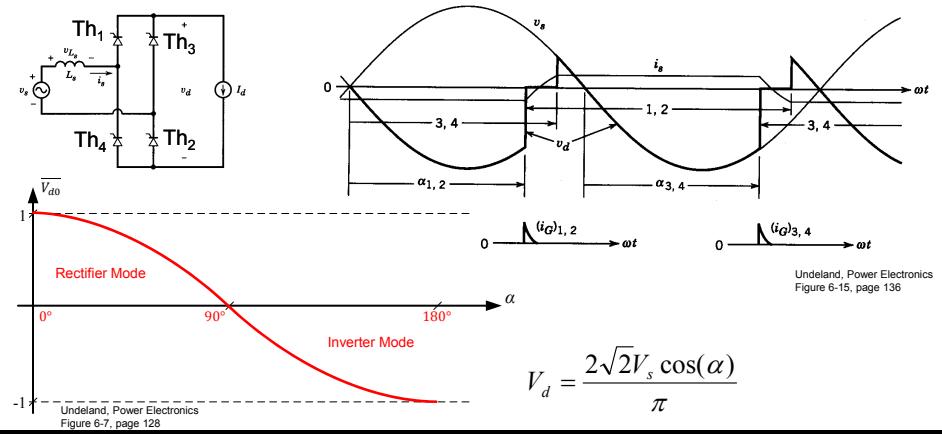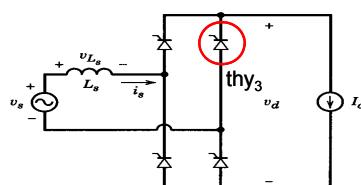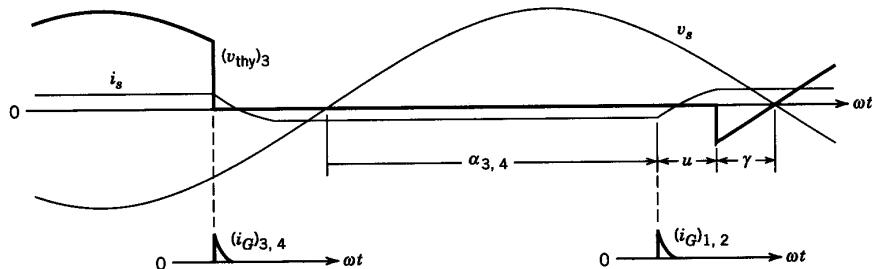

ENM061 – 2017

Lecture 14 – 14/18



Thyristor inverter mode Importance of extinction angle γ

Undeland, Power Electronics
Figure 6-17, page 137

ENM061 – 2017

Lecture 14 – 15/18


Practical thyristor converter

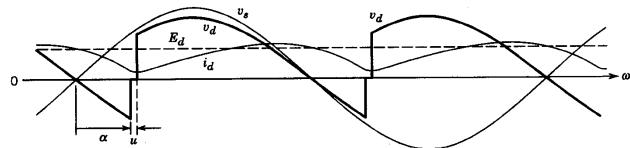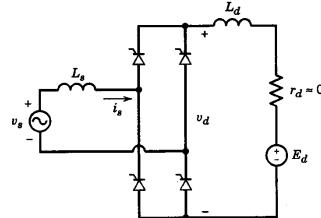

Undeland, Power Electronics
Figure 6-11, page 133

- Discontinuous mode: it can occur in a dc-drive at light loads

Tutorial 11

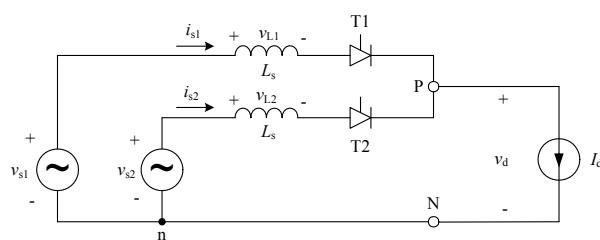

For two delay angles of 45° and 135° and with $L_s = 5 \text{ mH}$, v_{s1} and v_{s2} have 120 V RMS and phase shifted by 180° at 60 Hz, and $I_d = 10 \text{ A}$,

- Plot the waveforms of v_{s1} , i_{s1} and v_d
- Calculate the average output voltage V_d and the commutation interval u



Summary

- The operation principle of thyristors
- Single-phase thyristor rectifiers without source inductance
- Single-phase thyristor rectifiers with source inductance and current commutation
- Thyristor converters in inverter mode of operation
- Learning outcome:
 - ❖ Operation of a single-phase thyristor rectifier operating with a current-stiff DC-side and the impact of line impedance for current commutation.