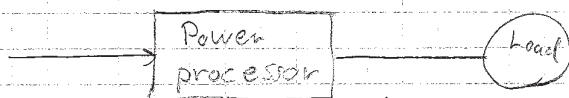


1-1

$$\eta = 0,95$$



$$V_i = 230 \text{ V} \quad \text{1-phase}$$

$$f = 50 \text{ Hz}$$

$$\text{power factor } 1$$

$$V_o = 200 \text{ V} \quad (\text{line-to-line}) \quad \text{3-phase}$$

$$f = 52 \text{ Hz}$$

$$I_o = 10 \text{ A}$$

$$\text{power factor } 0,8 \text{ (lagging)}$$

- Calculate input current and input power.

Output power $P_o = 3 \cdot V_o I_o \cos \phi = 3 \cdot \frac{V_o}{\sqrt{3}} I_o \cos \phi = \sqrt{3} \cdot 200 \cdot 10 \cdot 0,8 \Rightarrow$


$$P_o = 2,77 \text{ kW}$$

Input power $\eta = \frac{P_o}{P_i} \Rightarrow \underline{P_i} = \frac{P_o}{\eta} = \frac{2,77 \cdot 10^3}{0,95} = \underline{2,92 \text{ kW}}$

Input current $P_i = V_i I_i \cos \phi_i \Rightarrow$


$$\underline{I_i} = \frac{P_i}{V_i \cos \phi_i} = \frac{2,92 \cdot 10^3}{230 \cdot 1} = \underline{12,68 \text{ A}}$$

1-3

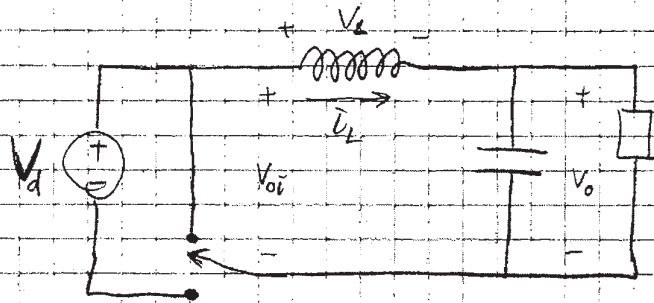

$$V_d = 20 \text{ V}$$

$$D = 0,75$$

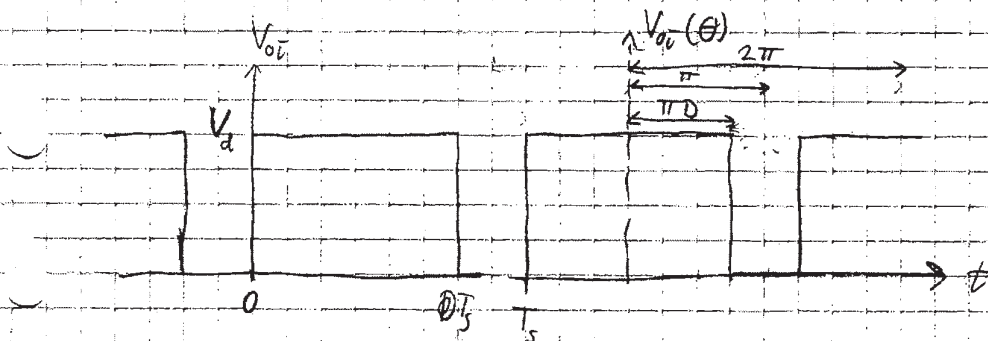

We select a "new" starting point for the Fourier analysis of V_{oi} . From this we see that

$$V_{oi}(\theta) \text{ is even } V_{oi}(\theta) = V_{oi}(-\theta) \Rightarrow$$

$$b_n = 0 \text{ for all } n$$

$$a_n = \frac{2}{\pi} \int_0^{\pi} V_{oi}(\theta) \cos(n\theta) d\theta = \frac{2}{\pi} \int_0^{\pi D} V_d \cos(n\theta) d\theta =$$

$$= \frac{2}{\pi} V_d \left[\frac{1}{n} \sin(n\theta) \right]_0^{\pi D} = \frac{2}{\pi n} V_d (\sin(n\pi D) - \sin(0)) =$$


$$= \frac{2}{\pi} \frac{V_d}{n} \sin(n\pi D) \quad n = 1, \dots, \infty$$

$$V_{oi,av} = \frac{1}{2} a_0 = \frac{1}{\pi} \int_0^{\pi D} V_d d\theta = V_d D = 20 \cdot 0,75 = \underline{\underline{15 \text{ V}}}$$

n a_n ← peak values


1	9,0 V
2	-6,37 V
3	3,0 V
4	0
5	-1,80 V
6	2,12 V

1-5

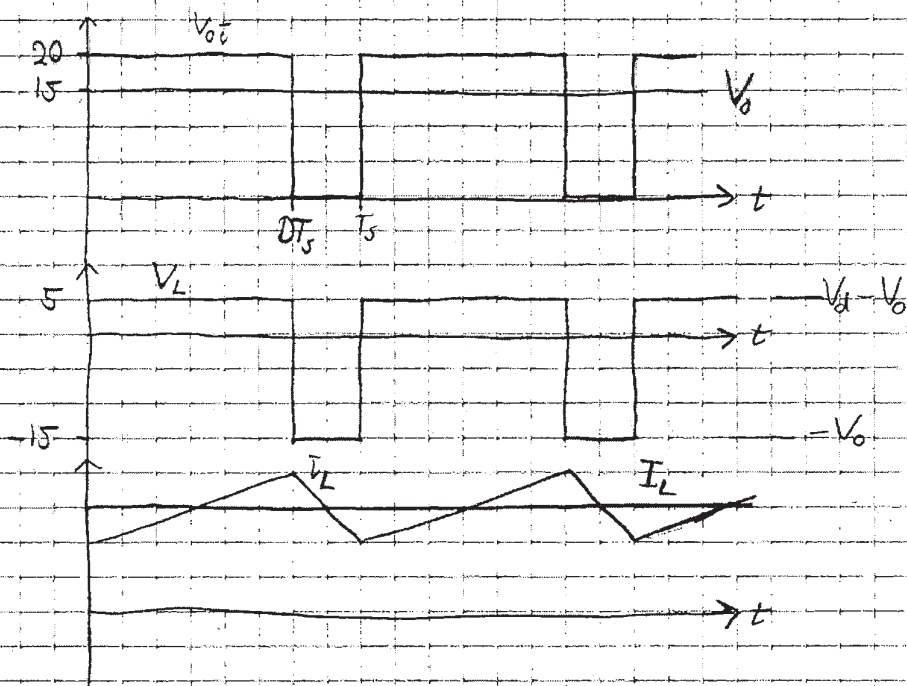

From $V_L = L \frac{di_L}{dt}$ we know that when $V_L > 0$ the inductor current must increase and when $V_L < 0$ it must decrease. Since $V_L = 5V$ during the time the switch is on i_L increases linearly (constant derivative of i_L).

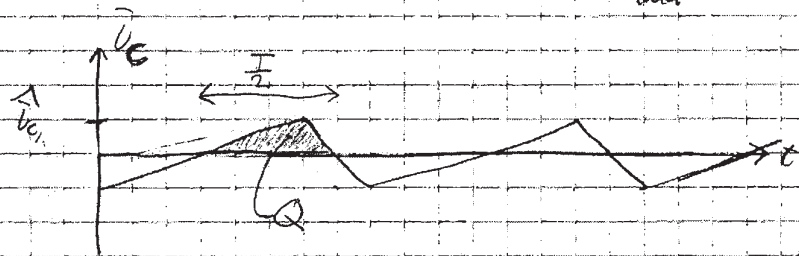We have also made the assumption that $V_0(t) = V_0 = \text{constant} \Rightarrow$ constant current through the resistor $\Rightarrow$ the ripple in i_L go through the capacitor. $\Rightarrow I_L = I_{R_{load}}$



$$\begin{aligned} \Delta V_C &= \frac{1}{C} Q = \\ &= \frac{1}{C} \hat{i}_L T_s = \\ &= \frac{4,8}{4,50 \cdot 10^{-6} \cdot 300 \cdot 10^3} = \\ &= 80 \text{ mV} \end{aligned}$$

The charge Q increases the voltage over the capacitance.

$$\hat{i}_L = \frac{(V_0 - V_L) DT_s}{2L} = \frac{5 \cdot 0,75}{2 \cdot 300 \cdot 10^3 \cdot 1,3 \cdot 10^{-6}} = 4,8 \text{ A}$$

