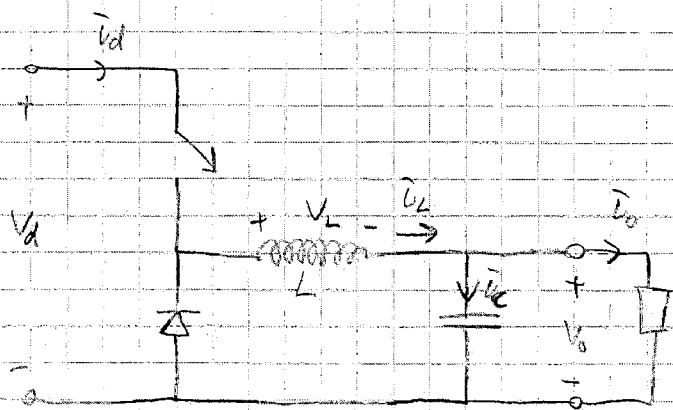


7-1

Step-down

1-2




Let $V_o \approx V_o$ be held constant 5V

V_d is 10-40V $P_o \geq 5W$ $f_s = 50kHz$

calculate L required to keep the converter in CCM

I assume steady state operation and CCM

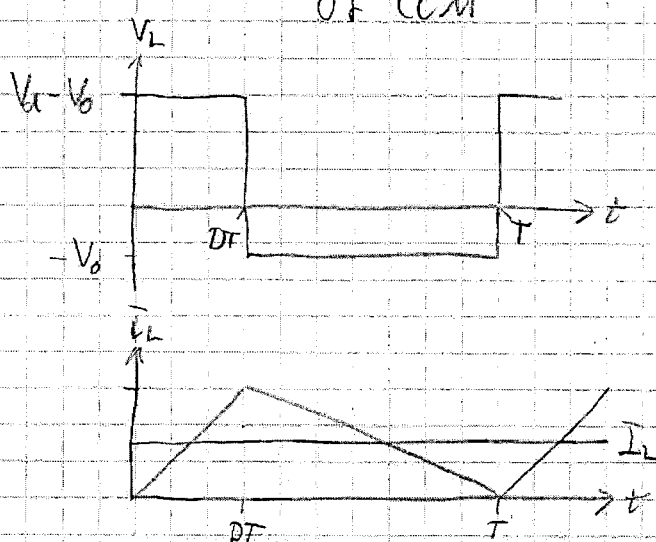The waveforms for the converter at the border of CCM



In steady state we know that $V_L = 0$

$$0 = V_L = \frac{1}{T} ((V_d - V_o)DT - V_o(1-D)T) \Rightarrow$$

$$V_o = V_d D$$

$$I_c = 0 \Rightarrow$$

$$i_L = i_c + i_o \text{ and } i_o = I_o$$

due to that $V_o \approx V_o \Rightarrow$

$$0 = I_c = \frac{1}{T} \int_0^T i_L - I_o dt = \frac{1}{T} \int_0^T i_L dt - I_o = I_L - I_o \Rightarrow I_L = I_o$$

for CCM we know that

$$\Delta i_L \leq 2 I_L = 2 I_o = 2 \frac{P_o}{V_o}$$

$$V_L = L \frac{di_L}{dt}, \text{ during the time the switch is open } V_L = -V_o = \text{const} \Rightarrow$$

$$V_L = L \frac{\Delta i_L}{\Delta t} \Rightarrow \Delta i_L = \frac{V_L \Delta t}{L} = \frac{V_o (1-D)T}{L} \Rightarrow$$

$$\frac{V_o(1-D)}{f_s L} \leq 2 \frac{P_o}{V_o} \Rightarrow$$

$$L \geq \frac{V_o^2(1-D)}{2f_s P_o}$$

We must now find D and P_o within the operation interval that gives the highest value of $\frac{V_o^2(1-D)}{2f_s P_o}$.


This due to the fact that this is the lowest value of L that guarantee CCM operation within the interval.

We directly see that the lowest D and lowest P_o gives the highest value $\Rightarrow$

$$V_o = V_d D \Rightarrow D_{\min} = \frac{V_o}{V_{d,\max}} = \frac{5}{40} = \frac{1}{8}$$

$$L_{\min} = \frac{5^2}{2 \cdot 50 \cdot 10^3 \cdot 5} \left(1 - \frac{1}{8}\right) = 43,75 \mu\text{H}$$

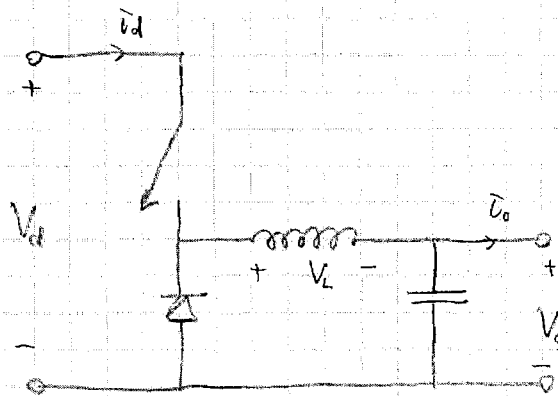
7.2 Step-Down converter, consider all components to be ideal. Assume: $V_o = 5V$, $f_s = 20kHz$, $L = 1mH$, $C = 47\mu F$ calculate ΔV_o (peak-peak) if $V_d = 12,6V$ and $I_o = 200mA$



As before, we start by assuming CCM. $\Rightarrow$

$$D = \frac{V_o}{V_d} = \frac{5}{12,6} \approx 0,40$$

We plot the inductor current:

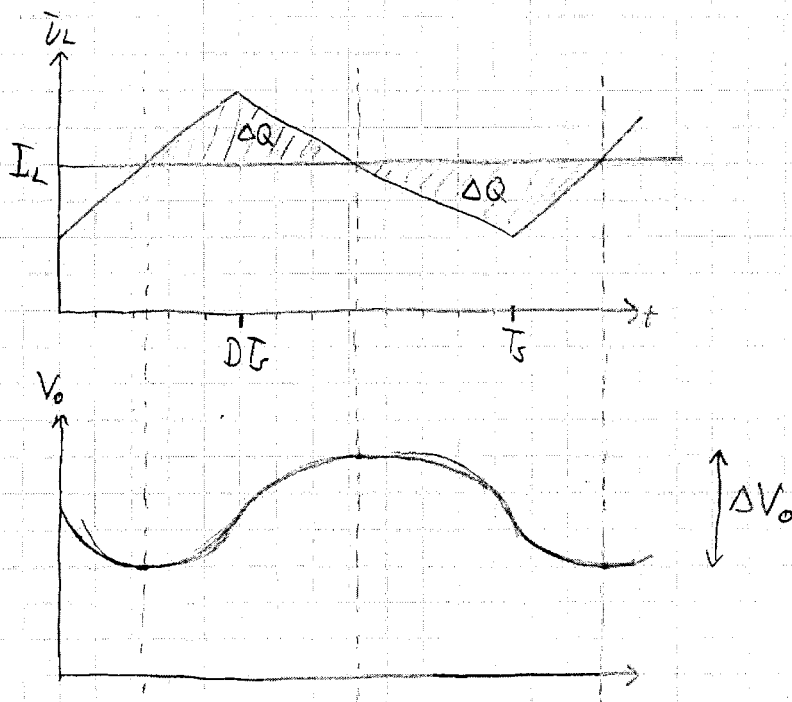

We check if the converter is operating in CCM

$$\Delta I_L = \frac{V_L}{L} \Delta t = \frac{-V_o}{L} (1-D) T_s = -\frac{5}{1 \cdot 10^{-3}} (1-0,4) \frac{1}{20 \cdot 10^3} \approx 151 mA$$

$$\text{We see that } \Delta I_L < 2I_L = 2I_o = 400mA \Rightarrow \text{CCM}$$

We assumed right!!!

7.2
Part 2:

We now assume that all current ripple through the inductance is taken care of by the capacitance $\Rightarrow$

$$\bar{i}_o = I_o = I_L \quad \text{and} \quad \bar{i}_c = \bar{i}_{L, \text{ripple}} \Rightarrow$$

When $\bar{i}_L > I_L$ the capacitor is charged and

When $\bar{i}_L < I_L$ ———— discharged.

We know that $V_c(t) = C \frac{d\bar{i}_c(t)}{dt} \Rightarrow$

$$V_c(t) = V_c(t_0) + \frac{1}{C} \int_{t_0}^t \bar{i}_c(\xi) d\xi \Rightarrow$$

$$\underbrace{V_c(t) - V_c(t_0)}_{\text{change in voltage}} = \frac{1}{C} \underbrace{\int_{t_0}^t \bar{i}_c(\xi) d\xi}_{\text{change in charge}} \Rightarrow$$

$$\Delta V_c = \frac{1}{C} \Delta Q$$

Shade ΔQ in the current plot.


$$\begin{aligned} \Delta V_o &= \frac{\Delta Q}{C} = \frac{1}{C} \left(\frac{\Delta I_L}{2} \cdot \frac{T_s}{2} \cdot \frac{1}{2} \right) = \frac{T_s}{8C} \frac{V_o}{L} (1-D) T_s = \frac{V_o}{8 f_s^2 C L} \left(1 - \frac{V_o}{V_d} \right) \\ &= \frac{5}{8 (20 \cdot 10^3)^2 \cdot 470 \cdot 10^{-6} \cdot 1 \cdot 10^{-3}} \left(1 - \frac{5}{12.8} \right) = \underline{\underline{2.01 \text{ mV}}} \end{aligned}$$

- Note that the ripple is independent of the output power when the converter operates in CCM

7.3

Assume CCM $\Rightarrow$

1-7

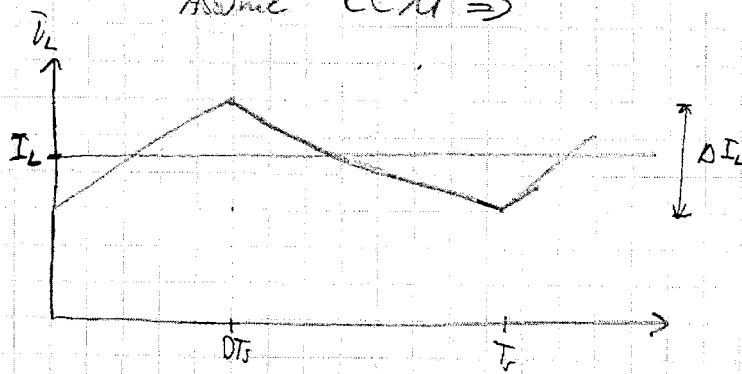


$$D = \frac{5}{12.6}$$

$$\Delta I_L = \frac{V_o}{L} (1-D) T_s = \frac{5}{1 \cdot 10^{-3}} \left(1 - \frac{5}{12.6}\right) \frac{1}{20 \cdot 10^3} \approx 15 \text{ mA}$$

$$I_L = I_o = 200 \text{ mA} > \frac{\Delta I_L}{2} \Rightarrow \text{CCM}$$

Calculate the rms value of the ripple current.

The ripple current can be drawn as

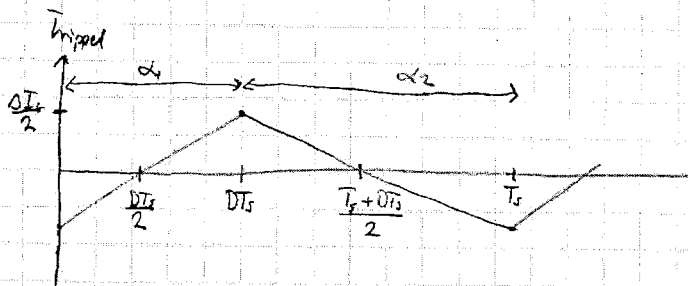

$$\frac{T_s - DT_s}{2} + DT_s = \frac{T_s + DT_s}{2}$$

$$I_{\text{ripple, RMS}} = \sqrt{\frac{1}{T_s} \int_0^{T_s} i_{\text{ripple}}^2(t) dt} = \sqrt{\frac{DT_s}{T_s} \frac{1}{DT_s} \int_0^{DT_s} i_{\text{ripple}}^2(t) dt + \frac{T_s - DT_s}{T_s} \frac{1}{T_s - DT_s} \int_{DT_s}^{T_s} i_{\text{ripple}}^2(t) dt}$$


$$= \sqrt{\frac{DT_s}{T_s} I_{\text{ripple, RMS}, \alpha_1}^2 + \frac{T_s - DT_s}{T_s} I_{\text{ripple, RMS}, \alpha_2}^2}$$

$$I_{\text{ripple, RMS}, \alpha_1}^2 = \frac{1}{DT_s} \int_0^{DT_s} i_{\text{ripple}}^2(t) dt \stackrel{\text{Simpson's}}{=} \frac{1}{6} \left(\frac{\Delta I_L}{2}\right)^2 + \frac{1}{6} \left(\frac{\Delta I_L}{2}\right)^2 = \frac{1}{12} \Delta I_L^2$$

$$I_{\text{ripple, RMS}, \alpha_2}^2 = \frac{1}{T_s - DT_s} \int_{DT_s}^{T_s} i_{\text{ripple}}^2(t) dt = \frac{1}{12} \Delta I_L^2$$

$$I_{\text{ripple, RMS}} = \sqrt{\frac{DT_s}{T_s} \frac{1}{12} \Delta I_L^2 + \frac{T_s - DT_s}{T_s} \frac{1}{12} \Delta I_L^2} = \frac{1}{\sqrt{12}} \Delta I_L = \frac{15 \cdot 10^{-3}}{\sqrt{12}} = 44 \text{ mA}$$

7.12

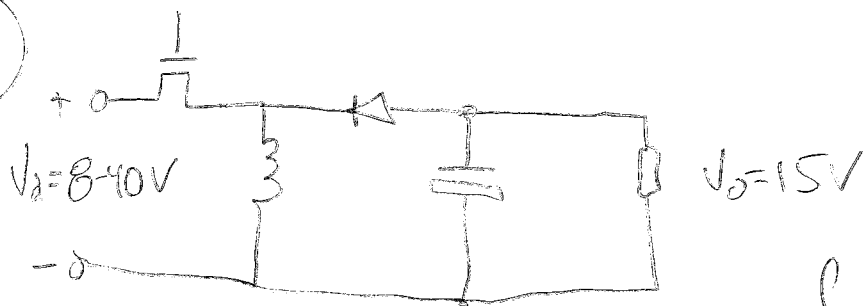


Calculate L_{min} required to operate in CCM ∇

$$f_{sw} = 20 \text{ kHz}$$

$$C = 470 \mu\text{F}$$

$$P_o \geq 2.0 \text{ W}$$

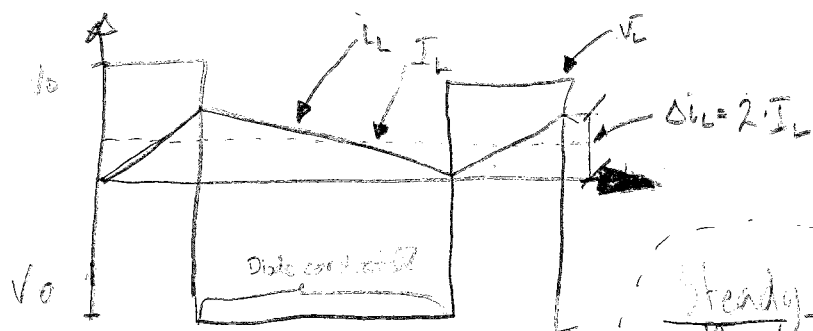

$$\Delta i_L = \frac{1}{L} \int_0^{DT} V_o dt = \frac{D \cdot T \cdot V_o}{L}$$

$$\Delta i_L = \frac{V_o (1-D)}{L f_{sw}}$$

We have to express Δi_L in terms of I_o or I_{in} .

$$I_o = I_D = \frac{1}{T} \int_0^T i_D dt = \frac{1}{T} \int_{DT}^T i_L dt$$

But i_D equals to i_L within this interval ∇

$$I_o = \frac{1}{T} \int_{DT}^T i_L dt = \frac{I_o}{T} \frac{1}{f_{sw}} \int_{DT}^T i_L dt \Rightarrow I_o = \frac{1-D}{T} \cdot I_L \Rightarrow I_o = (1-D) \cdot I_L$$

$$\text{This gives: } \frac{I_o}{1-D} = \frac{V_o (1-D)}{2 \cdot L \cdot f_{sw}} \Rightarrow L = \frac{V_o (1-D)^2}{2 \cdot I_o \cdot f_{sw}} = \frac{V_o^2 (1-D)^2}{2 P_o \cdot f_{sw}}$$

$\Delta i_L = 2 \cdot I_L$

ideal converter:

$$P_d = P_o \Rightarrow V_d I_d = V_o I_o$$

$$\text{Steady state: } 0 = \int_0^T v_L dt = \int_0^{DT} V_d dt + \int_{DT}^T -V_o dt = V_d \cdot DT - T V_o + DT V_o = 0$$

$$\Rightarrow V_d \cdot D = V_o (1-D) \Rightarrow V_o = V_d \cdot \frac{D}{1-D}$$

Steady state 2: $I_C = 0$

$$0 = \frac{1}{T} \int_0^T i_D - i_{out} dt = \frac{1}{T} \int_0^T i_D dt - \frac{1}{T} \int_0^T I_o dt = I_D - I_o = 0 \Rightarrow I_D = I_o$$

ideal converter: $V_o \cdot I_o = V_d I_D$

$$\Rightarrow V_d \cdot I_D = V_d \frac{D}{1-D} I_o \Rightarrow I_D = I_o \frac{D}{1-D}$$

$$L = \frac{V_o^2}{2P_{\text{fsw}}} \cdot (1-D)^2 \Rightarrow \left\{ \begin{array}{l} \text{A. max } D \text{ gives the highest value of } L \\ \text{A low } P_o \text{ gives the highest value of } L \end{array} \right\}$$


$$I_{\text{min}} \quad V_o = V_i \frac{D}{1-D} \Rightarrow D = \frac{V_o}{V_d} - \frac{V_o}{V_d} \cdot D = D \Rightarrow$$

$$\Rightarrow \frac{V_o}{V_d} = D \left(1 + \frac{V_o}{V_d} \right)$$


$$\Rightarrow D = \frac{V_o}{V_d + V_o} = \frac{15}{15 + 40} = 0,2727$$

$$L_{\text{min}} = \frac{15^2}{2 \cdot 20 \text{ k} \cdot 2} \cdot (1 - 0,2727)^2 = \underline{\underline{1,49 \text{ mH}}}$$

7.19

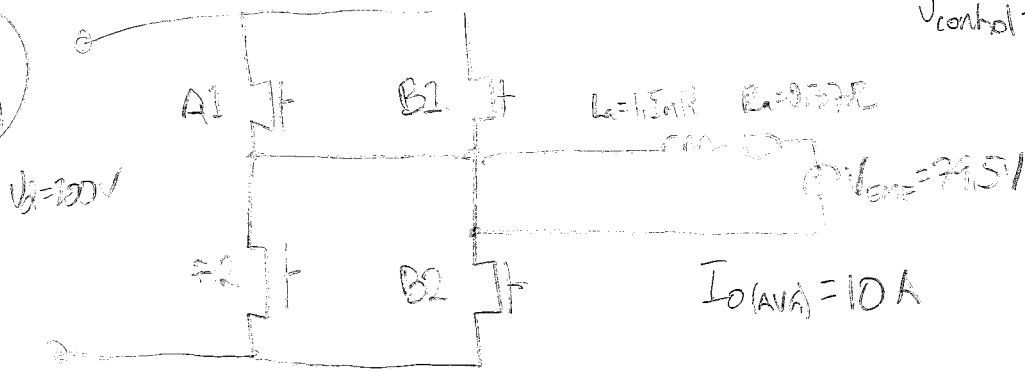

a

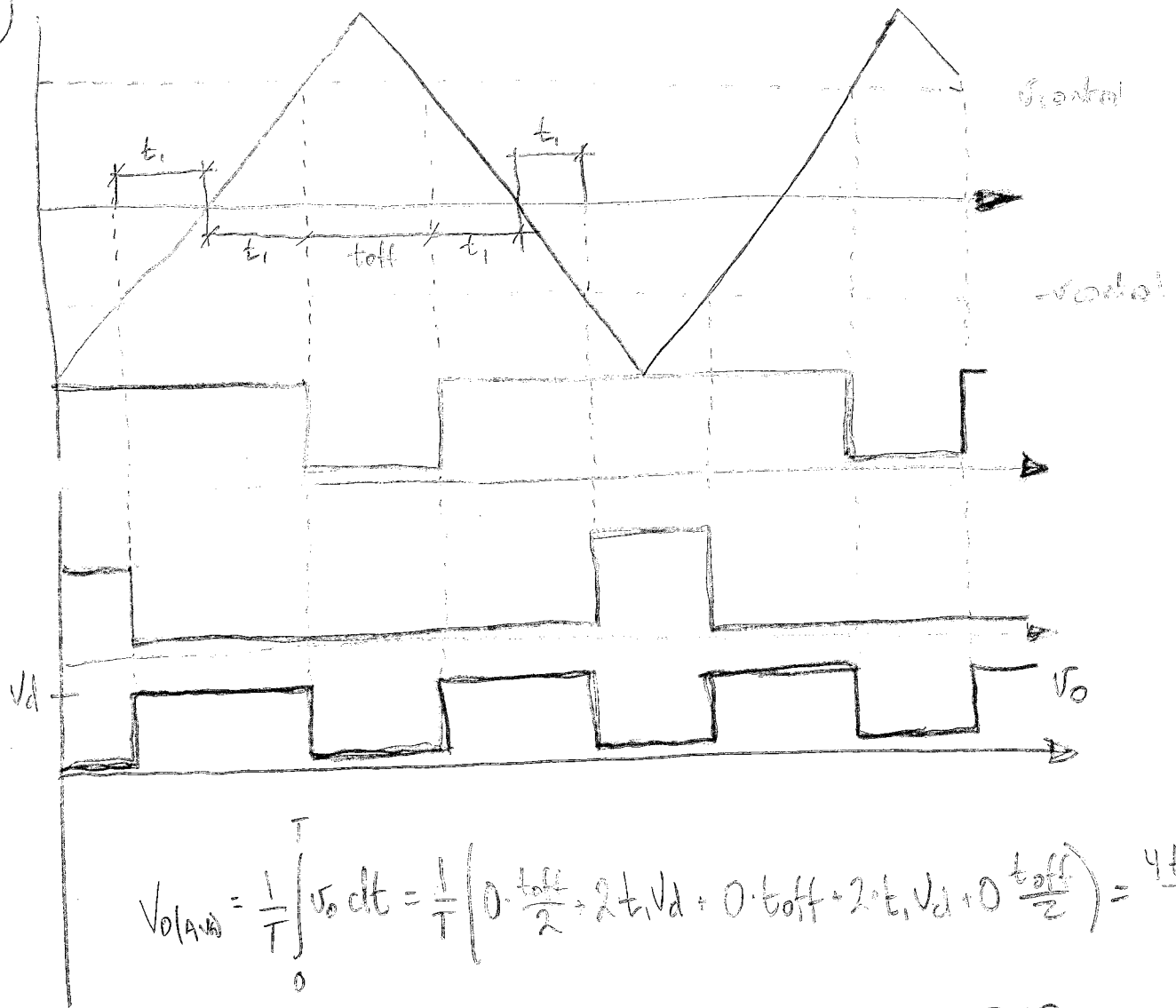

$$V_{O(AVA)} = \frac{1}{T} \int_0^T v_o dt = \frac{1}{T} \left(0 \cdot \frac{t_{off}}{2} + 2t_i V_d + 0 \cdot t_{off} + 2t_i V_d + 0 \cdot \frac{t_{off}}{2} \right) = \frac{4t_i V_d}{T}$$

So, we have to express t_i in known terms, see 7.18:

$$V_c = \frac{4}{T} t_i \cdot \hat{V}_{tri} \Rightarrow t_i = \frac{V_{control} \cdot T}{4 \cdot \hat{V}_{tri}}$$

$$V_{O(AVA)} = \frac{4V_d}{T} \cdot \frac{V_{control} T}{4 \hat{V}_{tri}} = V_d \cdot \frac{V_{control}}{\hat{V}_{tri}} = \underline{\underline{0.5 V_d}}$$


Same for the currents

$$I_{O(AVA)} = \frac{1}{T} \int_0^T i_o dt = \frac{4I}{T} \Rightarrow I_{O(AVA)} = I_0 \cdot \frac{V_{control}}{\hat{V}_{tri}} = \underline{\underline{0.5 I_0}}$$

5 Fourier Analysis

Calculate the Fourier coefficients for v_o and i_d

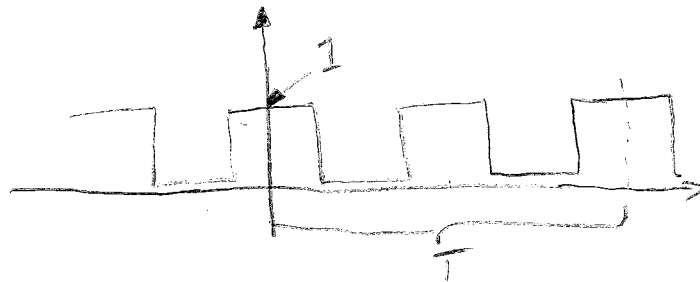⇒ normalize the axis, calculate the Fourier series for $\frac{v_o}{V_d}$ and $\frac{i_d}{I_o}$, gives unity axis.



Even function: $f(t) = f(-t)$ gives $b_n = 0_{\neq 2}$

Periodic function gives: $a_n = \frac{1}{T} \int_0^T f(t) \cos(n\omega t) dt$

$$a_n = \frac{1}{T} \int_0^{T/2} \cos(n\omega t) dt + \frac{1}{T} \int_{T/2}^T \cos(n\omega t) dt = \frac{1}{T} \left(\left[\frac{\sin(n\omega t)}{n\omega} \right]_0^{T/2} + \left[\frac{\sin(n\omega t)}{n\omega} \right]_{T/2}^T \right) =$$

$$= \frac{1}{n\omega T} \left(\sin(n\omega T/2) + \sin(n\omega T/2) - \sin(n\omega T/2) - \sin(n\omega T/2) \right) = \left[\omega = \frac{2\pi}{T} \right]$$

$$= \frac{2}{n\pi} \left(\sin\left(n \frac{2\pi}{T} \frac{V_{control} \cdot T}{2 \cdot \sqrt{V_{tri}}}\right) + \sin(n\pi) - \sin\left(n \frac{2\pi}{T} \left(\frac{T}{2} - \frac{V_{control} \cdot T}{2 \cdot \sqrt{V_{tri}}}\right)\right) \right) =$$

$$= \frac{2}{n\pi} \left(\sin\left(n\pi \cdot \frac{V_{control}}{2\sqrt{V_{tri}}}\right) - \sin\left(n\pi - n\pi \frac{V_{control} \cdot T}{2\sqrt{V_{tri}}}\right) \right) =$$

$$= \frac{2}{n\pi} \left(\sin(0.25n\pi) - \sin(n\pi) \cdot \cos\left(n\pi \frac{V_{control} \cdot T}{2\sqrt{V_{tri}}}\right) + \cos(n\pi) \sin\left(n\pi \frac{V_{control} \cdot T}{2\sqrt{V_{tri}}}\right) \right)$$


$$= \frac{2}{n\pi} \left(\sin(0.25n\pi) + (-1)^n \sin(0.25n\pi) \right)$$






The Fourier coefficients can then be calculated as

n		
1	$\frac{2}{1\pi} (\sin(0.25\pi) + (-1)^1 \sin(0.25\pi))$	0
2	$\frac{2}{2\pi} (\sin(0.5\pi) + (-1)^2 \sin(0.5\pi))$	0.6366
3	$\frac{2}{3\pi} (\sin(0.75\pi) + (-1)^3 \sin(0.75\pi))$	0
4	$\frac{2}{4\pi} (\sin(\pi) + (-1)^4 \sin(\pi))$	0
5	$\frac{2}{5\pi} (\sin(1.25\pi) + (-1)^5 \sin(1.25\pi))$	0
6	$\frac{2}{6\pi} (\sin(1.5\pi) + (-1)^6 \sin(1.5\pi))$	-0.212

7.22

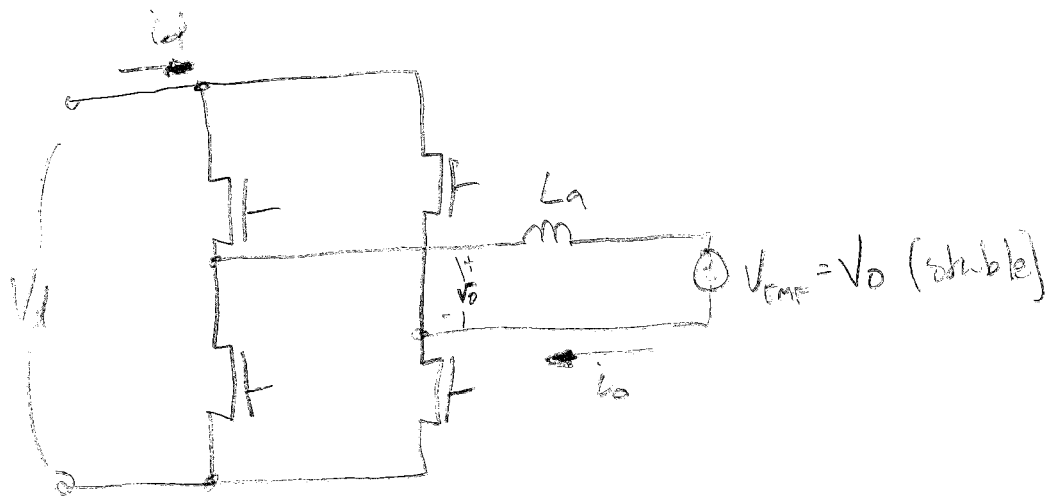

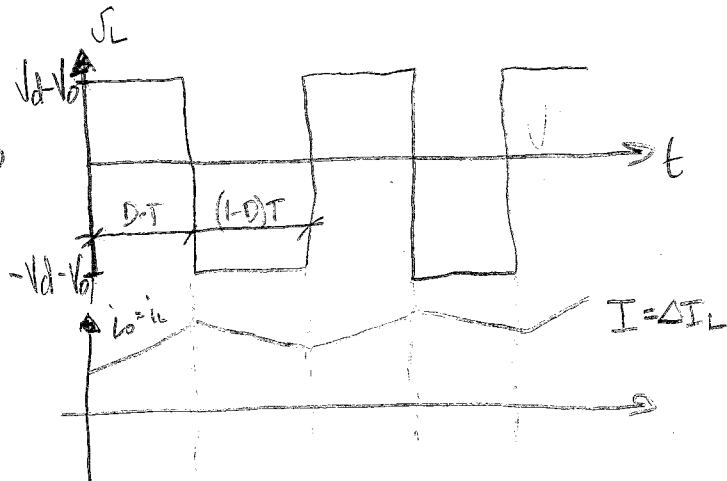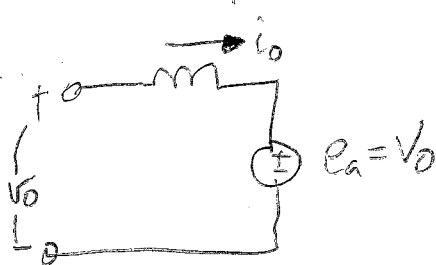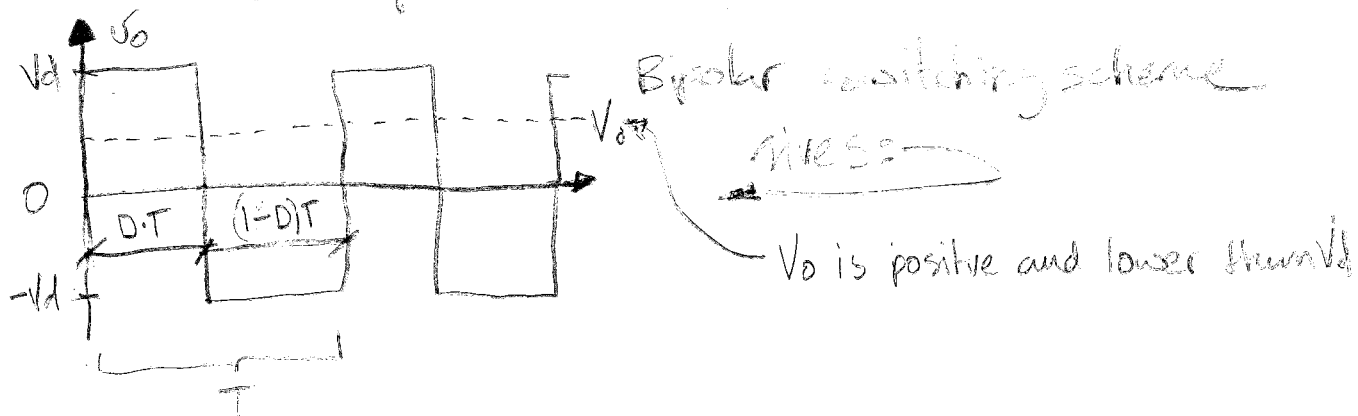Analytically obtain the value of $\frac{V_o}{V_d}$ which results in the maximum peak-to-peak ripple in the output current i_o



$$\Delta I_L = \frac{1}{L_a} \int_{D \cdot T}^{T} v_L(t) dt =$$

$$= \frac{1}{L_a} \int_0^{D \cdot T} (V_d - V_o) dt = \frac{V_d - V_o}{L_a} \cdot D \cdot T = \Delta I_L \quad \text{So, we have to find another expression for } \Delta I_L$$

$$\Rightarrow \text{D.C. } 0 = \frac{1}{L_a} \int_0^T v_L(t) dt = \frac{1}{L_a} \int_0^{D \cdot T} (V_d - V_o) dt + \int_{D \cdot T}^T (-V_d - V_o) dt = \frac{1}{L_a} (D \cdot T \cdot (V_d - V_o) + T \cdot (-V_d - V_o) \cdot (1 - D))$$

$$= \frac{1}{L_a} (V_d D T - D T V_o - T V_d + T V_o + V_d D T - D T V_o) = \frac{1}{L_a T} (V_d D T - V_d - V_o) = 0$$

$$\Rightarrow 0 = (2 \cdot V_d \cdot D \cdot V_d - V_0) \Rightarrow D = \frac{V_d + V_0}{2V_d} = \underline{\underline{\frac{1}{2} \left(1 + \frac{V_0}{V_d} \right)}}$$

$$\Rightarrow \Delta I_L = \frac{V_d - V_0}{L_n} DT = \frac{V_d - V_0}{L_n} \frac{1}{2} \left(1 + \frac{V_0}{V_d} \right) \cdot T = \frac{T}{2L_n} \left(1 + \frac{V_0}{V_d} \right) \left(\frac{V_d}{V_d} - \frac{V_0}{V_d} \right) \quad \text{lengthen with } \frac{V_d}{V_d}$$

$$= \frac{T}{2L_n} \left(1 + \frac{V_0}{V_d} \right) \left(\frac{V_d \cdot V_d - V_0 V_d}{V_d} \right) = \frac{T V_d}{2L_n} \left(1 + \frac{V_0}{V_d} \right) \left(\frac{V_d - V_0}{V_d} \right) =$$

$$= \frac{T V_d}{2L_n} \left(1 + \frac{V_0}{V_d} \right) \left(1 - \frac{V_0}{V_d} \right)$$

When you want to search for a maximum, find the first derivative and set it to 0, then find the correct $\frac{V_0}{V_d}$

$$\Delta I_L = \frac{T V_d}{2L_n} \left(1 - \left(\frac{V_0}{V_d} \right)^2 \right) \Rightarrow \frac{\partial \Delta I_L}{\partial \left(\frac{V_0}{V_d} \right)} = \frac{-T V_d}{2L_n} \cdot 2 \left(\frac{V_0}{V_d} \right) = 0 \Rightarrow$$

$$\Rightarrow \frac{V_0}{V_d} = 0 \text{ to get a stationary point?}$$

(A negative second derivative gives a maximum point)

Use $\frac{V_0}{V_d} = 0$ in the equation for ΔI_L gives

$$\Delta I_L(\text{max}) = \frac{T V_d}{2L_n} = \underline{\underline{\frac{V_d}{2L_{eff}}}}$$