


8-2

$$V_{o1} = 220V \text{ at } 47 \text{ Hz}$$


$$L = 100 \text{ mH}$$

1-01


Square-Wave operation

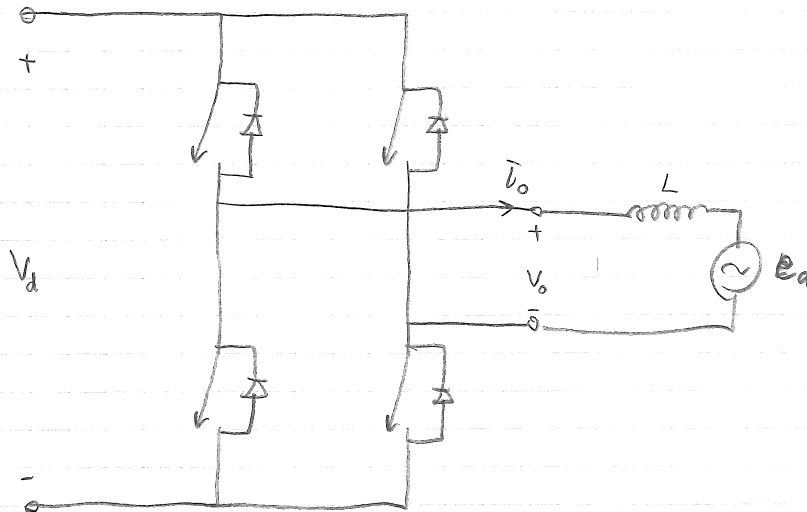

Since E_a is sinusoidal the ripple voltage over the inductor is equal to $V_{\text{ripple}} = V_o - V_{o1}$

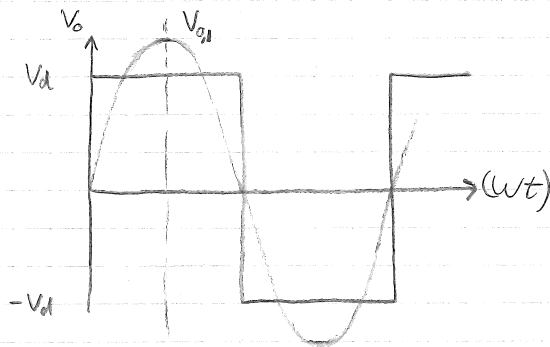Odd half wave function $\Rightarrow$
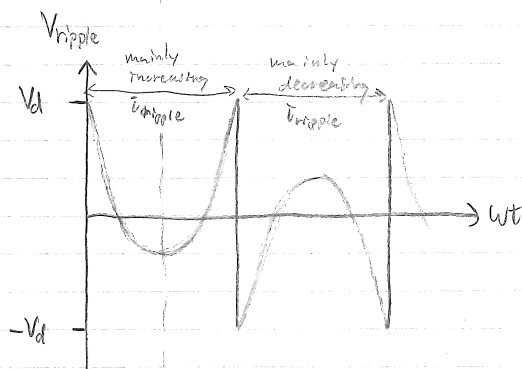
$$V_{o1} = \frac{4}{\sqrt{2}\pi} \int_0^{\frac{\pi}{2}} V_d \sin(\omega t) d\omega t = \frac{4V_d}{\sqrt{2}\pi} \Rightarrow V_d = \frac{\sqrt{2}\pi}{4} \cdot 220 = \underline{244.4V}$$




$$V_L = L \frac{di}{dt} \Rightarrow$$

$$\omega L \int_0^{I_{\text{ripple}}} di = \int_{\frac{\pi}{2}}^{\pi} (V_d - \sqrt{2}V_{o1} \sin(\omega t)) d\omega t \Rightarrow$$

$$I_{\text{ripple}} = \frac{1}{\omega L} \left(\left[V_d(\omega t) + \sqrt{2}V_{o1} \cos(\omega t) \right]_{\frac{\pi}{2}}^{\pi} \right) =$$
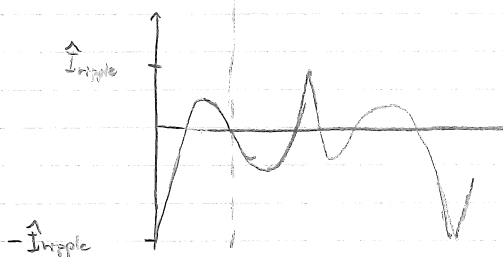
$$= \frac{1}{\omega L} \left(\frac{\pi}{2} V_d - \sqrt{2}V_{o1} + 0 \right) = \frac{\pi V_d - 2\sqrt{2}V_{o1}}{2\omega L}$$



$$\underline{I_{\text{ripple}}} = \frac{\pi \cdot 244.4 - 2\sqrt{2} \cdot 220}{2 \cdot 2 \cdot \pi \cdot 47 \cdot 0.1} = \underline{2.46A}$$

8-3


$m_f = 21$ and $m_a = 0.8$ bipolar voltage switching

$$m_f = \frac{f_s}{f_i} \quad \hat{V}_{o,i} = m_a V_d$$

We have a PWM generator $\Rightarrow V_{control} > V_{tri} \quad T_{a+}$ on

$V_{control} < V_{tri} \quad T_{a-}$ on

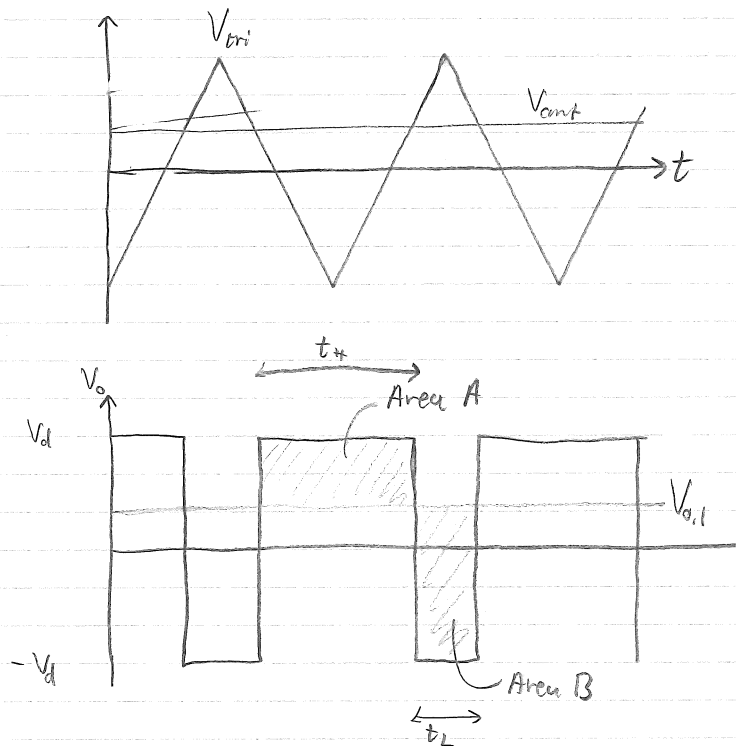Since m_f is large we approximate $V_{control}(t) = \hat{V}_c \sin(\omega t)$ to be constant during one switching period $\Rightarrow$



Since we have approximated the control signal to be constant during one switching period we can also approximate the fundamental to be constant during one switching period $\Rightarrow$ Area A increases the ripple current and Area B decrease the ripple current

$$A(t) = t_+ (V_d - m_a V_d \sin(\omega t))$$

$$B(t) = t_- (V_d + m_a V_d \sin(\omega t))$$

$$t_- = \frac{T_s}{2} \left(1 - \frac{\hat{V}_c \sin(\omega t)}{V_{tri}} \right) = \frac{T_s}{2} (1 - m_a \sin(\omega t))$$

$$t_+ = T_s - t_- = T_s - \frac{T_s}{2} + \frac{T_s}{2} m_a \sin(\omega t) = \frac{T_s}{2} (1 + m_a \sin(\omega t))$$

$\Rightarrow$

$$A(t) = \frac{I_s}{2} (1 + m_a \sin(\omega t)) (V_d + m_a V_d \sin(\omega t)) = \frac{V_d I_s}{2} (1 - m_a^2 \sin^2(\omega t))$$

$$B(t) = \frac{I_s}{2} (1 - m_a \sin(\omega t)) (V_d + m_a V_d \sin(\omega t)) = \frac{V_d I_s}{2} (1 - m_a^2 \sin^2(\omega t))$$

$\Rightarrow$ Area A = Area B as they should be. We see that the areas are greatest at $t=0$. Therefore the ripple current will also be greatest at $t=0 \Rightarrow$




$$I_{\text{ripple, p-p}} = \frac{A(t=0)}{L} = \frac{V_d}{2 f_s L} = \frac{\sqrt{2} V_{s1}}{2 m_a f_s m_a L} = \frac{\sqrt{2} 220}{2 \cdot 21.47 \cdot 0.8 \cdot 0.1} = 1.97 \text{ A} \Rightarrow$$

$$\text{Peak ripple current} = \frac{1.97}{2} = \underline{\underline{0.985 \text{ A}}}$$


8-4

Voltage Cancellation see page 218.
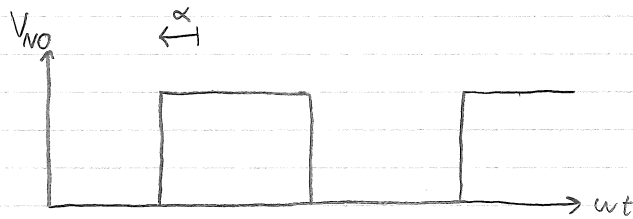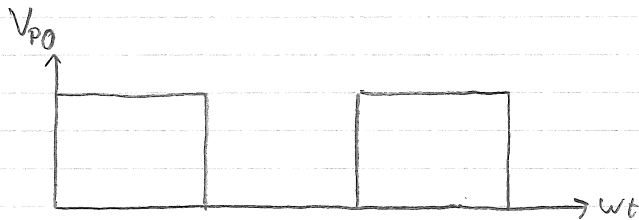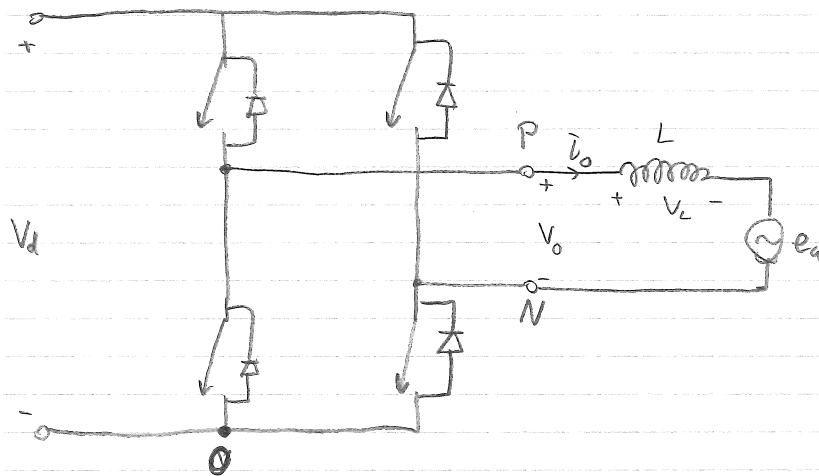
$$V_d = \frac{2 \cdot 220}{0,8} = \underline{\underline{389 V}}$$



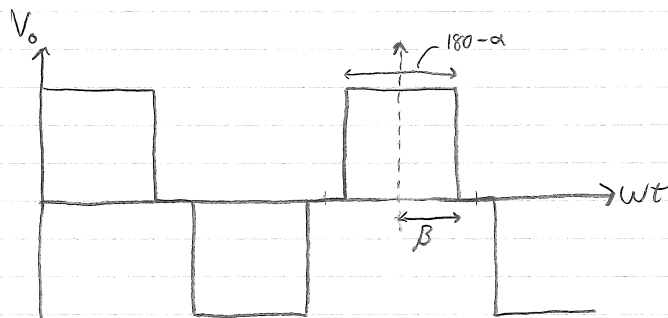These are always square-wave voltages. By changing α we see that we can change the output voltage





$$180 - \alpha = 2\beta \Rightarrow \beta = 90 - \frac{\alpha}{2}$$

We have an even function $\Rightarrow$

$$V_{o1} = \frac{a_1}{\sqrt{2}} = \frac{2}{\sqrt{2}\pi} \int_{-\frac{\pi}{2}}^{\frac{\pi}{2}} V_o(\omega t) \cos(\omega t) d(\omega t) = \frac{\sqrt{2}}{\pi} \int_{-\beta}^{\beta} V_d \cos(\omega t) d(\omega t) = \frac{2\sqrt{2}}{\pi} V_d \sin(\beta) \Rightarrow$$

$$\sin(\beta) = \frac{\pi}{2\sqrt{2}} \frac{V_{o1}}{V_d} = \frac{\pi}{2\sqrt{2}} \frac{220}{389} = 0,628 \Rightarrow \beta = 38,9^\circ \Rightarrow \alpha =$$

2-(2)

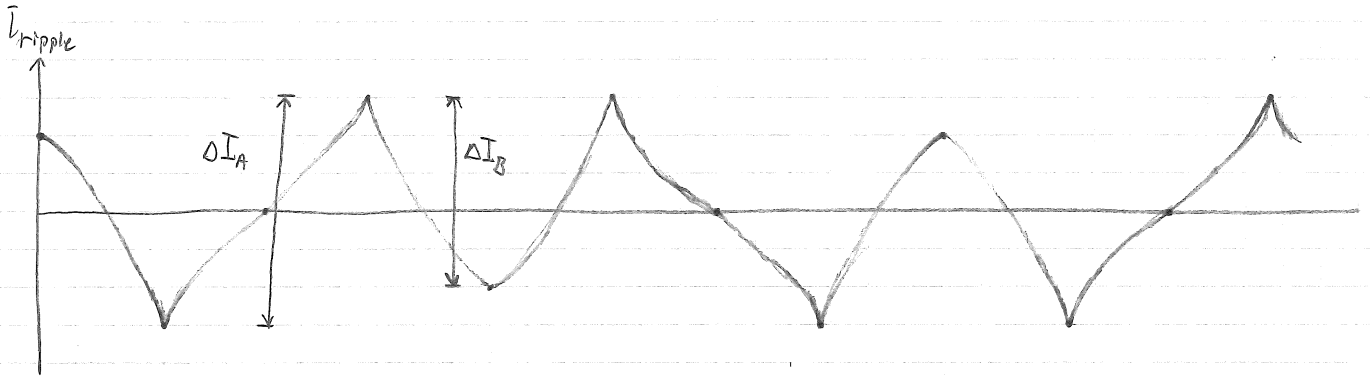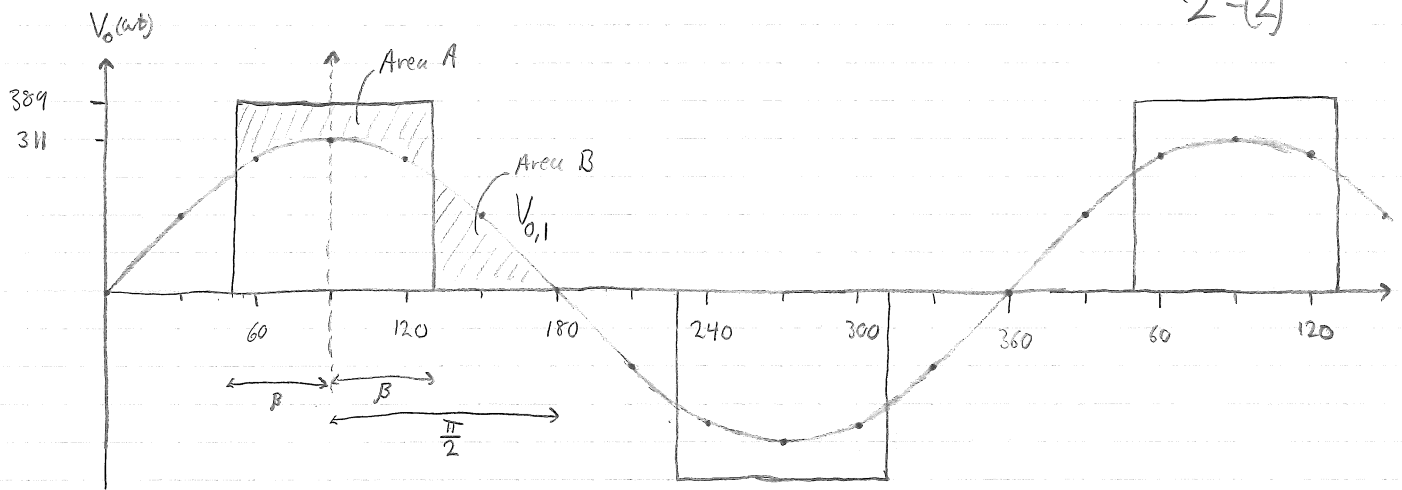

We know that: $\Delta I_A = \frac{\text{Area A}}{L}$ and $\Delta I_B = \frac{\text{Area B}}{L} \Rightarrow$

$$\Delta I_A = \frac{1}{\omega L} \int_{-\beta}^{\beta} (V_d - \sqrt{2} V_{o,1} \cos(\omega t)) d(\omega t) = \frac{2}{\omega L} (V_d \beta - \sqrt{2} V_{o,1} \sin(\beta))$$

$$\Delta I_B = \frac{1}{\omega L} \int_{\beta}^{\frac{\pi}{2}} \sqrt{2} V_{o,1} \cos(\omega t) d(\omega t) = \frac{\sqrt{2}}{\omega L} V_{o,1} (1 - \sin(\beta))$$

$$\Delta I_A = \frac{2}{2\pi 47 \cdot 0.1} \left(389 \cdot \frac{38.9^\circ \cdot \pi}{180^\circ} - \sqrt{2} 220 \sin(38.9^\circ) \right) = \underline{\underline{4.65 \text{ A}}}$$


$$\Delta I_B = \frac{\sqrt{2}}{2\pi 47 \cdot 0.1} 220 (1 - \sin(38.9^\circ)) = \underline{\underline{3.92 \text{ A}}}$$

$$\Delta I_A > \Delta I_B \Rightarrow$$

$$\text{Peak ripple current} = \frac{\Delta I_A}{2} = \frac{4.65}{2} = \underline{\underline{2.33 \text{ A}}}$$

1-(2)

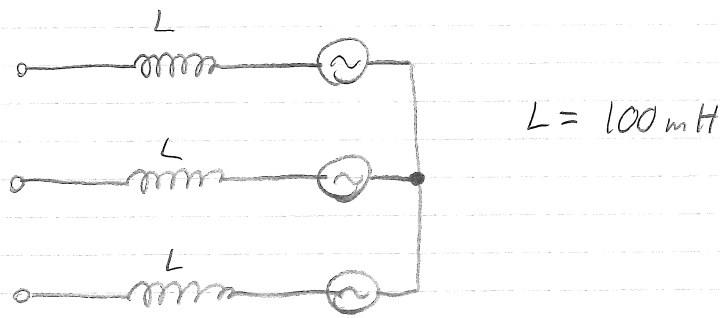8-8 Synchronous PWM $m_f = 39$, $m_a = 0,8$, $V_{LL} = 200V$ 52Hz
Three-phase load




As we can see from figure 8-26 b the peak ripple current occurs near the zero-crossing points of V_{AN} .

Since m_f is large, $V_{\text{control},A}$, $V_{\text{control},B}$ and $V_{\text{control},C}$ can be assumed to be constant during one switching period. At the zero-crossing of $V_{\text{control},A} \Rightarrow$

$$V_{\text{control},A} = 0$$

$$V_{\text{control},B} = 0,8 \hat{V}_{\text{tri}} \sin(0 - 120^\circ) = -0,8 \frac{\sqrt{3}}{2} \hat{V}_{\text{tri}} = -0,4\sqrt{3} \hat{V}_{\text{tri}}$$

$$V_{\text{control},C} = 0,8 \hat{V}_{\text{tri}} \sin(0 + 120^\circ) = 0,4\sqrt{3} \hat{V}_{\text{tri}}$$

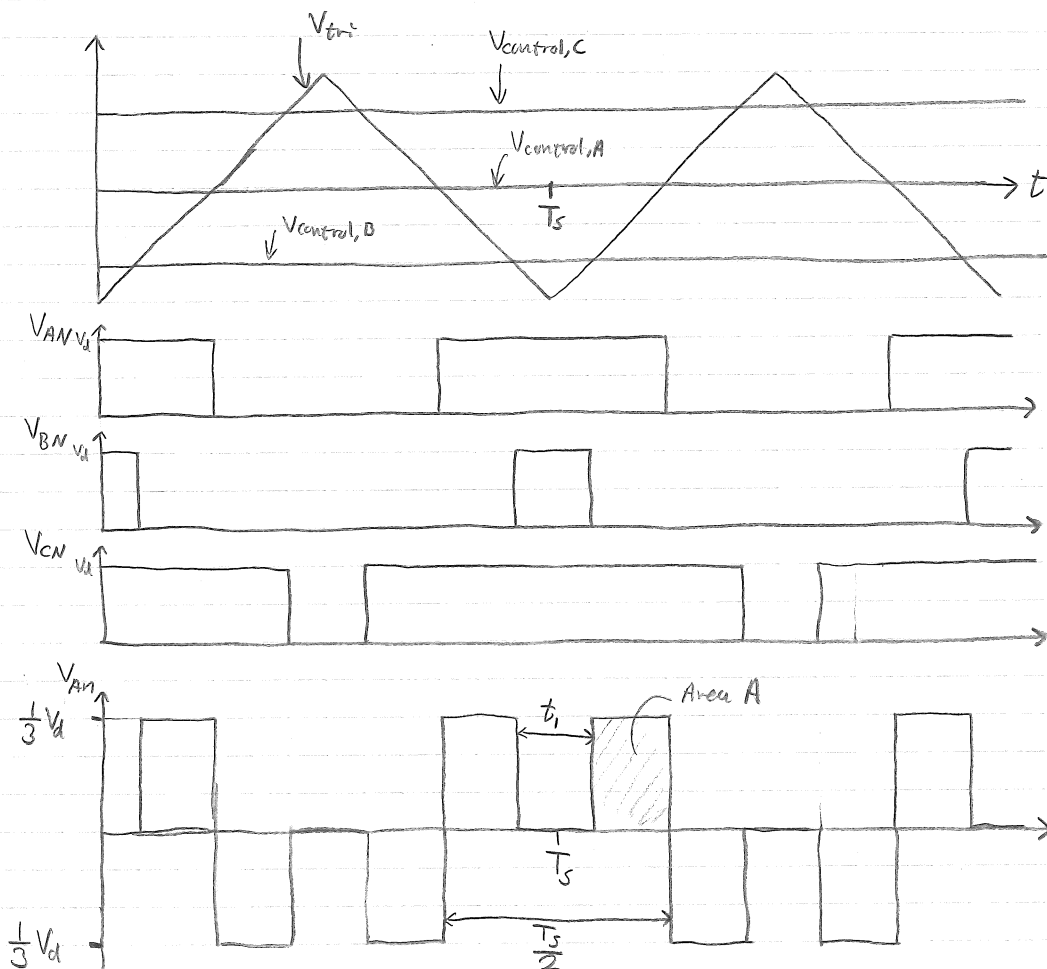


From 8-7 we know that

$$V_{An} = \frac{2}{3} V_{Am} - \frac{1}{3} (V_{on} + V_{cn})$$

We also know that $V_{An,1} = 0 \Rightarrow$

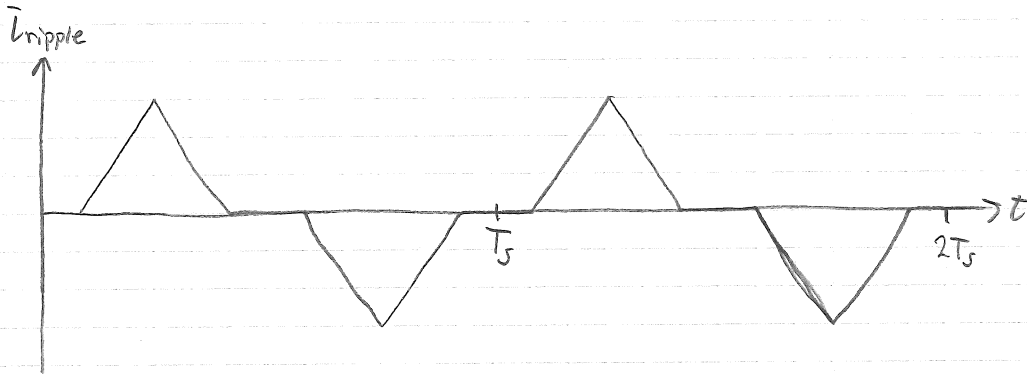$V_{ripple} = V_{Am}$ it is this voltage that drives the ripple current $\Rightarrow$



$$\Delta i_{ripple} = \frac{1}{L} \int_0^{T_s/4} V_{Am}(t) dt = \frac{\text{Area } A}{L}$$

$$t_1 = \frac{T_s}{2} \left(1 - \frac{|V_{control,s}|}{V_{tri}} \right) = \frac{T_s}{2} (1 - 0.4\sqrt{3}) \Rightarrow$$

$$\text{Area } A = \frac{1}{3} V_d \left(\frac{T_s}{4} - \frac{t_1}{2} \right) = \frac{1}{3} V_d \left(\frac{T_s}{4} - \frac{T_s}{4} (1 - 0.4\sqrt{3}) \right) = \frac{V_d T_s}{12} 0.4\sqrt{3} \Rightarrow$$

$$\Delta i_{ripple} = \frac{0.4\sqrt{3} V_d}{12 L f_s}$$







From equation 8-57 we know that

$$V_d = \frac{2\sqrt{2}}{\sqrt{3} m_a} V_{LL1} \Rightarrow$$

$$\Delta i_{ripple} = \frac{0.4\sqrt{3} \cdot 2\sqrt{2}}{\sqrt{3} m_a \cdot 12 L m_f f_s} V_{LL1} = \frac{0.4 \cdot 2 \cdot \sqrt{2}}{12} \cdot \frac{200}{0.8 \cdot 0.1 \cdot 52.39} = \underline{\underline{0.116}}$$

8-11




1-(2)

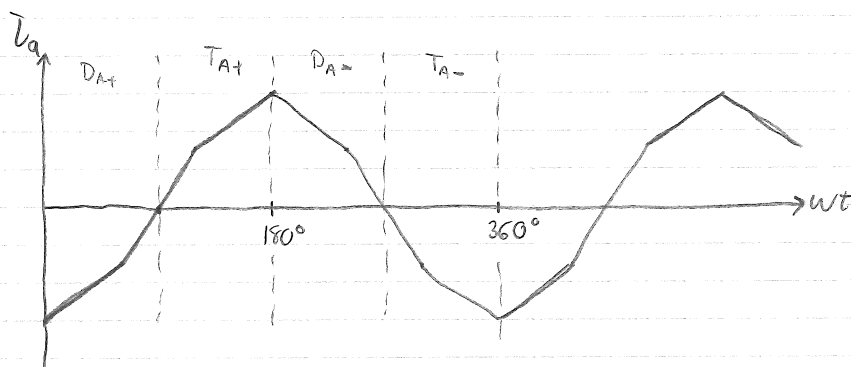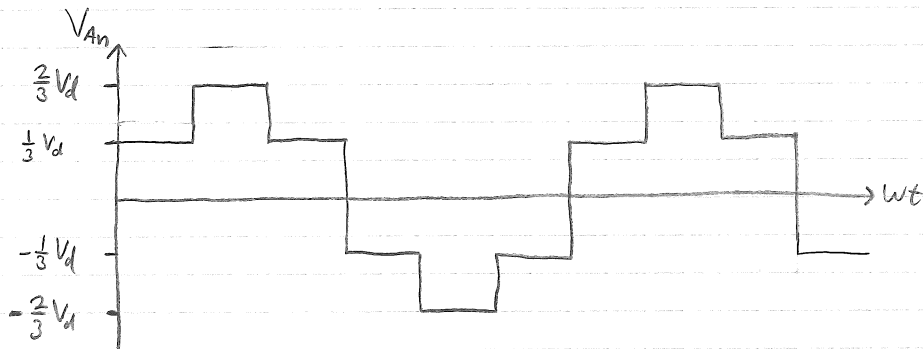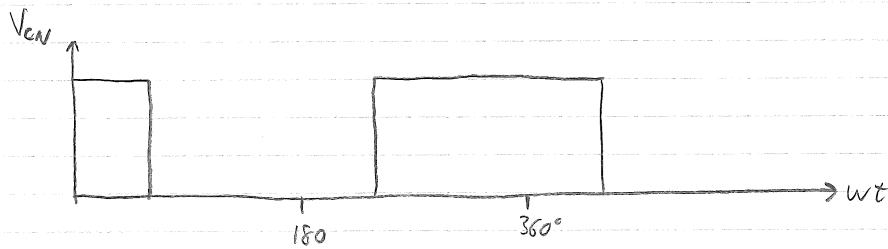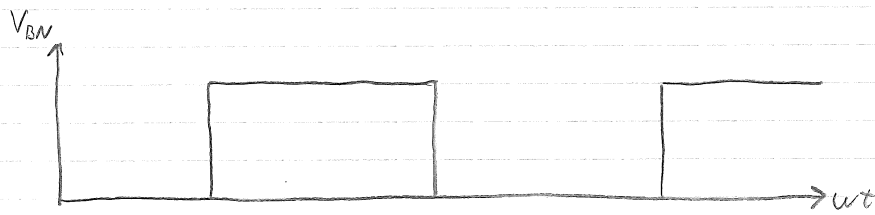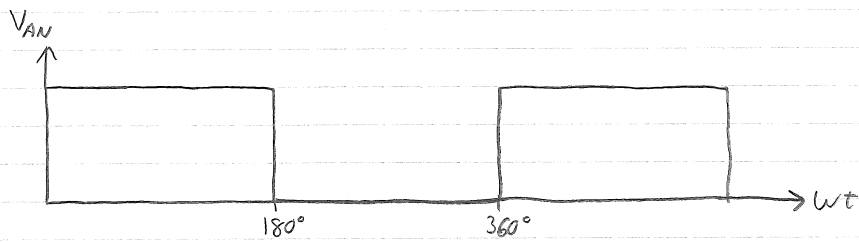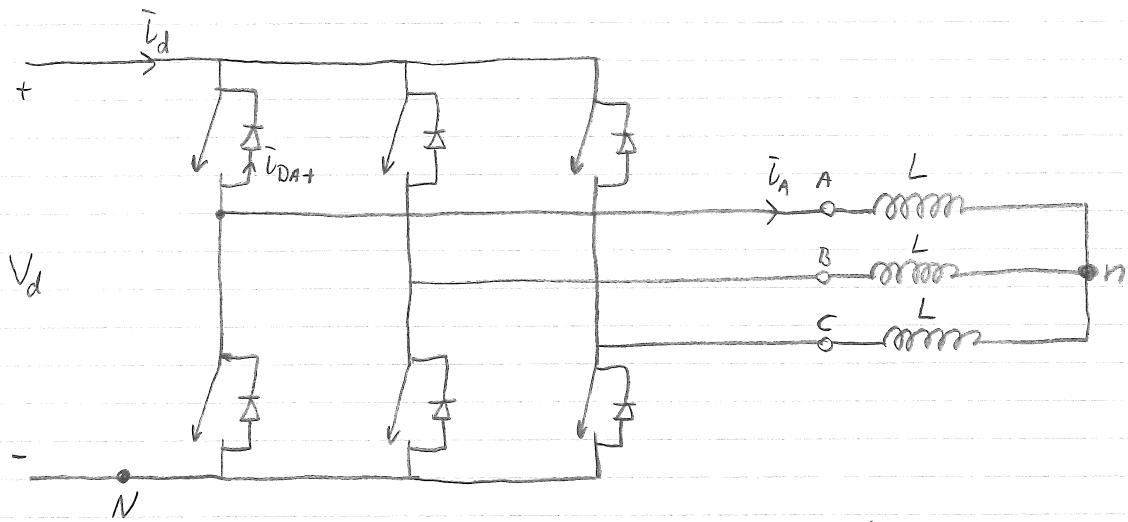


We have a three-phase balanced load $\Rightarrow$

$$V_{An} = \frac{2}{3}V_{AN} - \frac{1}{3}(V_{BN} + V_{CN})$$

2-(2)

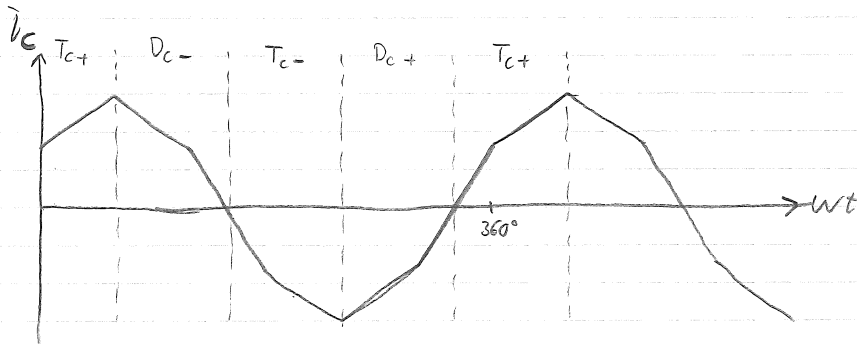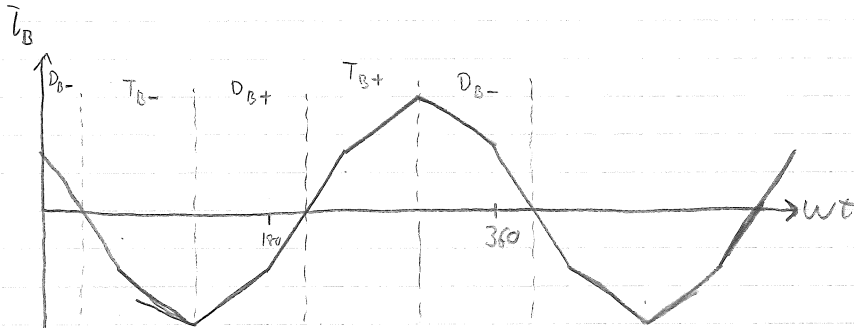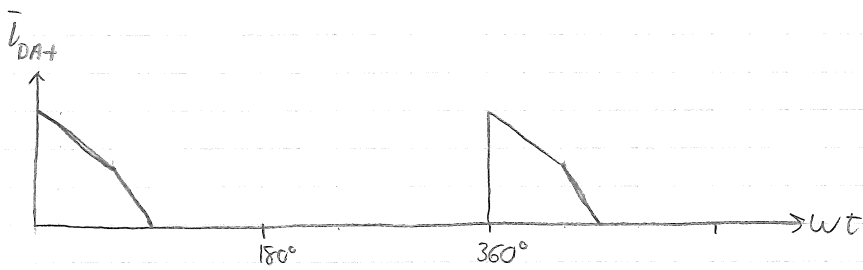
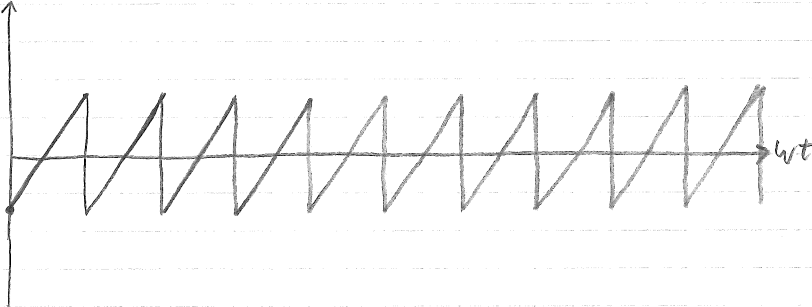
$$\bar{i}_d = \bar{i}_{TA+} - \bar{i}_{DA+} + \bar{i}_{TB+} - \bar{i}_{DB+} + \bar{i}_{TC+} - \bar{i}_{DC+}$$



We see that $I_d = 0$ as it should be since the load do not draw active power $P_{out} = 0 = P_{in} = V_d \cdot I_d$