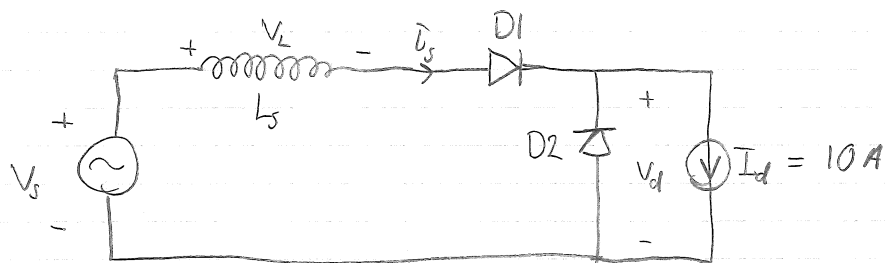



5-5

1-(4)



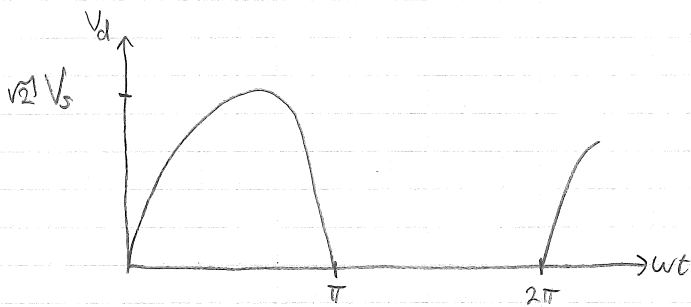a) $V_s = 120V$ at $60Hz$ $L_s = 0$

When $\begin{cases} V_s > 0 & D1 \text{ will conduct and } D2 \text{ will block} \\ V_s < 0 & D1 \text{ will block and } D2 \text{ will conduct} \end{cases} \Rightarrow$




$$V_d = \frac{1}{2\pi} \int_0^{2\pi} V_d(\omega t) d\omega t = \frac{1}{2\pi} \int_0^{\pi} \sqrt{2} V_s \sin(\omega t) d\omega t = \frac{\sqrt{2} V_s}{2\pi} [-\cos(\omega t)]_0^{\pi} =$$

$$= \frac{\sqrt{2} \cdot 2 V_s}{2\pi} = \frac{\sqrt{2}}{\pi} V_s = \frac{\sqrt{2}}{\pi} 120 = \underline{\underline{54V}}$$

$$P_d = V_d I_d = 54 \cdot 10 = \underline{\underline{540W}}$$

b) $V_s = 120V$ at $60Hz$ $L_s = 5mH$

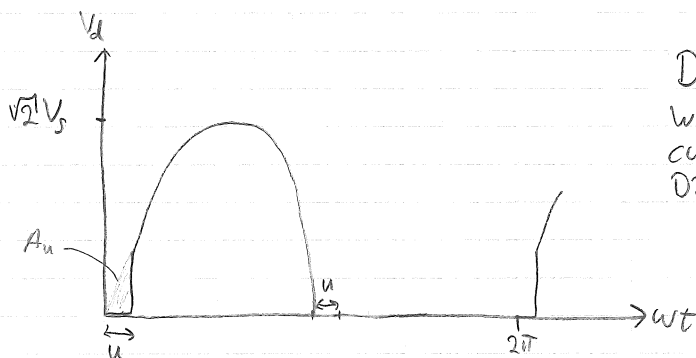


Due to the inductance L_s it will take some time to commutate the current from D1 to D2 and from D2 to D1.

As we can notice from the figure: When we should commutate the current from D2 to D1 ($\omega t = 0$) both D1 and D2 will conduct the current for a while $\Rightarrow$

2-(4)

During the commutation interval we can draw the circuit as:

$$0 < \omega t \leq \alpha$$

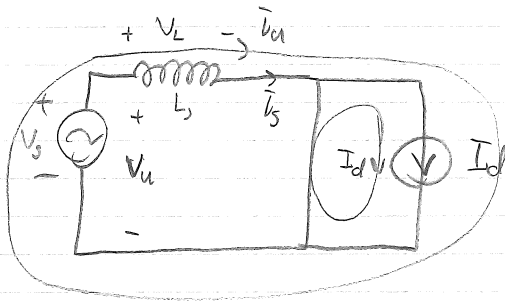

We see that when $i_s = i_u$ is equal to I_d the commutation is finished

$$\left. \begin{aligned} i_u &= i_s \\ V_u &= V_s = V_L \end{aligned} \right\} \Rightarrow$$

$V_L = L \frac{di_u}{dt}$ multiply both sides with $d(\omega t)$ and integrate over the commutation interval $\Rightarrow$

$$\omega L \int_0^{I_d} di_u = \int_0^{\alpha} V_L(\omega t) d(\omega t) = \int_0^{\alpha} \sqrt{2} V_s \sin(\omega t) d(\omega t) = A_u \Rightarrow$$

$$A_u = \omega L I_d = \sqrt{2} V_s [-\cos(\omega t)]_0^{\alpha} = \sqrt{2} V_s (1 - \cos(\alpha)) \Rightarrow$$

$$\cos(\alpha) = 1 - \frac{\omega L I_d}{\sqrt{2} V_s} = 1 - \frac{2\pi \cdot 60 \cdot 5 \cdot 10^{-3} \cdot 10}{\sqrt{2} \cdot 120} = 0,889 \Rightarrow$$

$$\alpha = 27,26^\circ$$


As we see the commutation from D1 to D2 is similar to the commutation from D2 to D1 and therefore the commutation angle is the same.

For the average output voltage V_d we calculate it in the same way as for problem a) but we subtract the area A_u from the integral to compensate for what we missed $\Rightarrow$


$$\begin{aligned} V_d &= \frac{1}{2\pi} \left(\int_0^{\pi} \sqrt{2} V_s \sin(\omega t) d(\omega t) - A_u \right) = \frac{1}{2\pi} (\sqrt{2} 2 V_s - \omega L I_d) = \\ &= \frac{\sqrt{2} V_s - 0,889 \omega L I_d}{\pi} = \frac{\sqrt{2} 120 - \frac{\pi \cdot 60 \cdot 5 \cdot 10^{-3} \cdot 10}{\pi}}{\pi} = 51 V \end{aligned}$$

$$P_d = V_d I_d = 51 \cdot 10 = 510 W$$

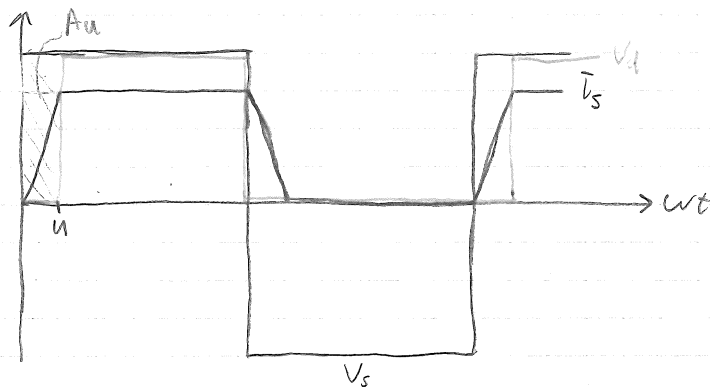c) V_s is a 60 Hz square wave form with 200V amplitude 3-(4)



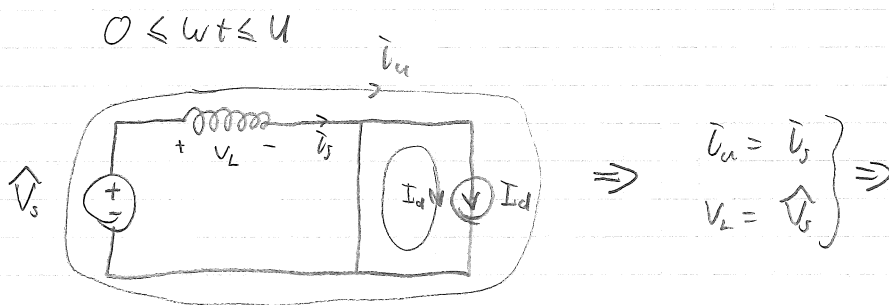During the commutation from D2 to D1 we can draw the circuit as



$$V_L = \hat{V}_s = L_s \frac{di_u}{dt} = L_s \frac{d\bar{i}_u}{dt} \quad \text{multiply with } d(\omega t) \text{ and integrate both sides over the commutation interval } \Rightarrow$$

$$\omega L \int_0^{\bar{I}_d} d\bar{i}_u = \int_0^{\mu} V_L(\omega t) d(\omega t) = \int_0^{\mu} \hat{V}_s d(\omega t) = A_u \Rightarrow$$

$$A_u = \omega L I_d = \hat{V}_s \mu \Rightarrow$$

$$\mu = \frac{\omega L I_d}{\hat{V}_s} = \frac{2\pi 60 \cdot 5 \cdot 10^{-3} \cdot 10}{200} = 0,0942 \text{ rad} = \underline{\underline{5,4^\circ}}$$


In the same way as before

$$V_d = \frac{1}{2\pi} \int_{\mu}^{\pi} \hat{V}_s d(\omega t) = \frac{\pi - \mu}{2\pi} \hat{V}_s = \frac{\pi - 0,0942}{2\pi} 200 = 97V$$

$$P_d = V_d I_d = 97 \cdot 10 = 970W$$

d)

4-(4)

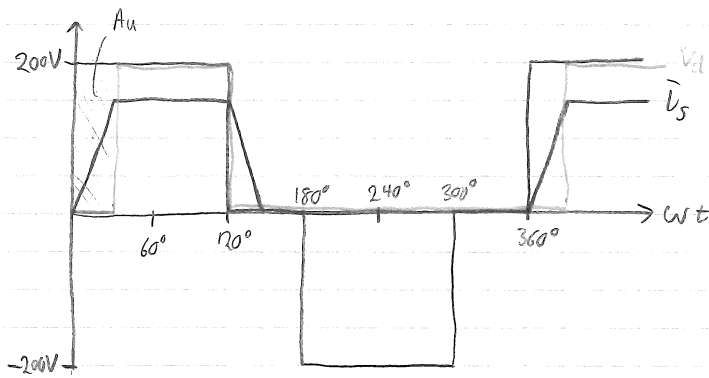

Since we have the same inductance $L_s = 5 \text{ mH}$ and the same peak value of the pulse waveform as for the square-wave in problem c) the commutation angle μ will be the same $\Rightarrow$





$$\underline{\underline{\mu = \frac{\omega L I_d}{V_s} = 5,4^\circ}}$$

The area A_u will also be the same $\Rightarrow A_u = \omega L I_d \Rightarrow$

$$\underline{\underline{V_d = \frac{1}{2\pi} \int_{\mu}^{\frac{2\pi}{3}} V_s d(\omega t) = \frac{\frac{2\pi}{3} - \mu}{2\pi} V_s = \frac{V_s}{3} - \frac{\omega L I_d}{2\pi} = \frac{200}{3} - \frac{2\pi \cdot 60 \cdot 5 \cdot 10^{-3} \cdot 10}{2\pi} = 63,7 \text{ V}}}$$

$$\underline{\underline{P_d = V_d I_d = 63,7 \cdot 10 = 637 \text{ W}}}$$

5-6

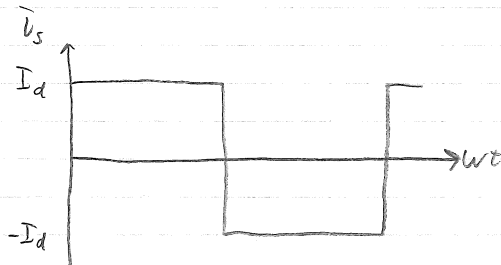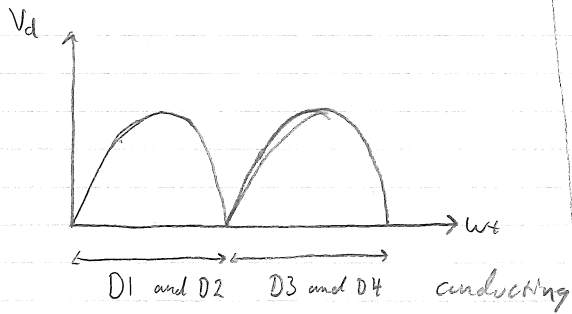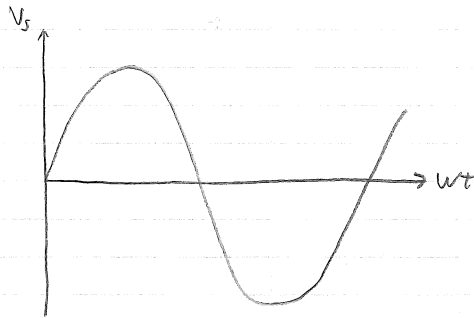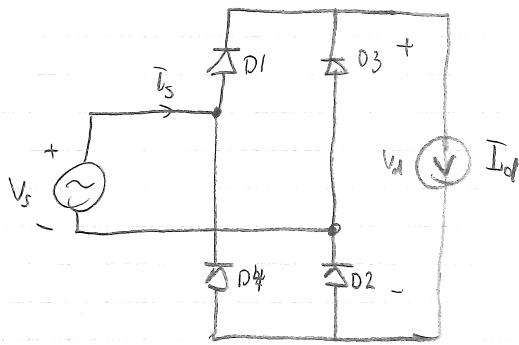

from the $\bar{I}_s$ plot we see that the average current through each diode can be calculated by

$$\begin{aligned} \underline{I_{diode, AVG}} &= \frac{1}{2\pi} \int_0^{\pi} \bar{I}_s(wt) dw = \\ &= \frac{\pi-0}{2\pi} I_d = \underline{\underline{\frac{1}{2} I_d}} \end{aligned}$$


and the rms

$$\begin{aligned} \underline{I_{diode, RMS}} &= \sqrt{\frac{1}{2\pi} \int_0^{\pi} \bar{I}_s^2(wt) dw} = \\ &= \sqrt{\frac{\pi-0}{2\pi} I_d^2} = \underline{\underline{\frac{1}{\sqrt{2}} I_d}} \end{aligned}$$

5-8



$V_s = 120V$ at $60Hz$ $L_s = 1mH$ and $I_d = 10A$

1-(2)

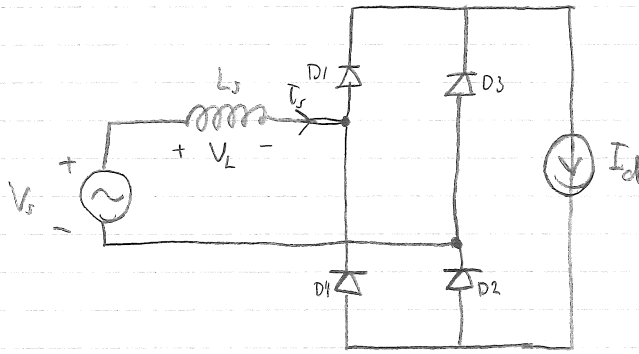


We start at a time somewhat smaller than zero. At this time we have a negative voltage V_s and a negative current $I_s = -I_d$ and Diode D_3 and D_4 are conducting.

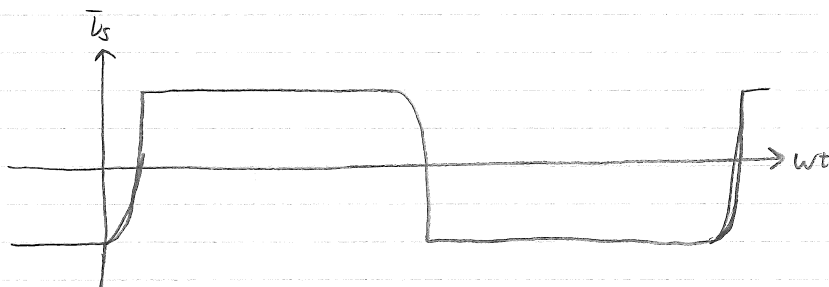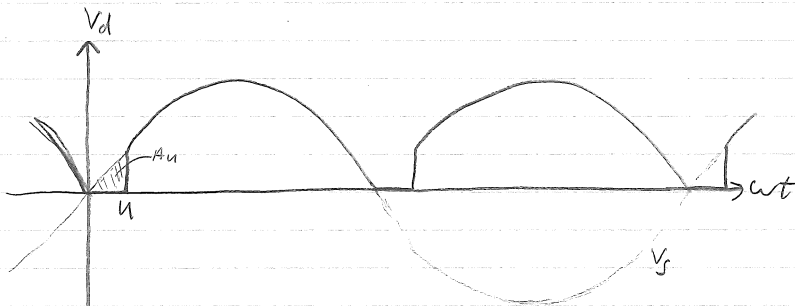After we have passed $\omega t = 0$ then we have a positive voltage V_s which means that diode D_1 and D_2 will conduct but due to the inductance L_s we will still have a negative current I_s and this gives that diode D_3 and D_4 are still conducting $\Rightarrow$ All four diodes are conducting.



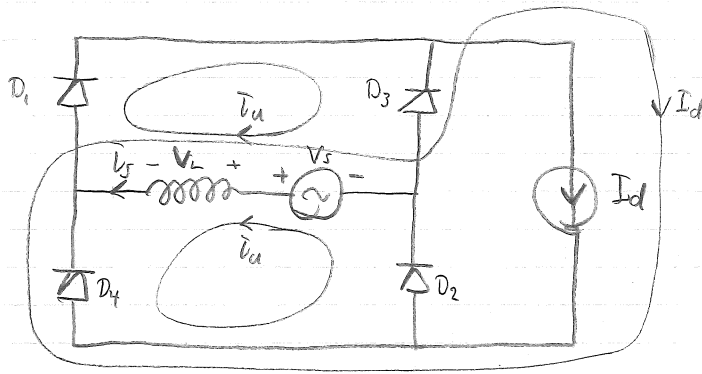During the commutation we can draw the circuit as 2-(2)
 $0 \leq \omega t \leq \alpha$



$$\Rightarrow \left. \begin{aligned} I_{D1} &= I_{D2} = \bar{i}_u \\ I_{D3} &= I_{D4} = I_d - \bar{i}_u \\ I_s &= -I_d + 2\bar{i}_u \\ V_L &= V_s \end{aligned} \right\} \text{ when } \bar{i}_u = I_d \text{ then the commutation is finished}$$

$$V_L = V_s = L_s \frac{d\bar{i}_s}{dt} \quad \text{multiply with } d(\omega t) \text{ and integrate } \Rightarrow$$

$$\omega L_s \int_{-I_d}^{I_d} d\bar{i}_s = \int_0^{\alpha} V_s(\omega t) d(\omega t) = \int_0^{\alpha} \sqrt{2} V_s \sin(\omega t) d(\omega t) = A_u \Rightarrow$$

$$A_u = 2\omega L_s I_d = \sqrt{2} V_s (1 - \cos(\alpha)) \Rightarrow$$

$$\cos(\alpha) = 1 - \frac{\sqrt{2} \omega L_s I_d}{V_s} = 1 - \frac{\sqrt{2} 2\pi 60 \cdot 10^{-3} \cdot 10}{120} = 0,9556 \Rightarrow$$

$$\alpha = 17,14^\circ$$

$$\underline{V_d} = \frac{1}{\pi} \left(\int_0^{\pi} \sqrt{2} V_s \sin(\omega t) d\omega t - A_u \right) = \frac{1}{\pi} (2\sqrt{2} V_s - 2\omega L_s I_d) \Rightarrow$$

$$V_d = \frac{2\sqrt{2} V_s - \omega L_s I_d}{\pi} = \frac{2\sqrt{2} 120 - 2\pi 60 \cdot 10^{-3} \cdot 10}{\pi} = \underline{\underline{105,6 V}}$$

$$\underline{P_d} = V_d I_d = 105,6 \cdot 10 = \underline{\underline{1056 W}}$$



$$\underline{\underline{\Delta V_d}} = 1 - \frac{V_d}{V_{d, L_s=0}} = 1 - \frac{105,6}{\frac{2\sqrt{2}}{\pi} V_s} = 1 - \frac{105,6}{0,9 \cdot 120} = \underline{\underline{2,22\%}}$$

5-11

$V_s = 120 \text{ V}$ at 60 Hz $L_s = 1 \text{ mH}$ $V_d = 150 \text{ V}$

1-(3)

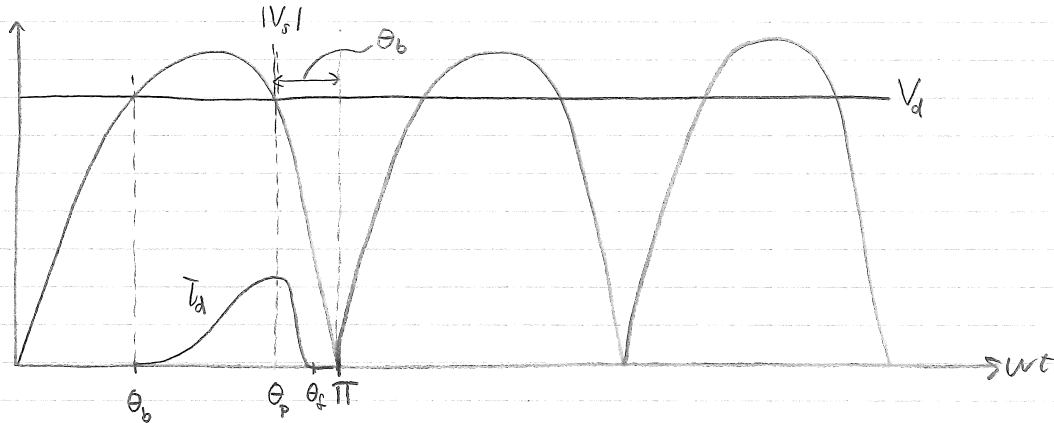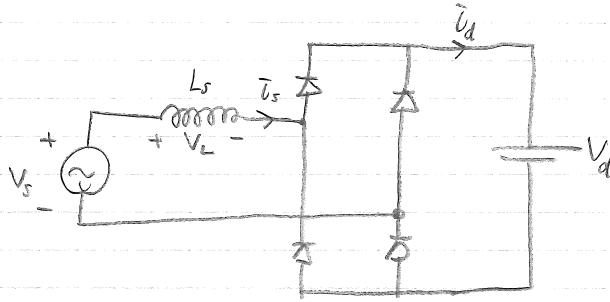Calculate $\bar{i}_d$ and indicate θ_b θ_r and $I_{d, \text{peak}}$ $I_{d, \text{avg}}$



From the figure we see that:

$$V_d = \sqrt{2} V_s \sin(\theta_b) \Rightarrow \sin(\theta_b) = \frac{V_d}{\sqrt{2} V_s} = \frac{150}{\sqrt{2} 120} = 0,884 \Rightarrow$$

$$\theta_b = \underline{\underline{62,11^\circ}} = \underline{\underline{1,084 \text{ rad}}}$$

We also see that during the interval $\theta_b \leq \omega t \leq \theta_r$

$$V_L = V_s - V_d = L_s \frac{d\bar{i}_d}{dt} = L_s \frac{d\bar{i}_d}{dt} \quad \text{Multiplying with } d(\omega t) \text{ and integrating gives}$$

$$\omega L_s \int_0^{\bar{i}_d(\theta)} d\bar{i}_d = \int_{\theta_b}^{\theta} (\sqrt{2} V_s \sin(\omega t) - V_d) d(\omega t) \Rightarrow$$

$$\bar{i}_d(\theta) = \frac{1}{\omega L_s} \int_{\theta_b}^{\theta} (\sqrt{2} V_s \sin(\omega t) - V_d) d(\omega t) = \frac{1}{\omega L_s} [-\sqrt{2} V_s \cos(\omega t) - V_d \omega t]_{\theta_b}^{\theta} \Rightarrow$$


$$\bar{i}_d(\theta) = \frac{1}{\omega L_s} (\sqrt{2} V_s \cos(\theta_b) - \sqrt{2} V_s \cos(\theta) - V_d (\theta - \theta_b)) =$$

$$= 641,9 - 450,2 \cos(\theta) - 397,9 \theta$$

5-11

2-(3)

$\theta_c = 2.556$

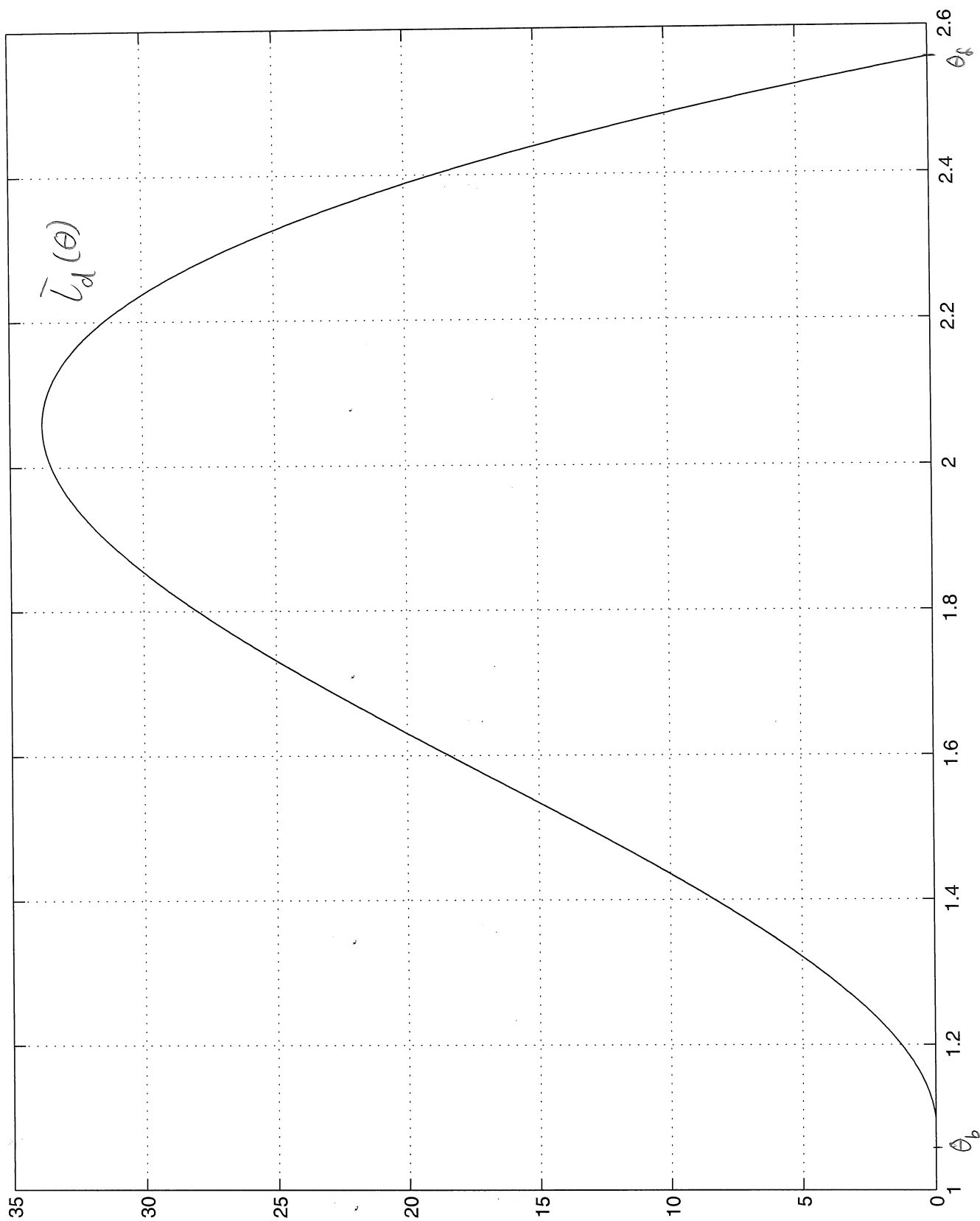

$$\underline{\underline{I_{d, peak}}} = I_d(\pi - \theta_b) = I_d(2,058) = 641,9 - 450,2 \cos(2,058) - 397,9 \cdot 2,058 =$$

$$= \underline{\underline{33,8 A}}$$

From the figure we see that

$$I_d(\theta_f) = 0 = 641,9 - 450,2 \cos(\theta_f) - 397,9 \cdot \theta_f \Rightarrow$$

$$\cos(\theta_f) + 0,884 \theta_f = 1,426$$

The solution to this equation we must find numerically

$$\underline{\underline{\theta_f = 2,556 \text{ rad}}}$$


$$\underline{\underline{I_{d, AVG}}} = \frac{1}{\pi} \int_{\theta_b}^{\theta_f} 641,9 - 450,2 \cos(\theta) - 397,9 \theta \, d\theta =$$

$$= \frac{1}{\pi} \left[641,9 \theta - 450,2 \sin(\theta) - \frac{397,9}{2} \theta^2 \right]_{1,084}^{2,556} =$$

$$= \frac{92,106 - 64,139}{\pi} = \underline{\underline{8,9 A}}$$

5-26

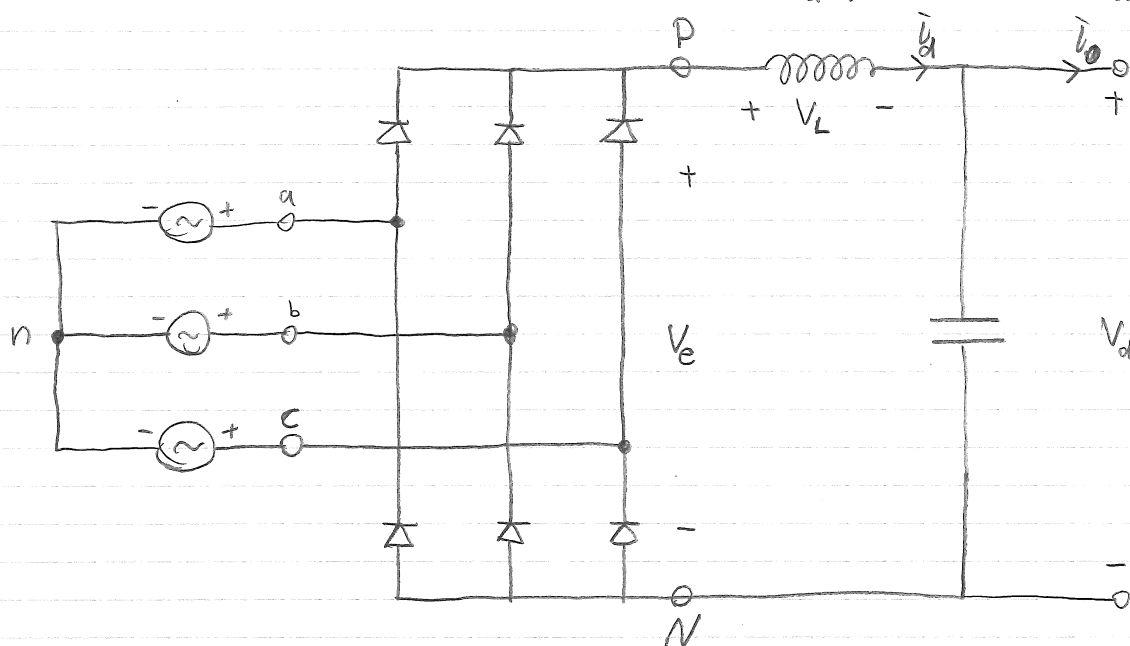Calculate the minimum L_d in terms of V_{LL} , ω , I_d that will result in a continuous $\bar{i}_d$, assume $v_d = V_d$




We know that the average of the inductor voltage must be zero in steady-state $\Rightarrow V_d = V_{e,AVG}$

From the figure on the next page we see that

$$V_{e,AVG} = 2 \frac{3}{\pi} \int_0^{\frac{\pi}{6}} \sqrt{2} V_{LL} \cos(\omega t) d\omega t = 2 \frac{3}{\pi} \sqrt{2} V_{LL} [\sin(\omega t)]_0^{\frac{\pi}{6}} = \frac{2 \cdot 3 \cdot \sqrt{2}}{\pi} \frac{1}{2} V_{LL} = \frac{3\sqrt{2}}{\pi} V_{LL} = 1.35 V_{LL} \Rightarrow$$

$$V_d = \frac{3\sqrt{2}}{\pi} V_{LL} \Rightarrow V_L(\omega t) = V_e(\omega t) - \frac{3\sqrt{2}}{\pi} V_{LL}$$

At the boudner off CCM

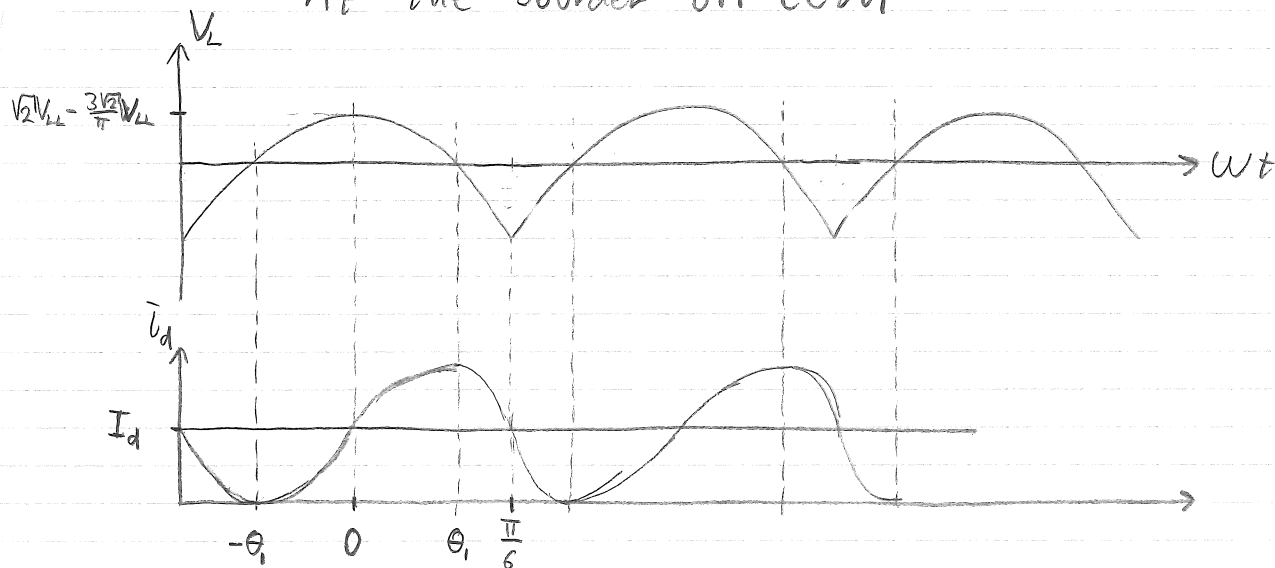

5-26

$$V_L(\omega t) = \sqrt{2} V_{LL} \cos(\omega t) - \frac{3\sqrt{2}}{\pi} V_{LL} = L_d \frac{d\bar{i}_d}{dt} \quad -\frac{\pi}{6} \leq \omega t \leq \frac{\pi}{6}$$

multiply with $d(\omega t)$ and integrate from $-\frac{\pi}{6}$ to $\theta \Rightarrow$

$$\omega L_d \int_{\bar{i}_d(-\frac{\pi}{6})}^{\bar{i}_d(\theta)} d\bar{i}_d = \omega L_d (\bar{i}_d(\theta) - \bar{i}_d(-\frac{\pi}{6})) = \int_{-\frac{\pi}{6}}^{\theta} \left(\sqrt{2} V_{LL} \cos(\omega t) - \frac{3\sqrt{2}}{\pi} V_{LL} \right) d(\omega t) \Rightarrow$$

$$\bar{i}_d(\theta) = \bar{i}_d(-\frac{\pi}{6}) + \frac{1}{\omega L_d} \left(\sqrt{2} V_{LL} \sin(\theta) - \frac{3\sqrt{2}}{\pi} V_{LL} \theta - \sqrt{2} V_{LL} \frac{1}{2} - \frac{3\sqrt{2}}{\pi} V_{LL} \frac{\pi}{6} \right)$$

$$\bar{i}_d(\theta) = \frac{\sqrt{2} V_{LL}}{\omega L_d} \left(\sin(\theta) - \frac{3}{\pi} \theta + k \right) \quad \text{where } k \text{ is a constant}$$

from the figure we notice that

$$\bar{i}_d(-\theta_1) = 0 \quad \text{and that} \quad \sqrt{2} V_{LL} \cos(\theta_1) = \frac{3\sqrt{2}}{\pi} V_{LL} \Rightarrow$$

$$\cos(\theta_1) = \frac{3}{\pi} \Rightarrow \theta_1 = 0,301 \text{ rad} \Rightarrow$$

$$\bar{i}_d(-0,301) = 0 = \frac{\sqrt{2} V_{LL}}{\omega L_d} \left(\sin(-0,301) + \frac{3}{\pi} 0,301 + k \right) \Rightarrow$$

$$k = -\sin(-0,301) - \frac{3}{\pi} 0,301 = 0,00904 \Rightarrow$$

$$\bar{i}_d(\theta) = \frac{\sqrt{2} V_{LL}}{\omega L_d} \left(\sin(\theta) + \frac{3}{\pi} \theta + 0,00904 \right) \quad -\frac{\pi}{6} \leq \theta \leq \frac{\pi}{6}$$

$$I_d = \frac{3}{\pi} \int_{-\frac{\pi}{6}}^{\frac{\pi}{6}} \bar{i}_d(\theta) d\theta = \frac{3}{\pi} \int_{-\frac{\pi}{6}}^{\frac{\pi}{6}} \frac{\sqrt{2} V_{LL}}{\omega L_d} \left(\sin(\theta) + \frac{3}{\pi} \theta + 0,00904 \right) d\theta =$$

$$= \frac{3}{\pi} \frac{\sqrt{2} V_{LL}}{\omega L_d} \left[-\cos(\theta) + \frac{3}{2\pi} \theta^2 + 0,00904 \theta \right]_{-\frac{\pi}{6}}^{\frac{\pi}{6}} =$$

$$= \frac{3}{\pi} \frac{\sqrt{2} V_{LL}}{\omega L_d} 0,00904 \cdot 2 \frac{\pi}{6} = 0,00904 \frac{\sqrt{2} V_{LL}}{\omega L_d} = \frac{0,013 V_{LL}}{\omega L_d} \Rightarrow$$

By looking in the $\bar{i}_d$ plot we see that if we have a load current $I_o = I_d$ then if we decrease the inductance we will have a larger ripple $\Rightarrow$ discontinuous current and therefore the equation gives the minimum inductance value that guarantees CCM operation $\Rightarrow$

$$L_{\min} = \frac{0,013 V_{LL}}{\omega I_d}$$