

EDA322

Digital Design

Lecture 16:



Pipelining

Ioannis Sourdis


Outline of Lecture 16

- Pipelining
- Latency & Throughput
- Examples
 - Ripple carry adder
 - Microprocessor
 - Graphics
 - Network processing
- Load balancing
- Stalling

  
Two ways to make things faster: pipeline and parallel



Pipelines

 

More Like an Assembly Line

 

Analogy: doing laundry

- Doing laundry:

- Wash 
- Dry 
- Iron 

- Can we do any better?



colored



whites




sweaters




Pipelines

 - Like an assembly line – each pipeline stage does part of the work and passes the ‘workpiece’ to the next stage
- Example 1: Pipelined 32b Adder




Split into 4 8-bit adders

 



Split into stages

4 problems 'in process' at once

 


Pipeline Diagram


Illustrates pipeline timing

  


Movie

 


Cycle 1

 


Cycle 2

 

Cycle 3

 

Cycle 4

 


Latency and Throughput of a Pipeline

- Suppose before pipelining the delay of our 32b adder is 3200ps (100ps per bit) and this adder can do one problem each 3200ps for a *throughput* of $1/3200\text{ps} = 312$ Millions of operations (additions) per second (Mops)
- What is the delay (latency, t_{pipe}) and throughput (Θ) of the adder with pipelining?
Suppose $t_{\text{dCQ}} = 120\text{ps}$, $t_{\text{setup}} = 80\text{ps}$, (200ps Overhead)



$$t_{\text{pipe}} = n(t_{\text{stage}} + t_{\text{dCQ}} + t_s) = 4(800 + 200) = 4000$$

$$\Theta = 1/(t_{\text{stage}} + t_{\text{dCQ}} + t_s) = 1/1000 = 1\text{Gops}$$


Example 2: Processor Pipeline

 

Example 3: Graphics rendering pipeline

  

Example 4 – Packet Processing Pipeline

 

And each of these modules is internally pipelined

You get the idea. Lots of systems are organized this way.


Issues with pipelines

(all deal with time per stage)

- Load balance (across stages)
 - one stage takes longer to process each input than the others – becomes a ‘bottleneck’
 - Example
 - Rasterizing an ‘average’ triangle in a graphics pipeline takes more time than ‘lighting’ its vertices.
- Variable load (across data)
 - A given stage takes more time on some inputs than others
 - Example
 - The the time needed to rasterize a triangle is proportional to the number of fragments in the triangle. The average triangle may contain 20 fragments, but triangles range from 0 to over 1M
- Long latency
 - A stage may require a long latency operation (e.g., texture access)



Load Balancing Pipelines

 - Suppose transform takes 2 cycles and clip 4 cycles
- Clip is a 'bottleneck' pipeline stage
- Xform unit is busy only half the time





Load Balancing Solutions

1 – Parallel copies of slow unit

  



Load Balancing Solutions

2 – Split slow pipeline stage

  

When is it better to split? To copy?

Throughput and latency are the same

  


Variable load


Stage A always takes 10 cycles.

Stage B takes 5 or 15 cycles – averages 10 cycles

 Pipeline averages _____ cycles per element





S: stall
I: idle

 


Elastic Pipelines

  
A FIFO between stages decouples timing
Allows stages to operate at their 'average' speed




Variable Load

 

(a)

 


(b)

 


(c)

Timing of an elastic pipeline

 

Resource Sharing

 
Suppose two pipeline stages need to access the same memory



How would you set the priority on the arbiter?




Stalling a *rigid* pipeline

 A stall in any stage halts *all* stages upstream of the stall point *instantly* (on the next clock)




What if we stopped all stages, not just upstream stages?
How does the delay of this structure *scale* with the number of stages?

Stalling a *rigid* pipeline

   


Double Buffer


 
Add an extra buffer to each stage that is filled during the first cycle of a stall.



 
What is the logic equation for
“next_full”? “next_buf”?
“mux_sel”?





Double Buffering

  



Double Buffer Timing

 



Double Buffer Timing

  



Double Buffer Timing

  



Double Buffer Timing

  



Double Buffer Timing

  

Double Buffer Timing

  

Double Buffer Timing

  

Pipeline overview

- Divide large problem into *stages* assembly-line style
- Divide evenly or *load imbalance* will occur
 - Fix by splitting or copying *bottleneck* stage
- Variable load results in *stalls* and *idle* cycles on a rigid pipeline
 - Make pipeline *elastic* by adding FIFOs between key stages
- Rigid pipelines have no extra storage between stages
 - A *stall* on any stage halts all *upstream* stages
 - Hard to stop 100 stages at once
 - Make this scalable with double-buffering

Quiz- 18-1


<http://m.socrative.com/student/#joinRoom>

room number: **713113**

- If washing takes 30 min, drying takes 2 hours and ironing takes 1 hour, how fast can you prepare 3 portions of cloths if I pipeline?

- a. 7.5 h
- b. 4.5 h
- c. 10 h
- d. 10.5 h

- Answer:**

 

Summary

- Pipelining
- Latency & Throughput
- Examples
 - Ripple carry adder
 - Microprocessor
 - Graphics
 - Network processing
- Load balancing
- Stalling
- Reading:
 - Chapter 23
- Next Lecture:
 - Timing, Delay, Power