

EDA322

Digital Design

Lecture 2:
Logic Minimization, Adders

Ioannis Sourdis

Lecture 2 outline

- Boolean logic refresher
- Logic minimization
 - Karnaugh
- Adders
 - Ripple-carry,
 - Carry-select
 - Carry-Lookahead

Boolean Logic refresher

Boolean Algebra

- 1) $X \cdot 0 = 0$
- 2) $X \cdot 1 = X$
- 3) $X \cdot X = X$
- 4) $X \cdot \bar{X} = 0$
- 5) $X + 0 = X$
- 6) $X + 1 = 1$
- 7) $X + X = X$
- 8) $X + \bar{X} = 1$
- 9) $\bar{\bar{X}} = X$

$$10A) \quad X \cdot Y = Y \cdot X$$

$$10B) \quad X + Y = Y + X$$

} Commutative
Law

$$11A) \quad X(YZ) = (XY)Z$$

$$11B) \quad X + (Y + Z) = (X + Y) + Z$$

} Associative
Law

$$12A) \quad X(Y + Z) = XY + XZ$$

$$12B) \quad X + (YZ) = (X + Y)(X + Z)$$

$$12C) \quad (X + Y)(W + Z) = XW + XZ + YW + YZ$$

} Distributive
Law

$$13A) \quad X + \bar{X}Y = X + Y$$

$$13B) \quad \bar{X} + XY = \bar{X} + Y$$

$$13C) \quad X + \bar{X}\bar{Y} = X + \bar{Y}$$

$$13D) \quad \bar{X} + X\bar{Y} = \bar{X} + \bar{Y}$$

} Consensus
Theorem

$$14A) \quad \overline{X \cdot Y} = \bar{X} + \bar{Y}$$

$$14B) \quad \overline{\bar{X} + \bar{Y}} = \bar{X} \cdot \bar{Y}$$

} DeMorgan's Theorem


Book Notations

- For AND logic function:
 - Book uses $\wedge$ or $\&$
 - e.g., : $(a \wedge b)$ ($a \& b$)
 - We are used to $\bullet$
 - e.g., : $(a \bullet b)$
- For OR logic function:
 - Book uses $\vee$ or $|$
 - e.g., : $(a \vee b)$ ($a | b$)
 - We are used to $+$
 - e.g., : $(a + b)$
- For NOT logic function:
 - Book uses $\neg$ or $\sim$
 - e.g., : $(\neg a)$ ($\sim a$)
 - We are used to $'$ or $-$
 - e.g., : (a') ($\bar{a}$)
- For XOR logic function:
 - Book and we use $\oplus$
 - e.g., : $(a \oplus b)$

Algebraic Forms of Logic Functions


- ***Literal***: A variable, complemented or uncomplemented.
- ***Product***: Literals ANDed together.
- ***Sum***: Literals ORed together.
- ***SOP (Sum of Products)***:
 - ORing product terms
 - $f(A, B, C) = ABC + A'C + B'C$
- ***POS (Product of Sums)***:
 - ANDing sum terms
 - $f(A, B, C) = (A' + B' + C')(A + C')(B + C')$

de Morgan theorem

 

$$(a) \overline{x_1 x_2} = \bar{x}_1 + \bar{x}_2$$


 
The inversion of a product is the sum of the inverted variable





$$(b) \overline{x_1 + x_2} = \bar{x}_1 \bar{x}_2$$

The inversion of a sum is the product of the inverted variable


SoP

  


PoS

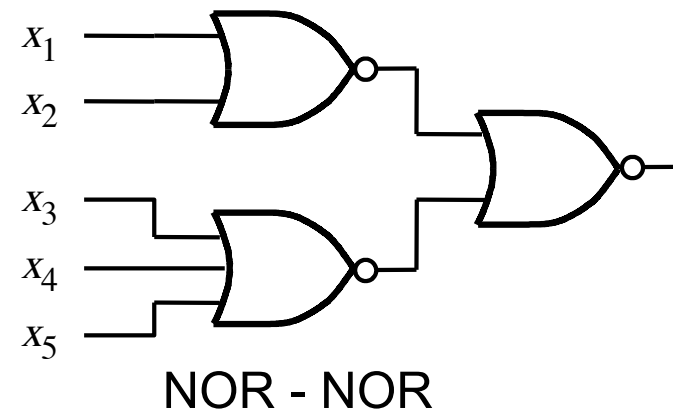 

The XOR gate

 

... is equivalent to ...

 

$$\mathbf{A \oplus B = A\bar{B} + \bar{A}B}$$

The XOR gate

Commutative Law

$$A \oplus B = B \oplus A$$

Associative Law

$$(A \oplus B) \oplus C = A \oplus (B \oplus C) = A \oplus B \oplus C$$

Distributive Law

$$(AB) \oplus (AC) = A(B \oplus C)$$

Algebraic Forms of Logic Functions

- A ***minterm*** is a product term in which all the variables appear exactly once either complemented or uncomplemented.
- ***Canonical Sum of Products (canonical SOP)***:
 - Represented as a sum of minterms only.
 - ***Example***: $f_1(A,B,C) = A'BC' + ABC' + A'BC + ABC$
 - Minterms of three variables:

Minterm	Minterm Code	Minterm Number
$A'B'C'$	000	m_0
$A'B'C$	001	m_1
$A'BC'$	010	m_2
$A'BC$	011	m_3
$AB'C'$	100	m_4
$AB'C$	101	m_5
ABC'	110	m_6
ABC	111	m_7

Algebraic Forms of Logic Functions

- A **maxterm** is a sum term in which all the variables appear exactly once either complemented or uncomplemented.
- **Canonical Product of Sums (canonical POS):**
 - Represented as a product of maxterms only.
 - **Example:** $f_2(A,B,C) = (A+B+C)(A+B+C')(A'+B+C)(A'+B+C')$
- Maxterms of three variables:

Maxterm	Maxterm Code	Maxterm Number
$A+B+C$	000	M_0
$A+B+C'$	001	M_1
$A+B'+C$	010	M_2
$A+B'+C'$	011	M_3
$A'+B+C$	100	M_4
$A'+B+C'$	101	M_5
$A'+B'+C$	110	M_6
$A'+B'+C'$	111	M_7

Canonical (Normal) Forms

SoP canonical form

$$F = \Sigma(1,3,5,6,7)$$

$$F = 001 \quad 011 \quad 101 \quad 110 \quad 111$$

$$F = A'B'C + A'BC + AB'C + ABC' + ABC$$

A	B	C	F	F'	#
0	0	0	0	1	0
0	0	1	1	0	1
0	1	0	0	1	2
0	1	1	1	0	3
1	0	0	0	1	4
1	0	1	1	0	5
1	1	0	1	0	6
1	1	1	1	0	7

$$F = \Pi(0,2,4)$$

PoS canonical form

$$F = (A + B + C) (A + B' + C) (A' + B + C)$$

$$F = 000 \quad 010 \quad 100$$

$$F' = A'B'C' + A'BC' + AB'C'$$

canonical form $\neq$ minimal form

Conversion between canonical forms

Relation between maxterms and minterms of a function

$$F(x,y,z) = \Sigma(1,3,5,6,7) = \Pi(0,2,4)$$

... and for the inverted function:

$$F'(x,y,z) = \Pi(1,3,5,6,7) = \Sigma(0,2,4)$$

Shannon's expansion theorem

- ***Shannon's expansion theorem***

(a). $f(x_1, x_2, \dots, x_n) = x_1 * f(1, x_2, \dots, x_n) + x_1' * f(0, x_2, \dots, x_n)$

(b). $f(x_1, x_2, \dots, x_n) = [x_1 + f(0, x_2, \dots, x_n)] [x_1' + f(1, x_2, \dots, x_n)]$

Example:

$$\begin{aligned} F(x_1, x_2, x_3) &= x_1x_2 + x_1x_3 + x_2x_3 \\ &= x_1'F(0, x_2, x_3) + x_1F(1, x_2, x_3) \\ &= x_1' (0x_2 + 0x_3 + x_2x_3) + x_1(1x_2 + 1x_3 + x_2x_3) \\ &= x_1' (x_2x_3) + x_1(x_2 + x_3 + x_2x_3) \\ &= x_1' (x_2x_3) + x_1(x_2 + x_3(1 + x_2)) \\ &= x_1' (x_2x_3) + x_1(x_2 + x_3) \end{aligned}$$

Derivation of Canonical Forms

- Derive canonical PoS or SoP using Boolean algebra.

- ***Shannon's expansion theorem***

$$(a). f(x_1, x_2, \dots, x_n) = x_1 * f(1, x_2, \dots, x_n) + x_1' * f(0, x_2, \dots, x_n)$$

$$(b). f(x_1, x_2, \dots, x_n) = [x_1 + f(0, x_2, \dots, x_n)] [x_1' + f(1, x_2, \dots, x_n)]$$

Convert a function to SoP (Two alternatives, **second is simpler!**)

1. Apply Shannon Theorem until you get sum of minterms
2. Get the function to a SoP form, as follows:
 - if a product of literals is a minterm, keep it
 - for every variable x_i that doesn't exist in a product we add $(x_i + x_i')$, e.g.:
 - $x_1 * x_2 = x_1 * x_2 * (x_3 + x_3') = x_1 * x_2 * x_3 + x_1 * x_2 * x_3'$
 - Continue and delete redundant products

Derivation of Canonical Forms

- Derive canonical PoS or SoP using Boolean algebra.

- ***Shannon's expansion theorem***

(a). $f(x_1, x_2, \dots, x_n) = x_1 * f(1, x_2, \dots, x_n) + x_1' * f(0, x_2, \dots, x_n)$

(b). $f(x_1, x_2, \dots, x_n) = [x_1 + f(0, x_2, \dots, x_n)] [x_1' + f(1, x_2, \dots, x_n)]$

- ***Example:*** $f(A,B,C) = AB + AC' + A'C$

– $f(A,B,C) = AB + AC' + A'C = A f(1,B,C) + A' f(0,B,C)$

$= A(1 \times B + 1 \times C' + 1' \times C) + A'(0 \times B + 0 \times C' + 0' \times C) = A(B + C') + A'C$

– $f(A,B,C) = A(B + C') + A'C = B[A(1+C') + A'C] + B'[A(0 + C') + A'C]$

$= B[A + A'C] + B'[AC' + A'C] = AB + A'BC + AB'C' + A'B'C$

– $f(A,B,C) = AB + A'BC + AB'C' + A'B'C$

$= C[AB + A'B \times 1 + AB' \times 1' + A'B' \times 1] + C'[AB + A'B \times 0 + AB' \times 0' + A'B' \times 0]$

$= ABC + A'BC + A'B'C + ABC' + AB'C'$

Derivation of Canonical Forms

- Derive canonical PoS or SoP using Boolean algebra.
- ***Shannon's expansion theorem***
 - (a). $f(x_1, x_2, \dots, x_n) = x_1 * f(1, x_2, \dots, x_n) + x_1' * f(0, x_2, \dots, x_n)$
 - (b). $f(x_1, x_2, \dots, x_n) = [x_1 + f(0, x_2, \dots, x_n)] [x_1' + f(1, x_2, \dots, x_n)]$
- ***Example:*** $f(A,B,C) = AB + AC' + A'C$
$$\begin{aligned} f(A,B,C) &= AB + AC' + A'C = \\ &= AB(C+C') + AC'(B+B') + A'C(B+B') \\ &= ABC + ABC' + ABC' + AB'C' + A'BC + A'B'C \\ &= ABC + ABC' + AB'C' + A'BC + A'B'C \end{aligned}$$

Logic Simplification

Karnaugh-diagram

		yz			
		00	01	11	10
wx	00				
	01		1	1	
	11				
	10				

$$\begin{aligned}W'XY'Z + W'XYZ &= \\(W'XZ)(Y'+Y) &= W'XZ\end{aligned}$$

Note: $(Y'+Y)=1$

Karnaugh of 4 variables

Minimize function $F = \sum m(0, 2, 7, 8, 14, 15) + d(3, 6, 9, 12, 13)$

		A			
CD\AB		00	01	11	10
C	00	1	0	X	1
	01	0	0	X	X
	11	X	1	1	0
	10	1	X	1	0

B

D

$$F = \cancel{AC'} + \cancel{A'C} + \cancel{BC} + \cancel{AB} + A'B'D' + B'C'D'$$

$$F = BC + A'B'D' + B'C'D'$$

$$F = A'C + AB + B'C'D'$$

		A			
		00	01	11	10
C	00	1	0	X	1
	01	0	0	X	X
	11	X	1	1	0
	10	1	X	1	0

B


D

		A			
		00	01	11	10
C	00	1	0	X	1
	01	0	0	X	X
	11	X	1	1	0
	10	1	X	1	0

B

D

Product of Sums (maxterms)

 


$$f = (x_3 + x_4)(x_2 + x_3)(\bar{x}_1 + \bar{x}_2 + \bar{x}_3 + \bar{x}_4)$$


**How would one
choose between
PoS and SoP?**

$$\text{POS } f(x_1, \dots, x_4) = \prod M(0, 1, 4, 8, 9, 12, 15).$$


Karnaugh of 5 variables

 

Minimizing multiple functions

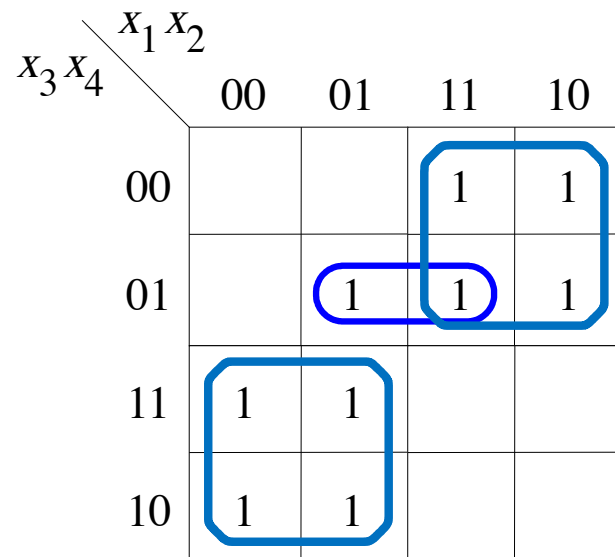

(a) Function f_1

 

(b) Function f_2


Minimizing multiple functions

$x_3 x_4 \backslash x_1 x_2$		$x_1 x_2$			
		00	01	11	10
$x_3 x_4$	00			1	1
	01		1	1	1
$x_3 x_4$	11	1	1		
	10	1	1		

(a) Function f_1

$x_3 x_4 \backslash x_1 x_2$		$x_1 x_2$			
		00	01	11	10
$x_3 x_4$	00			1	1
	01			1	1
	11	1	1	1	
	10	1	1		

(b) Function f_2

 

(c) Combined circuit for f_1 and f_2

Definition of terms

- A function F **covers** a function g , if it takes the value '1' when function g does.
- **Implicant**: a product of literals of a function f for which f gets the value '1'.
- **Prime implicant**: an implicant that cannot be covered by a more general (more reduced - meaning with fewer literals) implicant.
- **Essential prime implicant**: a prime implicant of function f that includes a minterm, not included by any other prime implicant of the function.

Examples to illustrate terms

	AB			
	00	01	11	10
CD 00	0	X	1	0
01	1	1	1	0
11	1	0	1	1
10	0	0	1	1

6 **prime implicants**:

$A'B'D$, BC' , AC , $A'C'D$, AB , $B'CD$

essential

minimum cover: $AC + BC' + A'B'D$

5 **prime implicants**:

BD , ABC' , ACD , $A'BC$, $A'C'D$

Essential prime implicants

minimum cover: 4 essential implicants

	AB			
	00	01	11	10
CD 00	0	0	1	0
01	1	1	1	0
11	0	1	1	1
10	0	1	0	0

D

B



From Boolean expressions to logic gates

- More than one way to map expressions to gates
 - e.g., $F = A' \cdot B' \cdot (C + D) = (A' \cdot (B' \cdot (C + D)))$

$$\frac{\overline{T2}}{T1}$$


VHDL:

`F <= not A and (not B and ( C or D ));`

  

Waveform view of logic functions

 
- Note how edges don't line up exactly
- It takes time for a gate to switch its output!




change in Y takes time to "propagate" through gates

Choosing different implementations of a function

A	B	C	Z
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

 

What is the difference?

 

- Delay
 - Number of gates in a row
- Area
 - fewer gates in total or
 - Smaller circuit
- Power?
- Tradeoffs:
 - More Area for lower delay
 - Higher Delay for lower power

Quiz 2-1

<http://m.socrative.com/student/#joinRoom>


room number: **713113**

- Q1: which is the number of minterm $AB'C$
- Q2: which is the number of maxterm $A+B'+C$
- Q3: What are the maxterms of $F(x_0, x_1, x_2) = \Sigma(0, 1, 2, 3, 4)$
- Q4: What are the minterms of F' if $F(x_0, x_1, x_2) = \Sigma(0, 1, 2, 3, 4)$
- Q5: Expand $F(x_0, x_1, x_2) = x_0 * x_1$ to its canonical SoP

Adders

Adders

Full-adder cell (FA) revisited:

 

a	b	cin	cout	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

		ab			
		00	01	11	10
cin	0				
	1				


cout

		ab			
		00	01	11	10
cin	0				
	1				

s


Boolean functions for the full adder
 
$$\begin{aligned} R &= AB'Ci_n' + A'BCi_n' + ABCi_n + A'B'Ci_n \\ &= Ci_n'(AB' + A'B) + Ci_n(AB + A'B') \\ &= Ci_n'(AB' + A'B) + Ci_n(AB' + A'B)' \\ &= Ci_n'(A \text{ xor } B) + Ci_n(A \text{ xor } B)' \\ &= Ci_n \text{ xor } (A \text{ xor } B) \end{aligned}$$



Critical path:
The longest path from an input to an output
 
$$\begin{aligned} Cout &= AB'Ci_n + A'BCi_n + AB \\ &= Ci_n(AB' + A'B) + AB \\ &= Ci_n(A \text{ xor } B) + AB \end{aligned}$$




Ripple-Carry Adder


- Each cell:

$$r_i = a_i \text{ XOR } b_i \text{ XOR } c_{in}$$
 
$$c_{out} = c_{in}(a_i \text{ XOR } b_i) + a_i b_i$$




- 4-bit adder:

 

- What about subtraction?

“Full adder cell”

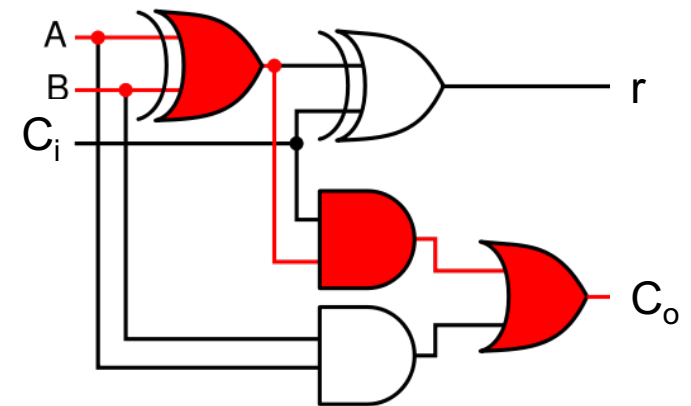


Subtractors

$$A - B = A + (-B)$$


How do we form $-B$?

1. complement B
2. add 1

 

Adders (cont.)

Ripple Adder

 


Ripple adder is inherently slow because, in general s_7 must wait for c_7 which must wait for c_6 ...

T is $O(n)$, **$Cost$** is $O(n)$

What's the
Critical path
here?


Critical Path Through a Ripple-Carry Adder
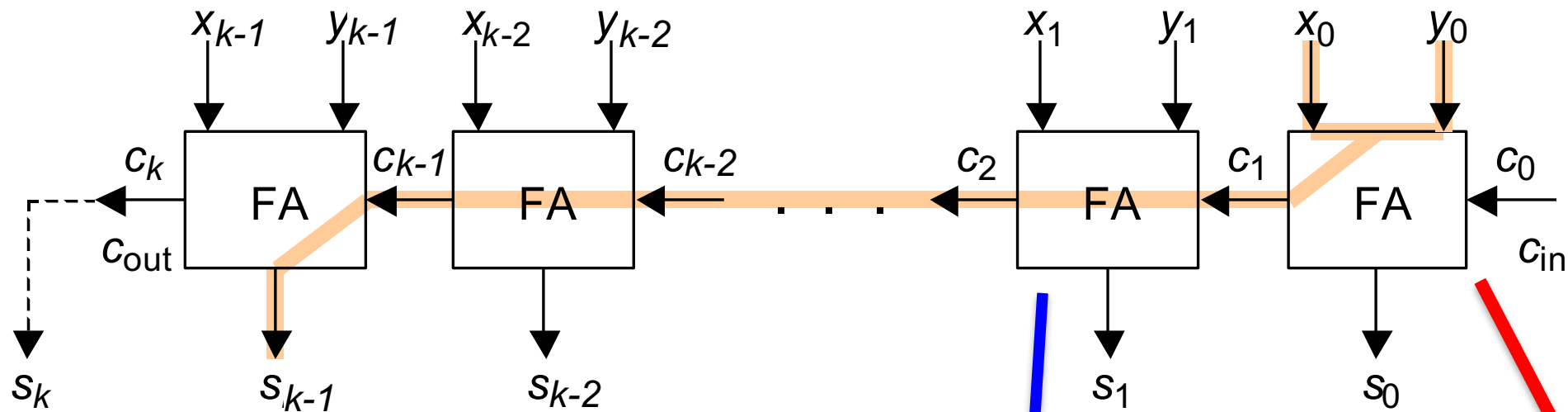
$$T_{\text{ripple-add}} = T_{\text{FA}}(x, y \rightarrow c_{\text{out}}) + (k - 2) \times T_{\text{FA}}(c_{\text{in}} \rightarrow c_{\text{out}}) + T_{\text{FA}}(c_{\text{in}} \rightarrow s)$$




*How do we make it faster,
perhaps with more cost?*

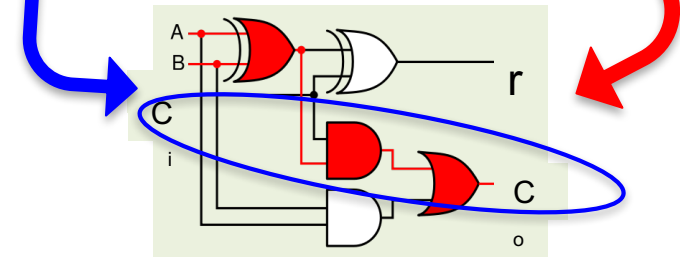Mechanical adder: <https://youtu.be/GcDshWmhF4A>



Carry Select Adder

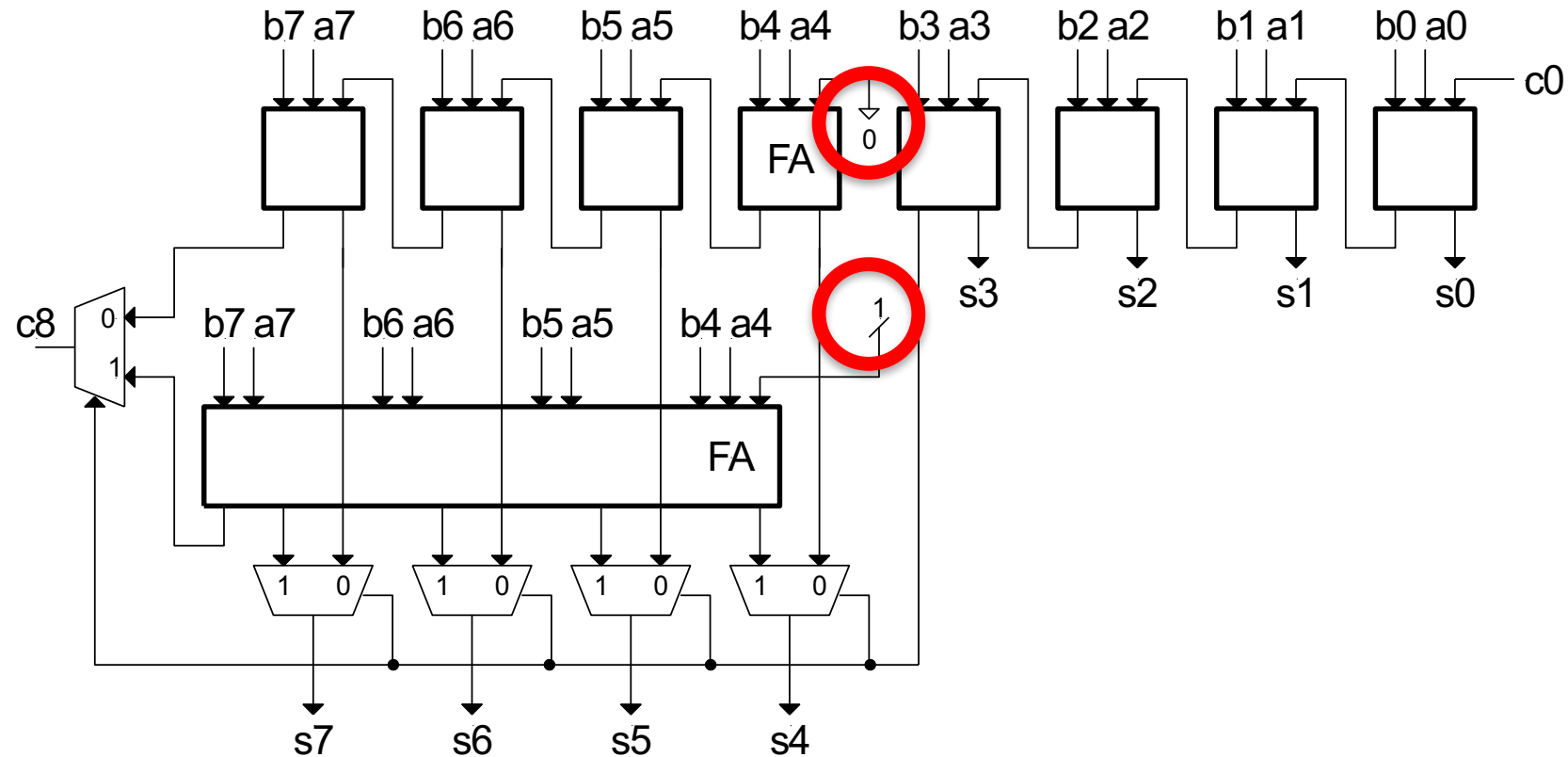


$$T = T_{\text{ripple_adder}} / 2 + T_{\text{MUX}}$$

$$\text{COST} = 1.5 * \text{COST}_{\text{ripple_adder}} + (n+1) * \text{COST}_{\text{MUX}}$$

Carry Select Adder

 - Extending Carry-select to multiple blocks




- What is the optimal # of blocks and # of bits/block?
 - If # blocks too large delay dominated by total mux delay
 - If # blocks too small delay dominated by adder delay

$\sqrt{N}$ stages of $\sqrt{N}$ bits


T is $O(\sqrt{N})$,
Cost $\approx 2 \cdot \text{ripple} + \text{muxes}$

Carry Select Adder

 

- $T_{\text{total}} = (2 \cdot \sqrt{N} - 1) T_{\text{FA}}$
 - assuming $T_{\text{FA}} = T_{\text{MUX}}$
- For ripple adder $T_{\text{total}} = N T_{\text{FA}}$
- Is $\sqrt{N}$ really the optimum?
 - From right to left increase size of each block to better match delays
 - E.g.: 16-bit adder, use block sizes [5 4 3 2 2]
 - E.g.: 64-bit adder, use block sizes [13 12 11 10 9 8 7]

Carry Select Adder variable size blocks

 

16-bit adder Carry select adder with variable block sizes [5 4 3 2 2]

Carry Look-ahead Adders

- In general, for n-bit addition best we can achieve is
delay $O(\log(n))$
- How do we arrange this? (think trees)
- First, reformulate basic adder stage:

a	b	c_i	c_{i+1}	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Diagram illustrating the basic adder stage. The table shows the relationship between inputs a, b, and carry-in c_i , and the resulting carry-out c_{i+1} and sum s. A blue box highlights the rows where $c_i = 0$ and $c_{i+1} = 0$ (rows 1-4), and an orange box highlights the rows where $c_i = 1$ and $c_{i+1} = 1$ (rows 7-8). A blue arrow labeled 'p' points to the first row of the blue box, and an orange arrow labeled 'g' points to the first row of the orange box.

carry “propagate”

$$p_i = a_i \oplus b_i$$

Exactly one of the 2 inputs is 1,
then propagate the carry you
received from the previous stage

carry “generate”

$$g_i = a_i b_i$$

If both inputs are 1, then no
matter what carry-in you
received, generate a carry

$$c_{i+1} = g_i + p_i c_i$$


Carry-out is one
if you generate a carry
or you have a carry-in
to propagate

$$s_i = p_i \oplus c_i$$

Result is 1 either when
exactly 1 of the
Inputs (a, b) is 1
(carry-propagate)
(exclusive) or
have a carry-in

Carry Look-ahead Adders

- Ripple adder using p and g signals:

 

- So far, no advantage over ripple adder: $T \propto N$

Carry Look-ahead Adders

- Expand carries:

$$c_0$$

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 c_1 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

$$c_3 = g_2 + p_2 c_2 = g_2 + p_2 g_1 + p_1 p_2 g_0 + p_2 p_1 p_0 c_0$$

$$c_4 = g_3 + p_3 c_3 = g_3 + p_3 g_2 + p_3 p_2 g_1 + \dots$$

.


.

.

- Why not implement these equations directly to avoid ripple delay?
 - Lots of gates. Redundancies (full tree for each).
 - Gate with high # of inputs.
- Let's reorganize the equations.

Carry Look-ahead Adders

 - “Group” propagate and generate signals:




- P true if the group as a whole propagates a carry to c_{out}
- G true if the group as a whole generates a carry

$$C_{out} = G + PC_{in}$$

- Group P and G can be generated hierarchically.

Carry Look-ahead Adders

 


9-bit Example of hierarchically generated P and G signals:

$$P = P_a P_b P_c$$


$$G = G_c + P_c G_b + P_b P_c G_a$$

$$c_9 = G + P c_0$$

 
8-bit Carry Look-ahead Adder with 2-input gates.



 8-bit Carry Look-ahead Adder with 2-input gates.



Carry Look-ahead adder

 

Quiz 2-2

<http://m.socrative.com/student/#joinRoom>

room number: **713113**

- Q1: a 8-bit ripple carry adder compared to a 4-bit ripple carry adder has:
 - 50% more area
 - 2 times more delay
- Q2: when adding 111 and 101 in a ripple carry adder, how many carries are generated?
- Q3: What is the delay and area of a 8-bit carry select adder of 2 blocks (each block 4-bits). Consider that:
 - FA delay=1, MUX delay= 1
 - FA area = 1 and MUX area = 1
- Q4: What is the delay of a carry-lookahead adder:
 - Linear, $O(n)$?
 - $O(\sqrt{N})$?
 - $O(\log N)$?

Summary of Lecture 2

- Boolean algebra basics
 - Axioms, theorems,
 - PoS, SoP, minterms, maxterms
- Logic minimization:
 - Karnaugh
 - Multiple variables
 - Multiple functions
- Adders
 - Ripple carry, Carry select, Carry lookahead
- Book sections (complimentary to the slide lectures):
 - 3.1, 3.2, 3.4, 3.5, 6.1-6.3, 6.5-6.9, 10.2, 10.3, 12.1
- Next Lecture 3 (Thursday):
 - Combinational logic (VHDL)