

EDA322

Digital Design

Lecture 3:
Combinational Logic - VHDL


Ioannis Sourdis

Outline of Lecture 3

- VHDL styles
- Dataflow style (combinational logic)
 - Multiplexers, decoders, adders, multipliers, comparators, buffers, encoders
 - Concurrent statements


VHDL Design Styles

VHDL Design Styles

 


Synthesizable VHDL

Dataflow VHDL
Design Style

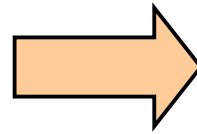

VHDL code
synthesizable

Dataflow VHDL
Design Style

 

VHDL code
synthesizable

Data-Flow VHDL

Concurrent Statements

concurrent signal assignment

($\Leftarrow$)

conditional concurrent signal assignment

(when-else)


selected concurrent signal assignment

(with-select-when)

generate scheme for equations

(for-generate)

Data-flow VHDL: Example

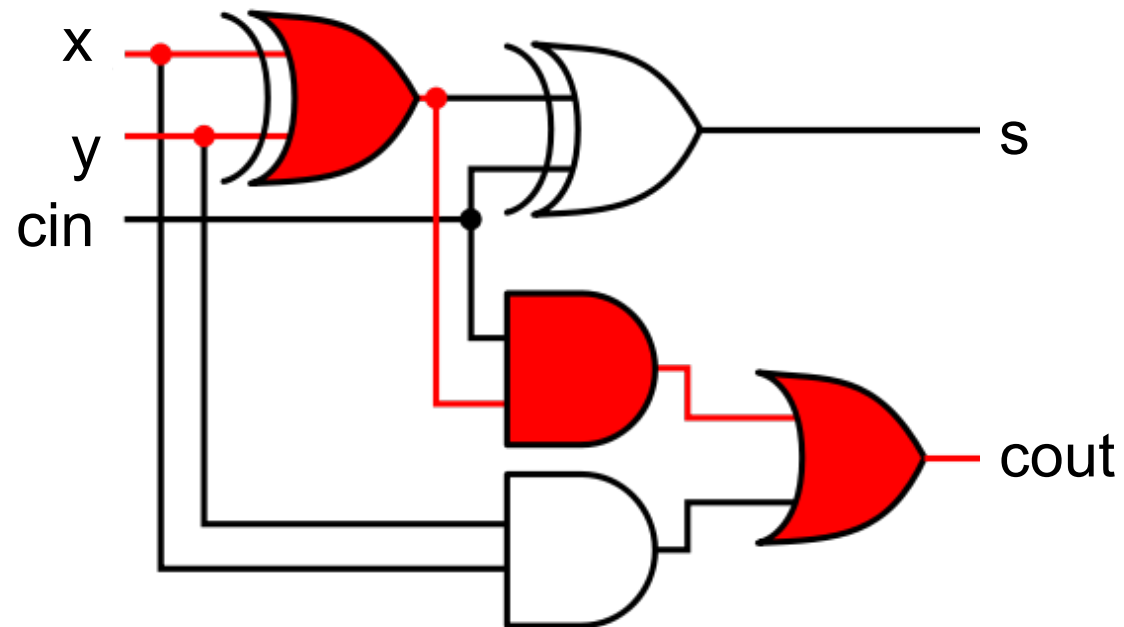

Data-flow VHDL: Example (1)

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;  
  
ENTITY fulladd IS  
    PORT ( x      : IN          STD_LOGIC ;  
          y      : IN          STD_LOGIC ;  
          cin     : IN          STD_LOGIC ;  
          s       : OUT         STD_LOGIC ;  
          cout    : OUT         STD_LOGIC ) ;  
END fulladd ;
```

Data-flow VHDL: Example (2)

ARCHITECTURE dataflow OF fulladd IS
BEGIN


 s <= x XOR y XOR cin ;

 cout <= (x AND y) OR (cin AND (x XOR y)) ;

END dataflow ;

Logic Operators

- Logic operators

 


- Logic operators precedence

only in VHDL-93

Highest



Lowest

 

No Implied Precedence

Wanted: $y = ab + cd$

Incorrect

$y \leq a \text{ and } b \text{ or } c \text{ and } d ;$

equivalent to

$y \leq ((a \text{ and } b) \text{ or } c) \text{ and } d ;$

equivalent to


$y = (ab + c)d$

Correct

$y \leq (a \text{ and } b) \text{ or } (c \text{ and } d) ;$

Multiplexers

2-to-1 Multiplexer

 

(a) Graphical symbol


s	f
0	w_0
1	w_1

(b) Truth table

VHDL code for a 2-to-1 Multiplexer

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;  
  
ENTITY mux2to1 IS  
    PORT ( w0, w1, s : IN    STD_LOGIC ;  
          f          : OUT  STD_LOGIC ) ;  
END mux2to1 ;  
  
ARCHITECTURE dataflow OF mux2to1 IS  
BEGIN  
    f <= w0 WHEN s = '0' ELSE w1 ;  
END dataflow ;
```

Cascade of two multiplexers

 

VHDL code for a cascade of two multiplexers

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux_cascade IS
    PORT ( w1, w2, w3: IN  STD_LOGIC ;
           s1, s2      : IN  STD_LOGIC ;
           f           : OUT STD_LOGIC ) ;
END mux_cascade ;

ARCHITECTURE dataflow OF mux_cascade IS
BEGIN
    f <= w1 WHEN s1 = '1' ELSE
        w2 WHEN s2 = '1' ELSE
        w3 ;
END dataflow ;
```

Operators

- Relational operators

=	/=	<	<=	>	>=
---	----	---	----	---	----

- Logic and relational operators precedence

Highest
↓
Lowest

			not			
=	/=	<	<=	>	>=	
and	or	nand	nor	xor	xnor	

Priority of logic and relational operators

compare $a = bc$

Incorrect

... when $a = b$ **and** c else ...

equivalent to

... when $(a = b)$ **and** c else ...


Correct

... when $a = (b$ **and** $c)$ else ...

VHDL operators

	Operator Class	Operator
Highest precedence	Miscellaneous	**, ABS, NOT
	Multiplying	*, /, MOD, REM
	Sign	+, -
	Adding	+, -, &
	Shift	SLL, SRL, SLA, SRA, ROL, ROR
	Relational	=, /=, <, <=, >, >=
Lowest precedence	Logical	AND, OR, NAND, NOR, XOR, XNOR

4-to-1 Multiplexer

 

(a) Graphic symbol

s_1	s_0	f
0	0	w_0
0	1	w_1
1	0	w_2
1	1	w_3

(b) Truth table

VHDL code for a 4-to-1 Multiplexer

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux4to1 IS
    PORT ( w0, w1, w2, w3 : IN      STD_LOGIC ;
           s               : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;
           f               : OUT      STD_LOGIC ) ;
END mux4to1 ;


ARCHITECTURE dataflow OF mux4to1 IS
BEGIN
    WITH s SELECT
        f <= w0 WHEN "00",
            w1 WHEN "01",
            w2 WHEN "10",
            w3 WHEN OTHERS ;
END dataflow ;
```

Decoders

2-to-4 Decoder

En	w_1	w_0	y_3	y_2	y_1	y_0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0
0	x	x	0	0	0	0

(a) Truth table

 

(b) Graphical symbol

VHDL code for a 2-to-4 Decoder


```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY dec2to4 IS
    PORT (
        w      : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;
        En     : IN      STD_LOGIC ;
        y      : OUT     STD_LOGIC_VECTOR(3 DOWNTO 0) ) ;
END dec2to4 ;

ARCHITECTURE dataflow OF dec2to4 IS
    SIGNAL Enw : STD_LOGIC_VECTOR(2 DOWNTO 0) ;
BEGIN
    Enw <= En & w ;
    WITH Enw SELECT
        y <= "0001" WHEN "100",
            "0010" WHEN "101",
            "0100" WHEN "110",
            "1000" WHEN "111",
            "0000" WHEN OTHERS ;
END dataflow ;
```

Adders

16-bit Unsigned Adder

 

Operations on Unsigned Numbers

For operations on unsigned numbers

USE `ieee.numeric_std.all`

and

signals of the type

UNSIGNED

and conversion functions:

`std_logic_vector()`, `unsigned()`

OR

USE `ieee.std_logic_unsigned.all`

and

signals of the type

STD_LOGIC_VECTOR

Addition of Unsigned Numbers (1)

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;  
USE ieee.numeric_std.all ;
```

```
ENTITY adder16 IS  
    PORT ( Cin          : IN      STD_LOGIC ;  
          X             : IN      STD_LOGIC_VECTOR(15 DOWNT0 0) ;  
          Y             : IN      STD_LOGIC_VECTOR(15 DOWNT0 0) ;  
          S             : OUT     STD_LOGIC_VECTOR(15 DOWNT0 0) ;  
          Cout          : OUT     STD_LOGIC ) ;  
END adder16 ;
```

Addition of Unsigned Numbers (2)

ARCHITECTURE dataflow OF adder16 IS

SIGNAL Xu : **UNSIGNED**(16 DOWNT0 0);

SIGNAL Yu : **UNSIGNED**(16 DOWNT0 0);

SIGNAL Su : **UNSIGNED**(16 DOWNT0 0) ;

SIGNAL Cinu : **UNSIGNED**(1 DOWNT0 0);

BEGIN

Xu <= unsigned('0' & X);

Yu <= unsigned(Y);

Cinu <= unsigned(Cin);

Su <= Xu + Yu + Cinu ;

S <= **std_logic_vector**(Su(15 DOWNT0 0)) ;

Cout <= Su(16) ;

END dataflow;

Operations on Signed Numbers

For operations on signed numbers

USE `ieee.numeric_std.all`,
signals of the type
SIGNED,
and conversion functions:
`std_logic_vector()`, `signed()`

OR

USE `ieee.std_logic_signed.all`
and signals of the type
`STD_LOGIC_VECTOR`

Signed and Unsigned Types

Behave exactly **like**

STD_LOGIC_VECTOR

plus, they determine whether a given vector should be treated as a signed or unsigned number.

Require

USE ieee.numeric_std.all;

General role:

Use the numeric library, avoid the signed and unsigned libraries.

Signed and unsigned libraries have problems when used together in the same file!

Multipliers

Unsigned vs. Signed Multiplication


Unsigned

1111	15
x 1111	x 15
11100001	225

Signed

1111	-1
x 1111	x -1
00000001	1

8x8-bit Unsigned Multiplier

 

Multiplication of unsigned numbers

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.all;
```

```
USE ieee.numeric_std.all ;
```

```
entity multiply is
```

```
    port(
```

```
        a : in STD_LOGIC_VECTOR(7 downto 0);
```

```
        b : in STD_LOGIC_VECTOR(7 downto 0);
```

```
        c : out STD_LOGIC_VECTOR(15 downto 0)
```

```
    );
```

```
end multiply;
```


```
architecture dataflow of multiply is
```

```
begin
```

```
    c <= STD_LOGIC_VECTOR(UNSIGNED(a)*UNSIGNED(b))
```

```
end dataflow;
```

8x8-bit Signed Multiplier

 

Multiplication of signed numbers

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
USE ieee.numeric_std.all ;
```

entity multiply is

```
    port(  
        a : in STD_LOGIC_VECTOR(7 downto 0);  
        b : in STD_LOGIC_VECTOR(7 downto 0);  
        c : out STD_LOGIC_VECTOR(15 downto 0)  
    );
```


end multiply;

architecture dataflow of multiply is
begin

```
    c <= STD_LOGIC_VECTOR(SIGNED(a)*SIGNED(b))
```

end dataflow;

8x8-bit Unsigned and Signed Multiplier

 

Multiplication of signed and unsigned numbers

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.all;
```

```
USE ieee.numeric_std.all ;
```

```
entity multiply is
```

```
    port(
```

```
        a : in STD_LOGIC_VECTOR(7 downto 0);
```

```
        b : in STD_LOGIC_VECTOR(7 downto 0);
```

```
        cu : out STD_LOGIC_VECTOR(15 downto 0);
```

```
        cs : out STD_LOGIC_VECTOR(15 downto 0)
```

```
    );
```

```
end multiply;
```

```
architecture dataflow of multiply is
```

```
begin
```

```
-- signed multiplication
```

```
    cs <= STD_LOGIC_VECTOR(SIGNED(a)*SIGNED(b));
```


```
-- unsigned multiplication
```

```
    cu <= STD_LOGIC_VECTOR(UNSIGNED(a)*UNSIGNED(b))
```

```
end dataflow;
```

Comparators

4-bit Number Comparator

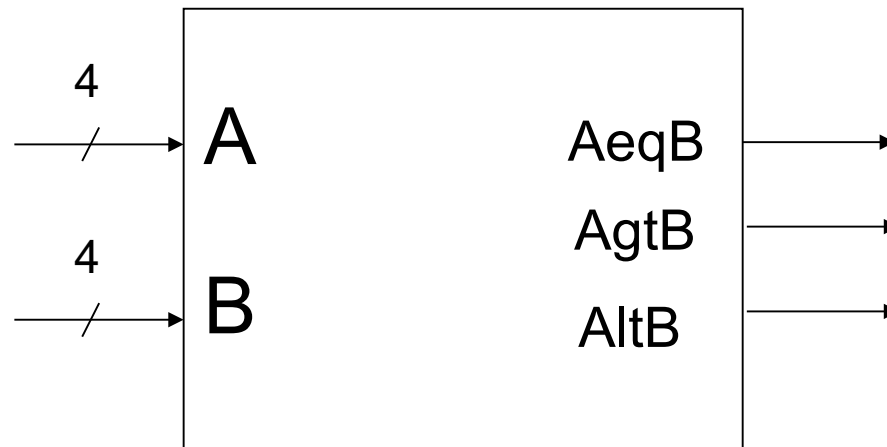

VHDL code for a 4-bit **Unsigned** Number Comparator

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.numeric_std.all ;

ENTITY compare IS
    PORT ( A, B          : IN      STD_LOGIC_VECTOR(3 DOWNT0 0) ;
          AeqB, AgtB, AltB : OUT    STD_LOGIC ) ;
END compare ;

ARCHITECTURE dataflow OF compare IS
BEGIN
    AeqB <= '1' WHEN unsigned(A)=unsigned(B) ELSE '0' ;
    AgtB <= '1' WHEN unsigned(A)>unsigned(B) ELSE '0' ;
    AltB <= '1' WHEN unsigned(A)<unsigned(B) ELSE '0' ;
END dataflow ;
```

VHDL code for a 4-bit **Signed** Number Comparator


```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.numeric_std.all ;

ENTITY compare IS
    PORT ( A, B          : IN      STD_LOGIC_VECTOR(3 DOWNT0 0) ;
           AeqB, AgtB, AltB : OUT   STD_LOGIC ) ;
END compare ;



ARCHITECTURE dataflow OF compare IS
BEGIN
    AeqB <= '1' WHEN signed(A)= signed(B) ELSE '0' ;
    AgtB <= '1' WHEN signed(A)>signed(B) ELSE '0' ;
    AltB <= '1' WHEN signed(A)<signed(B) ELSE '0' ;
END dataflow ;
```

Buffers

Tri-state Buffer

 

(a) A tri-state buffer

  


(b) Equivalent circuit


e	x	f
0	0	Z
0	1	Z
1	0	0
1	1	1

(c) Truth table


Four types of Tri-state Buffers

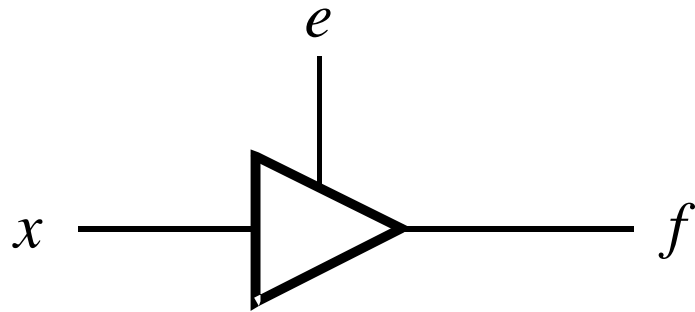


(a)

 

(b)

 

(c)

 

(d)

Tri-state Buffer – example (1)

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
  
ENTITY tri_state IS  
    PORT ( ena:   IN STD_LOGIC;  
          input: IN STD_LOGIC;  
          output: OUT STD_LOGIC  
        );  
END tri_state;
```

Tri-state Buffer – example (2)

ARCHITECTURE dataflow OF tri_state IS


BEGIN

 output <= input WHEN (ena = '1') ELSE 'Z';

END dataflow;

Encoders

Priority Encoder

 

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

VHDL code for a Priority Encoder

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;


ENTITY priority IS
    PORT ( w    : IN    STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          y    : OUT   STD_LOGIC_VECTOR(1 DOWNTO 0) ;
          z    : OUT   STD_LOGIC ) ;
END priority ;

ARCHITECTURE dataflow OF priority IS
BEGIN
    y <=  "11" WHEN w(3) = '1' ELSE
          "10" WHEN w(2) = '1' ELSE
          "01" WHEN w(1) = '1' ELSE
          "00" ;
    z <= '0' WHEN w = "0000" ELSE '1' ;
END dataflow ;
```

Describing Combinational Logic Using Dataflow Design Style

Multiple Logical Unit (MLU) Example

MLU Block Diagram

 

MLU: Entity Declaration

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY mlu IS
    PORT(
        NEG_A : IN STD_LOGIC;
        NEG_B : IN STD_LOGIC;
        NEG_Y : IN STD_LOGIC;
        A :     IN STD_LOGIC;
        B :     IN STD_LOGIC;
        L1 :    IN STD_LOGIC;
        L0 :    IN STD_LOGIC;
        Y :     OUT STD_LOGIC
    );
END mlu;
```

MLU: Architecture Declarative Section

```
ARCHITECTURE mlu_dataflow OF mlu IS
```

```
SIGNAL A1 : STD_LOGIC;
```

```
SIGNAL B1 : STD_LOGIC;
```

```
SIGNAL Y1 : STD_LOGIC;
```

```
SIGNAL MUX_0 : STD_LOGIC;
```

```
SIGNAL MUX_1 : STD_LOGIC;
```

```
SIGNAL MUX_2 : STD_LOGIC;
```

```
SIGNAL MUX_3 : STD_LOGIC;
```

```
SIGNAL L: STD_LOGIC_VECTOR(1 DOWNTO 0);
```

MLU - Architecture Body

```
BEGIN
```

```
  A1<= NOT A WHEN (NEG_A='1') ELSE
```

```
    A;
```

```
  B1<= NOT B WHEN (NEG_B='1') ELSE
```

```
    B;
```

```
  Y <= NOT Y1 WHEN (NEG_Y='1') ELSE
```

```
    Y1;
```

```
  MUX_0 <= A1 AND B1;
```

```
  MUX_1 <= A1 OR B1;
```

```
  MUX_2 <= A1 XOR B1;
```

```
  MUX_3 <= A1 XNOR B1;
```

```
  L <= L1 & L0;
```

```
  with (L) select
```

```
    Y1 <= MUX_0 WHEN "00",
```

```
          MUX_1 WHEN "01",
```

```
          MUX_2 WHEN "10",
```

```
          MUX_3 WHEN OTHERS;
```

```
END mlu_dataflow;
```

Logic Implied Most Often by Conditional and Selected Concurrent Signal Assignments

Data-flow VHDL

Major instructions

Concurrent statements

- concurrent signal assignment ($\Leftarrow$)
- **conditional concurrent signal assignment (when-else)**
- selected concurrent signal assignment (with-select-when)
- generate scheme for equations (for-generate)

Conditional concurrent signal assignment


When - Else

```
target_signal <= value1 when condition1 else  
                  value2 when condition2 else  
                  . . .  
                  valueN-1 when conditionN-1 else  
                  valueN;
```

Most often implied structure

When - Else
 
```
target_signal <= value1 when condition1 else  
                    value2 when condition2 else  
                    . . .  
                    valueN-1 when conditionN-1 else  
                    valueN;
```



Data-flow VHDL

Major instructions

Concurrent statements

- concurrent signal assignment ($\Leftarrow$)
- conditional concurrent signal assignment
(when-else)
- **selected concurrent signal assignment**
(with-select-when)
- generate scheme for equations
(for-generate)

Selected concurrent signal assignment


With –Select-When

```
with choice_expression select  
    target_signal <= expression1 when choices_1,  
                    expression2 when choices_2,  
                    . . .  
                    expressionN when choices_N;
```

Most Often Implied Structure

With –Select-When
 
```
with choice_expression select  
    target_signal <= expression1 when choices_1,  
                      expression2 when choices_2,  
                      . . .  
                      expressionN when choices_N;
```



Allowed formats of *choices_k*

WHEN value

WHEN value_1 | value_2 | | value N

WHEN OTHERS

Allowed formats of choice_k - example

```
WITH sel SELECT
```

```
    y <= a WHEN "000",
```

```
        c WHEN "001" | "111",
```

```
        d WHEN OTHERS;
```

Summary of Lecture 3

- VHDL styles
- Dataflow style (combinational logic)
 - Multiplexers, decoders, adders, multipliers, comparators, buffers, encoders
 - Concurrent statements
- Book Chapters: 3.6, 7.1.5-7.1.8
- Next Lecture 4:
 - Lab Processor, VHDL for regular structures