

EDA322

Digital Design

Lecture 4:

The ChAcc Processor & VHDL for regular structures

Ioannis Sourdis

Outline of Lecture 4

- Lab processor specifications
 - Datapath and control
 - Instruction Set
- Structural VHDL and tips for regular structures

The ChAcc Processor specifications

Angelos Arelakis

Ioannis Sourdis


EDA322 lab processor

- Chalmers Accumulator processor (ChAcc processor)
- In EDA322 lab, ChAcc will be:
 - Implemented
 - Verified using real programs
 - Downloaded on FPGA (optional)
 - Evaluated in terms of performance, area and power dissipation (optional)
- Processor specifications are very important for the implementation of ChAcc.
 - Study the processor specification document (processor.pdf): contains all the details
 - Ask the lab assistants
- ChAcc is based on the lab processor of HY-120 course, Institute of Computer Science, FORTH, Greece

ChAcc processor - Overview

- ChAcc: Chalmers **Accumulator** processor
 - Only one register to save data, as opposed to modern processors
 - Keeps the result of the most recent operation
 - Consecutive operations are performed → result is accumulated in the accumulator
- ChAcc:
 - Simple to implement, but slow (about 2-4 clock cycles per executed instruction)
 - Runs a variety of programs
- ChAcc is an 8-bit processor:
 - operates on 8-bit data

ChAcc processor - Overview

 

ChAcc processor - Overview

- **Datapath** is where data flow:
 - Are used or modified
 - Are read or written to memory
 - Are displayed in 7-segments
- Datapath consists of many components:
 - Memory, registers
 - ALU
 - 7-segments
 - ...
- **Controller**: synchronizes processor's components and orchestrates operations
- **Communications bus** (or just bus): transfers data between different components (e.g., between ALU and memory) of the datapath.

Memories




Adder ($PC = PC + 1$)




ChAcc processor – Datapath Muxes

Muxes

 

ChAcc processor – Datapath Displays

Displays

 

ChAcc processor – Datapath


Storage elements (1)

- Memory and Registers
- Memory stores either data or program instructions
- **Harvard architecture**: memory is organized in two separate memories:
 - Instruction memory (IM): saves program instructions (12-bit); cannot be written at runtime (ROM)
 - Data memory (DM): saves data (8-bit); can be written at runtime
- Both memories are accessed using an 8-bit address → each has 256 entries (memory locations)

ChAcc processor – Datapath

Storage elements (2)

 - Registers: store the content when:
 - Clk is in the rising edge
 - When load enable is set



ChAcc processor – Datapath

Storage elements (3)

Many types of registers in ChAcc:

- **ACC:** The main accumulator register
- **FReg:** Flag register keeps 4 1-bit flags (MSB to LSB order):
 - Ovf: overflow is set when an ALU operation results in overflow
 - NEQ: is set when the ALU operands are not equal
 - EQ: is set when the ALU operands are equal
 - Zero: is set when the ALU output is zero
- **Datapath registers (FE, FE/DE, DE/EX):**
 - Keep information needed in the next stage
- **Display register:**
 - Keeps the data to be displayed in a particular display

ChAcc processor – Datapath

ALU (1)

- ALU = Arithmetic and Logic Unit
- ALU performs all the arithmetic and logic operations.
 - Add 2 operands
 - Sub 2 operands
 - AND of two operands
 - NOT of one operand
 - Compare two operands and determine if they are equal or not
- It doesn't support:
 - Multiplication
 - Division
 - Floating point operations
 - Square root, etc...

ChAcc processor – Datapath


ALU (2)

- ALU inputs:
 1. ALU_inA (8 bits): connected to ACC output
 2. ALU_inB (8 bits): given by the bus (normally the data memory output)
 3. Operation(2 bits): given by the controller and determines the current ALU operation
- ALU outputs:
 1. ALU_out (8 bits)
 2. Carry (1 bit): is set if the carry out of the adder is 1
 3. NotEq (1 bit): is set if ALU_inA and ALU_inB are not equal
 4. Eq (1 bit): is set if ALU_inA and ALU_inB are equal
 5. isOutZero (1 bit): set if ALU_out is zero

ChAcc processor – Datapath Bus

- Bus: communicates data between different components
- Implemented with tri-states buffer
 - Need to be careful:
 - if more than one tri-state buffers are ON → bus takes an undefined value
 - Alternative implementation:
 - Using multiplexers + extra logic you will find out

ChAcc processor – Datapath

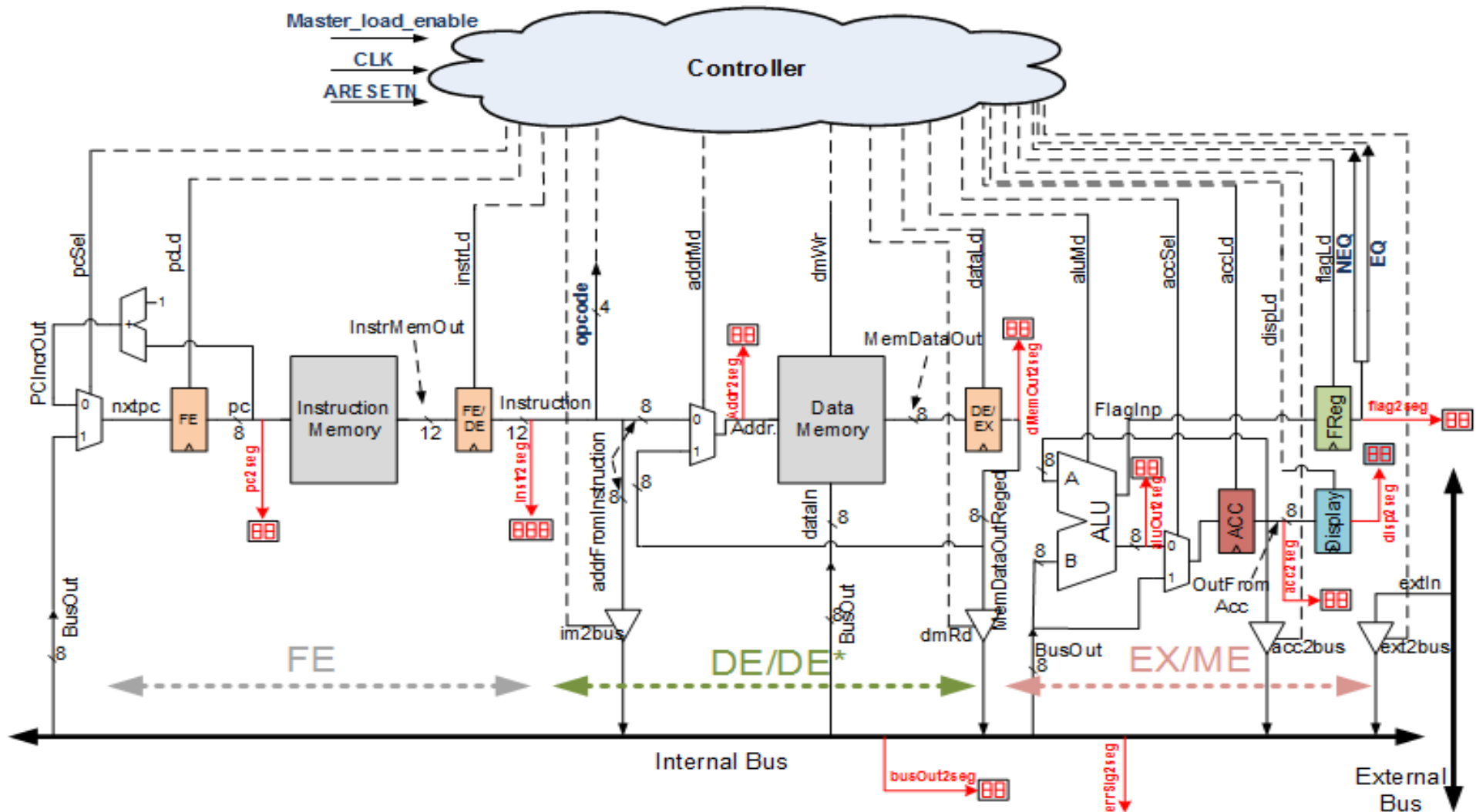


Keep the entity & signal names consistent!

- Signal names and their widths are given on the datapath.
 - If some names are not provided, set your own ones.
- In the lab assignments, for each unit, we provide:
 - The entity name (e.g. EDA322_processor is the name of the top-level design)
 - The names of the entity inputs/outputs
 - The widths of the entity inputs/outputs
- In the 6th lab assignment, we provide a wrapper that connects your implemented processor to the FPGA interface (pins, clk, switches, displays, etc)
- DON'T change any names/widths in the above specifications, otherwise the provided testbenches and the wrapper won't work!

ChAcc ISA and instruction format


ISA = Instruction Set Architecture: A set of the instructions that this processor can “recognize” and execute

 - Instruction consists of two parts:
 - Opcode (4 bit): Unique ID of the instruction
 - Argument (8 bits): Can be used in different ways



Machine code	Instruction Name	Assembly language	Comment	Extra info
000000000000	No operation	NOOP	Do nothing	—
0010aaaaaaaa	Subtract	SU ACC, DM[Addr]	ACC = ACC - DataMem[Addr]	may set "Ovf", "Zero"
0001aaaaaaaa	Add	AD ACC, DM[Addr]	ACC = ACC + DataMem[Addr]	may set "Ovf", "Zero"
010000000000	Not	NT ACC	ACC = ACC'	may set "Zero"
0011aaaaaaaa	And	NA ACC, DM[Addr]	ACC = (ACC & DataMem[Addr])'	may set "Zero"
0101aaaaaaaa	Compare	CMP ACC, DM[Addr]	Compare ACC vs. DataMem[Addr]	set EQ, NEQ
0110aaaaaaaa	Load Byte	LB ACC, DM[Addr]	Load 8 byte value from location DataMem[Addr] into ACC	—
0111aaaaaaaa	Store Byte	SB DM[Addr], ACC	Store contents of ACC into location DataMem[Addr]	—
1000aaaaaaaa	Add Index	ADX ACC, DM[DM[Addr]]	ACC = ACC + DataMem[DataMem[Addr]]	may set "Ovf", "Zero"
1001aaaaaaaa	Load Byte Index	LBX ACC, DM[DM[Addr]]	ACC = DataMem[DataMem[Addr]]	—
1010aaaaaaaa	Store Byte Index	SBX DM[DM[Addr]], ACC	DataMem[DataMem[Addr]] = ACC	—
1011aaaaaaaa	Input	IN DM[Addr], IO_BUS	DataMem[Addr] = value at IO_BUS	—
1100aaaaaaaa	Jump	J addr	Execute next instruction @ PC = Addr	—
1101aaaaaaaa	Jump Not Equal	JNE addr	Jump if the corresponding flag NEQ is set	—
1110aaaaaaaa	Jump Equal	JEQ addr	Jump if the corresponding flag EQ is set	—
111100000000	Display	DS	Move ACC to Display reg. (used for debugging)	—

Arithmetic and logic instructions

 

*

Memory instructions



Branch instructions




Arithmetic and logic instructions

Machine code	Instruction Name	Assembly language	Comment	Extra info
000000000000	No operation	NOOP	Do nothing	—
0010aaaaaaaa	Subtract	SU ACC, DM[Addr]	$ACC = ACC - DataMem[Addr]$	may set "Ovf", "Zero"
0001aaaaaaaa	Add	AD ACC, DM[Addr]	$ACC = ACC + DataMem[Addr]$	may set "Ovf", "Zero"
010000000000	NOT	NT ACC	$ACC = ACC'$	may set "Zero"
0011aaaaaaaa	AND	NA ACC, DM[Addr]	$ACC = ACC \& DataMem[Addr]$	may set "Zero"
0101aaaaaaaa	Compare	CMP ACC, DM[Addr]	Compare ACC vs. DataMem[Addr]	set EQ, NEQ
1000aaaaaaaa	Add Index	ADX ACC, DM[DM[Addr]]	$ACC = ACC + DataMem[DataMem[Addr]]$	may set "Ovf", "Zero"


ADX ACC, DM[DM[Addr]]

Fetch

 


ADX ACC, DM[DM[Addr]]

Decode

 


ADX ACC, DM[DM[Addr]] Decode*

 

ADX ACC, DM[DM[Addr]]


Execute

 


Memory instructions

Machine code	Instruction Name	Assembly language	Comment	Extra info
0110aaaaaaaa	Load Byte	LB ACC, DM[Addr]	Load 1 byte value from location DataMem[Addr] into ACC	—
0111aaaaaaaa	Store Byte	SB DM[Addr], ACC	Store contents of ACC into location DataMem[Addr]	—
1001aaaaaaaa	Load Byte Index	LBX ACC, DM[DM[Addr]]	ACC = DataMem[DataMem[Addr]]	—
1010aaaaaaaa	Store Byte Index	SBX DM[DM[Addr]], ACC	DataMem[DataMem[Addr]] = ACC	—
1011aaaaaaaa	Input	IN DM[Addr], IO_BUS	DataMem[Addr] = value at IO_BUS	—


SB DM[Addr], ACC Fetch

 

SB DM[Addr], ACC Decode

 

SB DM[Addr], ACC Memory

 


Branch instructions ++


Machine code	Instruction Name	Assembly language	Comment	Extra info
1100aaaaaaaa	Jump	J address	Execute next instruction @ PC = address	—
1101aaaaaaaa	Jump Not Equal	JNE address	Jump if the corresponding flag NEQ is set	—
1110aaaaaaaa	Jump Equal	JEQ address	Jump if the corresponding flag EQ is set	—
111100000000	Display	DS	Move ACC to Diplay reg. (used for debugging)	—

 **For Debug**

JEQ Addr Fetch

 

JEQ Addr Decode

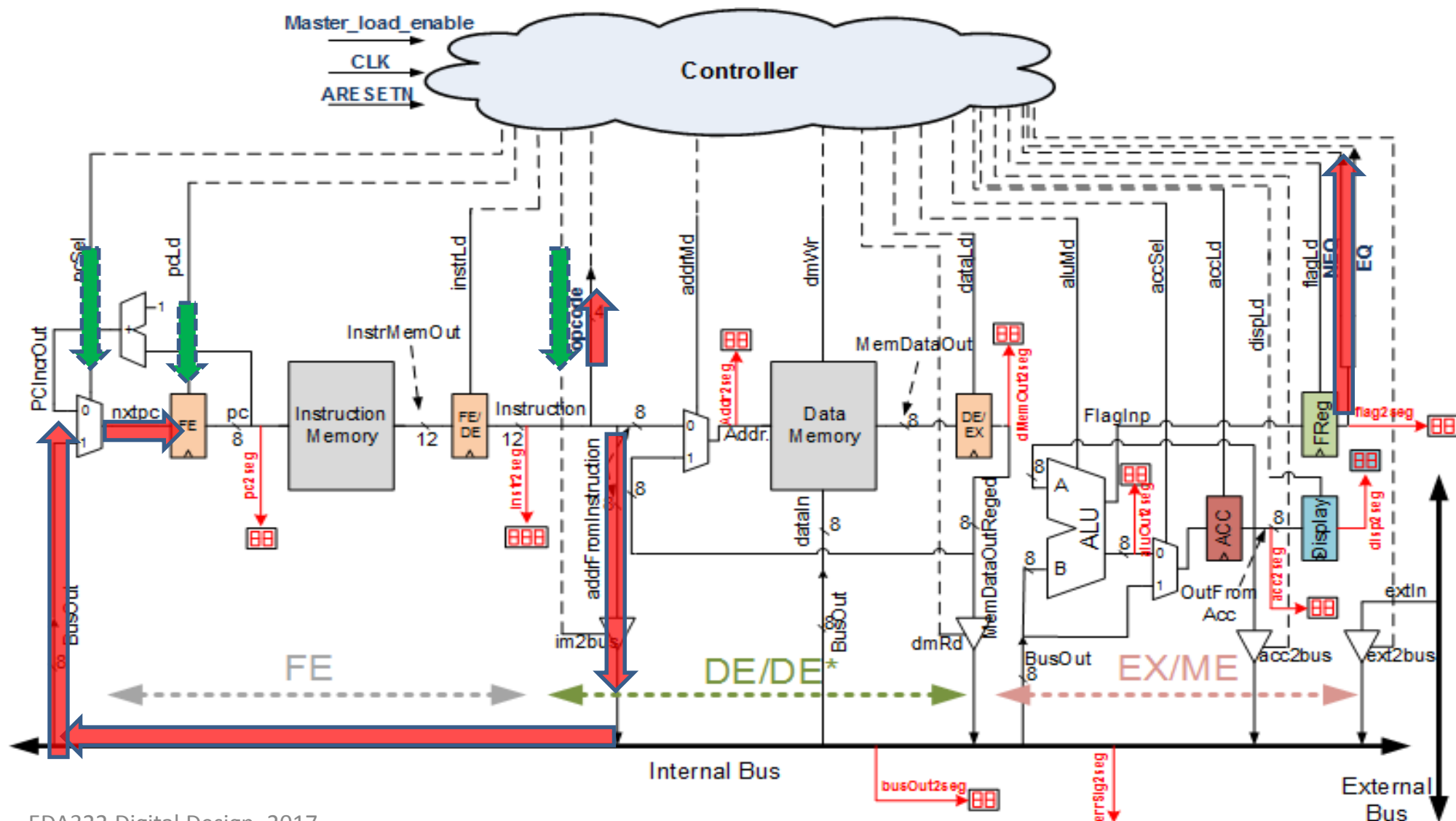

ChAcc processor – ISA

- **Arithmetic and logic instructions:**
 - perform arithmetic and logic operations between operands on the ALU.
 - Data memory is accessed using instruction's address-field to retrieve the second ALU operand (one is ACC).
- **Memory instructions:**
 - The memory instructions access the data memory using the address-field of the instruction. Accesses:
 - read something from the data memory and save it to the ACC (*Load Byte, Load Byte Index*)
 - write the content of the ACC into the data memory (*Store Byte, Store Byte Index*)
 - write the data that come from the I/O bus into the data memory (*Input*)
- **Branch instructions:**
 - change the program flow by modifying the program counter (PC) based on a condition (*JE, JNE*) or unconditionally (*J*), by jumping to a particular address

ChAcc processor – ISA

- Other instructions:
 - NOOP: keeps processor idle by doing nothing: adding DM[0] (is always 0) to the ACC
 - Display: displays the content of ACC register → useful for debugging
- ADX, LBX and SBX are special instructions:
 - they access the data memory twice. Mentioned as Index instructions

Index instructions

- **A** is an array of 10 1-byte numbers
- The data memory locations 100 to 109 have been allocated to save the array elements)

Pseudocode:

```
...  
x=1;  
for (i=0; i!=10; i++)  
{  
    A[i] += x;  
}
```

Assembly:

Initialize some memory locations

1. IN DM[1], IO_BUS # Write **1** from IO_BUS to DM[1]; x= 1 the value to add to the A[i]
2. IN DM[2], IO_BUS # Write **10** from IO_BUS to DM[2]; 10 --> Max loop iteration
3. IN DM[3], IO_BUS # Write **1** from IO_BUS to DM[3]; 1--> loop iteration step
4. IN DM[5], IO_BUS # Write **100** from IO_BUS to DM[5]; 100 → the location of A[0] in DM
5. IN DM[6], IO_BUS # Write **0** from IO_BUS to DM[6]; Initialize the current loop iteration to 0

Calculate new A[i]

6. LB ACC, DM[1] # Load x to ACC
7. ADX ACC, DM[DM[5]] # ACC = x + A[i]
8. SBX DM[DM[5]], ACC # A[i] = ACC

Calculate next address of A[i]

9. LB ACC, DM[3] # Load iteration step to ACC
10. AD ACC, DM[5] # Calculate next address of A[i]
11. SB DM[5], ACC # Save ACC (new calculated address) back to DM[5]

Increment the iteration counter (i) and check if done

12. LB ACC, DM[3] # Load iteration step to ACC
13. AD ACC, DM[6] # Calculate new iteration
14. SB DM[6], ACC # Save iteration counter back to DM[6]
15. CMP ACC, DM[2] # Compare current iteration (@ACC) to max iteration (10)
16. JNE 6 # Evaluate NEQ flag and if it was set PC=6 (instr #6)
17. ...

The array is stored in the DM locations 100-109

Initially DM[100-109] =
0,1,2,3,4,5,6,7,8,9

1st iteration (i=0) DM[5] = 100
2nd iteration (i=1) DM[5] = 101
3rd iteration (i=2) DM[5] = 102

At the end of the loop iteration the memory locations DM 100-109 will have
1,2,3,4,5,6,7,8,9,10 respectively

ChAcc processor – Global control signals


- Every sequential circuit is synchronized by a common signal → the global clock (CLK)
- Many components are initialized to zero when reset is on (ARESETn)
- Reset is asynchronous:
 - Effective when active and not dependent on the rising/falling edge of clock
 - Active when '0'

ChAcc processor – Controller

- Controller:
 - synchronizes the rest of the processor's units and orchestrates their operations
- Controller:
 - breaks the datapath into five stages
 - **Fetch, Decode, Decode*, Execute, Memory**
 - **Instructions DON'T pass through all stages**
 - **All instructions pass through Fetch and Decode**
 - Generates the control signals of the datapath units in these stages based on the executed instruction's opcode (part of the instruction)

ChAcc processor – Controller

Datapath stages

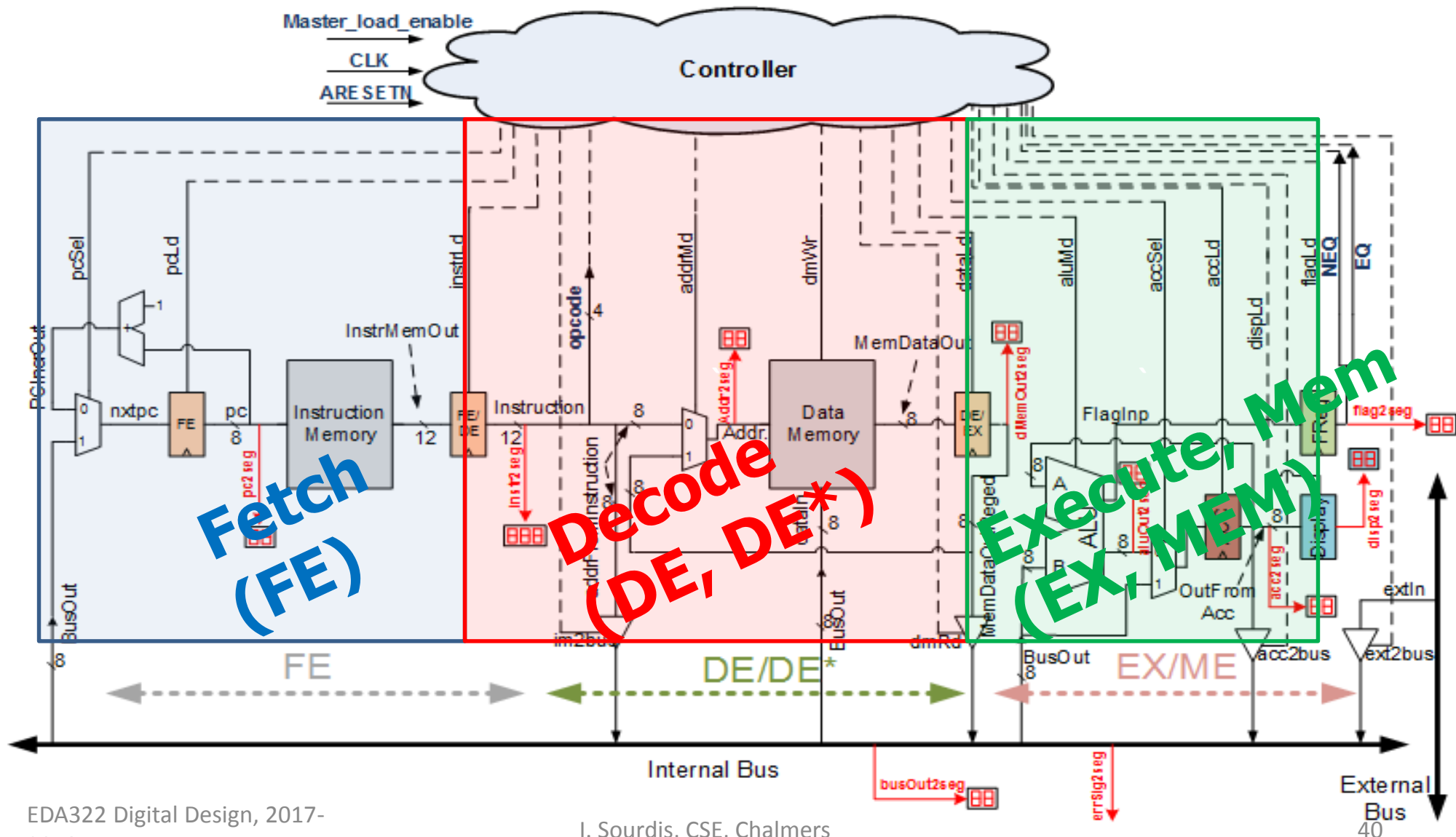

opcode	detailed instr	FE	DE	DE*	EX	MEM	#stages
0000	AD ACC, DM[0]	y	y	n	y	n	3
0010	SU ACC, DM[Addr]	y	y	n	y	n	3
0001	AD ACC, DM[Addr]	y	y	n	y	n	3
0100	NT ACC, DM[Addr]	y	y	n	y	n	3
0011	AND ACC, DM[Addr]	y	y	n	y	n	3
0101	CMP ACC, DM[Addr]	y	y	n	y	n	3
0110	LB ACC, DM[Addr]	y	y	n	y	n	3
0111	SB DM[Addr], ACC	y	y	n	n	y	3
1000	ADX ACC, DM[DM[Addr]]	y	y	y	y	n	4
1001	LBX ACC, DM[DM[Addr]]	y	y	y	y	n	4
1010	SBX DM[DM[Addr]], ACC	y	y	y	n	y	4
1011	IN DM[Addr], IO_BUS	y	y	n	n	n	2
1100	J address	y	y	n	n	n	2
1101	JNE address, NEQ	y	y	n	n	n	2
1110	JEQ address, EQ	y	y	n	n	n	2
1111	DS	y	y	n	y	n	3

- EX: uses the ALU
- MEM: writes ACC into data memory

Extra DE stage for the Index instructions → they access the data memory 2x

All enter FE and DE

opcode	detailed instr	FE	DE	DE*	EX	MEM	#stages
0000	AD ACC, DM[0]	y	y	n	y	n	3
0010	SU ACC, DM[Addr]	y	y	n	y	n	3
0001	AD ACC, DM[Addr]	y	y	n	y	n	3
0100	NT ACC, DM[Addr]	y	y	n	y	n	3
0011	AND ACC, DM[Addr]	y	y	n	y	n	3
0101	CMP ACC, DM[Addr]	y	y	n	y	n	3
0110	LB ACC, DM[Addr]	y	y	n	y	n	3
0111	SB DM[Addr], ACC	y	y	n	n	y	3
1000	ADX ACC, DM[DM[Addr]]	y	y	y	y	n	4
1001	LBX ACC, DM[DM[Addr]]	y	y	y	y	n	4
1010	SBX DM[DM[Addr]], ACC	y	y	y	n	y	4
1011	IN DM[Addr], IO_BUS	y	y	n	n	n	2
1100	J P Offset	y	y	n	n	n	2
1101	JNE P Offset, NEQ	y	y	n	n	n	2
1110	JEQ P Offset, EQ	y	y	n	n	n	2
1111	DS	y	y	n	y	n	3

**Variable
number of
stages per
instruction**

ChAcc processor – Controller

Control signals

- Controller sets/resets the signals that control the datapath units
- Certain signals must be set/reset in every stage

X_Y: where **X** is the value of the control signal, **Y** is the stage it gets that value.

Stages: Fetch: **FE**, Decode: **DE**, Decode*: **DE***, Execute: **EX**, Memory: **ME**

opcode	pcSel	pcLd	instrLd	addrMd	dmWr	dataLd	flagLd	accSel	accLd	im2bus	dmRd	acc2bus	ext2bus	dispLd	aluMd
0000	0	1_EX	1	0	0	1_DE	1_EX	0	1_EX	0	1_EX	0	0	0	00
0010	0	1_EX	1	0	0	1_DE	1_EX	0	1_EX	0	1_EX	0	0	0	01
0001	0	1_EX	1	0	0	1_DE	1_EX	0	1_EX	0	1_EX	0	0	0	00
0100	0	1_EX	1	0	0	1_DE	1_EX	0	1_EX	0	1_EX	0	0	0	11
0011	0	1_EX	1	0	0	1_DE	1_EX	0	1_EX	0	x	0	0	0	10
0101	0	1_EX	1	0	0	1_DE	1_EX	0	0	0	1_EX	0	0	0	xx
0110	0	1_EX	1	0	0	1_DE	0	1_EX	1_EX	0	1_EX	0	0	0	xx
0111	0	1_ME	1	0	1_ME	0	0	0	0	0	0	1	0	0	xx
1000	0	1_EX	1	1_DE*	0	1_DE/ 1_DE*	1_EX	0	1_EX	0	1_EX	0	0	0	00
1001	0	1_EX	1	1_DE*	0	1_DE/ 1_DE*	0	1_EX	1_EX	0	1_EX	0	0	0	xx
1010	0	1_ME	1	1_ME	1_ME	1_DE	0	0	0	0	0	1	0	0	xx
1011	0	1_DE	1	0	1_DE	0	0	0	0	0	0	0	1	0	xx
1100	1_DE	1_DE	1	0	0	0	0	0	0	1	0	0	0	0	xx
1101	1_DE	1_DE	1	0	0	0	0	0	0	1	0	0	0	0	xx
1110	1_DE	1_DE	1	0	0	0	0	0	0	1	0	0	0	0	xx
1111	0	1_EX	1	0	0	0	0	0	0	0	0	0	0	1_EX	00

ChAcc processor – Controller

Control signals


- **Opcode** (input): the opcode of the read instruction
- **EQ, NEQ** (input): used by the controller when determining the pcSel and pcLd
- **pcSel and pcLd**: control the logic that is relevant to the program counter (PC)
- **instrLd**: load enable of the register that keeps the read instruction
- **addrMd**: control the address input of the data memory. Can be:
 - The address field of the instruction (if normal instruction)
 - The data memory output (if Index instruction)

ChAcc processor – Controller

Control signals

- **dmWr**: enables the write operation in the data memory
- **dmRd**: enables the read operation in the data memory
- **dataLd**: enables “DE/EX” to store the output of the data memory
- **flagLd**: enables “FReg” to store *Flags*
- **accSel**: controls the source of “ACC” register’s input:
 - From ALU
 - From bus: If it is a load instruction
- **accLd**: enables the ACC register to save the input
- **dispLd**: load enable of the Display register
- **dmRd, acc2bus and ext2bus**: control signals of the bus
- **aluMd**: determines the operation of the ALU

ChAcc processor - Overview

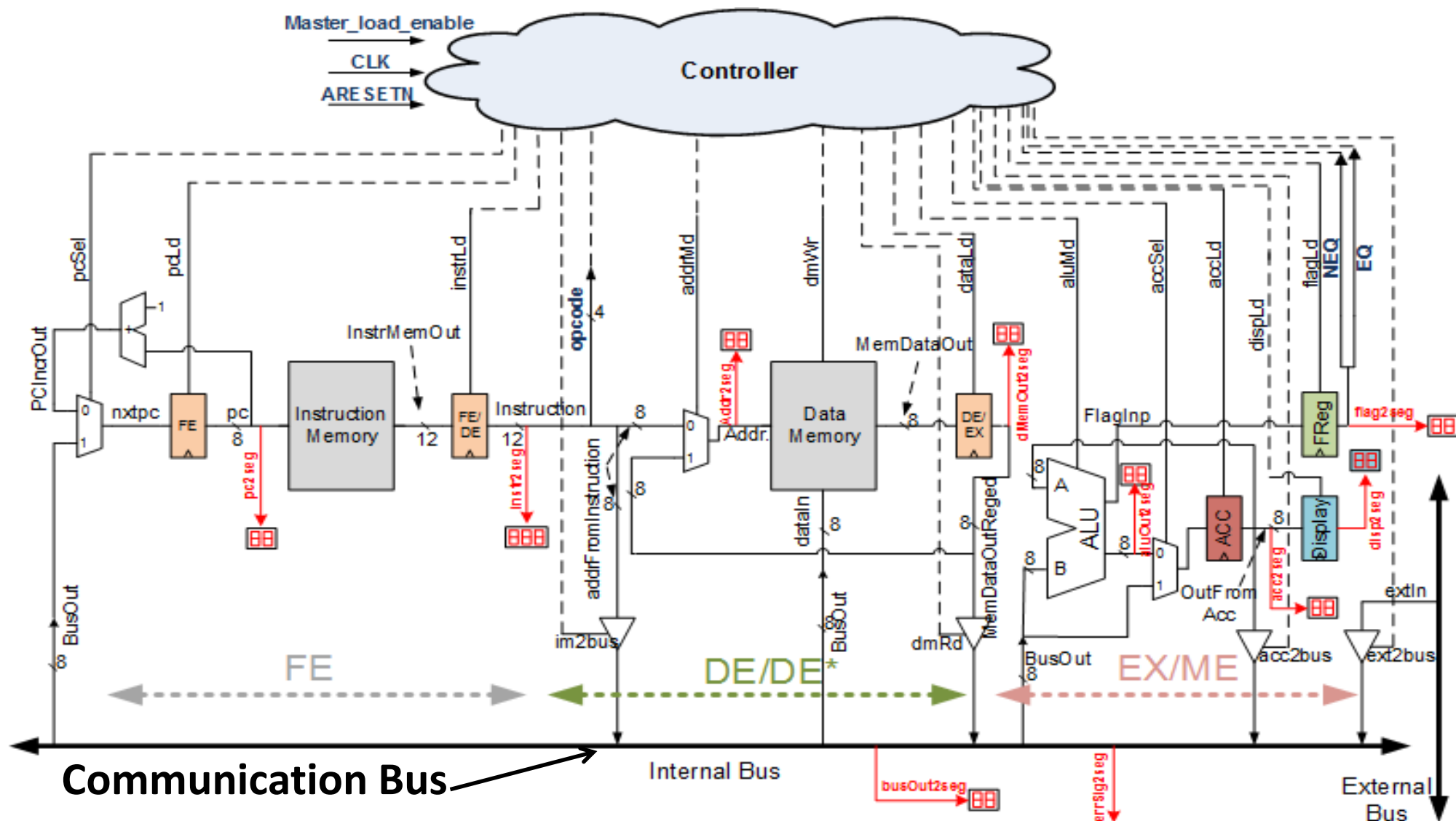

ChAcc processor – Controller

Control signals

- Registers have an additional enable signal (except for one of the previous load enable signals) → *master_load_enable*
- *master_load_enable*:
 - Controls the clock toggling manually
 - Controlled by the user through one FPGA switch
 - Affects FSMs and registers
- A register, in particular, is enabled if and only if:
 - Reset is disabled (ARESETN='1')
 - Positive edge of the clock
 - *master_load_enable* is set (*master_load_enable*='1')
 - load enable signal (given by the controller) is set

ChAcc processor – Controller

Controller:

- Is implemented as a Finite State Machine (FSM)
 - Instructions pass through a different number of stages and thus states
 - Different signals are set/reset based on the current stage and the executed instruction (opcode)
 - State transitions are enabled when *master_load_enable='1'*

Summary of the ChAcc processor

- Processor specifications are important for the correct implementation of ChAcc
- Always consult the processor.pdf document and this presentation, during the labs
- Ask the instructors, if you are unsure about something or if something is not clear
- Keep consistent with the processor specs:
 - entities, signal names or widths
 - files (memory initialization files, testbenches, wrapper, etc)

Quiz 6-1

<http://b.socrative.com/student/#joinRoom>

room number: 713113

- Q1: What does an “Add index” instruction do?
 - ADDs Acc register and a memory location and put the result to Acc
 - ADDs Acc register and a memory location and put the result to Mem
 - Uses the contains of a memory location as an address to access the memory again and ADD the contains of the second memory location to Acc. The result is put to Acc
 - Uses the contains of a memory location as an address to access the memory again and ADD the contains of the second memory location to Acc. The result is put to Memory
- Q2: In the ChAcc instruction set which are the stages that all instructions have in common and will pass through?
 - Fetch and Decode
 - Fetch and Execute
 - Fetch, Decode and Execute
 - All
- Q3: What are the 3 types of instructions in ChAcc?
- Q4: the flag register contains..
 - Exceptions
 - Results of comparison in the ALU
 - Both
 - None of the above

Lecture 6, part 2:

Modeling of Circuits with a Regular Structure

Generate scheme for equations

Data-flow VHDL

Major instructions

Concurrent statements

- concurrent signal assignment ($\Leftarrow$)
- **conditional concurrent signal assignment**
(when-else)
- selected concurrent signal assignment
(with-select-when)
- **generate scheme for equations**
(for-generate)

Conditional concurrent signal assignment


When - Else

```
target_signal <= value1 when condition1 else  
                  value2 when condition2 else  
                  . . .  
                  valueN-1 when conditionN-1 else  
                  valueN;
```

Most often implied structure

When - Else
 
```
target_signal <= value1 when condition1 else  
                value2 when condition2 else  
                . . .  
                valueN-1 when conditionN-1 else  
                valueN;
```



Data-flow VHDL

Major instructions

Concurrent statements

- concurrent signal assignment ($\Leftarrow$)
- conditional concurrent signal assignment
(when-else)
- **selected concurrent signal assignment**
(with-select-when)
- generate scheme for equations
(for-generate)

Selected concurrent signal assignment


With –Select-When

```
with choice_expression select  
    target_signal <= expression1 when choices_1,  
                    expression2 when choices_2,  
                    . . .  
                    expressionN when choices_N;
```

Most Often Implied Structure

With –Select-When
 
```
with choice_expression select  
    target_signal <= expression1 when choices_1,  
                      expression2 when choices_2,  
                      . . .  
                      expressionN when choices_N;
```



Allowed formats of *choices_k*

WHEN value

WHEN value_1 | value_2 | | value N

WHEN OTHERS

Allowed formats of choice_k - example

```
WITH sel SELECT
    y <= a WHEN "000",
        c WHEN "001" | "111",
        d WHEN OTHERS;
```

Data-flow VHDL


Major instructions

Concurrent statements

- concurrent signal assignment ($\Leftarrow$)
- conditional concurrent signal assignment
(when-else)
- selected concurrent signal assignment
(with-select-when)
- **generate scheme for equations**
(for-generate)

PARITY Example


PARITY: Block Diagram

 


PARITY: Entity Declaration

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;
```
 
```
ENTITY parity IS  
  PORT(  
    parity_in  : IN STD_LOGIC_VECTOR(7 DOWNTO 0);  
    parity_out : OUT STD_LOGIC  
  );  
END parity;
```



PARITY: Block Diagram

 

PARITY: Architecture

ARCHITECTURE parity_dataflow OF parity IS

SIGNAL xor_out: std_logic_vector (6 downto 1);

BEGIN

xor_out(1) <= parity_in(0) XOR parity_in(1);

xor_out(2) <= xor_out(1) XOR parity_in(2);

xor_out(3) <= xor_out(2) XOR parity_in(3);


xor_out(4) <= xor_out(3) XOR parity_in(4);

xor_out(5) <= xor_out(4) XOR parity_in(5);


xor_out(6) <= xor_out(5) XOR parity_in(6);

parity_out <= xor_out(6) XOR parity_in(7);

END parity_dataflow;

 

PARITY: Block Diagram (2)

 

PARITY: Architecture

ARCHITECTURE parity_dataflow OF parity IS

SIGNAL xor_out: STD_LOGIC_VECTOR (**7** downto **0**);

BEGIN

xor_out(0) <= parity_in(0);

xor_out(1) <= xor_out(0) XOR parity_in(1);

xor_out(2) <= xor_out(1) XOR parity_in(2);

xor_out(3) <= xor_out(2) XOR parity_in(3);

xor_out(4) <= xor_out(3) XOR parity_in(4);


xor_out(5) <= xor_out(4) XOR parity_in(5);

xor_out(6) <= xor_out(5) XOR parity_in(6);

xor_out(7) <= xor_out(6) XOR parity_in(7);

parity_out <= xor_out(7);

END parity_dataflow;

 

PARITY: Architecture

ARCHITECTURE parity_dataflow OF parity IS


SIGNAL xor_out: STD_LOGIC_VECTOR (**7** downto **0**);

BEGIN

```
xor_out(0) <= parity_in(0);  
xor_out(1) <= xor_out(0) XOR parity_in(1);  
xor_out(2) <= xor_out(1) XOR parity_in(2);  
xor_out(3) <= xor_out(2) XOR parity_in(3);  
xor_out(4) <= xor_out(3) XOR parity_in(4);  
xor_out(5) <= xor_out(4) XOR parity_in(5);  
xor_out(6) <= xor_out(5) XOR parity_in(6);  
xor_out(7) <= xor_out(6) XOR parity_in(7);  
parity_out <= xor_out(7);
```

END parity_dataflow;

 G2: FOR i IN 1 TO 7 GENERATE
 xor_out(i) <= xor_out(i-1) XOR
 parity_in(i);
END GENERATE G2;




For Generate Statement

For - Generate

```
label: FOR identifier IN range GENERATE  
    BEGIN  
        {Concurrent Statements}  
    END GENERATE;
```

Memory

Random Access Memory (RAM)

 

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all ;

```

entity SRAM is

```


generic(  width:      integer:=4;
          addr_bits:  integer:=2);

```

```

port(Clock:      in  std_logic;
      Read:      in  std_logic;
      Write:     in  std_logic;
      Address:    in  std_logic_vector(addr_bits-1 downto 0);
      Data_in:   in  std_logic_vector(width-1 downto 0);
      Data_out:  out std_logic_vector(width-1 downto 0)
);
end SRAM;

```

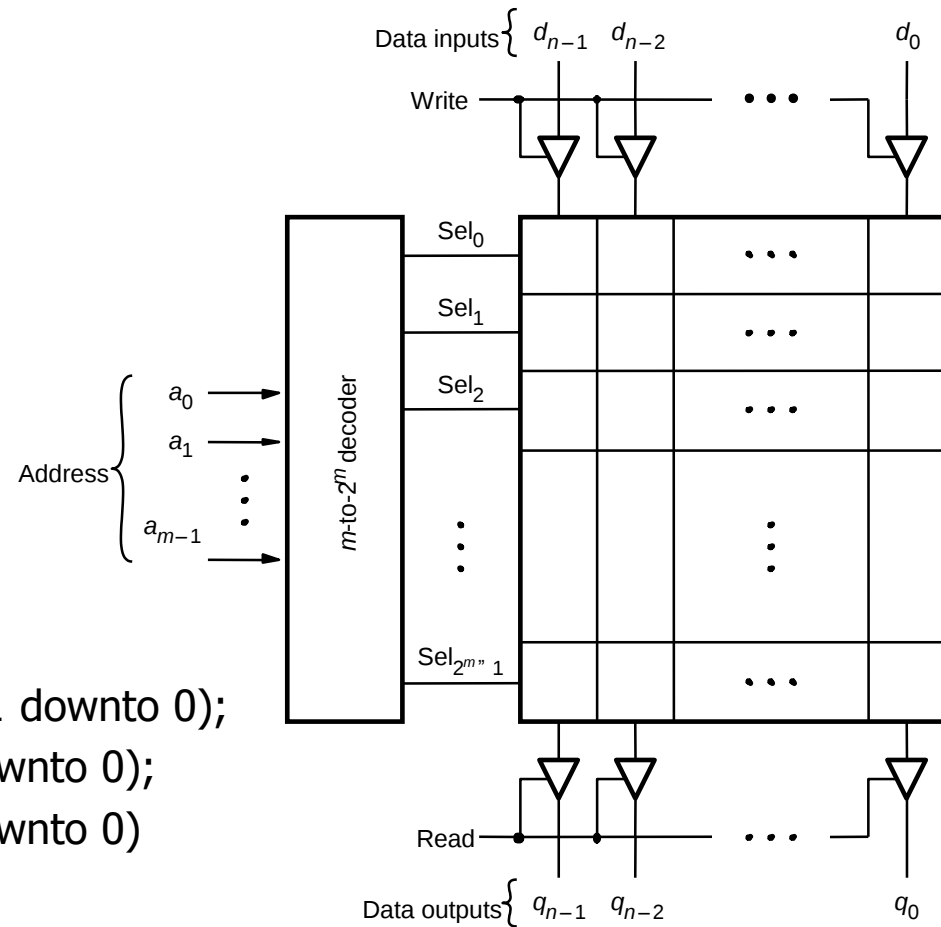



```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all ;
```

entity SRAM is

```
generic( width:      integer:=4;
         addr_bits: integer:=2);
```

```
port(Clock:      in  std_logic;
     Read:       in  std_logic;
     Write:      in  std_logic;
     Address:    in  std_logic_vector(addr_bits-1 downto 0);
     Data_in:    in  std_logic_vector(width-1 downto 0);
     Data_out:   out std_logic_vector(width-1 downto 0)
);
end SRAM;
```

OBS!

  

architecture behav of SRAM is

```
type ram_type is array (0 to (2**addr_bits)-1) of
    std_logic_vector(width-1 downto 0);
signal tmp_ram: ram_type := (OTHERS => (OTHERS => '0')); -- initialize memory with '0'

begin

process(Clock, Read, Write)
    begin
        if (Clock'event and Clock='1') then

            if Read='1' then
                -- build-in functions to_integer(unsigned(x)) change the type from std_logic_vector to integer
                Data_out <= tmp_ram(to_integer(unsigned(Address)));
            else
                Data_out <= (OTHERS => 'Z');
            end if;

            if Write='1' then
                tmp_ram(to_integer(unsigned(Address))) <= Data_in;
            end if;

        end if;
    end process;

end behav;
```

architecture behav of SRAM is

type `ram_type` is array (0 to (2**addr_bits)-1) of

std_logic_vector(width-1 downto 0);

signal tmp_ram: `ram_type` := (OTHERS => (OTHERS => '0')); -- initialize memory with '0'

begin

process(Clock, Read, Write)

begin

if (Clock'event and Clock='1') then

if Read='1' then

-- build-in functions **to_integer(unsigned(x))** change the type from std_logic_vector to integer

Data_out <= tmp_ram(to_integer(unsigned(Address)));

else

Data_out <= (OTHERS => 'Z');

end if;

if Write='1' then

tmp_ram(to_integer(unsigned(Address))) <= Data_in;

end if;

end if;

end process;

end behav;

Power

2 dimensions

architecture behav of SRAM is

```
type ram_type is array (0 to (2**addr_bits)-1) of  
    std_logic_vector(width-1 downto 0);
```

```
signal tmp_ram: ram_type := (OTHERS => (OTHERS => '0')); -- initialize memory with '0'
```

```
begin
```

```
process(Clock, Read, Write)
```

```
begin
```

```
    if (Clock'event and Clock='1') then
```

```
        if Read='1' then
```

```
-- build-in functions to_integer(unsigned(x)) change the type from std_logic_vector to integer
```

```
        Data_out <= tmp_ram(to_integer(unsigned(Address)));
```

```
    else
```

```
        Data_out <= (OTHERS => 'Z');
```

```
    end if;
```

```
    if Write='1' then
```

```
        tmp_ram(to_integer(unsigned(Address))) <= Data_in;
```

```
    end if;
```

```
end if;
```

```
end process;
```

```
end behav;
```

Power

2 dimensions

architecture behavior of SRAM is

type `ram_type` is array (0 to (2**addr_bits)-1) of
 std_logic_vector(width-1 downto 0);

signal tmp_ram: `ram_type` := (OTHERS => (OTHERS => '0')); -- initialize memory with '0'

begin

```
process(Clock, Read, Write)
```

```
begin
```

```
  if (Clock'event and Clock='1') then
```

```
    if Read='1' then
```

```
    -- build-in functions to_integer(unsigned(x)) change the type from std_logic_vector to integer
```

```
      Data_out <= tmp_ram(to_integer(unsigned(Address)));
```

```
    else
```

```
      Data_out <= (OTHERS => 'Z');
```

```
    end if;
```

```
    if Write='1' then
```

```
      tmp_ram(to_integer(unsigned(Address))) <= Data_in;
```

```
    end if;
```

```
  end if;
```

```
end process;
```

Sequential Part

```
end behavior;
```

architecture behav of SRAM is

type `ram_type` is array (0 to (2**addr_bits)-1) of
std_logic_vector(width-1 downto 0);

signal tmp_ram: `ram_type` := (OTHERS => (OTHERS => '0')); -- initialize memory with '0'

begin

process(Clock, Read, Write)

begin

if (Clock'event and Clock='1') then

if Read='1' then

-- build-in functions **to_integer(unsigned(x))** change the type from std_logic_vector to integer

Data_out <= tmp_ram(to_integer(unsigned(Address)));

else

Data_out <= (OTHERS => 'Z');

end if;

if Write='1' then

tmp_ram(to_integer(unsigned(Address))) <= Data_in;

end if;

end if;

end process;

end behav;

Power

2 dimensions

Sensitivity
List

Sequential Part

architecture behav of SRAM is

type `ram_type` is array (0 to (2**addr_bits)-1) of
std_logic_vector(width-1 downto 0);

signal tmp_ram: `ram_type` := (OTHERS => (OTHERS => '0')); -- initialize memory with '0'

begin

process(Clock, Read, Write)

begin

if (Clock'event and Clock='1') then

if Read='1' then

-- build-in functions **to_integer(unsigned(x))** change the type from std_logic_vector to integer

Data_out <= tmp_ram(to_integer(unsigned(Address)));

else

Data_out <= (OTHERS => 'Z');

end if;

if Write='1' then

tmp_ram(to_integer(unsigned(Address))) <= Data_in;

end if;

end if;

end process;

end behav;

Power

2 dimensions

Sensitivity
List

Better to use:
rising_edge(clk)

Sequential Part

Behavioral SRAM Memory

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all ;
```

entity SRAM is

```
generic(      width:      integer:=4;
             addr_bits: integer:=2);

port(Clock:      in      std_logic;
     Read:       in      std_logic;
     Write:      in      std_logic;
     Address:    in      std_logic_vector(addr_bits-1 downto 0);
     Data_in:    in      std_logic_vector(width-1 downto 0);
     Data_out:   out     std_logic_vector(width-1 downto 0)
);
end SRAM;
```

architecture **behav** of **SRAM** is

```
type ram_type is array (0 to (2**addr_bits)-1) of
    std_logic_vector(width-1 downto 0);
signal tmp_ram: ram_type := (OTHERS => (OTHERS => '0'));

begin

process(Clock, Read, Write)
begin
    if (Clock'event and Clock='1') then
        if Read='1' then
            Data_out <= tmp_ram(to_integer(unsigned(Address)));
        else
            Data_out <= (OTHERS => 'Z');
        end if;
        if Write='1' then
            tmp_ram(to_integer(unsigned(Address))) <= Data_in;
        end if;
    end if;
end process;

end behav;
```

Generate scheme for components


Structural VHDL

Major instructions


- component instantiation (port map)
- component instantiation with generic
(generic map, port map)
- **generate scheme for component instantiations
(for-generate)**

Example 1

Example 1

 

A 4-to-1 Multiplexer

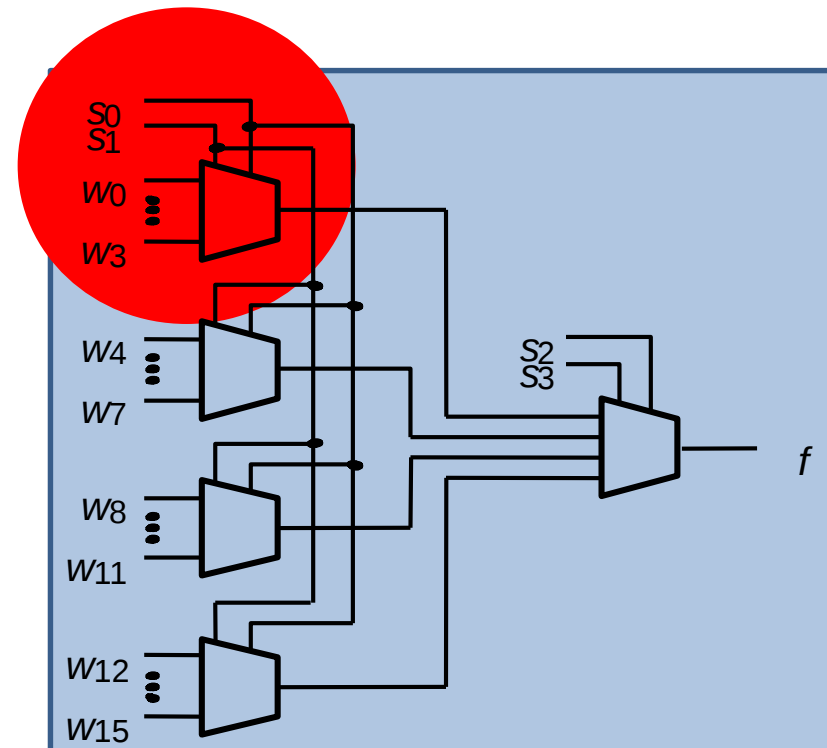

A 4-to-1 Multiplexer

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;
```


```
ENTITY mux4to1 IS  
    PORT (
```

```
        );
```

```
END mux4to1 ;
```

```
ARCHITECTURE Dataflow OF mux4to1 IS  
BEGIN
```

```
END Dataflow ;
```

 

A 4-to-1 Multiplexer

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;
```


```
ENTITY mux4to1 IS
```

```
    PORT (      w0, w1, w2, w3   : IN      STD_LOGIC ;  
               s                 : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;  
               f                 : OUT     STD_LOGIC ) ;
```

```
END mux4to1 ;
```

```
ARCHITECTURE Dataflow OF mux4to1 IS  
BEGIN
```

```
END Dataflow ;
```

 

A 4-to-1 Multiplexer

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;
```


```
ENTITY mux4to1 IS
```

```
    PORT (      w0, w1, w2, w3   : IN      STD_LOGIC ;  
                s                : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;  
                f                : OUT     STD_LOGIC ) ;
```

```
END mux4to1 ;
```

```
ARCHITECTURE Dataflow OF mux4to1 IS  
BEGIN
```

```
END Dataflow ;
```

 


A 4-to-1 Multiplexer

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux4to1 IS
    PORT (
        w0, w1, w2, w3 : IN      STD_LOGIC ;
        s               : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;
        f               : OUT     STD_LOGIC ) ;
END mux4to1 ;

 ARCHITECTURE Dataflow OF mux4to1 IS
    BEGIN
        WITH s SELECT
            f <= w0 WHEN "00",
              w1 WHEN "01",
              w2 WHEN "10",
              w3 WHEN OTHERS ;
    END Dataflow ;
```



A 4-to-1 Multiplexer

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;
```

```
ENTITY mux4to1 IS
```

```
    PORT (      w0, w1, w2, w3   : IN      STD_LOGIC ;  
               s                 : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;  
               f                 : OUT     STD_LOGIC ) ;
```

```
END mux4to1 ;
```


```
ARCHITECTURE Dataflow OF mux4to1 IS  
BEGIN
```

```
    WITH s SELECT
```

```
        f <= w0 WHEN "00",  
            w1 WHEN "01",  
            w2 WHEN "10",  
            w3 WHEN OTHERS ;
```

```
END Dataflow ;
```

Save it as
mux4to1.vhd
file.

 

Straightforward code for Example 1

```
LIBRARY ieee ;
```

```
USE ieee.std_logic_1164.all ;
```


```
ENTITY Example1 IS
```

```
    PORT ( w      : IN      STD_LOGIC_VECTOR(0 TO 15) ;
```

```
          s      : IN      STD_LOGIC_VECTOR(3 DOWNT0 0) ;
```

```
          f      : OUT     STD_LOGIC ) ;
```

```
END Example1 ;
```

 

Straightforward code for Example 1

ARCHITECTURE Structure OF Example1 IS

```

COMPONENT mux4to1
    PORT (
        w0, w1, w2, w3      : IN      STD_LOGIC ;
        s                    : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;
        f                    : OUT      STD_LOGIC ) ;
END COMPONENT ;

```

```


SIGNAL m : STD_LOGIC_VECTOR(0 TO 3) ;

```

```

BEGIN
    Mux1: mux4to1 PORT MAP ( w(0), w(1), w(2), w(3), s(1 DOWNTO 0), m(0) ) ;
    Mux2: mux4to1 PORT MAP ( w(4), w(5), w(6), w(7), s(1 DOWNTO 0), m(1) ) ;
    Mux3: mux4to1 PORT MAP ( w(8), w(9), w(10), w(11), s(1 DOWNTO 0), m(2) ) ;
    Mux4: mux4to1 PORT MAP ( w(12), w(13), w(14), w(15), s(1 DOWNTO 0), m(3) ) ;
    Mux5: mux4to1 PORT MAP ( m(0), m(1), m(2), m(3), s(3 DOWNTO 2), f ) ;
END Structure ;

```

 

Straightforward code for Example 1

ARCHITECTURE Structure OF Example1 IS

You can remove component declaration but then you have to use this format for calling a component:


Mux1: entity work.mux4to1 PORT MAP (...)

```
SIGNAL m : STD_LOGIC_VECTOR(0 TO 3) ;
```

BEGIN

```
Mux1: mux4to1 PORT MAP ( w(0), w(1), w(2), w(3), s(1 DOWNT0 0), m(0) ) ;  
Mux2: mux4to1 PORT MAP ( w(4), w(5), w(6), w(7), s(1 DOWNT0 0), m(1) ) ;  
Mux3: mux4to1 PORT MAP ( w(8), w(9), w(10), w(11), s(1 DOWNT0 0), m(2) ) ;  
Mux4: mux4to1 PORT MAP ( w(12), w(13), w(14), w(15), s(1 DOWNT0 0), m(3) ) ;  
Mux5: mux4to1 PORT MAP ( m(0), m(1), m(2), m(3), s(3 DOWNT0 2), f ) ;
```

END Structure ;

 

Modified code for Example 1

ARCHITECTURE Structure OF Example1 IS

```
COMPONENT mux4to1
  PORT (      w0, w1, w2, w3      : IN      STD_LOGIC ;
           s      : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;
           f      : OUT      STD_LOGIC ) ;
END COMPONENT ;
```

```
SIGNAL m : STD_LOGIC_VECTOR(0 TO 3) ;
```

BEGIN

```
G1: FOR i IN 0 TO 3 GENERATE
```

```
  Muxes: mux4to1 PORT MAP (
```

```
    w(4*i), w(4*i+1), w(4*i+2), w(4*i+3), s(1 DOWNTO 0), m(i) ) ;
```


```
END GENERATE ;
```

```
Mux5: mux4to1 PORT MAP ( m(0), m(1), m(2), m(3), s(3 DOWNTO 2), f ) ;
```

```
END Structure ;
```

Example 2

Example 2

 

A 2-to-4 binary decoder


```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY dec2to4 IS
    PORT ( w      : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;
          En      : IN      STD_LOGIC ;
          y      : OUT     STD_LOGIC_VECTOR(3 DOWNTO 0) ) ;
END dec2to4 ;

ARCHITECTURE Dataflow OF dec2to4 IS
    SIGNAL Enw : STD_LOGIC_VECTOR(2 DOWNTO 0) ;
BEGIN
    Enw <= En & w ;
    WITH Enw SELECT
        y <= "0001" WHEN "100",
            "0010" WHEN "101",
            "0100" WHEN "110",
            "1000" WHEN "111",
            "0000" WHEN OTHERS ;
END Dataflow ;

```

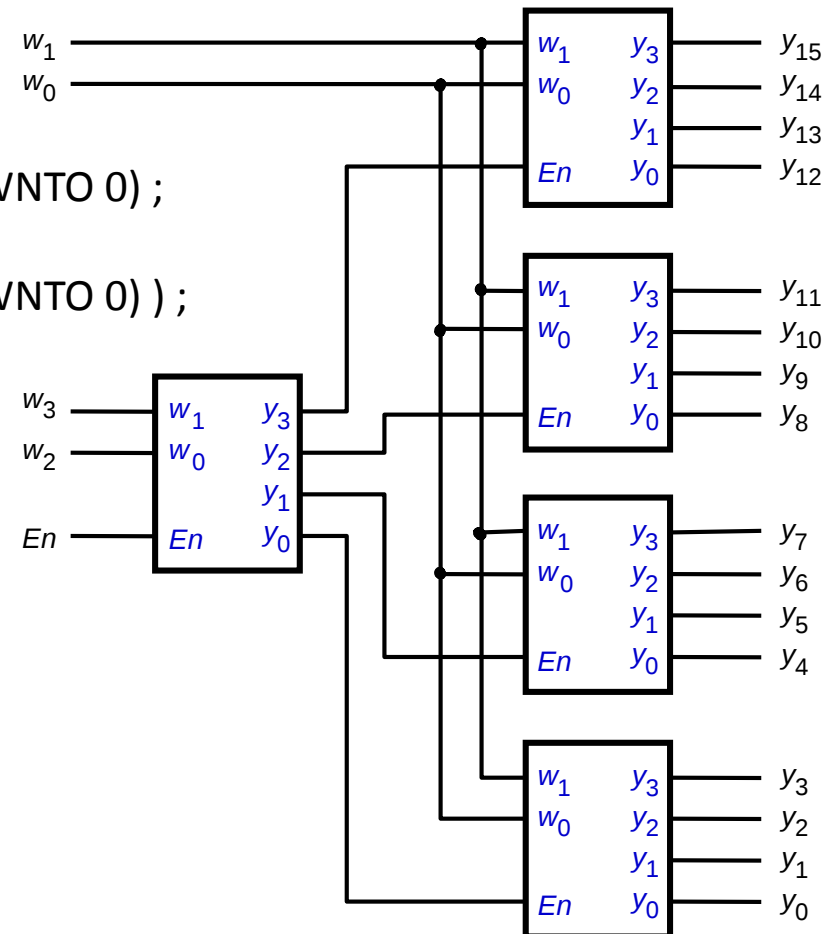

VHDL code for Example 2 (1)

```
LIBRARY ieee ;
```

```
USE ieee.std_logic_1164.all ;
```


```
ENTITY dec4to16 IS
```

```
    PORT (w      : IN      STD_LOGIC_VECTOR(3 DOWNTO 0) ;
```

```
          En     : IN      STD_LOGIC ;
```

```
          y      : OUT     STD_LOGIC_VECTOR(15 DOWNTO 0) ) ;
```

```
END dec4to16 ;
```

 

VHDL code for Example 2 (2)

ARCHITECTURE Structure OF dec4to16 IS

```

COMPONENT dec2to4
  PORT (
    w      : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;
    En     : IN      STD_LOGIC ;
    y      : OUT     STD_LOGIC_VECTOR(3 DOWNTO 0) ) ;
END COMPONENT ;

```

```

SIGNAL m : STD_LOGIC_VECTOR(3 DOWNTO 0) ;

```

BEGIN


G1: FOR i IN 0 TO 3 GENERATE

Dec_ri: dec2to4 PORT MAP (w(1 DOWNTO 0), m(i), y(4*i+3 DOWNTO 4*i));

END GENERATE ;

Dec_left: dec2to4 PORT MAP (w(3 DOWNTO 2), En, m) ;


END Structure ;

 


Example 3

Variable Rotator

Example 3: Variable rotator - Interface

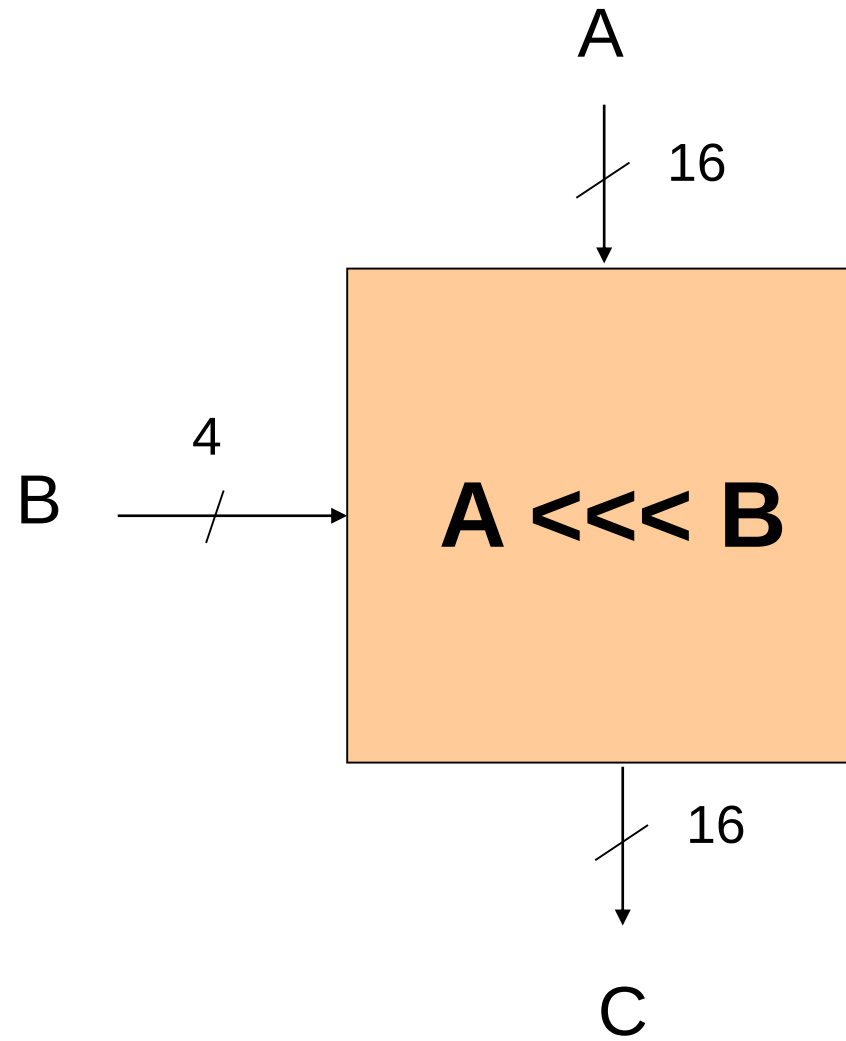

Block diagram

 

VHDL code for a 16-bit 2-to-1 Multiplexer

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;
```

```
ENTITY mux2to1_16 IS
```

PORT (	w0	: IN	STD_LOGIC_VECTOR(15 DOWNT0 0);
	w1	: IN	STD_LOGIC_VECTOR(15 DOWNT0 0);
	s	: IN	STD_LOGIC ;
	f	: OUT	STD_LOGIC_VECTOR(15 DOWNT0 0)) ;


```
END mux2to1_16 ;
```

```
ARCHITECTURE dataflow OF mux2to1_16 IS
```

```
BEGIN
```

```
f <= w0 WHEN s = '0' ELSE w1 ;
```

```
END dataflow ;
```

 

Fixed rotation

a(15) a(14) a(13) a(12) a(11) a(10) a(9) a(8) a(7) a(6) a(5) a(4) a(3) a(2) a(1) a(0)

<<< 3

a(12) a(11) a(10) a(9) a(8) a(7) a(6) a(5) a(4) a(3) a(2) a(1) a(0) a(15) a(14) a(13)

y <= a(12 downto 0) & a(15 downto 13);

a(15) a(14) a(13) a(12) a(11) a(10) a(9) a(8) a(7) a(6) a(5) a(4) a(3) a(2) a(1) a(0)

<<< 5

a(10) a(9) a(8) a(7) a(6) a(5) a(4) a(3) a(2) a(1) a(0) a(15) a(14) a(13) a(12) a(11)

y <= a(10 downto 0) & a(15 downto 11);

Fixed rotation by L positions

a(15) a(14) a(13) a(12) a(11) a(10) a(9) a(8) a(7) a(6) a(5) a(4) a(3) a(2) a(1) a(0)

<<< L

a(15-L) a(15-L-1) a(1) a(0) a(15) a(14) a(15-L+2) a(15-L+1)

y <= a(15-L downto 0) & a(15 downto 15-L+1);

VHDL code for for a fixed 16-bit rotator

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
```

```
ENTITY fixed_rotator_left_16 IS
```

```
    GENERIC ( L : INTEGER := 1);
```


```
    PORT (      a      : IN      STD_LOGIC_VECTOR(15 DOWNT0 0);
             y          : OUT     STD_LOGIC_VECTOR(15 DOWNT0 0) );
```

```
END fixed_rotator_left_16 ;
```

```
ARCHITECTURE dataflow OF fixed_rotator_left_16 IS
BEGIN
```

```
    y <= a(15-L downto 0) & a(15 downto 15-L+1);
```


```
END dataflow ;
```

 

Structural VHDL code for for a variable 16-bit rotator (1)

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

 ENTITY variable_rotator_16 is
    PORT(
        A : IN STD_LOGIC_VECTOR(15 downto 0);
        B : IN STD_LOGIC_VECTOR(3 downto 0);
        C : OUT STD_LOGIC_VECTOR(15 downto 0)
    );
END variable_rotator_16;
```



Structural VHDL code for for a variable 16-bit rotator (2)

ARCHITECTURE structural OF variable_rotator_16 IS

COMPONENT mux2to1_16

PORT (	w0	: IN	STD_LOGIC_VECTOR(15 DOWNT0 0);
	w1	: IN	STD_LOGIC_VECTOR(15 DOWNT0 0);
	s	: IN	STD_LOGIC ;
	f	: OUT	STD_LOGIC_VECTOR(15 DOWNT0 0)) ;

END COMPONENT ;

COMPONENT fixed_rotator_left_16

GENERIC (L : INTEGER := 1);

PORT (	a	: IN	STD_LOGIC_VECTOR(15 DOWNT0 0);
	y	: OUT	STD_LOGIC_VECTOR(15 DOWNT0 0)) ;

END COMPONENT ;

Structural VHDL code for for a variable 16-bit rotator (3)

```

TYPE array1 IS ARRAY (0 to 4) OF STD_LOGIC_VECTOR(15 DOWNT0 0);
TYPE array2 IS ARRAY (0 to 3) OF STD_LOGIC_VECTORS(15 DOWNT0 0);
SIGNAL Al : array1;
SIGNAL Ar : array2;

```

```

BEGIN

```

```

    Al(0) <= A;

```

```

    G: FOR i IN 0 TO 3 GENERATE

```

```

        ROT_I: fixed_rotator_left_16

```

```

            GENERIC MAP (L => 2** i)

```

```

            PORT MAP ( a => Al(i) ,

```

```

                        y => Ar(i));

```

```

        MUX_I: mux2to1_16 PORT MAP (w0 => Al(i),

```

```

                                w1 => Ar(i),

```

```

                                s => B(i),

```

```

                                f => Al(i+1));

```

```

    END GENERATE;

```

```


    C <= Al(4);

```


```

END variable_rotator_16;

```

 

Block diagram

 

Summary of Lecture 4

- Lab processor specifications
 - Datapath and control
 - Instruction Set
- Structural VHDL and tips for regular structures
- Additional Reading material:
 - Lab processor specifications
 - Book (complimentary to the slides):
 - 8.9
- Next Lecture 5:
 - Sequential circuits