

EDA322

Digital Design

Lecture 6:

Sequential Circuits


Ioannis Sourdis

Outline of Lecture 6

- Introduction to sequential circuits
- Latches, Flip-flops
- Registers, Shift-registers, Counters
- Manual design steps
- Two design examples

Sequential circuits

 - The outputs depend not only on the **present inputs** but also on the **past behavior** of the circuit.
- Include memory elements
 - in addition to combination logic
- The contents of the memory elements represent the *state* of the circuit
- The circuit state transitions through a sequence of states




The general form of a sequential circuit.

$Q1 \rightarrow Q2 \rightarrow Q3 \dots$


State-Holding Memory Elements

- Latch versus Flip-Flop
 - Latches are level-sensitive:
 - whenever clock is high, latch is transparent (output $\leq$ input)
 - whenever clock is low, latch keeps its previous value
 - Flip-flops are edge-sensitive: data passes through (i.e. data is sampled) only on a rising (or falling) edge of the clock
 - Latches cheaper to implement than flip-flops
 - Flip-flops are easier to design with than latches
- In this course, primarily use D flip-flops


Cross-coupled NOR gates

 

 - If both $R=0$ & $S=0$, then cross-coupled NORs equivalent to a stable latch:




 - What happens if R or S or both become $= 1$?




NOR	
00	1
01	0
10	0
11	0

Cross-coupled NOR gates

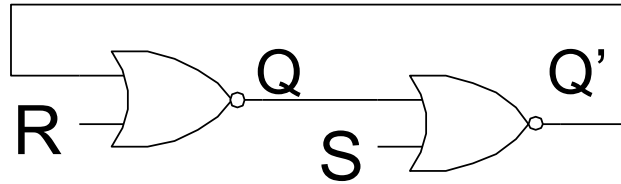


NOR	
00	1
01	0
10	0
11	0

 
- If both $R=0$ & $S=0$, then cross-coupled NORs equivalent to a stable latch:



 - What happens if R or S or both become = 1?




Cross-coupled NOR gates

 


NOR	
00	1
01	0
10	0
11	0

 
- If both $R=0$ & $S=0$, then cross-coupled NORs equivalent to a stable latch:



 - What happens if R or S or both become $= 1$?



Asynchronous State Transition Diagram

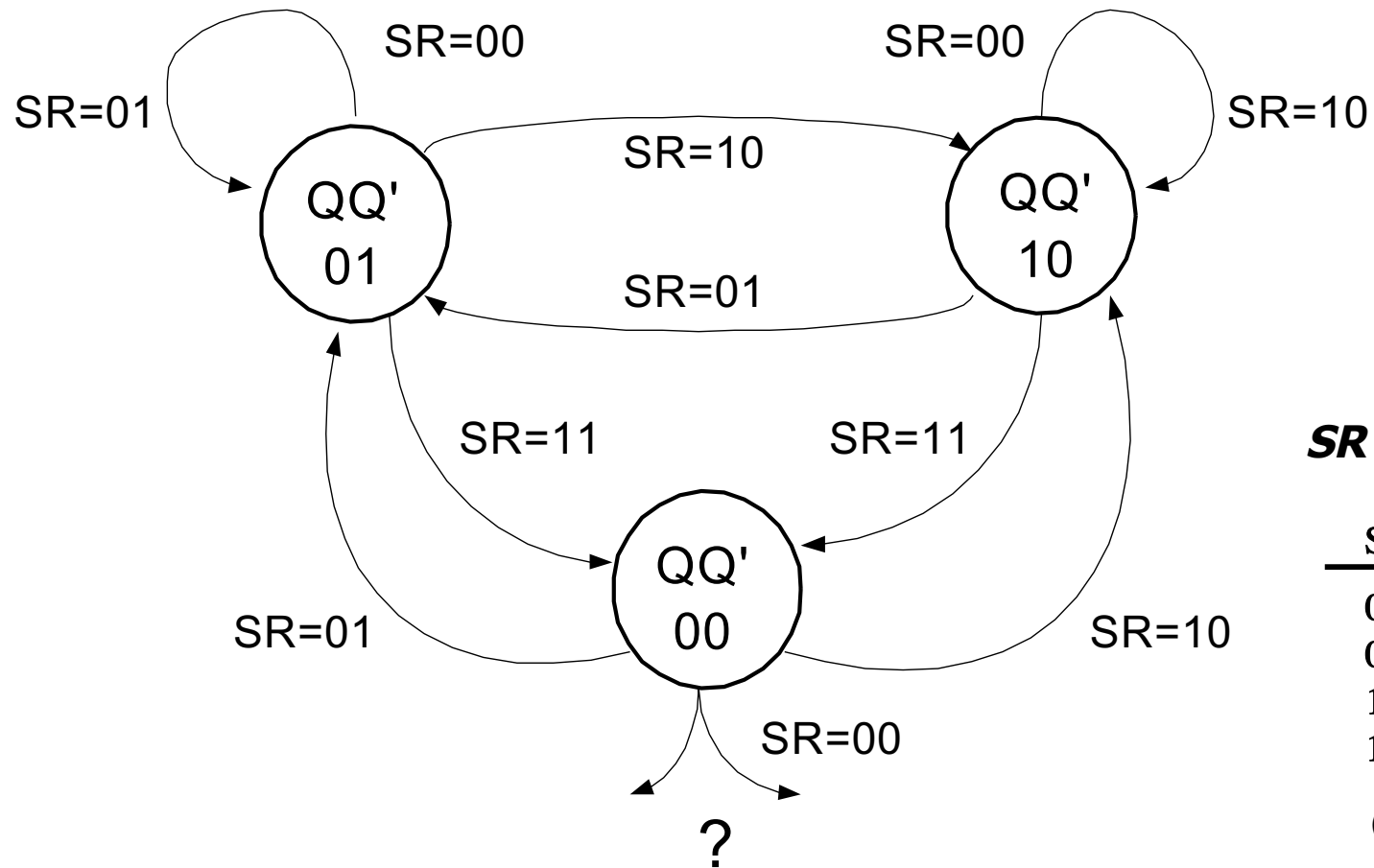


SR Latch:

S	R	Q	Q'
0	0	0/1	1/0 (no change)
0	1	0	1
1	0	1	0
1	1	0	0

(b) Truth table

SR-latch timing diagram

 


(c) Timing diagram

SR Latch:


S	R	Q	Q'
0	0	0/1	1/0 (no change)
0	1	0	1
1	0	1	0
1	1	0	0

(b) Truth table

 

(a) Circuit

NAND-gate based SR latch

 


(a) Logic diagram

S	R	Q	Q'
1	0	0	1
1	1	0	1 (after $S = 1, R = 0$)
0	1	1	0
1	1	1	0 (after $S = 0, R = 1$)
0	0	1	1

(b) Function table


Level-sensitive SR latch

 

(a) Circuit

Clk	S	R	$Q(t+1)$
0	x	x	$Q(t)$ (no change)
1	0	0	$Q(t)$ (no change)
1	0	1	0
1	1	0	1
1	1	1	x

(b) Truth table

 


(a) Logic diagram

C	S	R	Next state of Q
0	x	x	No change
1	0	0	No change
1	0	1	$Q = 0$; Reset state
1	1	0	$Q = 1$; set state
1	1	1	Indeterminate

(b) Function table

Requires fewer transistors


D-latch

 

(a) Logic diagram


C	D	Next state of Q
0	X	No change
1	0	$Q = 0$; Reset state
1	1	$Q = 1$; Set state

(b) Function table

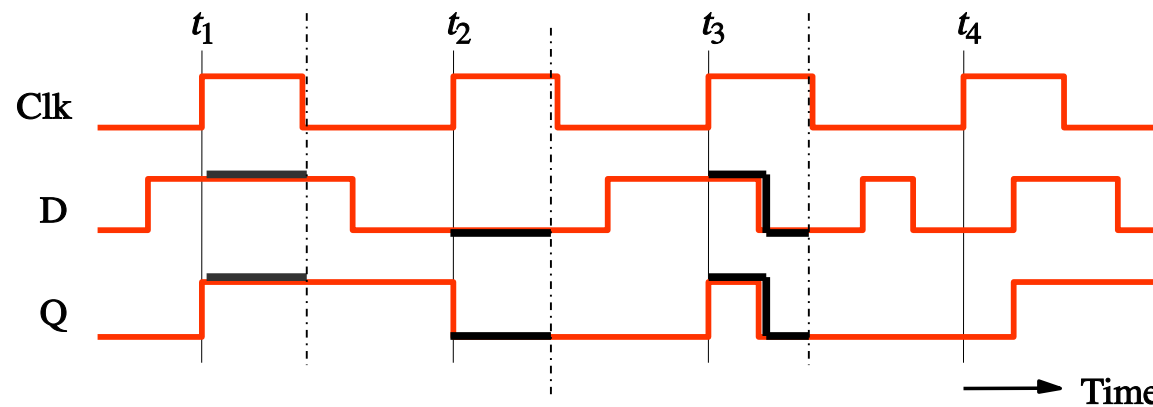


(d) Timing diagram

Master-Slave D Flip-flop

 


(a) Circuit

 


(b) Timing diagram

Positive edge triggered D-Flip-flops

 


D-Type Positive-Edge-Triggered Flip-Flop

Positive edge triggered D-Flip-flops

 

Positive edge triggered D-Flip-flops

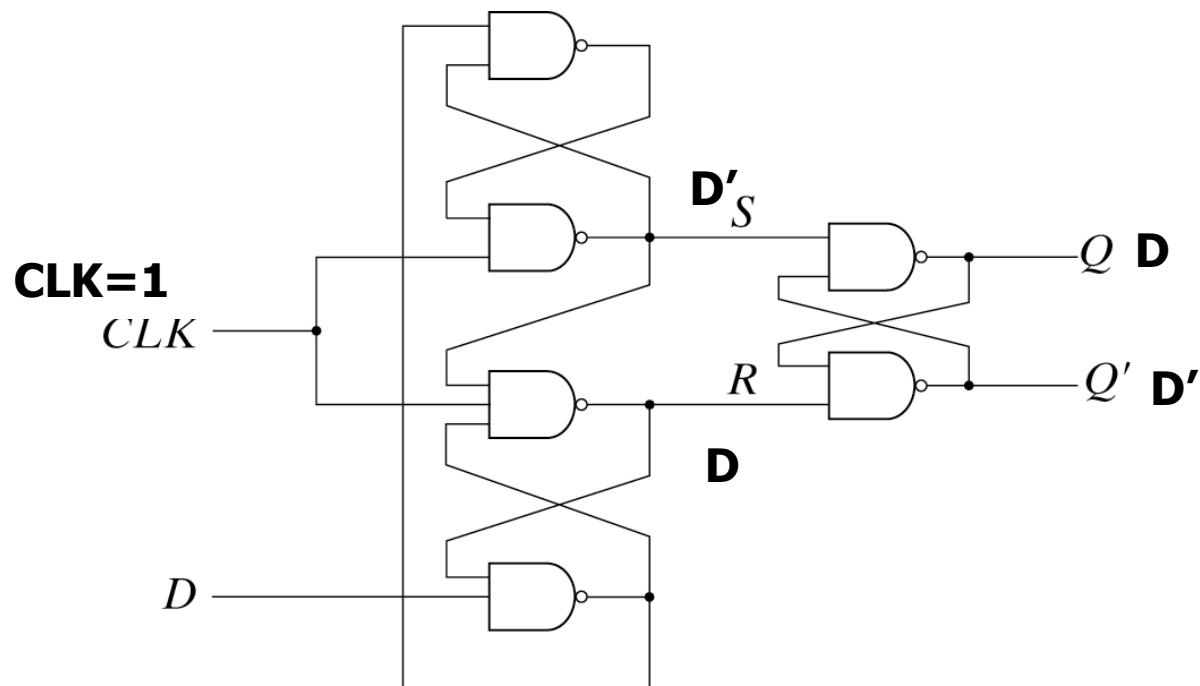


D-Type Positive-Edge-Triggered Flip-Flop


Setup & Holdtime

D must be stable when clock is changing from 0->1 (setup time)

 D must remain stable for a while after clock change from 0-> 1 (hold time)




D Flip-flop

 

Negative-edge DFF



Positive-edge

 **Preset and clear:
active low;
not 0 at same time**






with preset and Clear

  Latch vs. Positive triggered FF vs. Negative triggered FF




Reset of D flip-flop

  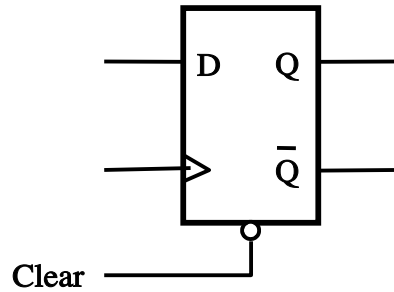


T Flip-flop

T	$Q(t+1)$
0	$Q(t)$
1	$\bar{Q}(t)$

(b) Truth table

 

(c) Graphical symbol

 


(d) Timing diagram

JK Flip-flop

J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\bar{Q}(t)$

(b) Truth table

 

(c) Graphical symbol

Quiz 4-1

<http://m.socrative.com/student/#joinRoom>

room number: 713113


- Q2: What happens to the Q and Q' outputs of an SR-latch when S-R are:
 - 00
 - 01
 - 10
 - 11

Registers, Shift Registers, Counters

Register

- A register contains **N** flip-flops.
- A flip-flop stores 1-bit information; a register stores N-bit information.
- Usually a common clock is used for each flip-flop in the register.


Shift register

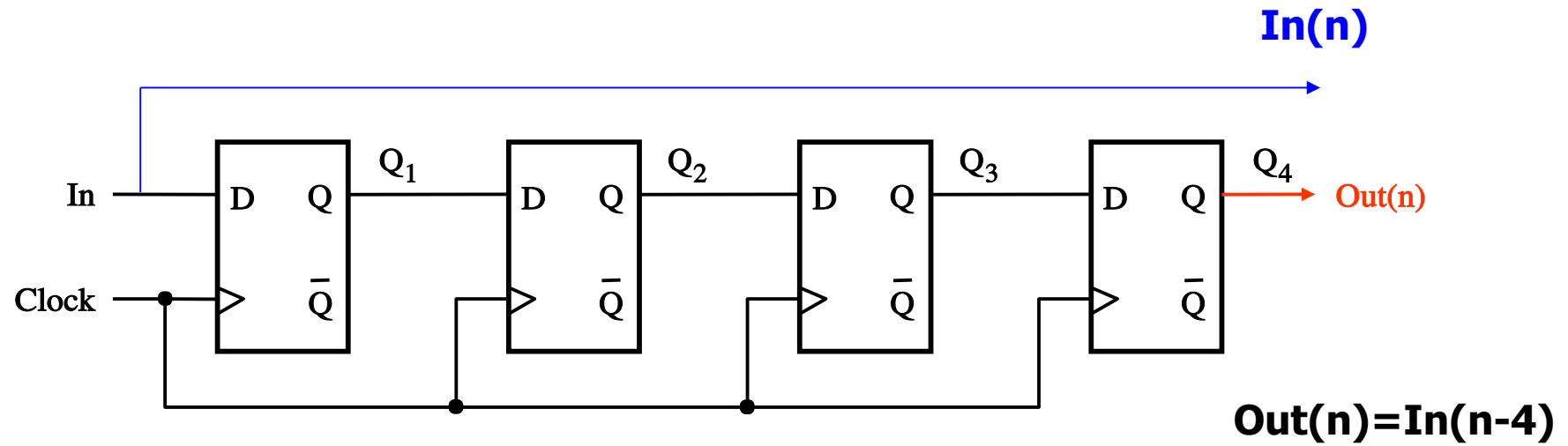


	In	Q ₁	Q ₂	Q ₃	Q ₄ = Out
t_0	1	0	0	0	0
t_1	0	1	0	0	0
t_2	1	0	1	0	0
t_3	1	1	0	1	0
t_4	1	1	1	0	1
t_5	0	1	1	1	0
t_6	0	0	1	1	1
t_7	0	0	0	1	1

Applications:


 
- 1) division by 2 $\leftrightarrow$ shift right by 1bit
- 2) implement delay elements in DSP




 


Parallel-shift register



Up-Counter

  

Down-counter

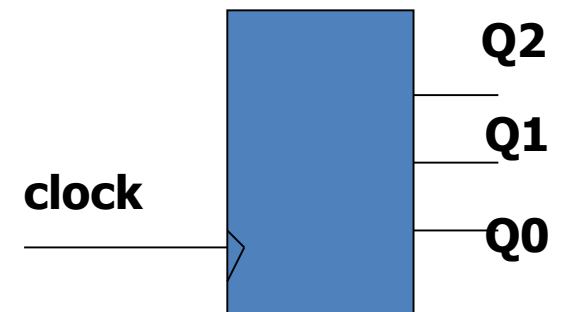 


Counter with parallel load

  

Design of Sequential circuits

 Example of sequential circuit

- Sequence detector
 - To detect two consecutive 1s in an input sequence.
 - Output will indicate if there are two immediate 1s.



Clockcycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	0	1	0	0	1	1	0

General form of a sequential circuit

Realized using combinational logic and flip-flops


Primary inputs: w

Outputs: z

State: Q

Moore FSMs: outputs depend only on the state

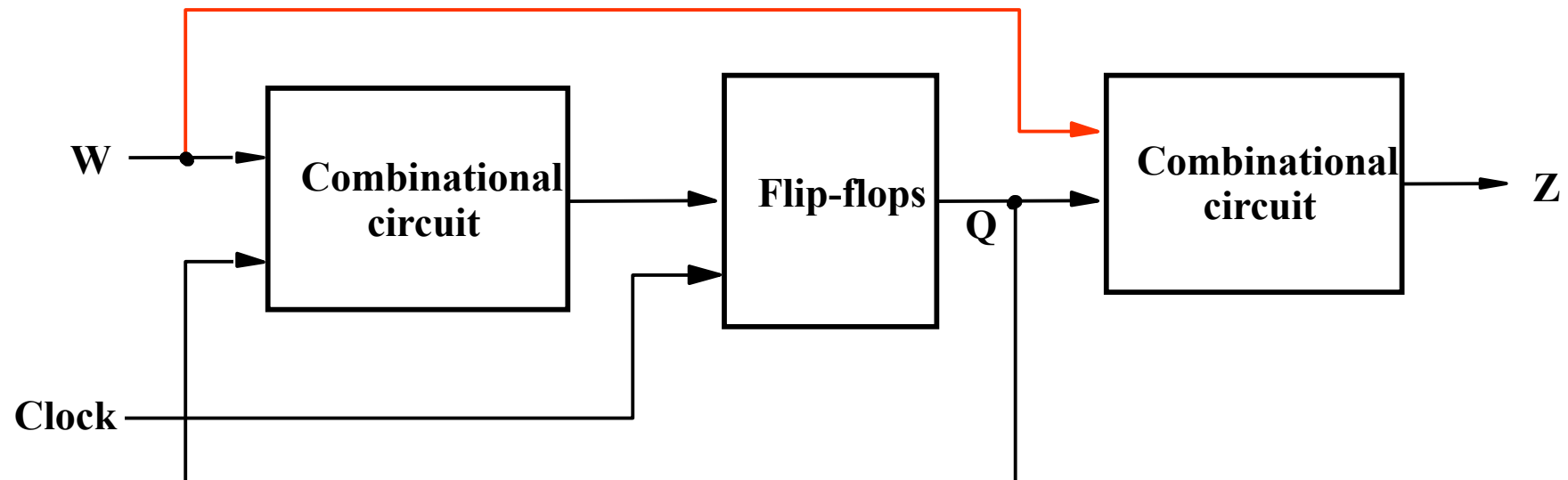Mealy FSMs: outputs depend on both state and primary inputs



Manual design steps (1): specifications

Specifications:

1. the circuit has one input, w , and one output, z .
2. all changes in the circuit occur on the positive edge of a clock signal.
3. the output z is equal to 1 if during two immediately preceding clock cycles the input w was equal to 1. otherwise, the value of z is equal to 0.

Clockcycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	0	1	0	0	1	1	0

Manual design steps (2): state diagram

- *starting* state **A**: when power is on or *reset* signal is applied.
- As long as w is 0, it remains in **A**.
- After $w \rightarrow 1$, it moves to state **B**.
- Then,
 - If $w \rightarrow 0$, it moves back to state **A**.
 - If $w \rightarrow 1$, it moves to state **C**, and $z=1$.
- When in state **C**,
 - If $w \rightarrow 0$, back to state **A**, and $z=0$;
 - If $w \rightarrow 1$, remain in state **C**.

 


Figure 8.3. State diagram of a simple sequential circuit.

Manual design steps (3): state table

From the state diagram, we have the state table

Flip-flops

Present state	Next state		Output z
	$w = 0$	$w = 1$	
A	A	B	0
B	A	C	0
C	A	C	1

Combinational circuit


Combinational circuit

Manual design steps (4): state assignment

A: 00
B: 01
C: 10

	Present state $y_2 y_1$	Next state		Output z
		$w = 0$	$w = 1$	
		$Y_2 Y_1$	$Y_2 Y_1$	
A	00	00	01	0
B	01	00	10	0
C	10	00	10	1
	11	<i>dd</i>	<i>dd</i>	<i>d</i>

Circuit diagram

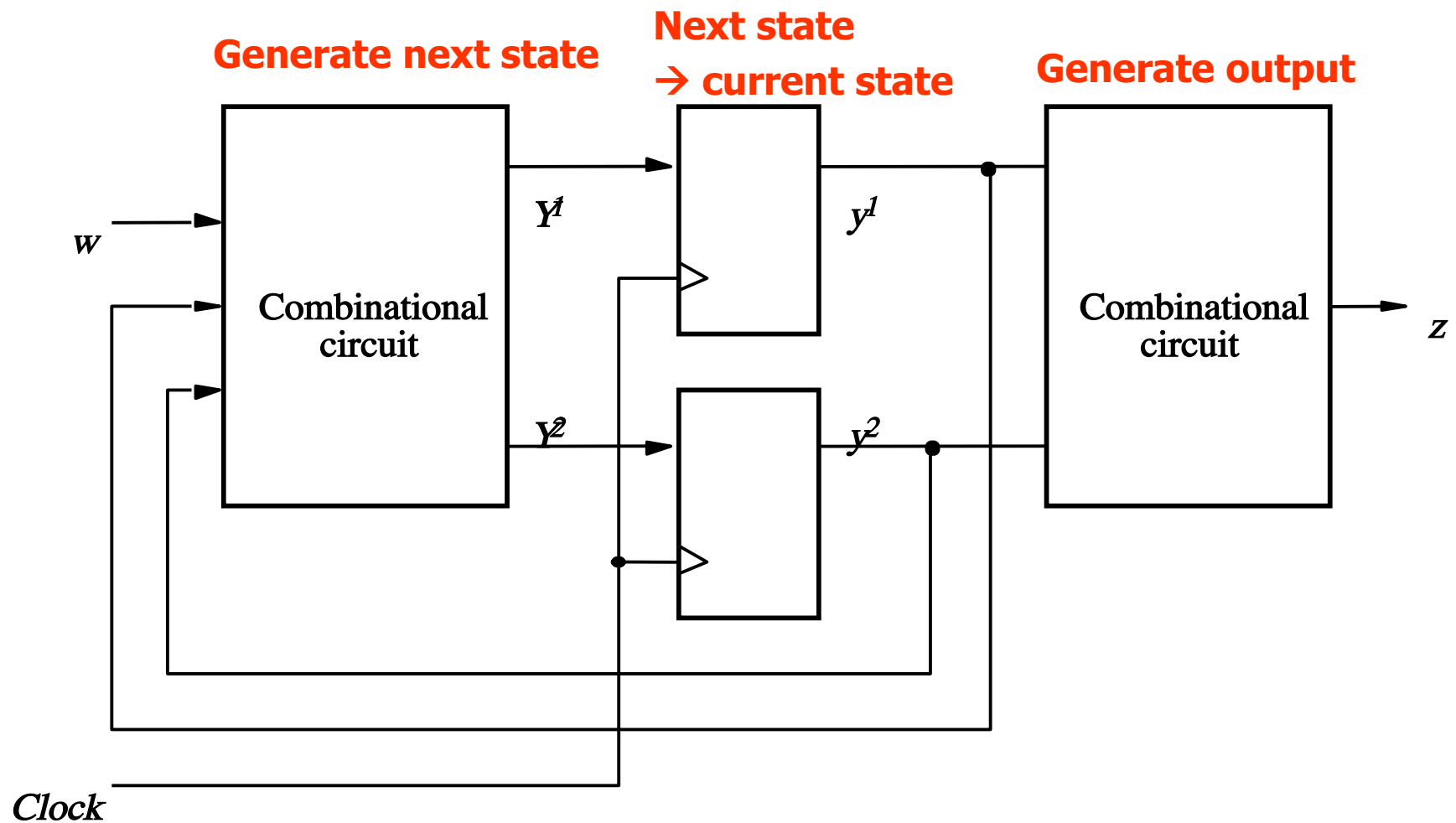

Manual design steps (5): implementation

From state-assigned table: we have the following Karnaugh maps

$y_2 y_1$		00	01	11	10
w	0	0	0	d	0
	1	1	0	d	0

$$Y_1 = w\bar{y}_1\bar{y}_2$$


y_1		0	1
y_2	0	0	0
	1	1	d

$$z = y_2$$


$y_2 y_1$		00	01	11	10
w	0	0	0	d	0
	1	0	1	d	1

$$\begin{aligned} Y_2 &= wy_1 + wy_2 \\ &= w(y_1 + y_2) \end{aligned}$$


Final implementation

 

Timing diagram

 


One more example

 

Specifications:

- 1) After *w*: 0 → 1, R2 → R3 (*R2 out* = 1, *R3 in* = 1).
- 2) then, R1 → R2 (*R1 out* = 1, *R2 in* = 1), regardless of *w*
- 3) then, R3 → R1 (*R3 out* = 1, *R1 in* = 1), regardless of *w*, *done* = 1.

State diagram

 


State table


Present state	Next state		Outputs						
	$w = 0$	$w = 1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	$Done$
A	A	B	0	0	0	0	0	0	0
B	C	C	0	0	1	0	0	1	0
C	D	D	1	0	0	1	0	0	0
D	A	A	0	1	0	0	1	0	1

	Present state	Nextstate		Outputs						
		$w = 0$	$w = 1$							
	y_2y_1	Y_2Y_1	Y_2Y_1	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	$Done$
A	00	00	0 1	0	0	0	0	0	0	0
B	01	10	1 0	0	0	1	0	0	1	0
C	10	11	1 1	1	0	0	1	0	0	0
D	11	00	0 0	0	1	0	0	1	0	1

Expressions of next state and outputs

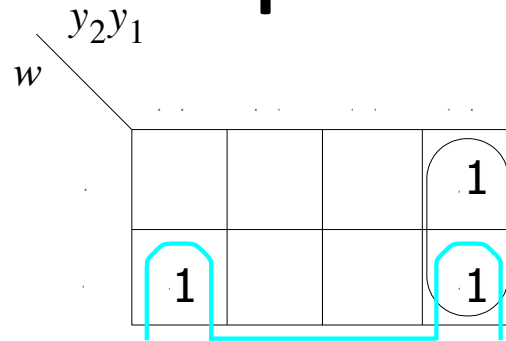

$$Y_1 = w\bar{y}_1 + \bar{y}_1y_2$$

 


$$Y_2 = y_1\bar{y}_2 + \bar{y}_1y_2$$

$$R1_{out} = R2_{in} = \bar{y}_1y_2$$

$$R1_{in} = R3_{out} = Done = y_1y_2$$

$$R2_{out} = R3_{in} = y_1\bar{y}_2$$

Final implementation

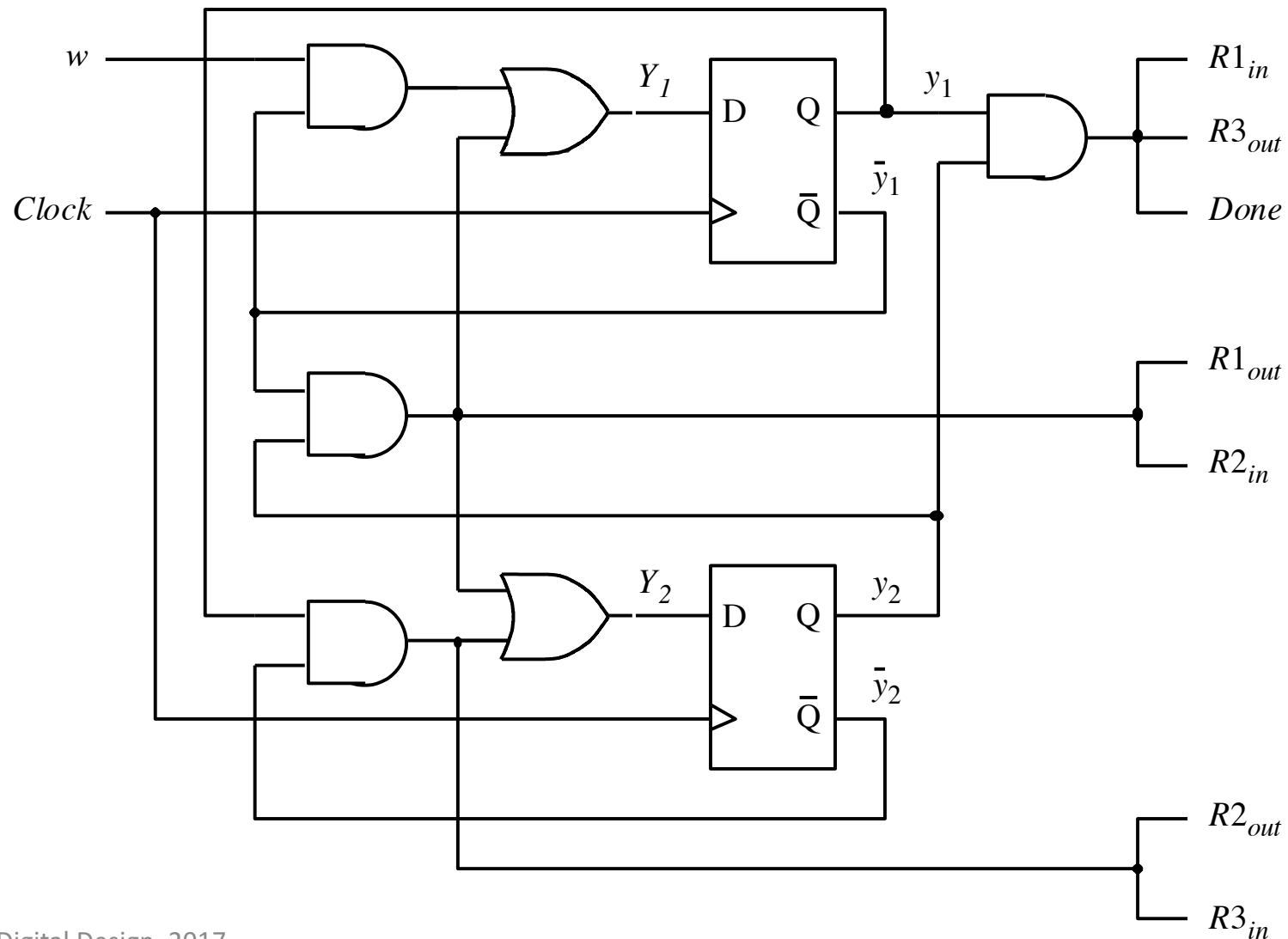

Summary of design steps

- Specifications
- Derive the states, and create a state diagram
- Create a state table
- (State minimization)
- State assignment
- Choose flip-flops
- Derive logic expressions for state and outputs
- Implementation

Quiz 4-2

<http://m.socrative.com/student/#joinRoom>

room number: 713113

- Q1: A D-flipflop is edge triggered when input is stored when
 - Clock =1
 - Clock is changing from 0 to 1
- Q2: An (active when '1') asynchronous reset resets the value of a D-flip-flop to zero when:
 - Reset=1 and clock =1
 - Reset=1
 - Reset=1, and D=0
 - Reset=1, clock=1, and D=0
- Q3: A sequential circuit that the output depends both at the current state and its inputs is
 - A Mealy
 - A Moore

Summary of Lecture 6

- Introduction to sequential circuits
- Latches
- flip-flops
- Registers, Shift-registers, Counters
- Manual design steps
- Two design examples
- Book (complimentary to the slides):
 - Chapters 14, 27.1, 27.2
- Next Lecture 7:
 - Sequential circuits **VHDL**