

EDA322

Digital Design

Lecture 8:

Finite State Machines (FSMs)

Ioannis Sourdis

Outline of Lecture 8

- Finite State Machines
 - Moore
 - Mealy
- State assignment
- State minimization

General form of a sequential circuit

Realized using combinational logic and flip-flops


Primary inputs: w

Outputs: z

State: Q


Moore FSMs: outputs depend only on the state

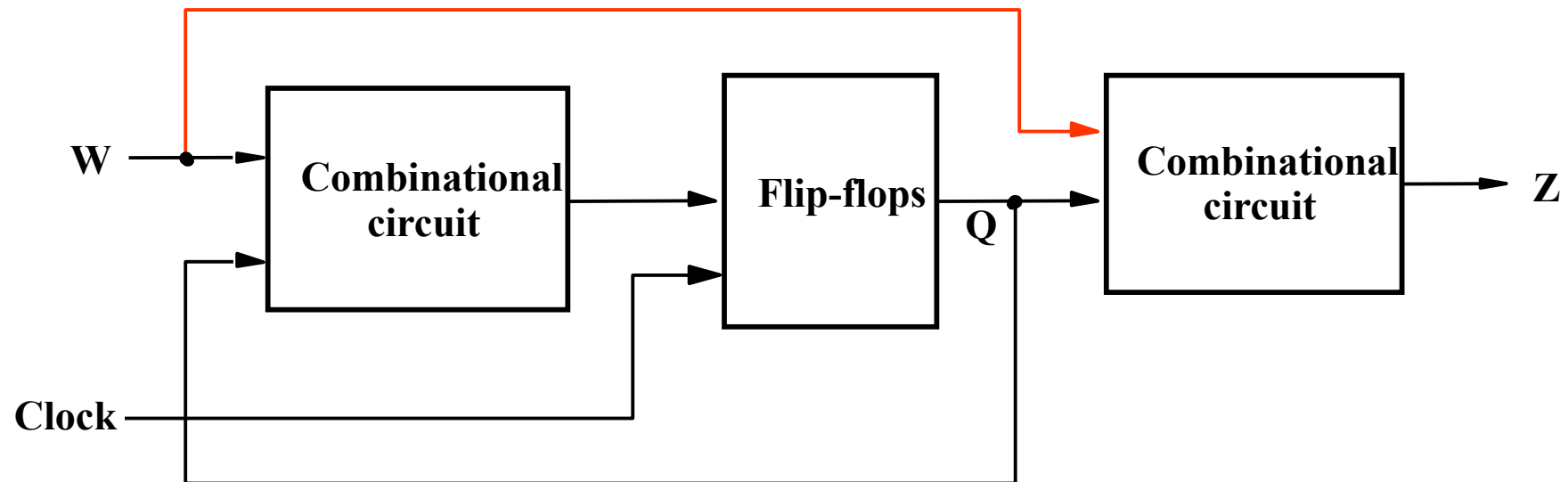Mealy FSMs: outputs depend on both state and primary inputs




Two types of FSMs

Moore-type

 

Mealy-type

 

Example: 1-1 detector

1-1 detector: generate an output $z=1$ whenever a second $w=1$ is detected in consecutive clock cycles

Moore-type


The output z be equal to 1 in the clock Cycle that follows the detection of the second $w=1$



Clockcycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	0	1	0	0	1	1	0

Mealy-type

 
The output z be equal to 1 in the same clock cycle when the second $w=1$ is detected




Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	1	0	0	1	1	0	0

Example: 1-1 detector: state diagram

Moore-type

 

Mealy-type

 

Fewer states

Example: 1-1 detector state table

Moore-type

Present state	Next state		Output z
	$w = 0$	$w = 1$	
A	A	B	0
B	A	C	0
C	A	C	1

Mealy-type

Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	A	B	0	1

	Present state $y_2 y_1$	Next state		Output z
		$w = 0$	$w = 1$	
		$Y_2 Y_1$	$Y_2 Y_1$	
A	00	00	01	0
B	01	00	10	0
C	10	00	10	1
	11	dd	dd	d

	Present state y	Next state		Output	
		$w = 0$	$w = 1$	$w = 0$	$w = 1$
		Y	Y	z	z
A	0	0	1	0	0
B	1	0	1	0	1

Example: 1-1 detector

Boolean expressions derivation (Moore)

From state-assigned table: we have the following Karnaugh maps

		$y_2 y_1$			
		00	01	11	10
w	0	0	0	d	0
	1	1	0	d	0

$$Y_1 = w\bar{y}_1\bar{y}_2$$

		y_1	
		0	1
y_2	0	0	0
	1	1	d


$$z = y_2$$

		$y_2 y_1$			
		00	01	11	10
w	0	0	0	d	0
	1	0	1	d	1

$$\begin{aligned} Y_2 &= wy_1 + wy_2 \\ &= w(y_1 + y_2) \end{aligned}$$

Example: 1-1 detector

Final implementation (Moore)

 


Example: 1-1 detector

Final implementation (Mealy)


$$Y = w$$

$$z = wy$$

 


Example: 1-1 detector

Moore-type

 

Mealy-type

 


Simpler!

Note that the function is not exactly the same


Example: 1-1 detector

Timing diagram

Moore-type

 


Mealy-type

 

Swapping Register contents

$R2 \leftrightarrow R1$, using R3 as tmp

 


Specifications:

- 1) After *w*: 0 → 1, $R2 \rightarrow R3$ ($R2out=1$, $R3in=1$).
- 2) then, $R1 \rightarrow R2$ ($R1out=1$, $R2in=1$), regardless of *w*
- 3) then, $R3 \rightarrow R1$ ($R3out=1$, $R1in=1$), regardless of *w*, *done*=1.


Example: control circuit for swapping registers

Moore-type

 


4 states

Mealy-type

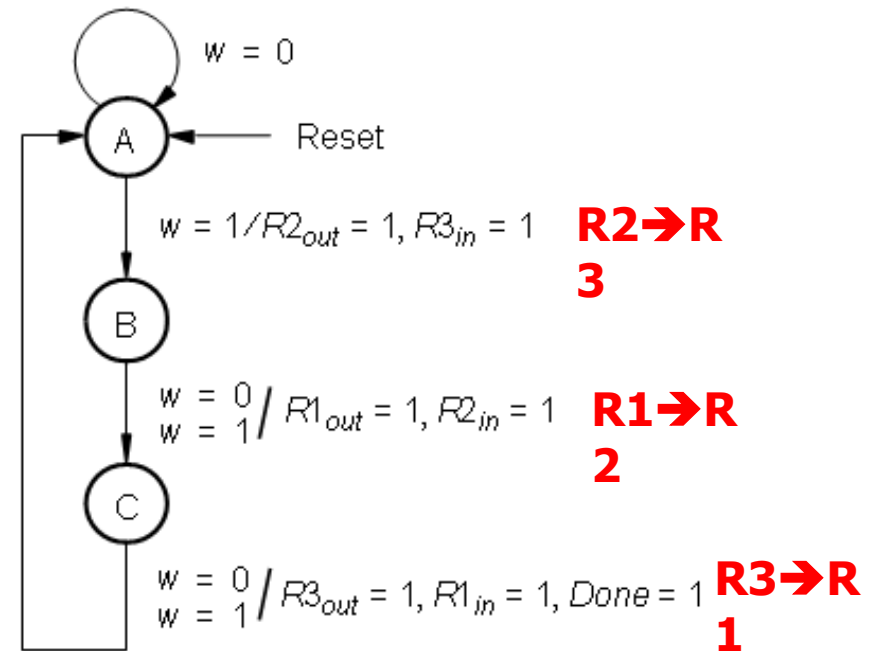

3 states

Moore State diagram

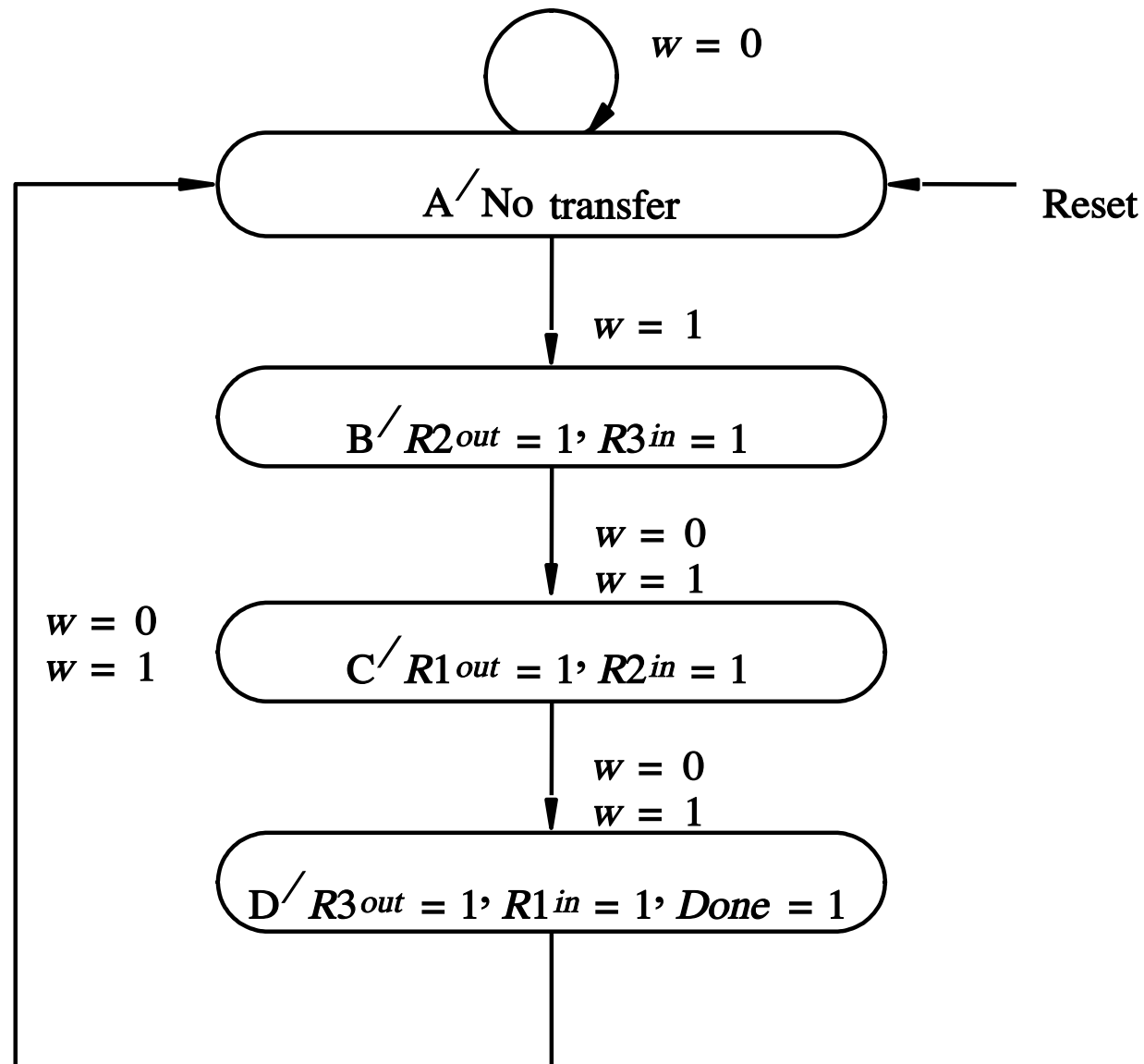


Moore State table

Present state	Next state		Outputs						
	$w = 0$	$w = 1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	$Done$
A	A	B	0	0	0	0	0	0	0
B	C	C	0	0	1	0	0	1	0
C	D	D	1	0	0	1	0	0	0
D	A	A	0	1	0	0	1	0	1


	Present state	Nextstate		Outputs						
		$w = 0$	$w = 1$							
	y_2y_1	Y_2Y_1	Y_2Y_1	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	$Done$
A	00	00	0 1	0	0	0	0	0	0	0
B	01	10	1 0	0	0	1	0	0	1	0
C	10	11	1 1	1	0	0	1	0	0	0
D	11	00	0 0	0	1	0	0	1	0	1

Moore:

Expressions of next state and outputs

 

$$Y_1 = w\bar{y}_1 + \bar{y}_1y_2$$

 


$$Y_2 = y_1\bar{y}_2 + \bar{y}_1y_2$$

$$R1_{out} = R2_{in} = \bar{y}_1y_2$$


$$R1_{in} = R3_{out} = Done = y_1y_2$$

$$R2_{out} = R3_{in} = y_1\bar{y}_2$$


Final Moore implementation

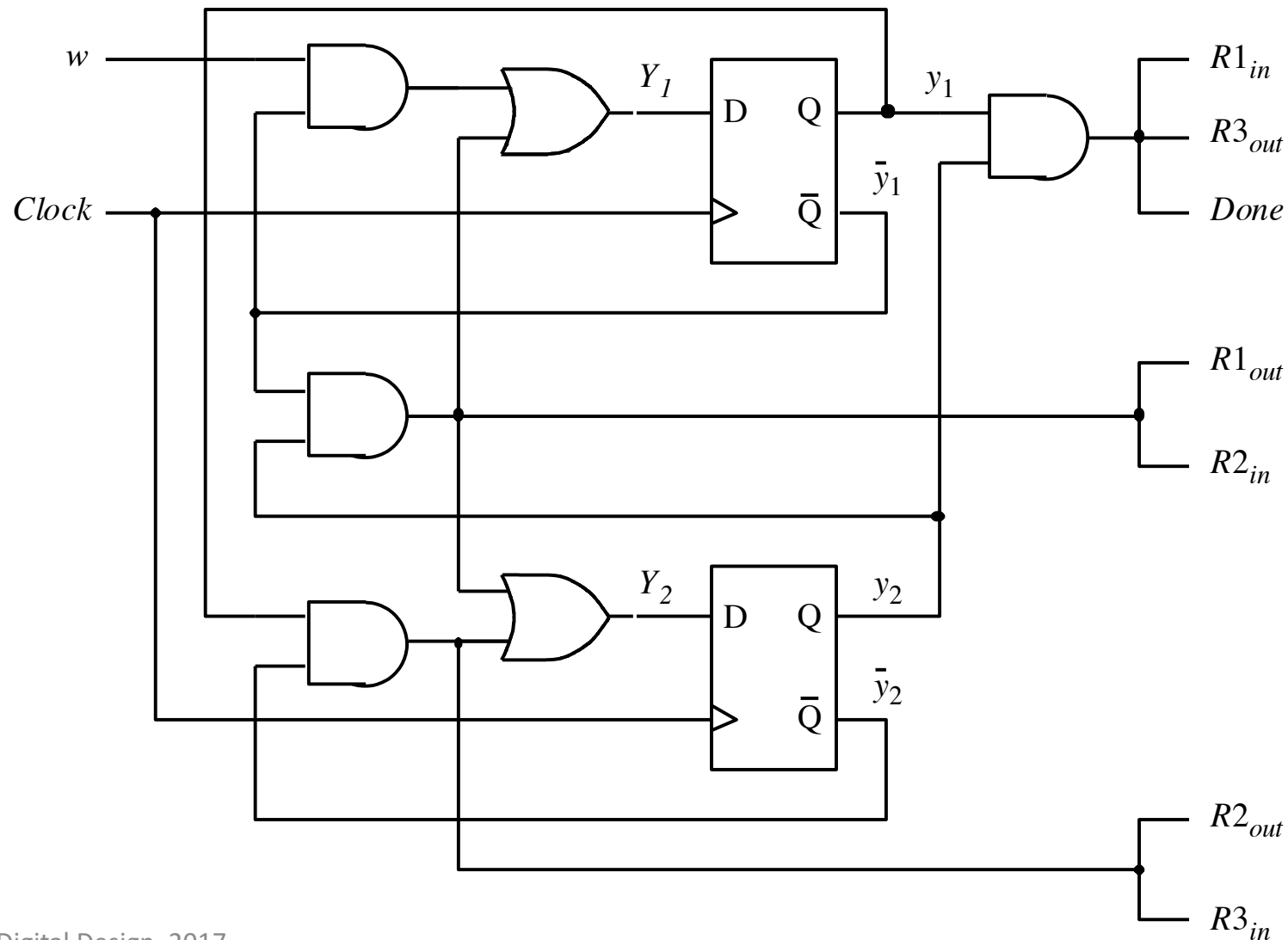

Mealy state diagram

 

Mealy-type

 

3 states

Present state	Next state		Outputz	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	R2out, R3in
B	C	C	R1out, R2in	
C	A	A	R3out, R1in, Done	

By inspection

y3y2y1

A: 0 0 1
B: 0 1 0
C: 1 0 0


One-hot

$$Y1 = \overline{w}y1 + y3 \quad R2_{out} = R3_{in} = wy1$$


$$Y2 = wy1 \quad R1_{out} = R2_{in} = y2$$

$$Y3 = y2 \quad R3_{out} = R1_{in} = done = y3$$

 Example: control circuit for swapping registers



Mealy-type

 

Summary of FSMs

Most of tasks can be realized by Moore-type FSM, as well as by Mealy-type FSM, although these two type FSMs don't have the exact same logic function

Compared to Moore-type FSMs, Mealy-type FSMs have following features:

Less states;

Quicker response;

Usually, simpler circuit implementation;

**But, sometimes longer critical path, all the way from input to output
(v.s. Moore: from state registers to output)**

- one solution: registered outputs in Mealy

FSM design by CAD tools

- Different ways of FSM design using CAD tools:
 - Derive circuits from a state diagram manually → draw a schematic into CAD systems or HDL code → simulate → implement in a chip (e.g. PLD).
 - Enter state diagram into CAD systems using a graphical tool → automatically synthesize.
 - Write HDL code for state diagram → automatically synthesize. (✓)

Quiz 7-1

<http://m.socrative.com/student/#joinRoom>

room number: 713113

- Q1: A Mealy machine would change its output at the same clock cycle an input is modified.
 - True/false
- Q2: Each state of a Mealy machine has a single set of outputs
 - True/false
- Q3: The circuit of a Mealy machine is usually simpler
 - True/false

State Assignment Problem

State Assignment Problem

- Some state assignments are better than others.
- The state assignment influences the complexity of the state machine.
 - **The combinational logic required in the state machine design is dependent on the state assignment.**
- Types of state assignment
 - Binary encoding: 2^N states $\rightarrow$ N Flip-Flops
 - Gray-code encoding: 2^N states $\rightarrow$ N Flip-Flops
 - One-hot encoding: N states $\rightarrow$ N Flip-Flops

FSM: State Assignment

Example:

Design a FSM that detects a sequence of two or more consecutive ones on an input bit stream.


The FSM should output a 1 when the sequence is detected, and a 0 otherwise.

This is another example of a *sequence detector*.

FSM: State Assignment

Input: 0 1 1 1 0 1 0 1 1 0 1 1 1 0 1 ...
Output: 0 0 1 1 0 0 0 0 1 0 0 1 1 0 0 ...

FSM: State Assignment

 

**State
Diagram**

FSM: State Assignment

Present State	Next State		Output
	w = 0	w = 1	
S_0	S_0	S_1	0
S_1	S_0	S_2	0
S_2	S_0	S_2	1

State Table

FSM: State Assignment #1

State Assigned Table

Present State			Next State						Output
			w = 0			w = 1			
	Q_A	Q_B		Q_A^+	Q_B^+		Q_A^+	Q_B^+	z
S_0	0	0	S_0	0	0	S_1	0	1	0
S_1	0	1	S_0	0	0	S_2	1	0	0
S_2	1	0	S_0	0	0	S_2	1	0	1
	1	1		d	d		d	d	d

Using Binary Encoding
for the State Assignment

FSM: State Assignment #1

State Assigned Table

Present State			Next State				FF Inputs			
			w = 0		w = 1		w = 0		w = 1	
	Q_A	Q_B	Q_A^+	Q_B^+	Q_A^+	Q_B^+	D_A	D_B	D_A	D_B
S_0	0	0	0	0	0	1	0	0	0	1
S_1	0	1	0	0	1	0	0	0	1	0
S_2	1	0	0	0	1	0	0	0	1	0
	1	1	d	d	d	d	d	d	d	d

Characteristic Equation: $D = Q^+$

FSM: State Assignment #1

$Q_A Q_B$		00	01	11	10
w	0	0	0	d	0
	1	1	0	d	0

$$D_B = w\bar{Q}_A\bar{Q}_B$$


$Q_A Q_B$		0	1
Q_B	0	0	0
	1	1	d

$$z = Q_A$$

$Q_A Q_B$		00	01	11	10
w	0	0	0	d	0
	1	0	1	d	1

$$\begin{aligned} D_A &= wQ_A + wQ_B \\ &= w(Q_A + Q_B) \end{aligned}$$

FSM: State Assignment #1

 

FSM: State Assignment #2

State Assigned Table

Present State			Next State						Output
			w = 0			w = 1			
	Q_A	Q_B		Q_A^+	Q_B^+		Q_A^+	Q_B^+	z
S_0	0	0	S_0	0	0	S_1	0	1	0
S_1	0	1	S_0	0	0	S_2	1	1	0
S_2	1	1	S_0	0	0	S_2	1	1	1
	1	0		d	d		d	d	d

Using Gray-code Encoding
for the State Assignment

FSM: State Assignment #2

State Assigned Table

Present State			Next State				FF Inputs			
			w = 0		w = 1		w = 0		w = 1	
	Q_A	Q_B	Q_A^+	Q_B^+	Q_A^+	Q_B^+	D_A	D_B	D_A	D_B
S_0	0	0	0	0	0	1	0	0	0	1
S_1	0	1	0	0	1	1	0	0	1	1
S_2	1	1	0	0	1	1	0	0	1	1
	1	0	d	d	d	d	d	d	d	d

Characteristic Equation: $D = Q^+$

FSM: State Assignment #2

$Q_A Q_B$		00	01	11	10
w	0	0	0	0	d
	1	1	1	1	d

$$D_B = w$$


$Q_A Q_B$		00	01	11	10
w	0	0	0	d	0
	1	0	1	1	d

$$D_A = wQ_B$$

Q_B		0	1
Q_A	0	0	0
	1	1	d

$$z = Q_A$$

FSM: State Assignment #2

 

FSM: State Assignment #3

State Assigned Table

Present State				Next State							
				w = 0				w = 1			
	Q_A	Q_B	Q_C		Q_A^+	Q_B^+	Q_C^+		Q_A^+	Q_B^+	Q_C^+
S_0	0	0	1	S_0	0	0	1	S_1	0	1	0
S_1	0	1	0	S_0	0	0	1	S_2	1	0	0
S_2	1	0	0	S_0	0	0	1	S_2	1	0	0

Using One-hot Encoding
for the State Assignment

For each state only one flip-flop is set to 1.
The remaining combination of state variables are not used.

Characteristic Equation: $D = Q^+$

FSM: State Assignment #3

$Q_B Q_C$		$w Q_A$			
		00	01	11	10
00		d	0	d	0
01		0	d	d	d
11		1	d	d	d
10		d	0	d	1

$$D_A = w\bar{Q}_C$$


$Q_B Q_C$		$w Q_A$			
		00	01	11	10
00		d	0	d	0
01		0	d	d	d
11		0	d	d	d
10		d	1	d	0

$$D_B = wQ_C$$


$Q_B Q_C$		$w Q_A$			
		00	01	11	10
00		d	1	d	1
01		1	d	d	d
11		0	d	d	d
10		d	0	d	0

$$D_C = \bar{w}$$


FSM: State Assignment #3

 


State Assignments: comparison

 

Binary

 

Gray

 

One-hot

State Minimization

FSM: State Minimization

Definition:


Two states S_i and S_j are said to be equivalent if and only if for every possible input sequence, the same output sequence will be produced regardless of whether S_i or S_j is the initial state.

State Minimization: Partitioning

Definition:

A partition consists of one or more blocks, where each block comprises a subset of states that *may* be equivalent, but the states in a given block are *definitely not* equivalent to the states in other blocks.

Example:

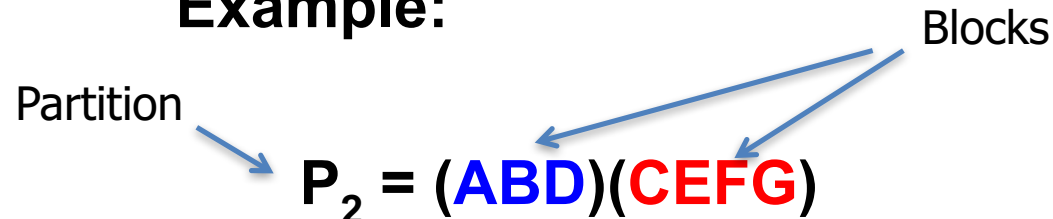Partition  $P_2 = (\text{ABD})(\text{CEFG})$ Blocks

State Minimization: Partitioning

- State Minimization through Partitioning:
 - Form an initial partition (P_1) that includes **all** states.
 - Form a second partition (P_2) by separating the states into blocks based upon their output values.
 - Form a third partition (P_3) by separating the states into blocks corresponding to the next state values.
 - Continue partitioning until two successive partitions are the same (i.e. $P_{N-1} = P_N$).
 - All states in any one block are equivalent.
 - Equivalent states can be combined into a single state.


State Minimization: Partitioning

Example:

Use partitioning to minimize the number of states in the following Finite State Machine (FSM).


State Minimization: Partitioning

State
Diagram

 

State Minimization: Partitioning

Present state	Next state		Output z
	$w=0$	$w=1$	
A	B	C	1
B	D	F	1
C	F	E	0
D	B	G	1
E	F	C	0
F	E	D	0
G	F	G	0

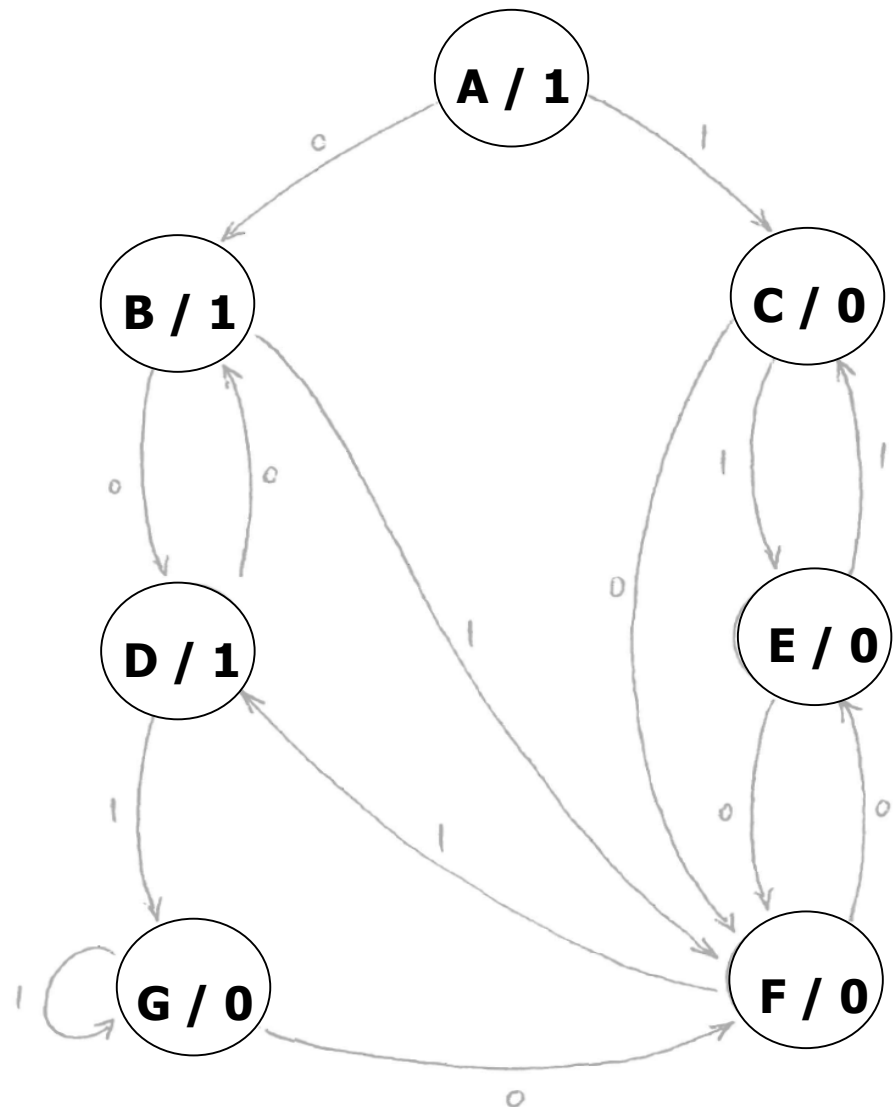

State Minimization: Partitioning

Initial Partition:

$$P_1 = (ABCDEFGG)$$

Present state	Next state		Output z
	$w=0$	$w=1$	
A	B	C	1
B	D	F	1
C	F	E	0
D	B	G	1
E	F	C	0
F	E	D	0
G	F	G	0

The initial partition contains all states in the state diagram / table.

State Minimization: Partitioning


- Separate states based on output value.
 - $P_2 = (\text{ABD})(\text{CEFG})$

Present state	Next state		Output z
	$w=0$	$w=1$	
A	B	C	1
B	D	F	1
C	F	E	0
D	B	G	1
E	F	C	0
F	E	D	0
G	F	G	0

State Minimization: Partitioning

- Separate states based on next state values.
- $P_2 = (\text{ABD})(\text{CEFG})$

Present state	Next state		Output z
	w=0	w=1	
A	B	C	1
B	D	F	1
C	F	E	0
D	B	G	1
E	F	C	0
F	E	D	0
G	F	G	0

 


– $P_3 = (\text{ABD})(\text{CEG})(\text{F})$ → unique state

State Minimization: Partitioning

- Separate states based on next state values.
- $P_3 = (ABD)(CEG)(F)$



Present state	Next state		Output z
	w=0	w=1	
A	B	C	1
B	D	F	1
C	F	E	0
D	B	G	1
E	F	C	0
F	E	D	0
G	F	G	0

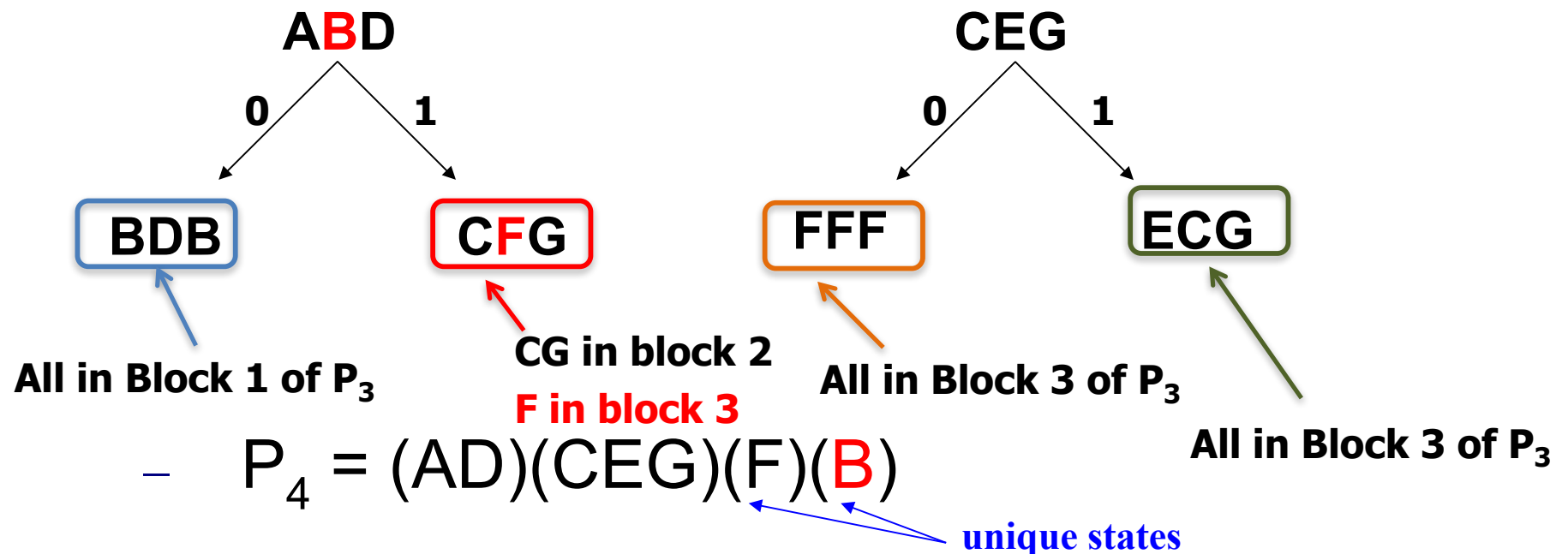

State Minimization: Partitioning

- Separate states based on next state values.

Present state	Next state		Output z
	w=0	w=1	
A	B	C	1
B	D	F	1
C	F	E	0
D	B	G	1
E	F	C	0
F	E	D	0
G	F	G	0

  

$$- P_5 = (AD)(CEG)(F)(B)$$

P_5 same as previous partition (P_4) $\Rightarrow$ state minimization is completed

State Minimization: Partitioning


- Since $P_4 = P_5$, state minimization is complete.
- The equivalent states are:
 - $A = D$
 - $C = E = G$
 - B
 - F
- Thus, the FSM can be realized with just 4 states.

FSM: State Minimization

Present state	Next state		Output z
	w = 0	w = 1	
A	B	C	1
B	A	F	1
C	F	C	0
F	C	A	0

Minimized State Table


FSM: State Minimization

 

State minimization: Implication Table

■ Multiple input example

inputs here

 


present state	next state				output
	00	01	10	11	
S0	S0	S1	S2	S3	1
S1	S0	S3	S1	S4	0
S2	S1	S3	S2	S4	1
S3	S1	S0	S4	S5	0
S4	S0	S1	S2	S5	1
S5	S1	S4	S0	S5	0

symbolic state
transition table

■ Implication Table Method

- Build a table and label vertical axis: $S_1, S_2, \dots, S_N$ and horizontal $S_0, S_1, \dots, S_{N-1}$
 - **Each cell is the crossection of a pair of states S_i-S_j**
- Cross out pairs of states with different outputs
- In the rest of the cells put the pairs of **next**-states that need to be the same for S_i-S_j to be the same
- Then cross-out more cells if at least one next-state pair has been already

 


present state	00	01	10	11	output
S0	S0	S1	S2	S3	1
S1	S0	S1	S2	S3	0
S2	S0	S1	S2	S3	1
S3	S0	S1	S2	S3	0
S4	S0	S1	S2	S3	1
S5	S0	S1	S2	S3	0

minimized state table
($S_0 = S_4$) ($S_3 = S_5$)

Implication Table Method

example 2

Current state	NxtState IN:		OUT
	0	1	
a	d	c	0
b	f	h	0
c	e	d	1
d	a	e	0
e	c	a	1
f	f	b	1
g	b	h	0
h	c	g	1

 

1. Build a table and label vertical axis: $S_1, S_2, \dots, S_N$ and horizontal $S_0, S_1, \dots, S_{N-1}$
2. Each cell is the cross-section of a pair of states S_i-S_j

Implication Table Method

example 2

Current state	NxtState IN:		OUT
	0	1	
a	d	c	0
b	f	h	0
c	e	d	1
d	a	e	0
e	c	a	1
f	f	b	1
g	b	h	0
h	c	g	1

b	d-f c-h						
c	×	×					
d	c-e	a-f e-h	×				
e	×	×	a-d	×			
f	×	×	e-f b-d	×	c-f a-b		
g	b-d c-h	b-f	×	a-b e-h	×	×	
h	×	×	c-e d-g	×	a-g	c-f b-g	×
	a	b	c	d	e	f	g

3. Cross out pairs of states with different outputs
4. In the rest of the cells put the pairs of next-states that need to be the same for S_i-S_j to be the same

Implication Table Method example 2

Current state	NxtState IN:		OUT
	0	1	
a	d	c	0
b	f	h	0
c	e	d	1
d	a	e	0
e	c	a	1
f	f	b	1
g	b	h	0
h	c	g	1

b	a-f c-h					
c	×	×				
d	c-e	a-f e-h	×			
e	×	×	a-d	×		
f	×	×	a-f b-d	×	a-f a-b	
g	b-d c-h	b-f	×	a-b e-h	×	×
h	×	×	c-e d-g	×	a-g	c-f b-g
	a	b	c	d	e	f

5. cross-out more cells if at least one next-state pair has been already crossed out

Implication Table Method example 2

Current state	NxtState IN:		OUT
	0	1	
a	d	c	0
b	f	h	0
c	e	d	1
d	a	e	0
e	c	a	1
f	f	b	1
g	b	h	0
h	c	g	1

7. The cells that are not crossed out indicate states that can be merged

b	a-f c-h						
c	X	X					
d	c-e	a-f e-h	X				
e	X	X	a-d	X			
f	X	X	b-d	X	e-f		
g	b-d c-h	a-f	X	a-b e-h	X	X	
h	X	X	c-e d-g	X	a-g b-g	c-f d-g	X
	a	b	c	d	e	f	g

cross-out
any more
cells

6. Repeat last step until you cannot cross-out any more cells

Cu-state	Nstate IN:		OUT
	0	1	
a	a	c	0
b	f	h	0
c	c	a	1
f	f	b	1
g	b	h	0
h	c	g	1

a=d
C=e

Quiz 7-2

<http://m.socrative.com/student/#joinRoom>

room number: 713113

- Q1: How many states can be represented by N bits in:
 - a. Binary encoding
 - b. Gray-code encoding
 - c. One-hot encoding
- Q2: One hot encoding requires fewer flipflops than binary and gray-code
 - True/false
- Q3: One hot encoding has usually simpler output logic than the binary and gray-code
 - True/false
- Q4: In the partitioning state minimization algorithm: A state needs to be removed from a block if:
 - Its next state (for a particular input) is different than the next states of the rest
 - Its next state (for a particular input) does not belong to the same group as the other state
 - Its next state (for a particular output) belongs to the same group as the other state

Summary of Lecture 8

- Finite State Machines
 - Moore
 - Mealy
- State assignment
- State minimization
- Book (complimentary to the slides):
 - Sections 14, 19.1 - 19.3
- Next Lecture 9:
 - VHDL for Finite State Machines

FSMs intro:

https://www.youtube.com/watch?v=vhiia1_hC4