

EDA322

Digital Design

Lecture 9:

Finite State Machines - VHDL


Ioannis Sourdis

Outline of Lecture 9

- Control vs. Datapath
- More FSM examples
- FSMs in VHDL
 - Moore and Mealy FSMs in VHDL
 - State processes
 - State Coding
 - More VHDL alternatives (Mealy, Moore, registered output)

Datapath vs. Controller

Structure of a Typical Digital System

 

Datapath (Execution Unit)

- Manipulates and processes data
- Performs arithmetic and logic operations, shifting, and other data-processing tasks
- Is composed of registers, gates, multiplexers, decoders, adders, comparators, ALUs, etc.
- Provides all necessary resources and interconnects among them to perform specified task
- Interprets control signals from the Controller and generates status signals for the Controller

Controller (Control Unit)

- Controls data movements in the Datapath by switching multiplexers and enabling or disabling resources

Example: enable signals for registers

Example: control signals for muxes

- Provides signals to activate various processing tasks in the Datapath
- Determines the sequence the operations performed by Datapath
- Follows Some 'Program' or Schedule


Controller

- Controller can be programmable or non-programmable
- Programmable
 - Has a program counter which points to next instruction
 - Instructions are held in a RAM or ROM externally
 - Microprocessor is an example of programmable controller
- Non-Programmable
 - Once designed, implements the same functionality
 - Another term is a “hardwired state machine” or “hardwired instructions”

Finite State Machines

- Digital Systems and especially their Controllers can be described as Finite State Machines (FSMs)
- Finite State Machines can be represented using
 - **State Diagrams and State Tables** - suitable for simple digital systems with a relatively few inputs and outputs
 - **Algorithmic State Machine (ASM) Charts** - suitable for complex digital systems with a large number of inputs and outputs

Hardware Design with RTL VHDL

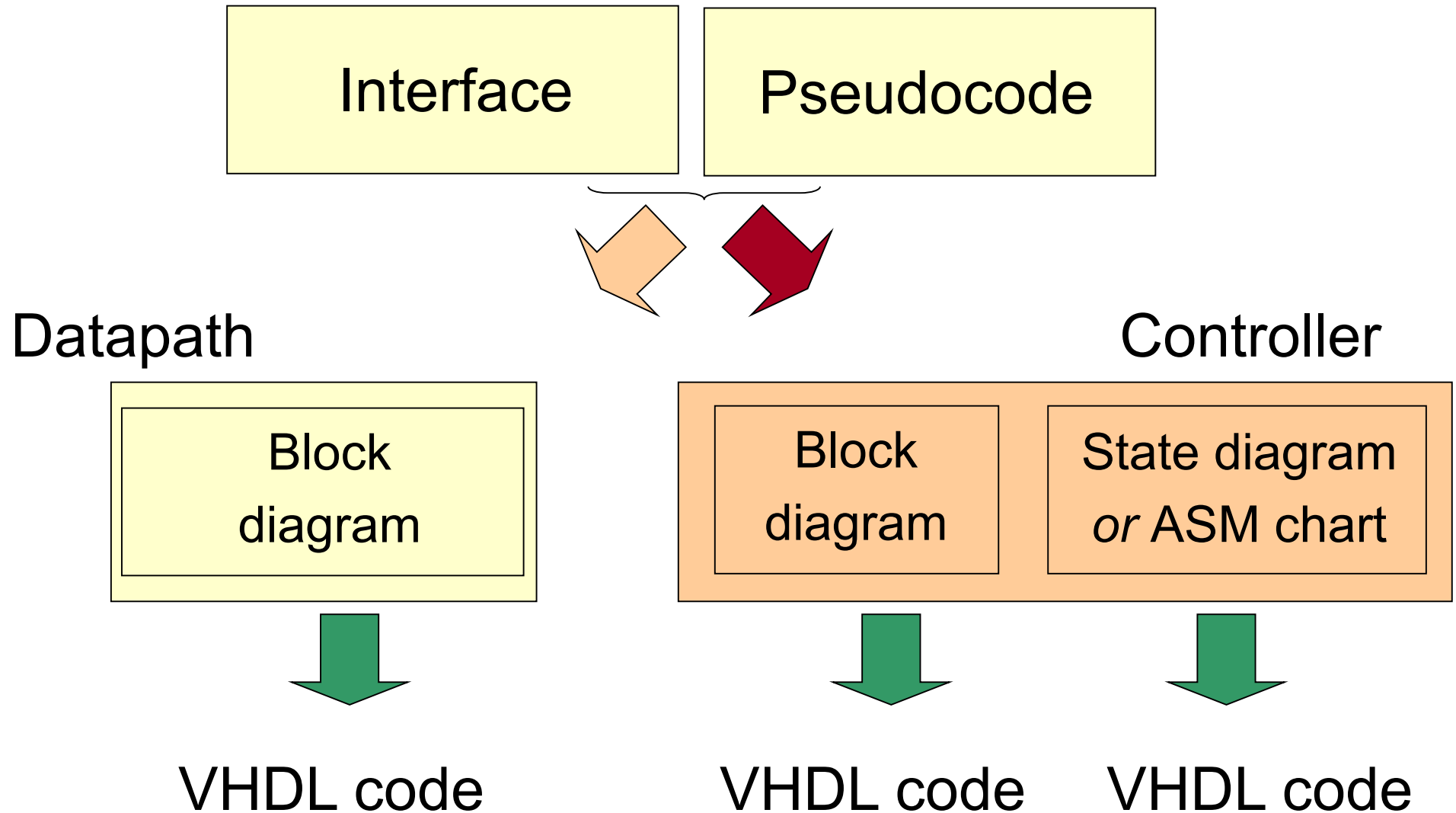


Finite State Machines Refresher

Finite State Machines (FSMs)

- A machine/mathematical model with a finite amount of memory to represent its finite set of internal states, has a set of defined inputs and outputs and a set of transitions between selected states
 - Even computers can be viewed as huge FSMs
- Design of FSM
 - Defining states
 - Defining transitions between states
 - Optimization / minimizations
 - **Manual Optimization/Minimization Is Practical for Small FSMs Only**


Moore FSM

 - Output Is a Function of a Present State Only




Mealy FSM

 - Output Is a Function of a Present State and Inputs




State Diagrams

Moore Machine

 

Mealy Machine

 

Moore vs. Mealy FSM (1)


- Moore and Mealy FSMs Can Be Functionally Equivalent
 - Equivalent Mealy FSM can be derived from Moore FSM and vice versa
- Mealy FSM Has Richer Description and Usually Requires Smaller Number of States
 - Smaller circuit area

Moore vs. Mealy FSM (2)

- Mealy FSM Computes Outputs as soon as Inputs Change
 - Mealy FSM responds one clock cycle sooner than equivalent Moore FSM
- Moore FSM Has No Combinational Path Between Inputs and Outputs
 - Moore FSM is more likely to have a shorter critical path

Moore FSM - Example 1

 
- Moore FSM that Recognizes Sequence “10”



Meaning of states:	S0: No elements of the sequence observed	S1: “1” observed	S2: “10” observed

Mealy FSM - Example 1

 - Mealy FSM that Recognizes Sequence “10”




Meaning
of states:


S0: No
elements
of the
sequence
observed

S1: “1”
observed

Moore & Mealy FSMs – Example 1

 

Moore & Mealy FSMs – Example 1

 


Finite State Machines in VHDL

FSMs in VHDL

- Finite State Machines Can Be Easily Described With Processes
- Synthesis Tools Understand FSM Description If Certain Rules Are Followed
 - State transitions should be described in a process sensitive to *clock* and *asynchronous reset* signals **only**
 - Outputs described as concurrent statements outside the process


Moore FSM

process(clock, reset)

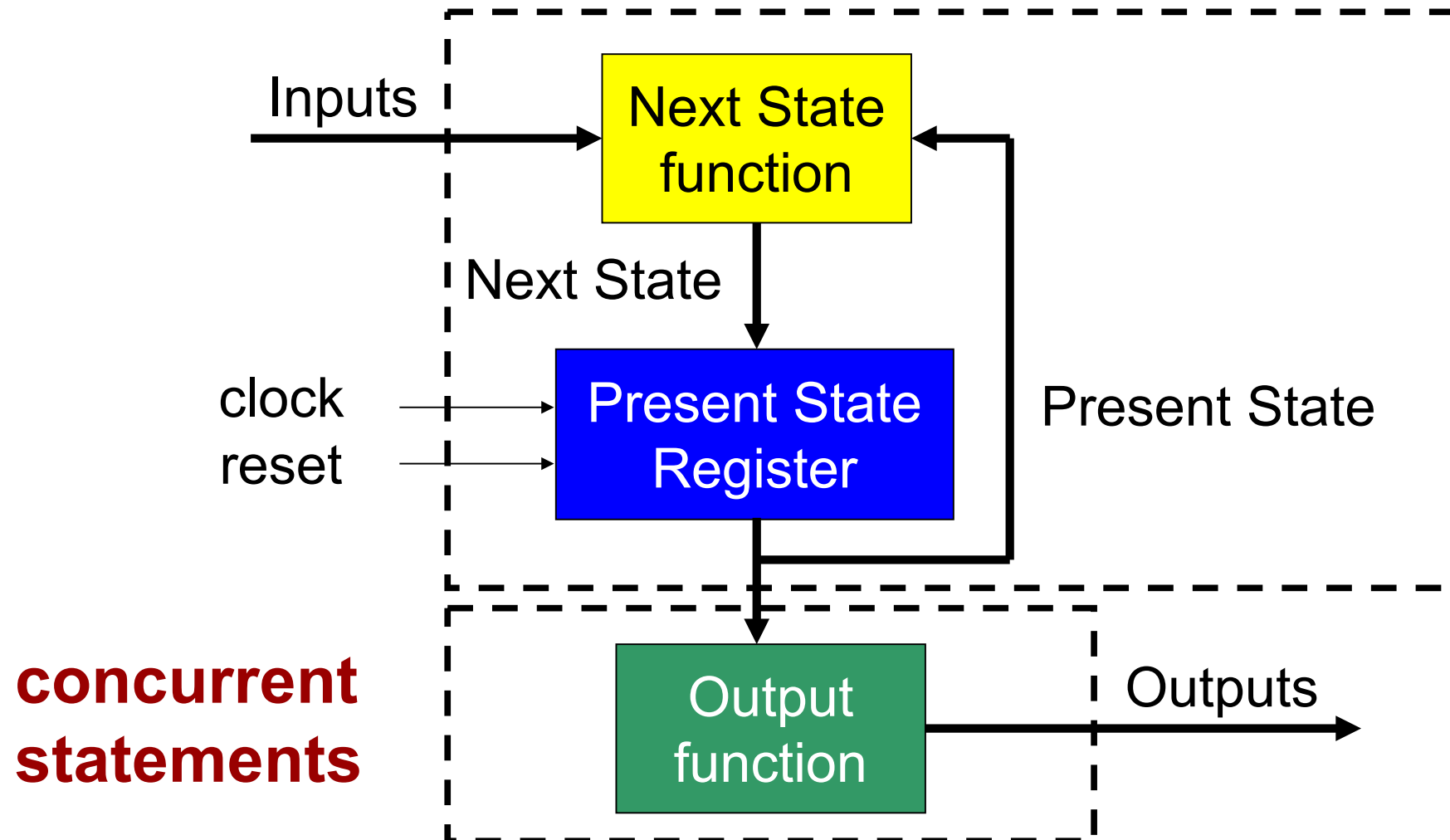

Mealy FSM


process(clock, reset)

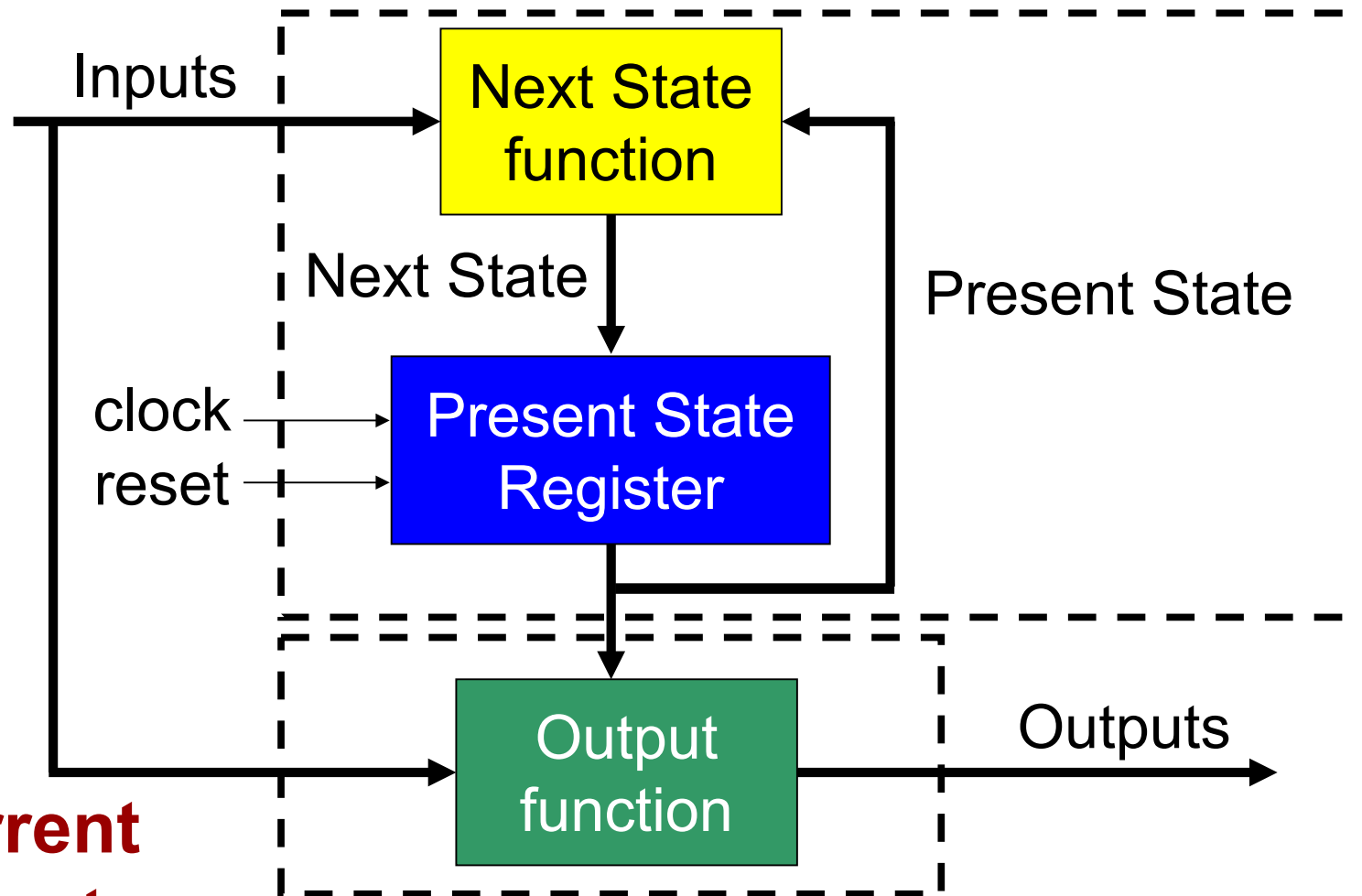

**concurrent
statements**

Moore FSM - Example 1

 - Moore FSM that Recognizes Sequence “10”



Moore FSM in VHDL (1)

TYPE state **IS** (S0, S1, S2);

SIGNAL Moore_state: state;

U_Moore: **PROCESS** (clock, reset)

BEGIN

IF(reset = '1') **THEN**

 Moore_state <= S0;

ELSIF (clock = '1' AND clock'event) **THEN**

CASE Moore_state **IS**

WHEN S0 =>


IF input = '1' **THEN**

 Moore_state <= S1;

ELSE

 Moore_state <= S0;


END IF;

 

Moore FSM in VHDL (2)


```
WHEN S1 =>  
    IF input = '0' THEN  
        Moore_state <= S2;  
    ELSE  
        Moore_state <= S1;  
    END IF;  
WHEN S2 =>  
    IF input = '0' THEN  
        Moore_state <= S0;  
    ELSE  
        Moore_state <= S1;  
    END IF;  
END CASE;  
END IF;  
END PROCESS;
```
 
```
Output <= '1' WHEN Moore_state = S2 ELSE '0';
```



Mealy FSM - Example 1

 - Mealy FSM that Recognizes Sequence “10”



Mealy FSM in VHDL (1)

TYPE state **IS** (S0, S1);

SIGNAL Mealy_state: state;

U_Mealy: **PROCESS**(clock, reset)

BEGIN

IF(reset = '1') **THEN**

 Mealy_state <= S0;

ELSIF (clock = '1' AND clock'event) **THEN**

CASE Mealy_state **IS**

WHEN S0 =>


IF input = '1' **THEN**

 Mealy_state <= S1;

ELSE


 Mealy_state <= S0;

END IF;

 


Mealy FSM in VHDL (2)
 
```
    WHEN S1 =>  
      IF input = '0' THEN  
        Mealy_state <= S0;  
      ELSE  
        Mealy_state <= S1;  
      END IF;  
    END CASE;  
  END IF;  
END PROCESS;
```



```
Output <= '1' WHEN (Mealy_state = S1 AND input = '0') ELSE '0';
```

Moore FSM – Example 2: State diagram

 


Moore FSM – Example 2: State table

Present state	Next state		Output z
	$w = 0$	$w = 1$	
A	A	B	0
B	A	C	0
C	A	C	1

Moore FSM

process(clock, reset)

**concurrent
statements**

 

Moore FSM – Example 2: VHDL code (1)

```
USE ieee.std_logic_1164.all ;
```

```
ENTITY simple IS
```

```
    PORT ( clock   : IN STD_LOGIC ;  
          resetn   : IN STD_LOGIC ;  
          w        : IN STD_LOGIC ;  
          z        : OUT STD_LOGIC ) ;
```

```
END simple ;
```

```
ARCHITECTURE Behavior OF simple IS
```

```
    TYPE State_type IS (A, B, C) ;
```

```
    SIGNAL y : State_type ;
```

```
BEGIN
```

```
    PROCESS ( resetn, clock )
```

```
    BEGIN
```

```
        IF resetn = '0' THEN
```

```
            y <= A ;
```

```
        ELSIF (Clock'EVENT AND Clock = '1') THEN
```

Moore FSM – Example 2: VHDL code (2)

```
CASE y IS  
  WHEN A =>  
    IF w = '0' THEN  
      y <= A ;  
    ELSE  
      y <= B ;  
    END IF ;  
  WHEN B =>  
    IF w = '0' THEN  
      y <= A ;  
    ELSE  
      y <= C ;  
    END IF ;  
  WHEN C =>  
    IF w = '0' THEN  
      y <= A ;  
    ELSE  
      y <= C ;  
    END IF ;  
END CASE ;
```


Moore FSM – Example 2: VHDL code (3)

```
END IF ;  
END PROCESS ;
```

```
z <= '1' WHEN y = C ELSE '0' ;
```

```
END Behavior ;
```

Mealy FSM – Example 2: State diagram

 

Example 2: VHDL code (1)

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;  
  
ENTITY Mealy IS  
    PORT ( clock    : IN          STD_LOGIC ;  
           resetn   : IN          STD_LOGIC ;  
           w        : IN          STD_LOGIC ;  
           z        : OUT         STD_LOGIC ) ;  
END Mealy ;  
  
ARCHITECTURE Behavior OF Mealy IS  
    TYPE State_type IS (A, B) ;  
    SIGNAL y : State_type ;  
BEGIN  
    PROCESS ( resetn, clock )  
    BEGIN  
        IF resetn = '0' THEN  
            y <= A ;  
        ELSIF (clock'EVENT AND clock = '1') THEN
```


Example 2: VHDL code (2)

```
        CASE y IS
            WHEN A =>
                IF w = '0' THEN
                    y <= A ;
                ELSE
                    y <= B ;
                END IF ;
            WHEN B =>
                IF w = '0' THEN
                    y <= A ;
                ELSE
                    y <= B ;
                END IF ;
        END CASE ;
    END IF ;
END PROCESS ;
```


```
z <= '1' WHEN (y = B) AND (w='1') ELSE '0' ;
```

END Behavior ;


Control Unit Example: Arbiter (1)

 

Control Unit Example: Arbiter (2)

 

Control Unit Example: Arbiter (3)

 

Example 3: VHDL code (1)

LIBRARY ieee;

USE ieee.std_logic_1164.all;

ENTITY arbiter **IS**

PORT (Clock, Resetn : **IN** STD_LOGIC ;
 r : **IN** STD_LOGIC_VECTOR(1 TO 3) ;
 g : **OUT** STD_LOGIC_VECTOR(1 TO 3)) ;

END arbiter ;

ARCHITECTURE Behavior **OF** arbiter **IS**

TYPE State_type IS (Idle, gnt1, gnt2, gnt3) ;

SIGNAL y : State_type ;

Example 3: VHDL code (2)

BEGIN

PROCESS (Resetn, Clock)

BEGIN

IF Resetn = '0' **THEN** y <= Idle ;

ELSIF (Clock'EVENT AND Clock = '1') **THEN**

CASE y **IS**

WHEN Idle =>

IF r(1) = '1' **THEN** y <= gnt1 ;

ELSIF r(2) = '1' **THEN** y <= gnt2 ;

ELSIF r(3) = '1' **THEN** y <= gnt3 ;

ELSE y <= Idle ;

END IF ;

WHEN gnt1 =>

IF r(1) = '1' **THEN** y <= gnt1 ;

ELSE y <= Idle ;

END IF ;

WHEN gnt2 =>

IF r(2) = '1' **THEN** y <= gnt2 ;

ELSE y <= Idle ;

END IF ;

Example 3: VHDL code (3)


```
        WHEN gnt3 =>
            IF r(3) = '1' THEN y <= gnt3 ;
            ELSE y <= Idle ;
            END IF ;
        END CASE ;
    END IF ;
END PROCESS ;

g(1) <= '1' WHEN y = gnt1 ELSE '0' ;
g(2) <= '1' WHEN y = gnt2 ELSE '0' ;
g(3) <= '1' WHEN y = gnt3 ELSE '0' ;
END Behavior ;
```

FSMs with VHDL


- State Processes
- State Coding
- Additional ways to implement FSMs
 - Moore
 - Mealy
 - Registered Output

One "State" Process

 


```

FSM_FF: process (CLK, RESET)
begin
  if RESET='1' then
    STATE <= START ;
  elsif CLK'event and CLK='1' then
    case STATE is
      when START => if X=GO_MID then
        STATE <= MIDDLE ;
      end if ;
      when MIDDLE => if X=GO_STOP then
        STATE <= STOP ;
      end if ;
      when STOP => if X=GO_START then
        STATE <= START ;
      end if ;
      when others => STATE <= START ;
    end case ;
  end if ;
end process FSM_FF ;
    
```

 


Two "State" Processes

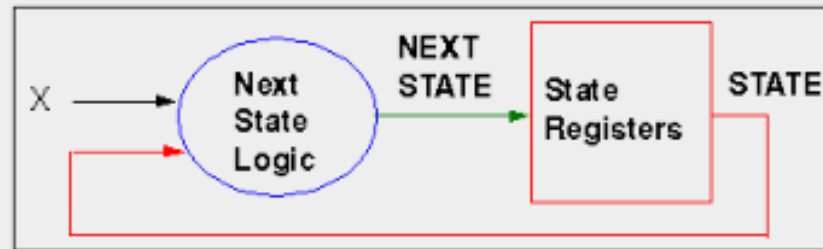

```

FSM_FF: process (CLK, RESET) begin
  if RESET='1' then
    STATE <= START ;
  elsif CLK'event and CLK='1' then
    STATE <= NEXT_STATE ;
  end if;
end process FSM_FF ;

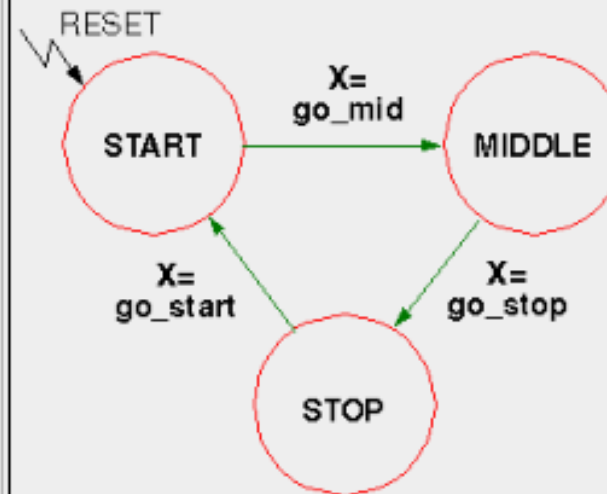FSM_LOGIC: process ( STATE , X)
begin
  NEXT_STATE <= STATE ;
  case STATE is
    when START => if X=GO_MID then
      NEXT_STATE <= MIDDLE ;
    end if ;
    when MIDDLE => ...
    when others => NEXT_STATE <= START ;
  end case ;
end process FSM_LOGIC ;
  
```



How Many Processes?

- Structure and Readability
 - Asynchronous combinatoric $\neq$ synchronous storing elements
=> 2 processes
 - FSM states change with special input changes
=> 1 process more comprehensible
 - Graphical FSM (without output equations) resembles one state process
=> 1 process
- Simulation
 - Error detection easier with two state processes
=> 2 processes
- Synthesis
 - 2 state processes can lead to smaller generic netlist
and therefore to better synthesis results
=> 2 processes

State Encoding

- type STATE_TYPE is (**START**, **MIDDLE**, **STOP**) ;
signal STATE : STATE_TYPE ;
- START -> " **00** "
MIDDLE -> " **01** "
STOP -> " **10** "
- START -> " **001** "
MIDDLE -> " **010** "
STOP -> " **100** "
- State encoding responsible for safety of FSM
- Default encoding: **binary**
- Speed optimized default encoding: **one hot**

Extension of Case Statement

- type STATE_TYPE is (START, MIDDLE, STOP);
signal STATE : STATE_TYPE ;
...
case STATE is
when START => ...
when MIDDLE => ...
when STOP => ...

when others => ...

end case ;
- Adding the "when others" choice


Hand Coding

```
subtype STATE_TYPE is
    std_logic_vector(1 downto 0) ;

signal STATE : STATE_TYPE ;
constant START : STATE_TYPE := "01";
constant MIDDLE : STATE_TYPE := "11";
constant STOP : STATE_TYPE := "00";
...
case STATE is
    when START => ...
    when MIDDLE => ...
    when STOP => ...
    when others => ...
end case ;
```

- Defining constants
- Control of encoding
- Safe FSM
- Simulatable
- Portable design
- More effort

FSM: Moore

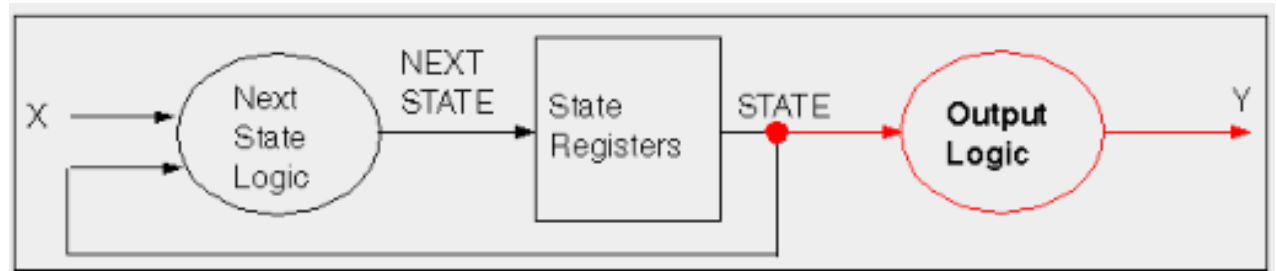

The output vector is a function of the state vector: $Y = f(S)$

■ Three Processes

architecture RTL of MOORE is

...

REG: -- Clocked Process
CMB: -- Combinational Process

OUTPUT: process (STATE)
begin
 -- Output Logic
end process OUTPUT ;

end RTL ;

■ Two Processes

architecture RTL of MOORE is

...

REG: process (CLK, RESET)
begin
 -- State Registers Inference with
 Next State Logic
end process REG ;

OUTPUT: process (STATE)
begin
 -- Output Logic
end process OUTPUT ;

end RTL ;


Moore: 3 Process Example

architecture RTL of MOORE_TEST is

```
  signal STATE,NEXTSTATE : STATE_TYPE ;
begin
```

```
  REG: process (CLK, RESET) begin
    if RESET='1' then STATE <= START ;
    elsif CLK`event and CLK='1' then
      STATE <= NEXTSTATE ;
    end if ;
```

```
end process REG ;
```

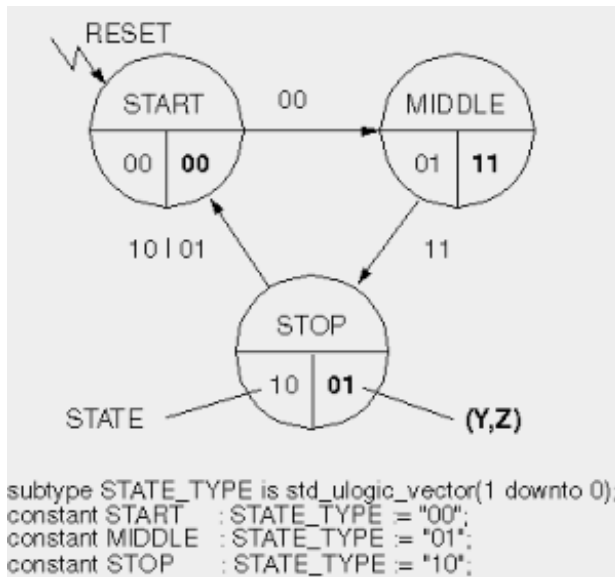

```
  CMB: process (A,B,STATE) begin
```

```
    NEXT_STATE <= STATE;
```

```
  case STATE is
```

```
    when START => if (A or B)='0' then
      NEXTSTATE <= MIDDLE ;
```

```
    end if ;
```

```
    when MIDDLE => if (A and B)='1' then
      NEXTSTATE <= STOP ;
```

```
    end if ;
```

```
    when STOP => if (A xor B)='1' then
      NEXTSTATE <= START ;
```

```
    end if ;
```

```
    when others => NEXTSTATE <= START ;
```

```
  end case ;
```

```
end process CMB ;
```


-- concurrent signal assignments for output

Y <= '1' when STATE=MIDDLE else '0' ;


Z <= '1' when STATE=MIDDLE or STATE=STOP else '0' ;

```
end RTL ;
```

Waveform Moore Example

 

 - (Y,Z) changes simultaneously with STATE => Moore machine



The output vector is a function of the state vector and the input vector: $Y = f(X, S)$

■ Three Processes

architecture RTL of MEALY is

```

...
begin
  REG: -- Clocked Process

  CMB: -- Combinational Process

```

```

OUTPUT: process (STATE, X)
begin
  -- Output Logic
end process OUTPUT ;
end RTL ;

```

■ Two Processes

architecture RTL of MEALY is

```

...
begin
  MED: process (CLK, RESET)
  begin
    -- State Registers Inference with
    Next State Logic
  end process MED ;

```

```

OUTPUT: process (STATE, X)
begin
  -- Output Logic
end process OUTPUT ;
end RTL ;

```

Mealy Example

```
architecture RTL of MEALY_TEST is
    signal STATE,NEXTSTATE : STATE_TYPE ;
begin
    REG: . . . -- clocked STATE process
    CMB: . . . -- Like Moore Examples

    OUTPUT: process (STATE, A, B)
    begin
        case STATE is
            when START =>
                Y <= '0' ;
                Z <= A and B ;


            when MIDLLE =>
                Y <= A nor B ;
                Z <= '1' ;

            when STOP =>
                Y <= A nand B ;
                Z <= A or B ;

            when others =>
                Y <= '0' ;
                Z <= '0' ;

        end case;
    end process OUTPUT;
end RTL ;
```


Waveform Moore Example

 

- (Y,Z) changes with input => Mealy machine
- Note the "spikes" of Y and Z in the waveform
 - FSM has to be modeled carefully in order to avoid spikes in normal operation.


Modelling Aspects

 - Moore is preferred because of safe operation
- Mealy more flexible, but danger of
 - Spikes
 - Unnecessary long paths (maximum clock period)
 - Combinational feed back loops




Registered Output

 - Avoiding long paths and uncertain timing
- With one additional clock period



 - Without additional clock period (Mealy)



Registered Output Example (1)

architecture RTL of REG_TEST is

```

    signal Y_I, Z_I : std_ulogic ;
    signal STATE, NEXTSTATE : STATE_TYPE ;
begin

```

```

    REG: ... -- clocked STATE process

```

```

    CMB: ... -- Like other Examples

```

```

    OUTPUT: process (STATE, A, B)

```

```

begin

```

```

    case STATE is

```

```

        when START =>

```

```

            Y_I <= '0' ;

```

```

            Z_I <= A and B ;

```

```

        ...

```

```

    end process OUTPUT

```

```

-- clocked output process

```

```

OUTPUT_REG: process(CLK) begin

```

```

    if CLK'event and CLK='1' then

```

```

        Y <= Y_I ;

```

```

        Z <= Z_I ;

```

```

    end if ;

```

```


end process OUTPUT_REG ;

```


```

end RTL ;

```

 

Waveform Registered Output Example (1)

 

- One clock period delay between STATE and output changes.
- Input changes with clock edge result in an output change.
(Danger of unmeant values)

Registered Output Example (2)

architecture RTL of REG_TEST2 is

signal **Y_I**, **Z_I** : std_ulogic ;

signal STATE,NEXTSTATE : STATE_TYPE ;

begin

REG: . . . -- clocked STATE process

CMB: . . . -- Like other Examples

OUTPUT: process (**NEXTSTATE** , A, B)

begin

case NEXTSTATE is

when START =>

Y_I <= '0' ;

Z_I <= A and B ;

. . .

end process OUTPUT

OUTPUT_REG: process(CLK)

begin

if CLK'event and CLK='1' then


Y <= **Y_I** ;

Z <= **Z_I** ;


end if ;

end process **OUTPUT_REG** ;

end RTL ;

 

Waveform Registered Output Example (2)

 

- No delay between STATE and output changes.
- "Spikes" of original Mealy machine are gone!

Summary of Lecture 9

- Control vs. Datapath
- More FSM examples
- FSMs in VHDL
 - Moore and Mealy FSMs in VHDL
 - State processes
 - State Coding
 - More VHDL alternatives (Mealy, Moore, registered output)
- Book (complimentary to the slides):
 - Sections 14.6
- Next Lecture 10:
 - Testbenches VHDL