

DAT093

Lab Feedback and Guidance 2

Mehrzed Nejat

Department of Computer Science & Engineering
Chalmers University of Technology

Sep. 2017


How to design a complex system in VHDL?

The answer is **ORGANIZATION**

- Code → Indentation, spacing, ...
- Components and hierarchy → Hierarchical Design
- Your mind! → Solve one problem at a time

Solve one problem at a time

 You have been doing that in your hierarchical design




Solve one problem at a time

You can use the same approach in one design

Example: Saturation logic

Step1: Pen and paper

 

Step2: Decompose the problem (The question mark technique !)

Max_pos<= ?
Max_neg<= ?

 $y \leq \text{Max_pos} \text{ when } ? \text{ else } \text{Max_neg} \text{ when } ? \text{ else } \text{sum};$

Step3: Solve each sub-problem in English


Max_pos<= ? -- First bit zero, the rest one
Max_neg<= ? -- First bit one, the rest zero

 $y \leq \text{Max_pos} \text{ when } ? \text{ else } \text{when there is overflow and ... } \text{Max_neg} \text{ when } ? \text{ else } \text{when there is overflow and ... sum};$

Step4: Replace the question marks with VHDL code

State machine

 You can use a state machine to design your sequential systems



Step1: Define your states
Step2: Define what should happen in each state
Step3: Define the transitions between states

The process statement

You must be able to easily understand the logical flow in your process statement


```
Process (clk)
Begin
If rising_edge(clk) then
    if (...) then -- State1
        [redacted]
    elsif (...) then -- State2
        [redacted]
    else -- State3
        [redacted]
    end if;
End if;
```

- ❖ Try to use nested “if...elsif...else...end-if” statements rather than consecutive “if...end-if...if...end-if”. You might overwrite something by mistake.
- ❖ Assign some value to each process output in any possible condition. Even if you don’t want to change it, assign its previous value
- ❖ Always have an “else” condition. Otherwise, you don’t clearly understand what happens if the condition is not true.
- ❖ Be careful with the timing of signals!

The process statement

Be careful with the timing of signals
 
```
Process (clk)
Begin
If rising_edge(clk) then
  S1<=S0;
  S2<=S1;
End if;
```



Here, at each cycle:

S1 gets the previous value of S0 (the new value of S1),
S2 gets the previous value of S1 (not the new value!)