

Lecture 4 follow-up


Tapered CMOS Inverter stages

Dynamic properties

Introduction


- In these set of slides some supplementary information and material for self studies is presented.
- The importance of the FO4 delay as 5tau is again high-lighted.
- An attempt to show values for tau vs. technology as measured by its minimum feature size (i.e. minimum channel length) is shown in the trend graph.
- A published comparison of different processor cycle time trends in terms of FO4 delays is shown.
- The tapered buffer is analyzed in detail in terms of path electrical effort H , and stage electrical effort h .
- A stage electrical effort, or fanout, of four is shown to be very close to the optimal solution for minimum delay.
- An H-tree clock distribution network is used to show how branching affects the fanout of a critical timing path. The path fanout, F , becomes the product of the path branching, B , and the path electrical effort, H !
$$F = B \cdot H$$
- Conclusion $F=BH$ and $h=N\sqrt{F}$

Inverter FO4 delay

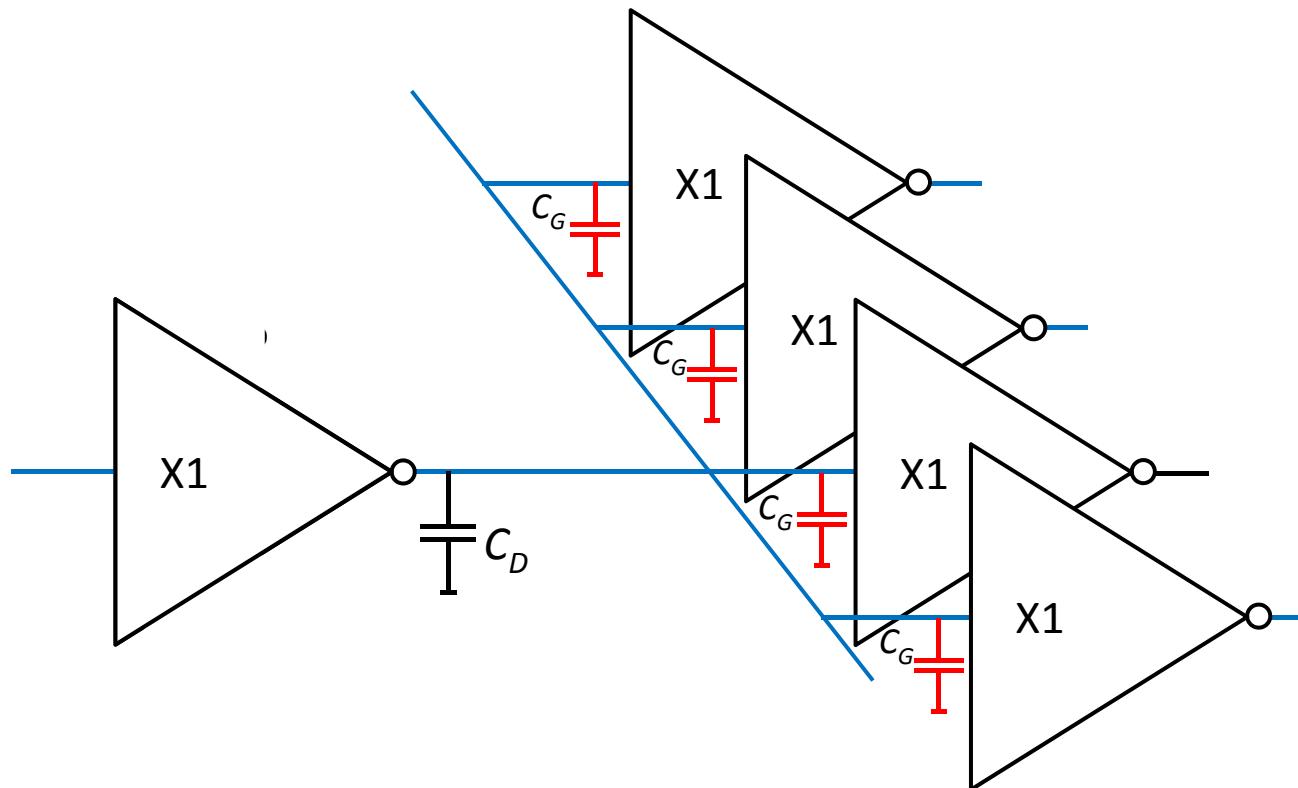


The FO4 propagation delay becomes $t_{pd} = 0.7R_{eff} (C_D + 4C_G) = \underbrace{0.7R_{eff} C_G}_{\tau_{au}} (p + 4) = 5 \text{ ps} \times 5 = 25 \text{ ps}$

FO4 delay trends vs. feature size

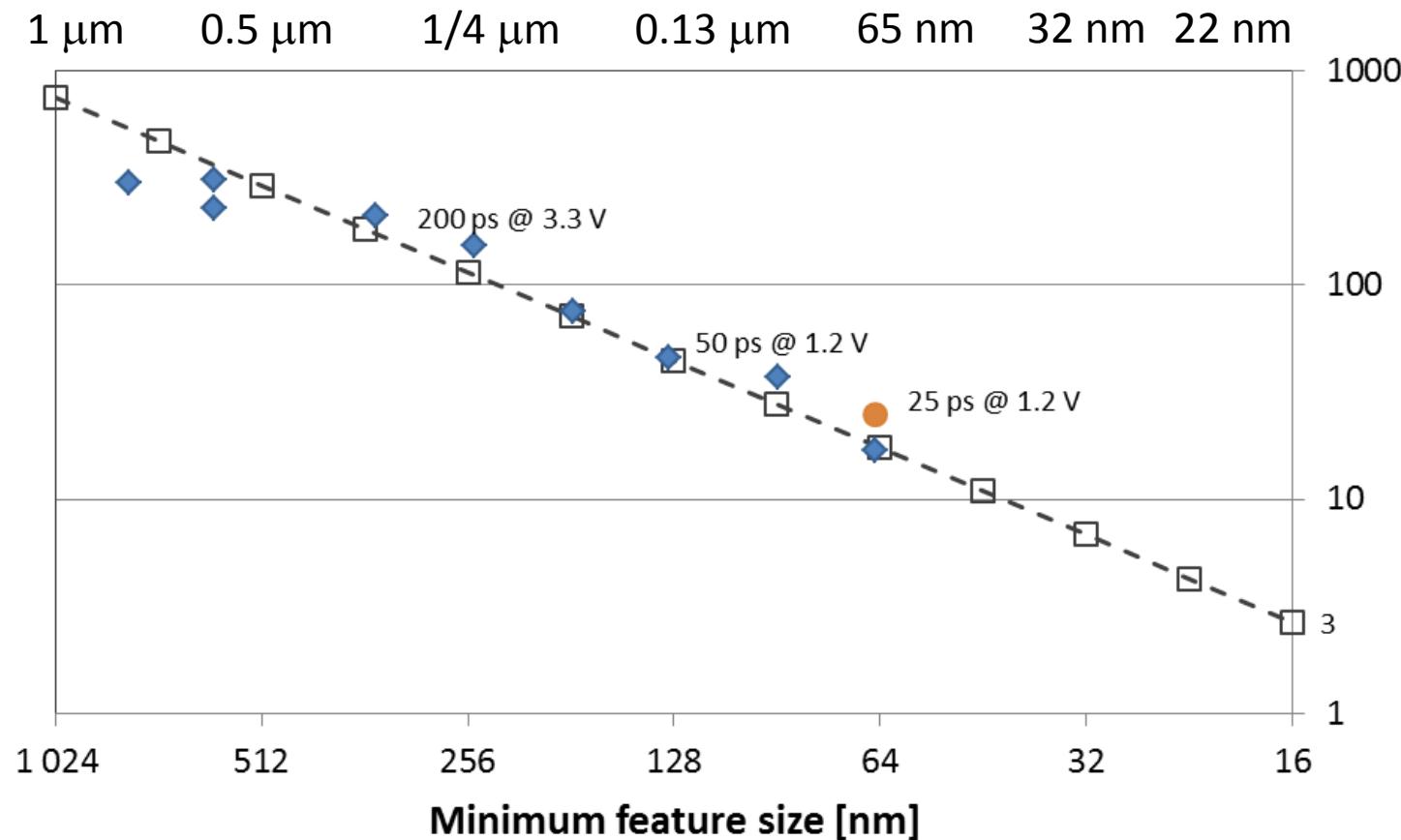

Microprocessor cycle time trends

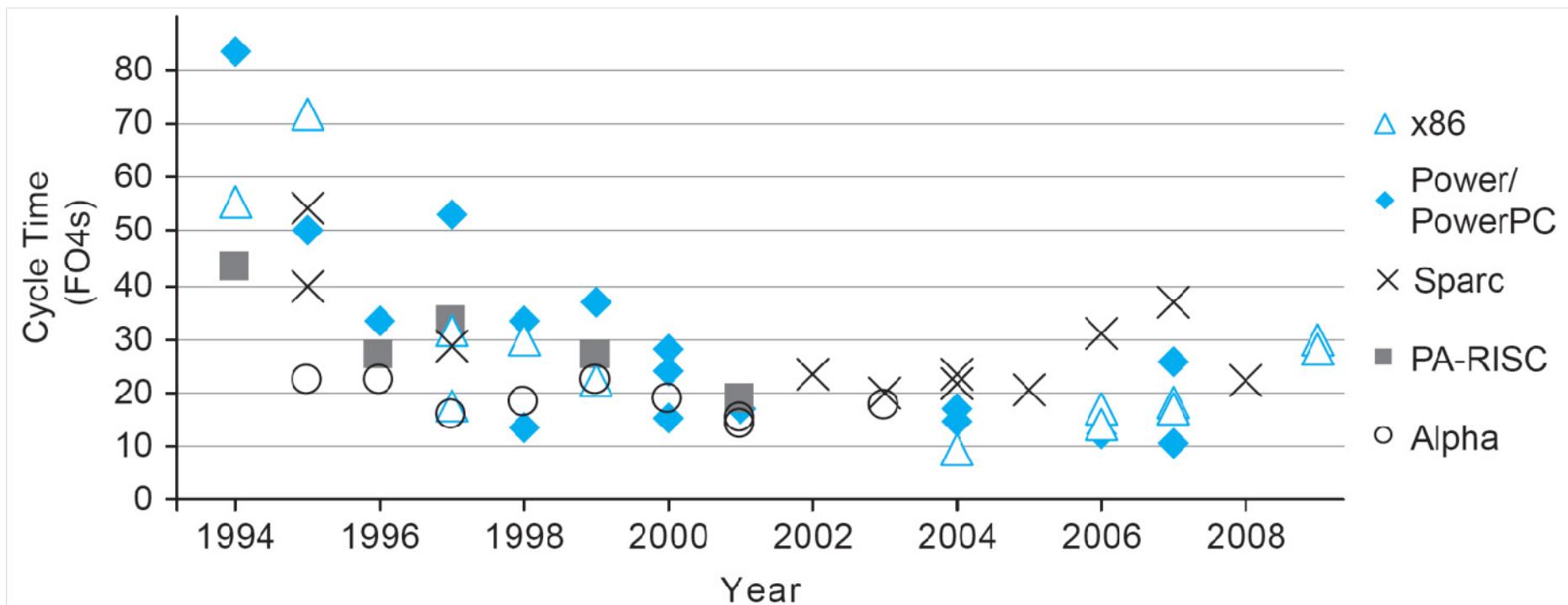


From Weste & Harris.

The tapered buffer

Please note that H is the path electrical effort while h is the stage electrical effort.

Reference inverter . . .

and two inserted buffer inverters

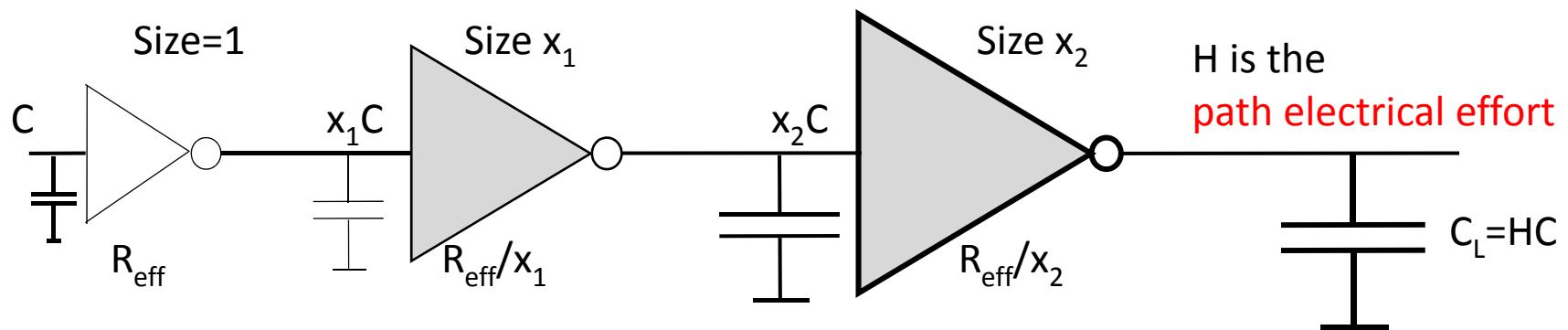

With two intermediate buffer inverters we obtain a normalized delay relative to tau:

$$d = (p_{inv} + h_1) + (p_{inv} + h_2) + (p_{inv} + h_3)$$

where we have defined the **stage electrical efforts**, or fanouts, h .

Here $h_1 = x_1$, $h_2 = x_2/x_1$, and $h_3 = x_3/x_2$.

Only h_1 and h_2 are independent variables, the third h_3 becomes $h_3 = H/h_1 h_2$.


TASK: Show that minimum delay is obtained for $h_1 = h_2 = h_3 = h = \sqrt[3]{H} \gg d = 3(p_{inv} + \sqrt[3]{H})$

The tapered buffer

Please note that H is the path electrical effort while h is the stage electrical effort.

Reference inverter . . .

and two inserted buffer inverters

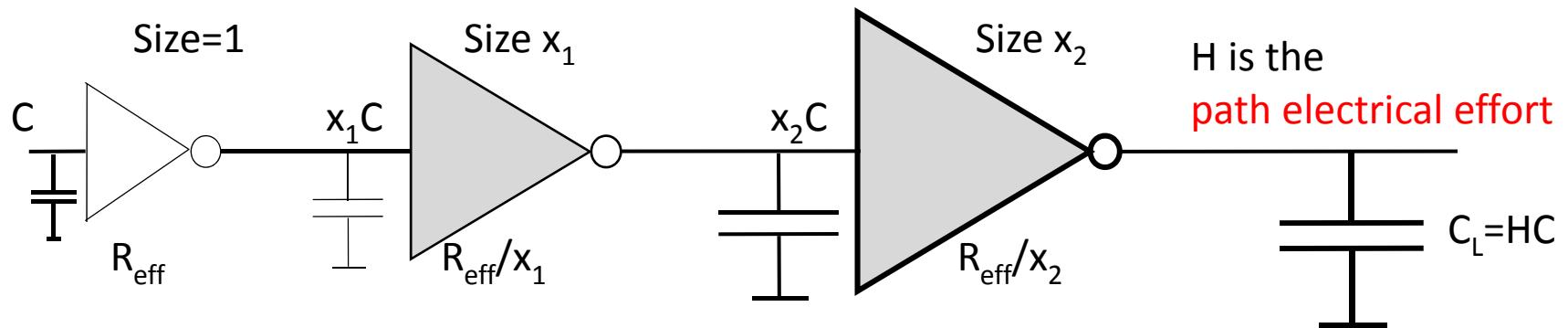

With two intermediate buffer inverters we obtain a normalized delay relative to tau: $d = (p_{\text{inv}} + h_1) + (p_{\text{inv}} + h_2) + (p_{\text{inv}} + H/h_1 h_2)$.

Taking partial derivatives wrt h_1 and h_2 we obtain


$$\frac{d}{dh_1} d(h_1, h_2) = 1 - \frac{H}{h_1^2 h_2} = 0, \text{ and } \frac{d}{dh_2} d(h_1, h_2) = 1 - \frac{H}{h_1 h_2^2} = 0$$

This yields $h = h_1 = h_2$ and $H = h^3 \rightarrow h = \sqrt[3]{H}$

The tapered buffer

Reference inverter . . .

and two inserted buffer inverters

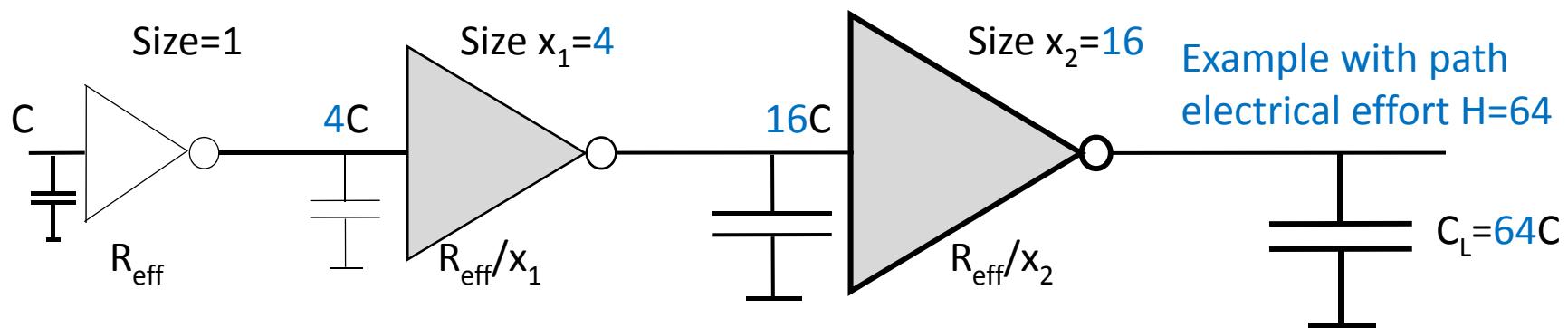


Sharing the load equally between the inverters yields equal stage fanouts $h = \sqrt[3]{64} = 4$

The total delay is then equal to 3 FO4 delays, i.e. $15\tau = 75$ ps (assuming $p_{\text{inv}}=1$).

The Tapered Buffer

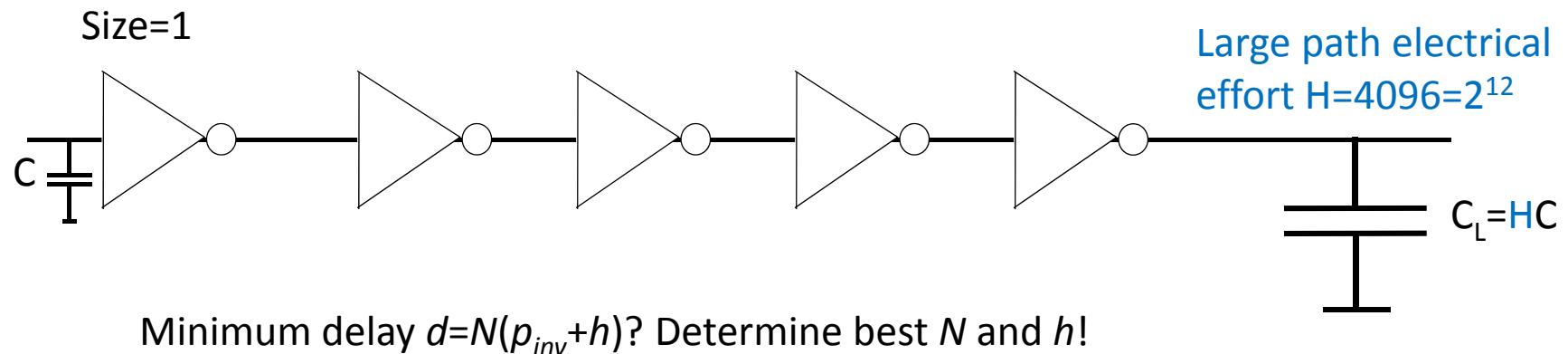- What if the path electrical effort, for some reason, is very large, e.g. $H=4096$.
- How many inverters, N , are needed to minimize the delay?





The Tapered Buffer

- Solving this problem we start by having accepted that minimum delay occurs when stage electrical efforts, h , are shared equally between the inverter stages.
- Hence propagation delay is given by $d = N(p_{inv} + h)$
- Furthermore, $h = \sqrt[N]{H}$, i.e. $H = h^N$.
- Taking natural logarithms we obtain number of inverters $N = \frac{\ln H}{\ln h}$
- Rewrite delay equation $d = N(p_{inv} + h) = \frac{p_{inv} + h}{\ln h} \ln H$
- Looking for minimum delay by taking derivatives wrt h
- We obtain $\ln H \frac{\ln h - (p_{inv} + h)/h}{(\ln h)^2} = 0$, i.e. $\ln h = \frac{p_{inv} + h}{h}$
- Analytical solution only for $p_{inv}=0$, namely $h=e=2.72$

The Tapered Buffer

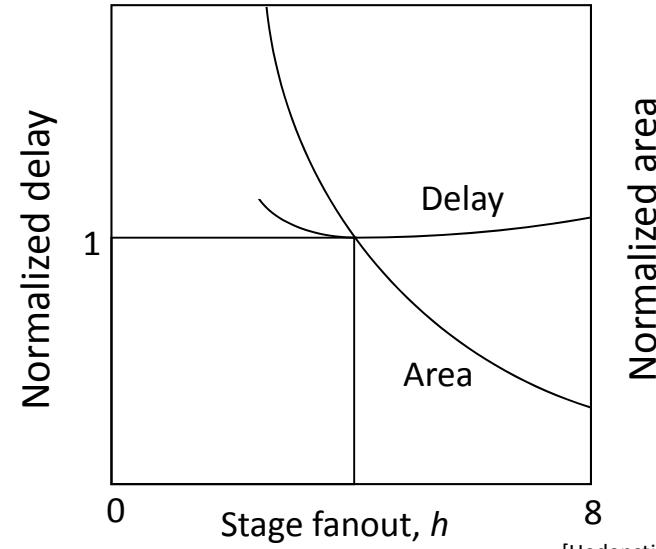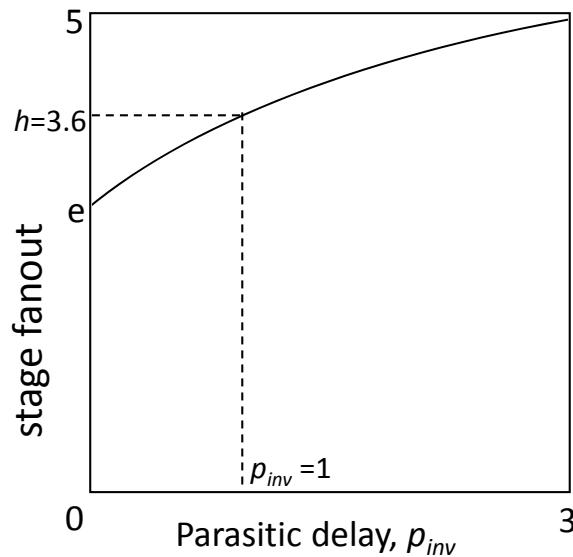- For $p_{inv} \neq 0$ the equation has to be solved numerically



[Hedenstierna & Jeppson 1987]

For typical values of p_{inv} the optimum tapering factor is between 3.6 and 5. Typically a FO4!


Please, note that the propagation delay minimum is rather flat, while total inverter area on the silicon decreases rapidly when larger stage fanout is used. Silicon real estate (=cost) can be saved for relatively little loss of speed!

The Tapered Buffer

- So for a path electrical effort $H=4096=4^6$, minimum delay is obtained for $N=6$ inverters with a stage fanout of four!!
- Minimum normalized delay $d=6(p_{inv}+4)=30$, and $t_{pd}=150$ ps
- What if we choose $N=4$? That is $h=8$?
- What would be the propagation delay?
- Normalized delay $d=4(p_{inv}+8)=36$, and $t_{pd}=180$ ps.
- At the same time the inverter area would be reduced from
- $A=1+4+16+64+256+1024=1365$ to $A=1+8+64+512=585$ units. That is a reduction by more than 55%.

H-tree clock distribution

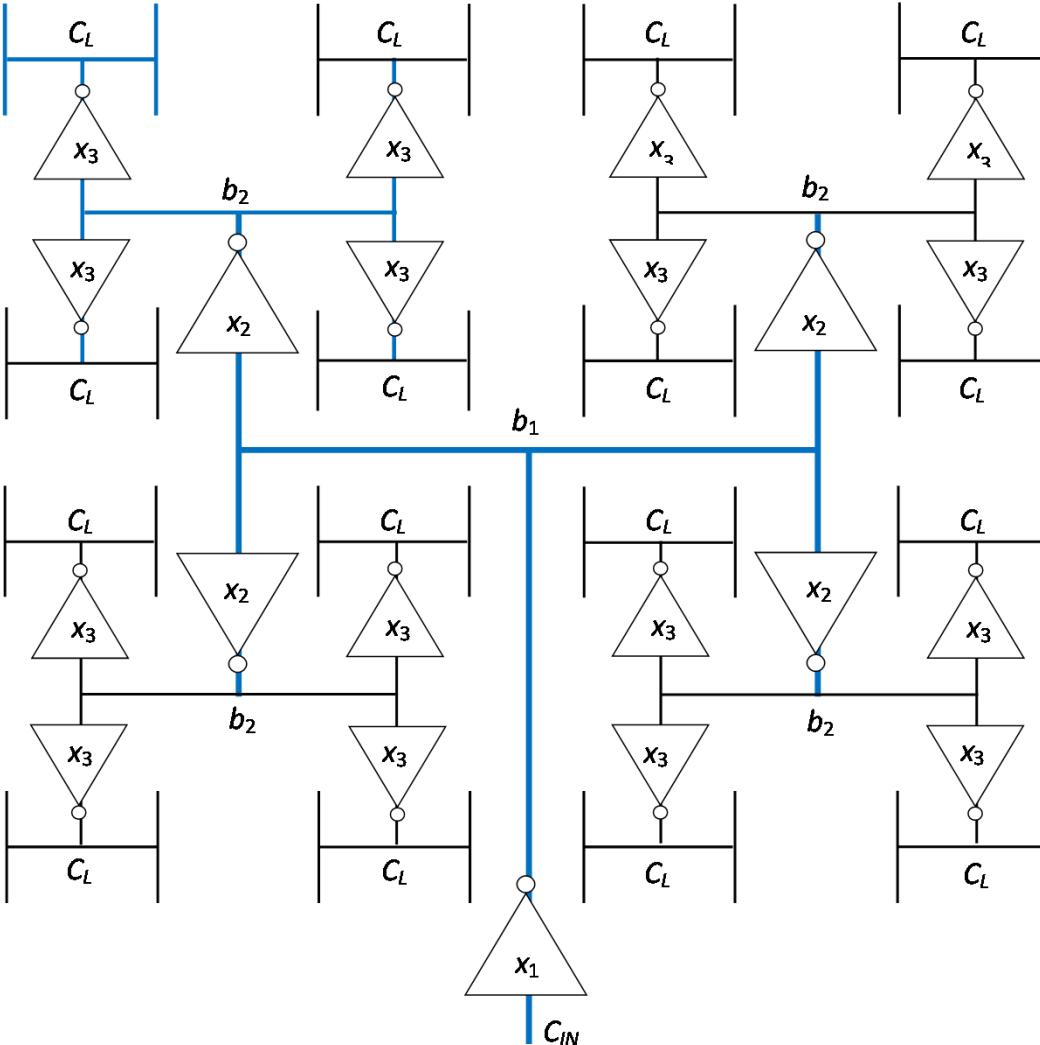Problem: To distribute a clock signal across the chip area so that it arrives simultaneously to all chip corners, i.e no clock skew, and with sharp clock edges!




One approach is to use balanced H-trees!

The load capacitances C_L are due to the input capacitances of all clocked register cells.

H-tree clock distribution

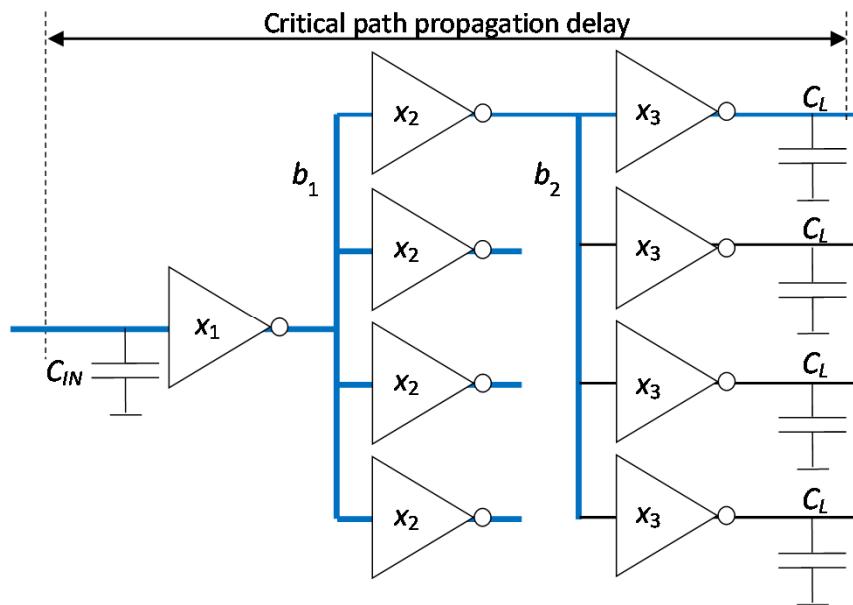- What is the electrical effort of the timing paths considering also the branching?
- What sizes to choose for the inverters of the H-tree?




H-tree clock distribution

- As before, assume stage fanouts h_1, h_2, h_3 .
- Path delay is then given by $d = (p_{inv} + h_1) + (p_{inv} + h_2) + (p_{inv} + h_3)$
- How are stage efforts related considering the branching where the first inverter has a branching $b_1=4$ and the second stage a branching $b_2=4$?
- We have the following relationships: $h_1 = b_1 \frac{x_2}{x_1}$, $h_2 = b_2 \frac{x_3}{x_2}$, $h_3 = \frac{C_L}{\frac{x_3}{x_1} C_{IN}} = \frac{x_1}{x_3} H$
- Hence, $h_1 h_2 h_3 = b_1 \frac{x_2}{x_1} b_2 \frac{x_3}{x_2} \frac{x_1}{x_3} H = b_1 b_2 H$
- Now, let us introduce the path branching $B = b_1 b_2$!
- The path fanout is now $F=BH$, and stage fanout $h=3\sqrt{F}$.
- In an example with $B=16$ and $H=256$ we obtain $F=4096=16^3$.

Example solution for $C_L=256 C_{IN}$!

H-tree clock distribution

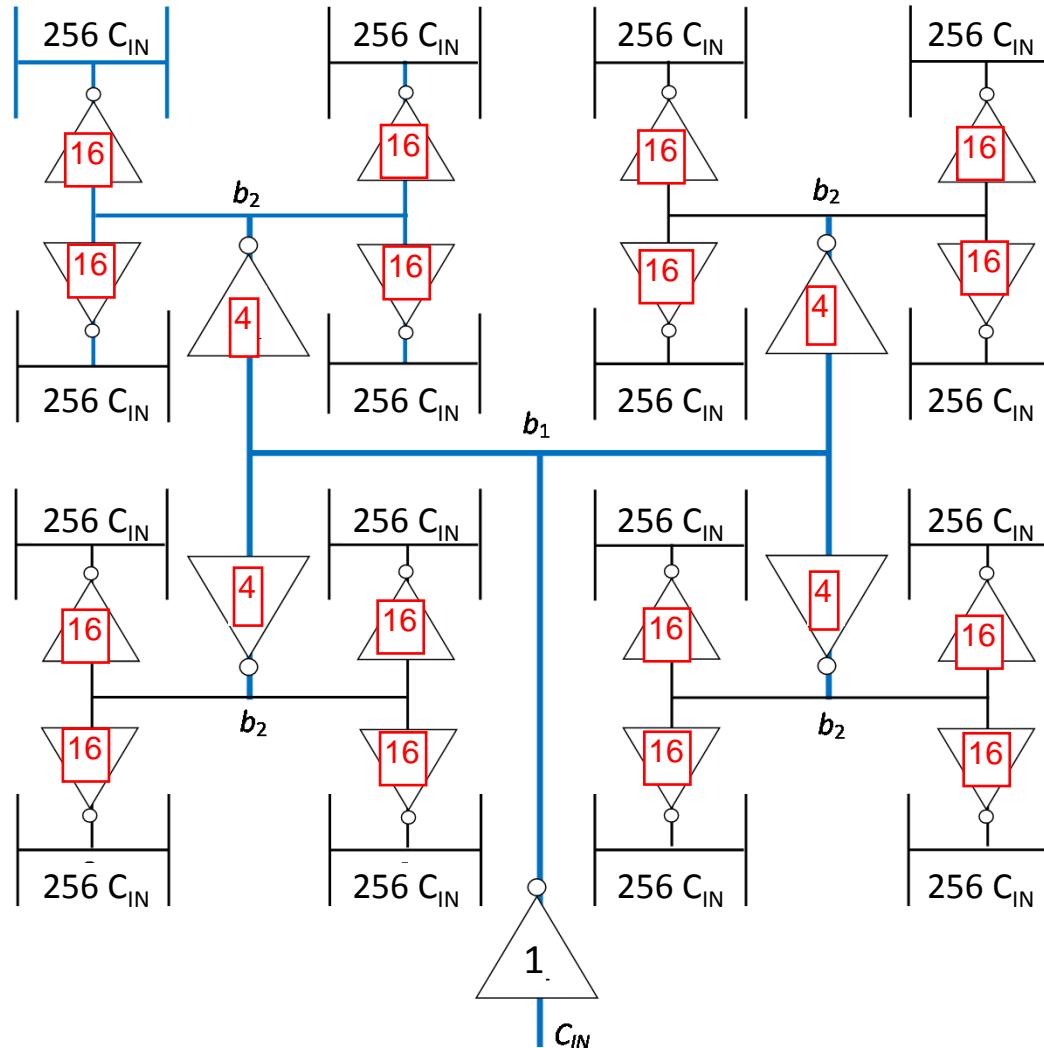

The sizes have
been updated
by Lena on
2017-10-23